

12.7 "Dengeli" Bir Sistende Güç:

Y-bağlantılı yükler: (V_p rms)

$$v_{AN} = \sqrt{2} V_p \cos(\omega t) \quad v_{BN} = \sqrt{2} V_p \cos(\omega t - 120^\circ)$$

$$v_{CN} = \sqrt{2} V_p \cos(\omega t + 120^\circ)$$

$$Z_Y = Z \angle \theta$$

$$i_a = \sqrt{2} I_p \cos(\omega t - \theta) \quad i_b = \sqrt{2} I_p \cos(\omega t - 120^\circ - \theta)$$

$$i_c = \sqrt{2} I_p \cos(\omega t + 120^\circ - \theta)$$

$$P = P_a + P_b + P_c = v_{AN} i_a + v_{BN} i_b + v_{CN} i_c$$

$$= 2 V_p I_p \cos(\omega t) \cos(\omega t - \theta) + 2 V_p I_p \cos(\omega t - 120^\circ) \cos(\omega t - 120^\circ - \theta) \\ + 2 V_p I_p \cos(\omega t + 120^\circ) \cos(\omega t + 120^\circ - \theta)$$

$$= V_p I_p \left[\underbrace{\cos(2\omega t - \theta)}_{\downarrow} + \cos \theta + \underbrace{\cos(2\omega t - 240^\circ - \theta)}_{\downarrow} + \cos \theta \right. \\ \left. + \underbrace{\cos(2\omega t + 240^\circ - \theta)}_{\downarrow} + \cos \theta \right]$$

Toplamları sıfır.

$$P = V_p I_p 3 \cos \theta \rightarrow \text{Üç fazlı bir sistende anlık güç zamanla bağımsız, yani sabittir.}$$

Bu, üç faz kullanmanın avantajlarından biridir.

$$\bar{S}_A = \overline{V_{AN}} \bar{I}_a^* = V_p I_p \angle \theta = \bar{S}_B = \bar{S}_C$$

$$P = P_A + P_B + P_C = 3 V_p I_p \cos \theta$$

$$Q = Q_A + Q_B + Q_C = 3 V_p I_p \sin \theta$$

Y-bağlantılı yük için: $V_L = \sqrt{3} V_p$ $I_L = I_p$

$\downarrow$ hat gerilimi $\downarrow$ hat akımı

$\downarrow$ faz g. $\downarrow$ faz akımı


$$P = 3 V_p I_p \cos \theta = \sqrt{3} V_L I_L \cos \theta \rightarrow$$

Δ -bağlantılı yük için: $V_L = V_p$ $I_L = \sqrt{3} I_p$ AYNI!

$$P = 3 V_p I_p \cos \theta = \sqrt{3} V_L I_L \cos \theta \rightarrow$$

İletim Hattı Kaybı

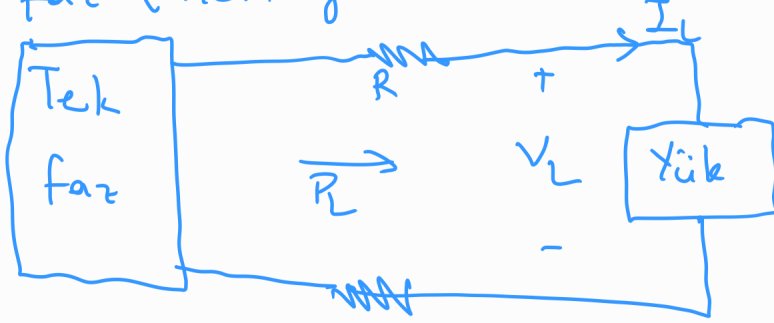
Tek faz (hem gidiste, hem de dönüşte kayıp var)



$$P_L = I_L V_L$$

$$P_{\text{kayıp}} = 2 I_L^2 R = 2 R \frac{P_L^2}{V_L^2}$$

Üç faz

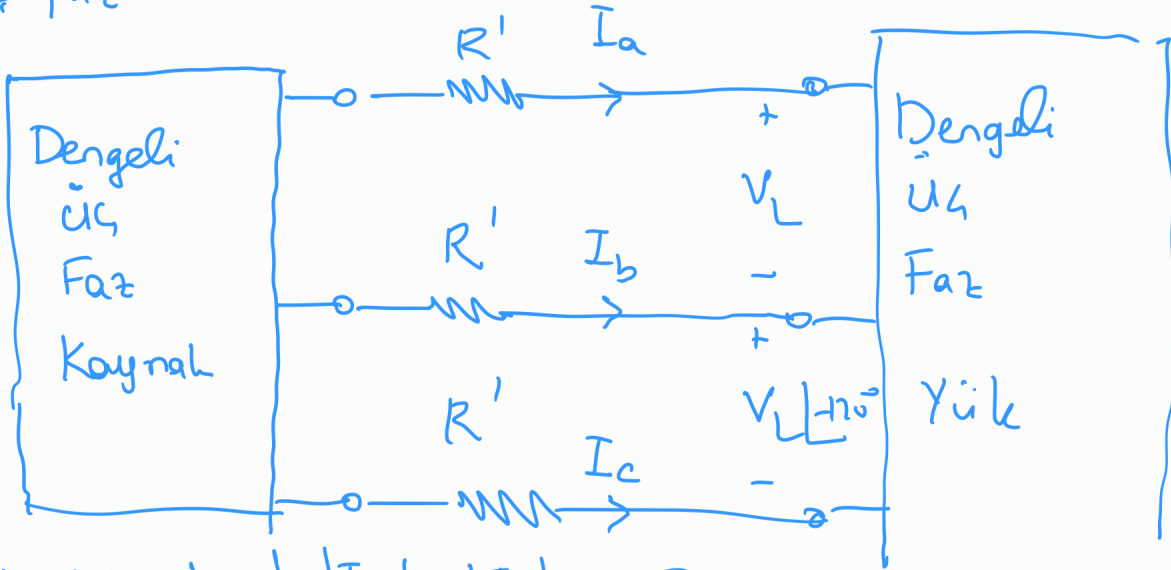

$$|I_L'| = |I_a| = |I_b| = |I_c| = \frac{P_L}{\sqrt{3} V_L} \text{ hat akımı büyüklükleri}$$

$$P'_{\text{kayıp}} = 3 (I_L')^2 R' = 3 R' \frac{P_L^2}{3 V_L^2} = R' \frac{P_L^2}{V_L^2}$$

Direnc: kesit alanının karesi ile ters orantılı

$$\frac{P_{loss}}{P'_{loss}} = \frac{2R \cancel{P_L} / V_L^2}{R' \cancel{P_L} / V_L^2} = \frac{2r'^2}{r^2}$$

İki sisten aynı kayba sahipse $r^2 = 2r'^2$ olur.

$$\frac{\text{Tek faz malzeme}}{\text{Üç faz malzeme}} = \frac{2\pi r^2 l}{3\pi r'^2 l} = \frac{4\pi r'^2 l}{3\pi r'^2 l} = \frac{4}{3}$$

Tek faz %33 daha fazla malzeme gerektirir

Problem 12.6 Probl 12.2'deki Y-Y devresi için

kaynak ve yükteki kompleks gücü bulun.

Practice Problem 12.2

A Y-connected balanced three-phase generator with an impedance of $0.4 + j0.3 \Omega$ per phase is connected to a Y-connected balanced load with an impedance of $24 + j19 \Omega$ per phase. The line joining the generator and the load has an impedance of $0.6 + j0.7 \Omega$ per phase. Assuming a positive sequence for the source voltages and that $V_{an} = 120/30^\circ \text{ V}$, find: (a) the line voltages, (b) the line currents.

Answer: (a) $207.8/60^\circ \text{ V}$, $207.8/-60^\circ \text{ V}$, $207.8/-180^\circ \text{ V}$,
(b) $3.75/-8.66^\circ \text{ A}$, $3.75/-128.66^\circ \text{ A}$, $3.75/111.34^\circ \text{ A}$.

$\sqrt{3}V_L I_L \cos \theta + j\sqrt{3}V_L I_L \sin \theta$
 $\tan^{-1} \frac{19}{24} = 38.66^\circ$

Yük: $S = \sqrt{3} \times \underset{V_L}{207.8} \times \underset{I_L}{3.75} \angle 38.66^\circ \rightarrow \varnothing$
 $= 1058.2 + j837.81 \text{ VA}$ ✓

Kaynak: $\sqrt{3} V_L I_L \cos \theta$

$3 \times \underbrace{120 \angle 30^\circ \times I_a^*}_{a} = 3 \times 120 \angle 30^\circ \times 3.75 \angle 8.66^\circ$
 $= 1054 + j843.34 \text{ VA}$



Aslında $-1054 - j843.34 \text{ VA}$ ✓

Example 12.7

A three-phase motor can be regarded as a balanced Y-load. A three-phase motor draws 5.6 kW when the line voltage is 220 V and the line current is 18.2 A. Determine the power factor of the motor.

$$P = \sqrt{3} V_L I_L \cos \theta$$

$\downarrow$ 5600 $\downarrow$ 220 $\downarrow$ 18.2 $\underbrace{\cos \theta}_{?}$

$$\cos \theta \approx 0.8$$

g-f 0.8

Calculate the line current required for a 30-kW three-phase motor having a power factor of 0.85 lagging if it is connected to a balanced source with a line voltage of 550 V.

Practice Problem 12.7

Answer: 37.05 A.

$$P = \sqrt{3} V_L I_L \cos \theta$$

$$30000 = \sqrt{3} \times 550 \times \tilde{I}_L \times 0.85$$


$I_L = 37.05 \text{ A}$

Example 12.8

Two balanced loads are connected to a 240-kV rms 60-Hz line, as shown in Fig. 12.22(a). Load 1 draws 30 kW at a power factor of 0.6 lagging, while load 2 draws 45 kVAR at a power factor of 0.8 lagging. Assuming the *abc* sequence, determine: (a) the complex, real, and reactive powers absorbed by the combined load, (b) the line currents, and (c) the kVAR rating of the three capacitors Δ -connected in parallel with the load that will raise the power factor to 0.9 lagging and the capacitance of each capacitor.

$$V_L = 240 \text{ kV}$$

a)

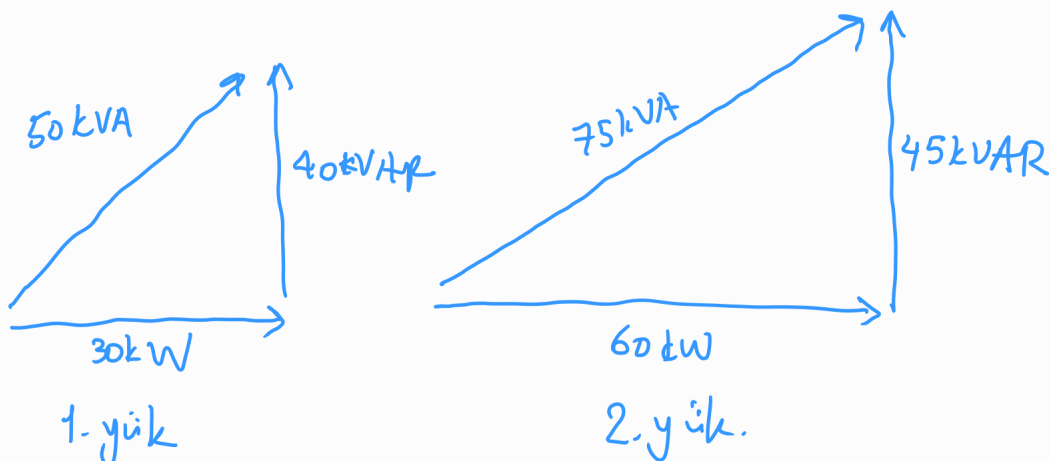

Güç toplanır. Birleşik yük: $\bar{S} = 90 \text{ kW} + j85 \text{ kVAR}$

$$S = \sqrt{3} V_L \overset{?}{\bar{I}_L} \rightarrow \bar{I}_L \cong \underline{0.3 \text{ A}} \rightarrow a, b, c \text{ fazları için.}$$

$$\downarrow \approx 124 \text{ kVA}$$

$$\downarrow 240 \text{ kV}$$

$$\rightarrow \bar{S} = 124 \angle 43.36^\circ = \sqrt{3} \bar{V}_L \bar{I}_L^* = \sqrt{3} V_L I_L \angle \theta_v - \theta_i \left. \begin{array}{l} \text{a faz için} \\ \text{a faz için} \end{array} \right\}$$


$$\theta_v = 0 \rightarrow \text{a faz için}$$

$$\theta_i = -43.36^\circ$$


$$\rightarrow \underline{\bar{I}_{La} = 0.3 \angle -43.36^\circ \text{ A}}$$

$$\bar{I}_{Lb} = 0.3 \angle -163.36^\circ \text{ A}$$

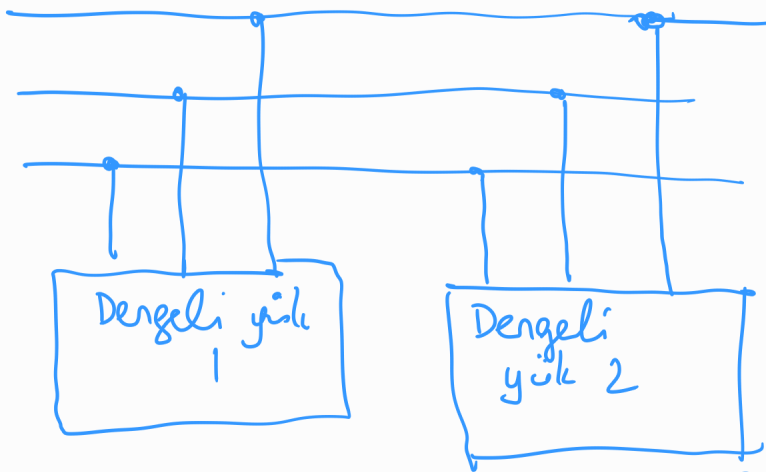
$$\bar{I}_{Lc} = 0.3 \angle +76.64^\circ \text{ A}$$



$\equiv$

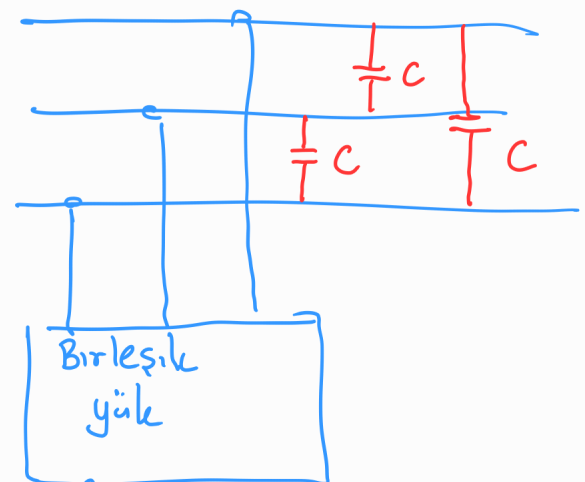

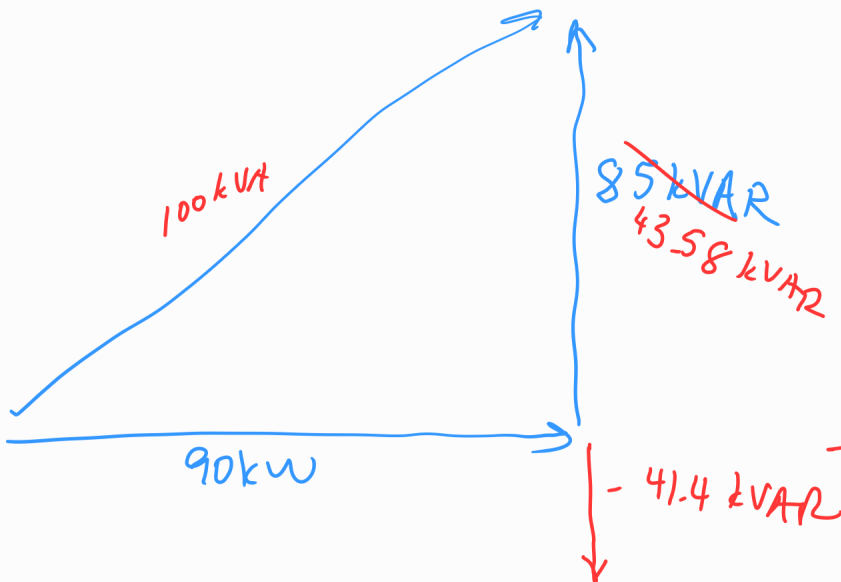Şu anda g.f. 0.73. (takip eden)
Bunu 0.9 (takip eden) yapmak için C ekliyoruz.



bunu 3'e böleriz
 $Q_c = -13.8 \text{ kVAR}$
rating

$$S' = \frac{90 \text{ kW}}{0.9} = 100 \text{ kVA}$$


$$S = \bar{V} \bar{I}^* = \bar{V} \frac{\bar{V}^*}{Z^*} = \frac{|V|^2}{Z^*}$$

$$-j 13800 = \frac{(240000)}{j \omega C}$$

$$\begin{aligned} 13800 &= (240000)^2 2\pi 60 C \\ &= 6.355 \times 10^{-10} \text{ F} \\ &= 635.5 \text{ pF} \end{aligned}$$

Assume that the two balanced loads in Fig. 12.22(a) are supplied by an 840-V rms 60-Hz line. Load 1 is Y-connected with $30 + j40 \Omega$ per phase, while load 2 is a balanced three-phase motor drawing 48 kW at a power factor of 0.8 lagging. Assuming the *abc* sequence, calculate: (a) the complex power absorbed by the combined load, (b) the kVAR rating of each of the three capacitors Δ -connected in parallel with the load to raise the power factor to unity, and (c) the current drawn from the supply at unity power factor condition.

Practice Problem 12.8

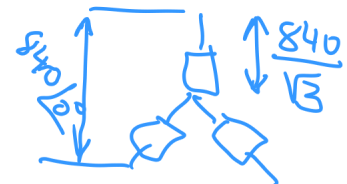

Answer: (a) $56.47 + j47.29 \text{ kVA}$, (b) 15.76 kVAR , (c) 38.81 A .

Yük 1:


$$S = \sqrt{3} V_L (\bar{I}_L) \cos \theta + j \sqrt{3} V_L I_L \sin \theta$$

$\downarrow 840$ $\downarrow 0.6$ $\downarrow 840$ $\downarrow 0.8$

$I_L = \frac{840}{50\sqrt{3}}$

$$\begin{aligned} &= 14112 \times 0.6 + j 14112 \times 0.8 \\ &= 8467 + j 11290 \text{ VA} \checkmark \end{aligned}$$

Yük 2:

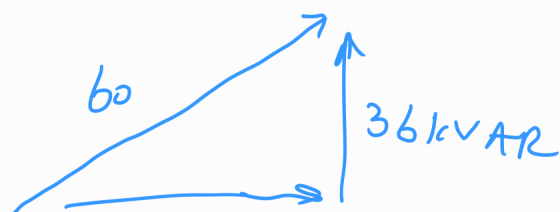

$$\bar{S}^2 = 48000 + j 36000 \text{ VA}$$

$$\bar{S} = \bar{S}^1 + \bar{S}^2 = 56467 + j 47290 \checkmark$$

b)



g.f. 1 olacak

Özetle: Her bir C'nin kVAR rating'i:
 $\frac{47290}{3} = 15.76 \text{ kVAR}$

c) Yeni durumda $\bar{S} = 56467$ (resistif)

$$\bar{S} = \sqrt{3} V_L I_L \cos \theta$$


$\downarrow$ $\downarrow$ $\downarrow$
 56467 840 1

$$I_L = 38.81 \text{ A}$$

12.8 Dengesiz Üç Fazlı Sistem:

Yükler eşit olmazsa üç fazlı sistem dengesiz olarak adlandırılır.

$$Z_A \neq Z_B \neq Z_C$$

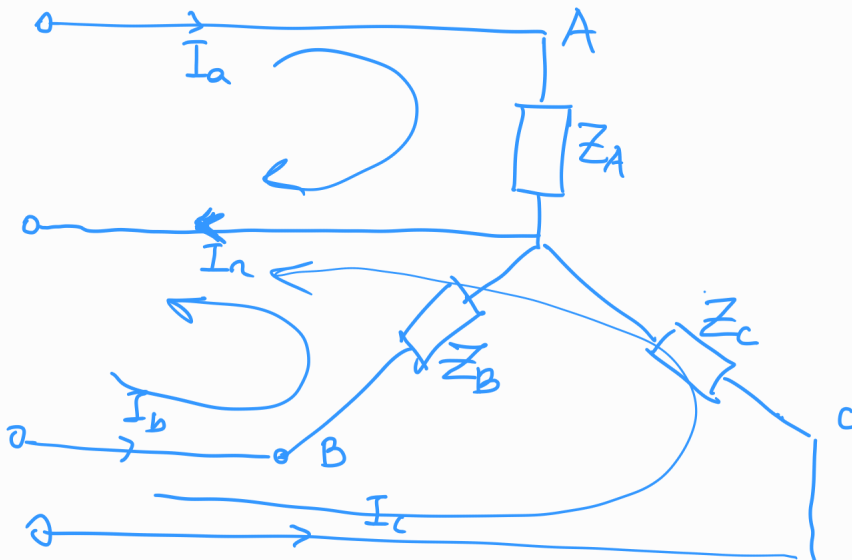

$$\bar{I}_a = \frac{\bar{V}_{AN}}{Z_A}$$

$$\bar{I}_b = \frac{\bar{V}_{BN}}{Z_B}$$

$$\bar{I}_c = \frac{\bar{V}_{CN}}{Z_C}$$

$$\bar{I}_n = \bar{I}_a + \bar{I}_b + \bar{I}_c$$

Nötr bağlantısı yoksa, Gerre akım yöntemi kullanılabilir.
Benzer analizler $Y-\Delta$, $\Delta-Y$, $\Delta-\Delta$ için de yapılabilir.
Güç hesabını bütün fazlar için ayrı ayrı yapmak gerekir.

Practice Problem 12.9

The unbalanced Δ -load of Fig. 12.24 is supplied by balanced line-to-line voltages of 440 V in the positive sequence. Find the line currents. Take V_{ab} as reference.

Answer: $39.71 \angle -41.06^\circ$ A, $64.12 \angle -139.8^\circ$ A, $70.13 \angle 74.27^\circ$ A.

440

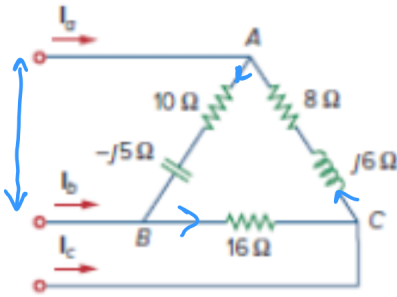


Figure 12.24

Unbalanced Δ -load; for Practice Prob. 12.9.

$$V_{AB} = 440$$

$$V_{BC} = 440 \angle -120^\circ$$

$$V_{CA} = 440 \angle +120^\circ$$

$$\bar{I}_{AB} = \frac{440}{10 - j5}$$

$$\bar{I}_{BC} = \frac{440 \angle -120^\circ}{16}$$

$$\bar{I}_{CA} = \frac{440 \angle +120^\circ}{8 + j6}$$

$$\bar{I}_a + \bar{I}_{CA} = \bar{I}_{AB} \Rightarrow \bar{I}_a = \bar{I}_{AB} - \bar{I}_{CA}$$

$$\bar{I}_b + \bar{I}_{AB} = \bar{I}_{BC} \Rightarrow \bar{I}_b = \bar{I}_{BC} - \bar{I}_{AB}$$

$$\bar{I}_c = \bar{I}_{CA} - \bar{I}_{BC}$$