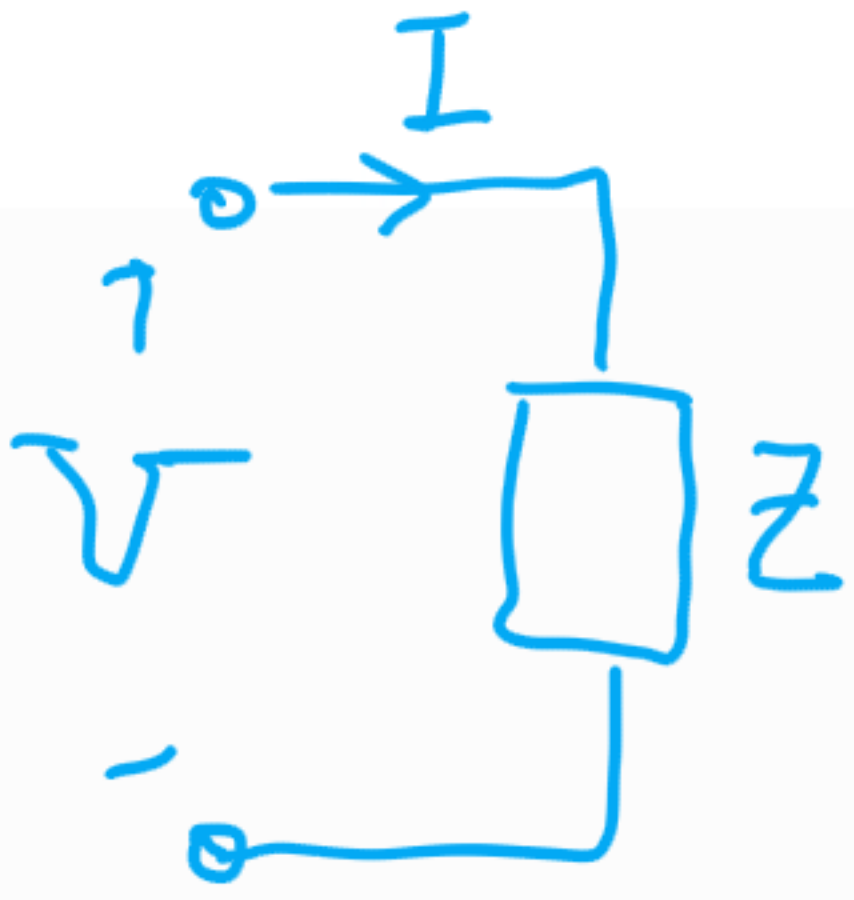



EXAMPLE 11.12

A load Z draws 12 kVA at a power factor of 0.856 lagging from a 120-V rms sinusoidal source. Calculate: (a) the average and reactive powers delivered to the load, (b) the peak current, and (c) the load impedance.



$$S = 12 \text{ kVA}$$

g.f. lagging : inaktif
güç içeri yutar

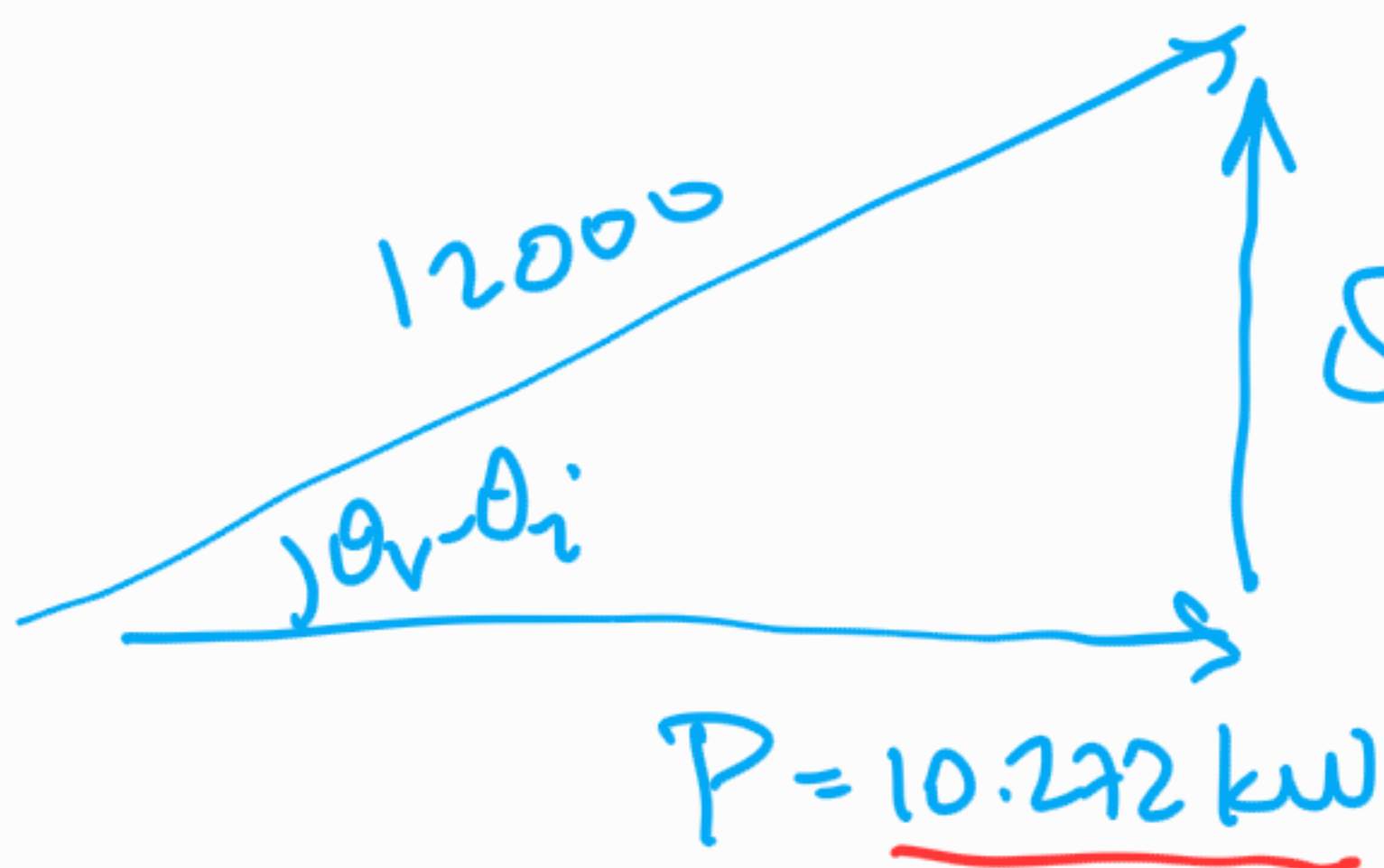

$$\frac{P}{12000} = 0.856 = 10.272 \text{ kW}$$

$$Q = \sqrt{12^2 - 10.272^2} \text{ kVAR}$$

$$= 6.204 \text{ kVAR}$$

$$S = V_{\text{rms}} \bar{I}_{\text{rms}} \text{ görünen güç.}$$

$\downarrow$ $\downarrow$
 12000 120

$$\bar{I}_{\text{rms}} = \frac{12000}{120} = 100 \text{ A (rms)}$$

$$I_m = 100\sqrt{2} \text{ A}$$

$$\bar{S} = \bar{V}_{\text{rms}} \bar{I}_{\text{rms}}^*$$

$$\bar{S} = \bar{I}_{\text{rms}} Z \bar{I}_{\text{rms}}^* = \underbrace{|\bar{I}_{\text{rms}}|^2}_{100^2} Z$$


$\downarrow$
 10272 + j6204

$$Z = 1.0272 + j0.6204 \Omega$$

$$= 1.2 \angle 31.13^\circ$$

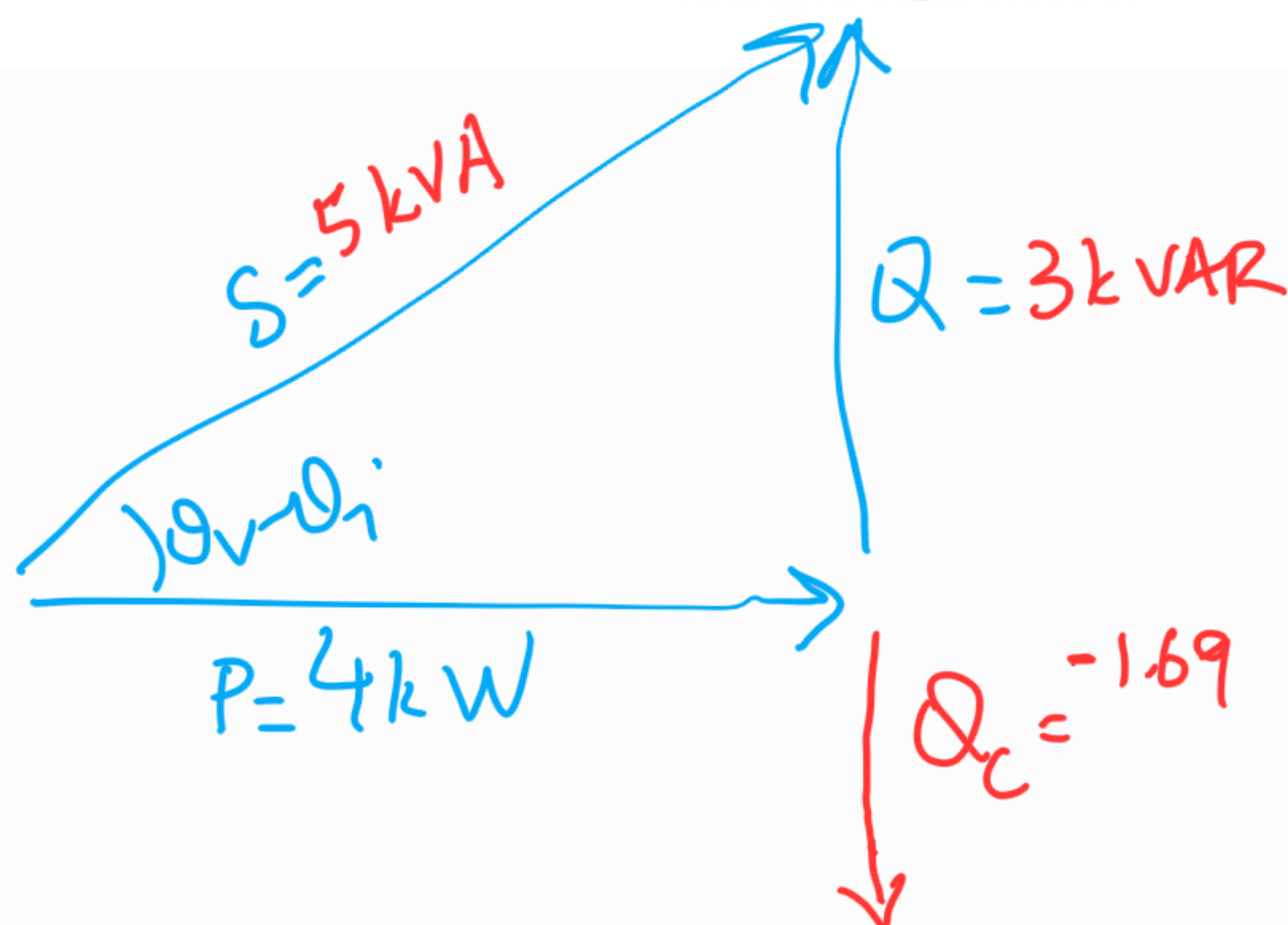EXAMPLE 11.15

When connected to a 120-V (rms), 60-Hz power line, a load absorbs 4 kW at a lagging power factor of 0.8. Find the value of capacitance necessary to raise the pf to 0.95.




0.95 is in:

$$0.95 = \frac{4}{S}$$

$$\rightarrow S = 4.21 \text{ kVA (new)}$$

$$\rightarrow \text{new } Q: 1.31 \text{ kVAR}$$
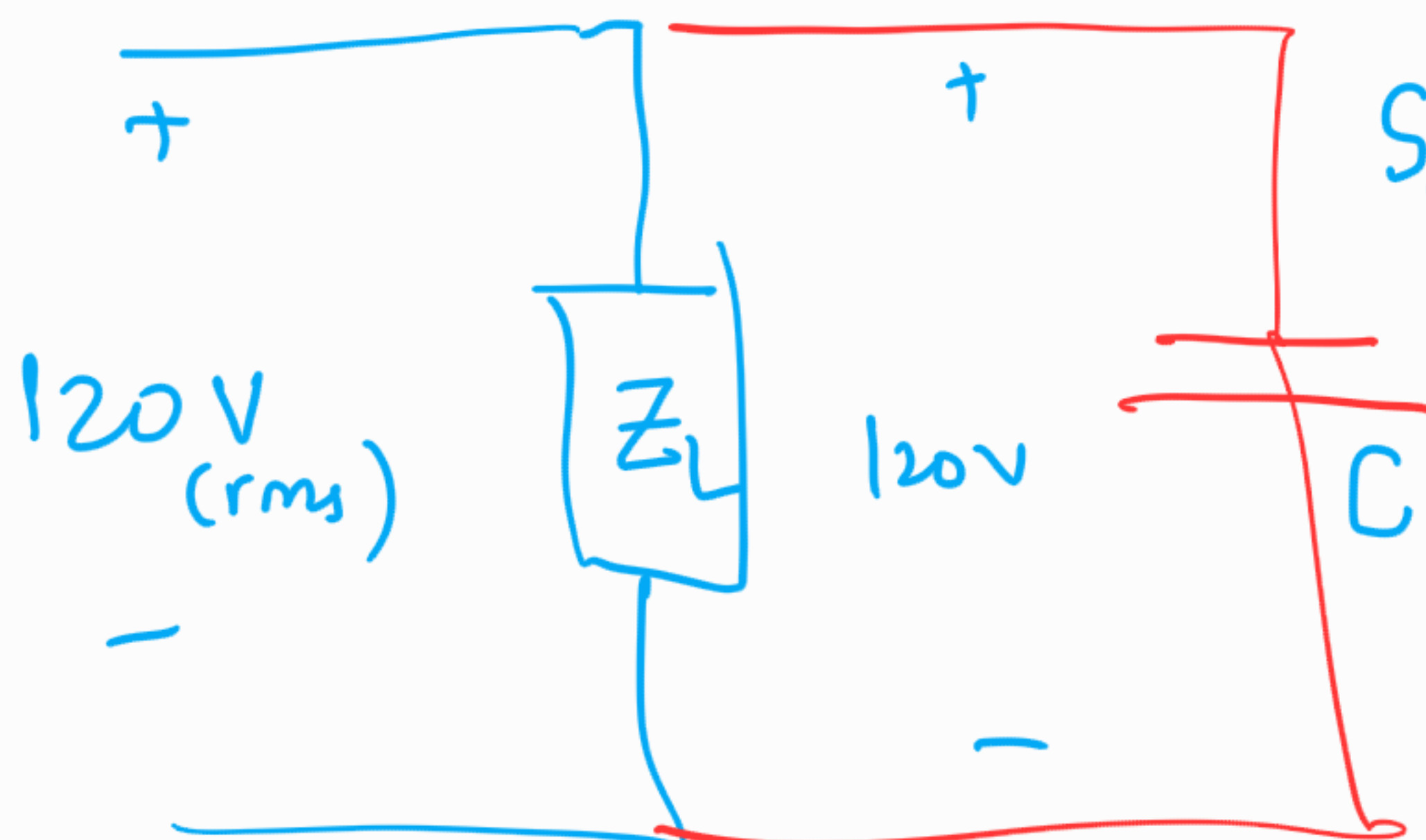
$$Q_c = 3 - 1.31 \approx 1.69 \text{ kVA}$$



$$S_c = Q_c = 120 \bar{I}_c^*$$

$$P_c = 0$$

$$Q_c = 120 \times \frac{120}{Z_c^*}$$

$$Q_c = \frac{120^2}{+j/\omega C} = \frac{120^2 \omega C}{+j}$$

$$-j1690 = -j120^2 \omega C$$


$\downarrow$
120π

$$C = \frac{1690}{120^2 \times 120 \times \pi} = 311 \mu\text{F}$$

Practice Problem 11.15

Find the value of parallel capacitance needed to correct a load of 140 kVAR at 0.85 lagging pf to unity pf. Assume that the load is supplied by a 220-V (rms), 60-Hz line.

Answer: 7.673 mF.

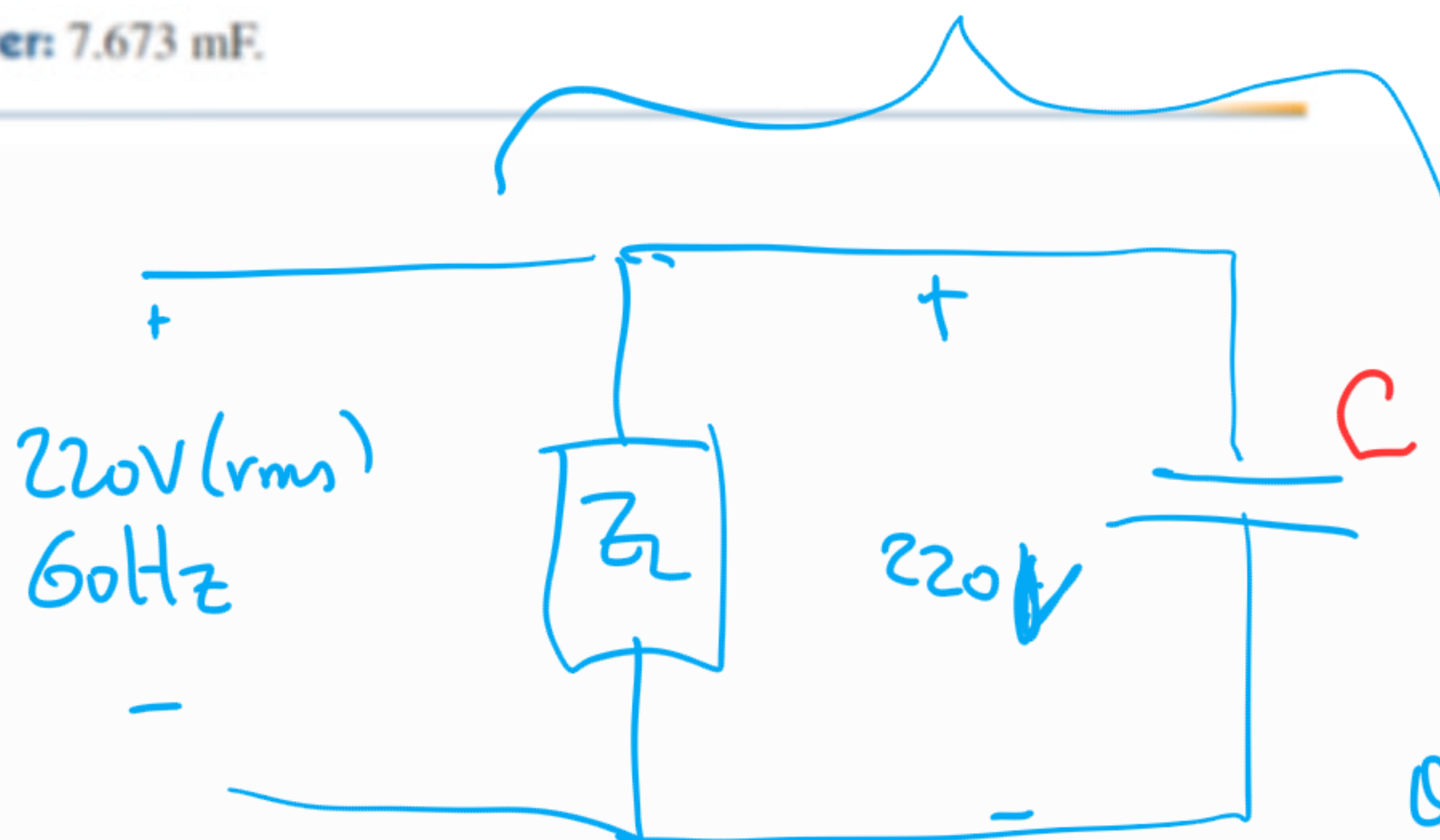


$$\begin{aligned} \text{Eslu:} \\ Q_V - Q_C &= \cos^{-1}(0.85) \\ &= 31.8^\circ \end{aligned}$$

$$\tan 31.8 = \frac{140000}{P}$$

$$P = 226 \text{ kW}$$

$$S = 266 \text{ kVA}$$

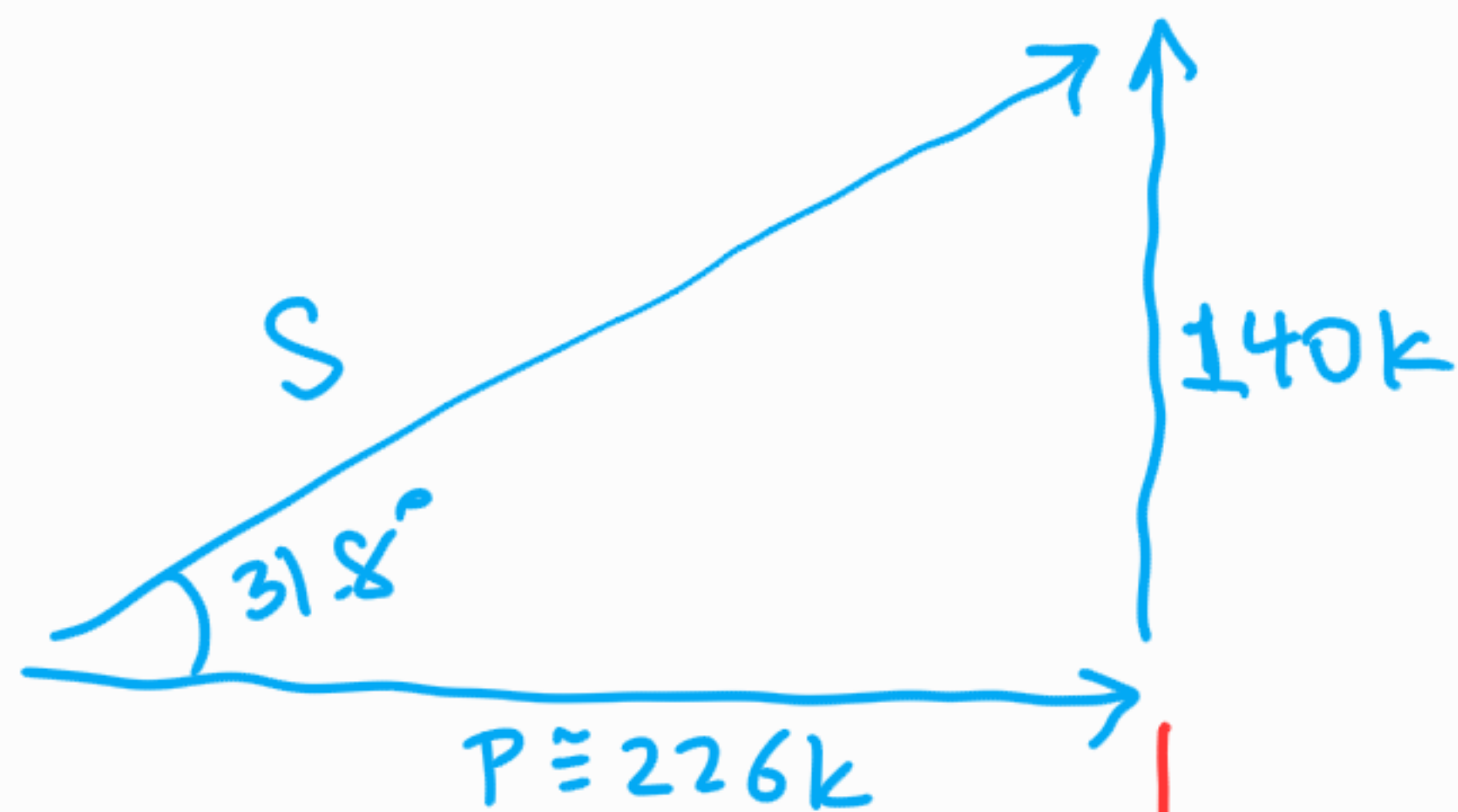

$$Q_C = -j140k$$

$$220 I_C^* = -j140000$$

$$220 \times \frac{220}{Z_C^*} = -j140000$$

$$\frac{220^2}{j/\omega C} = -j140000 \Rightarrow -j220^2 \omega C = 140000$$

$$C = 7.7 \text{ mF}$$

11.8 UYGULAMALAR

Güç Ölçümü (AC wattmeter)

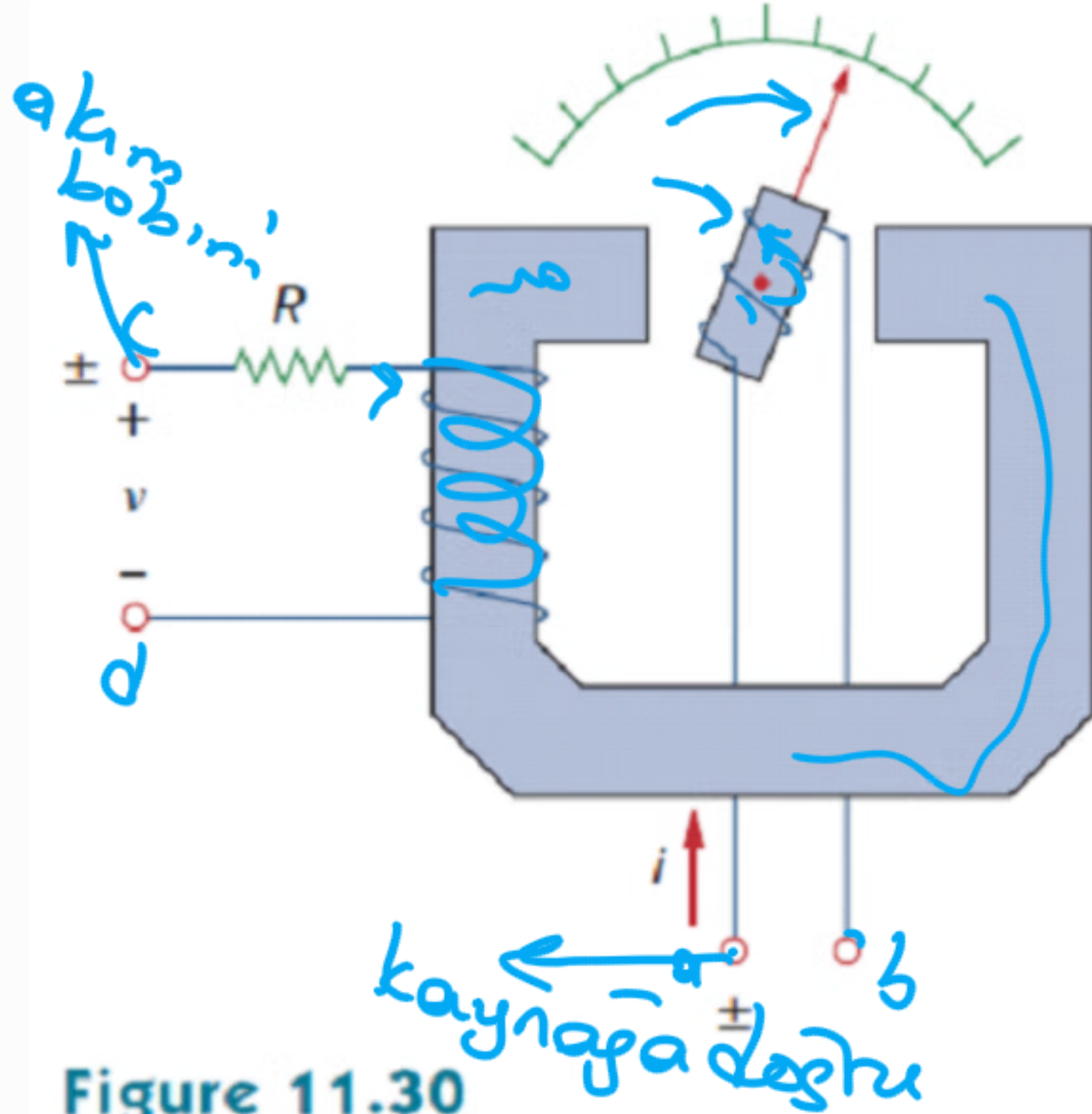


Figure 11.30
A wattmeter.


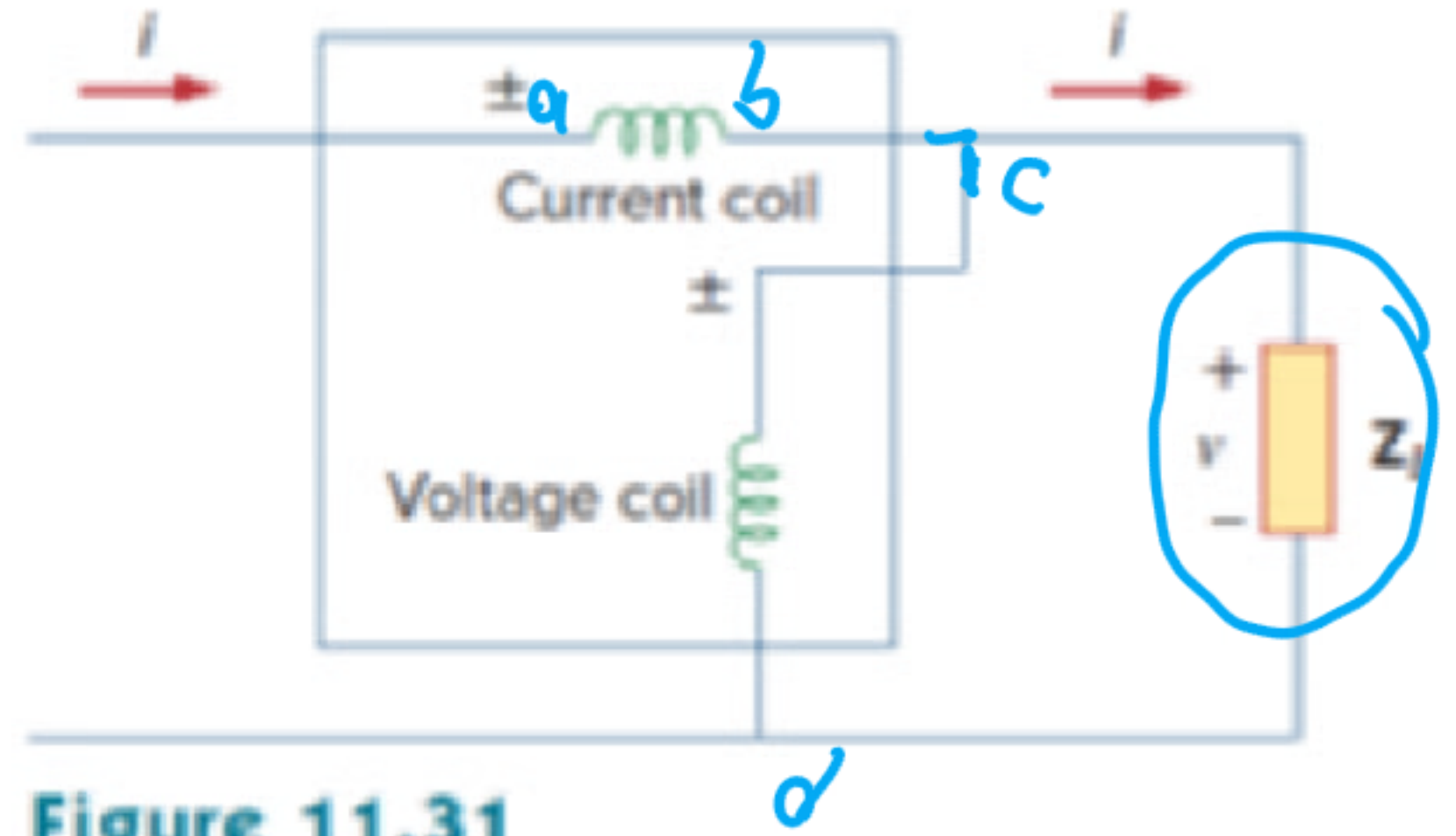


Figure 11.31
The wattmeter connected to the load.

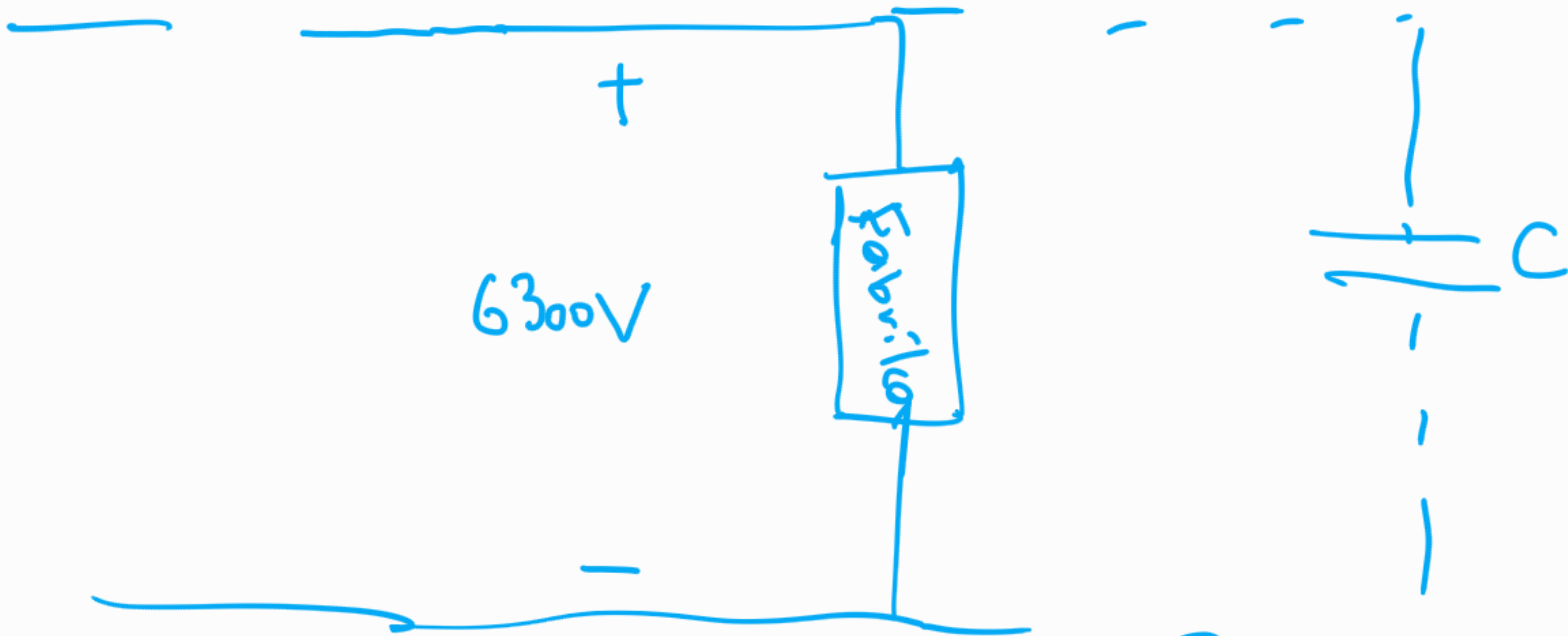Akım bobini düşük endüktansa
Sahip olmalı (az gerilim çekmeli)
Gerilim bobini büyük endüktansa
Sahip olmalı (az akım çekmeli)




$$Eski = P + jQ = S = 120 \text{ kW} + j140 \text{ kVAR}$$

Yeni: g.f. 0.95 olması için ne kadar kapasitif reaktif güç gerekir?

$$\frac{120}{0.95} = 126.3 \text{ kVA} = Y_{eni} S$$

$$Y_{eni}: Q = 39.4 \text{ kVAR}$$

$$Q_c = 39.4 - 140 \\ = -100.6$$

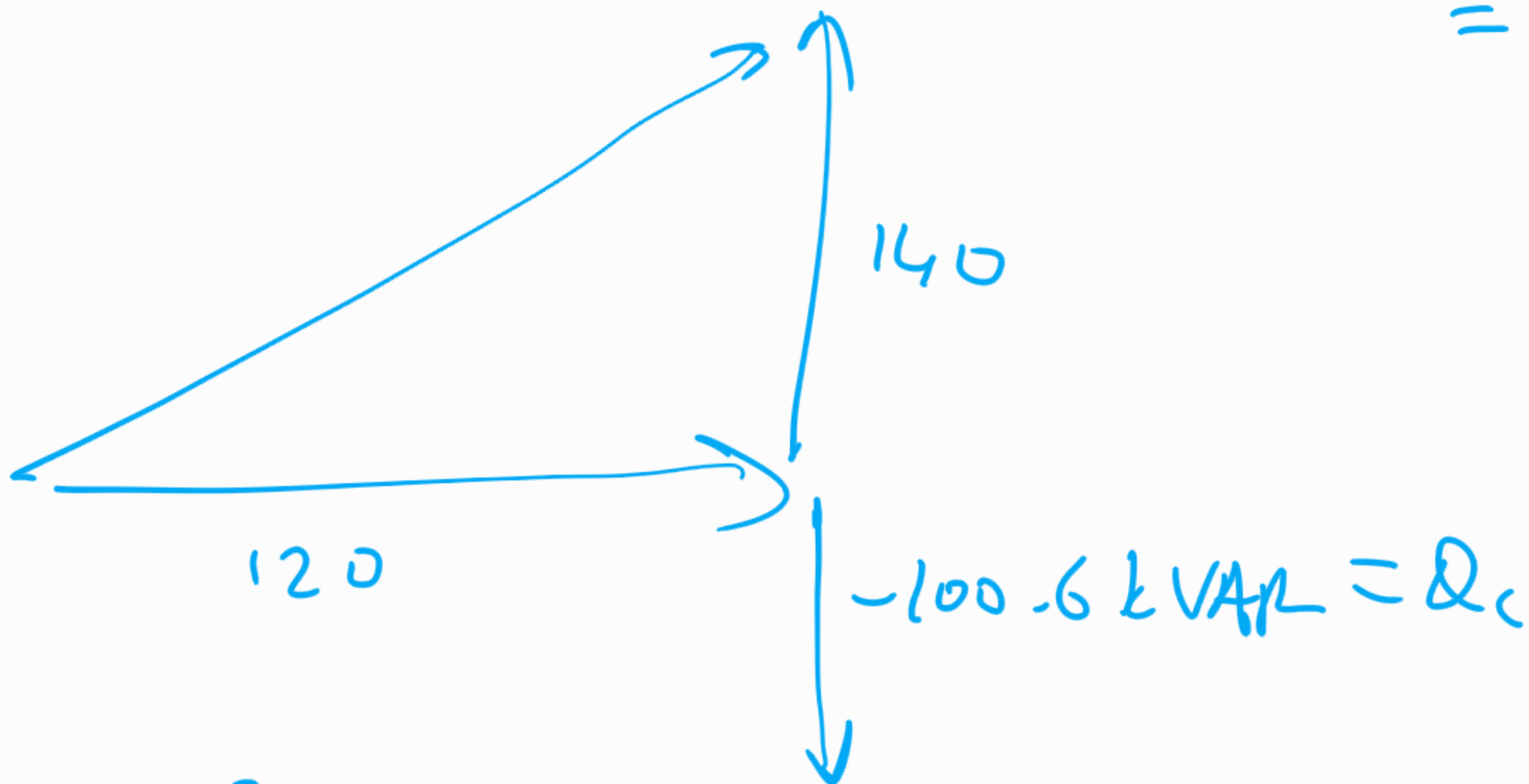

$$\frac{6300^2}{j\omega C} = -j100.6 \times 10^3$$

$$-j \frac{6300^2}{2\pi \times 50 \times C} = -j100600$$

$$C = \frac{100600}{6300^2 \times 100 \times \pi} = 8.06 \mu F$$