

~

13.9 UYGULAMALAR

Trafo'nun Kullanım Alanları:

- İzolasyon Aracı Olarak Kullanım:

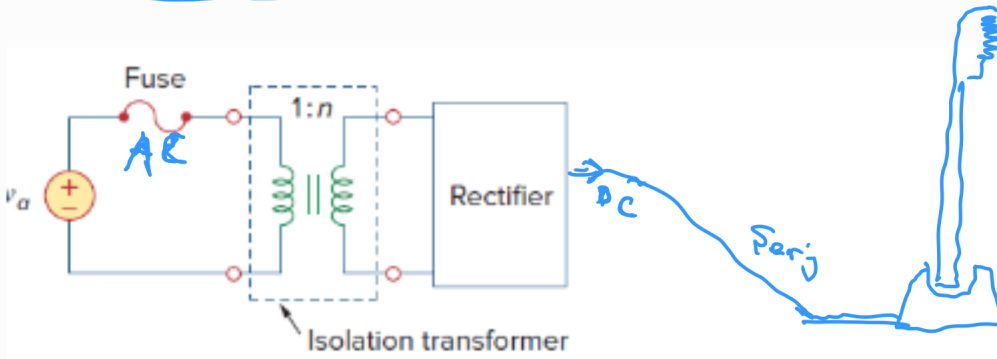


Figure 13.59

A transformer used to isolate an ac supply from a rectifier.

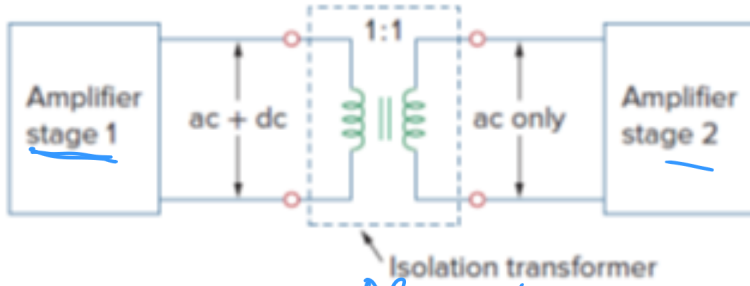


Figure 13.60

A transformer providing dc isolation between two amplifier stages.

- Yüksek gerilim hatlarındaki gerilimi güvenli bir şekilde ölçmek için trafo kullanılır.

Gerilim düşürülür, ölçülür, sarım oranı kullanılarak gerçek gerilim bulunur

Determine the voltage across the load in Fig. 13.62.

Solution:

We can apply the superposition principle to find the load voltage. Let $v_L = v_{L1} + v_{L2}$, where v_{L1} is due to the dc source and v_{L2} is due to the ac source. We consider the dc and ac sources separately, as shown in Fig. 13.63. The load voltage due to the dc source is zero, because a time-varying voltage is necessary in the primary circuit to induce a voltage in the secondary circuit. Thus, $v_{L1} = 0$. For the ac source and a value of R_s so small it can be neglected.

Example 13.15


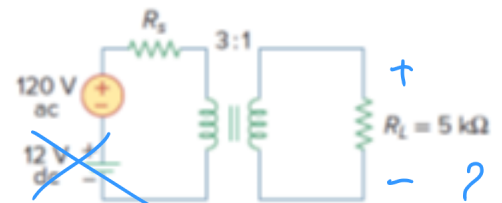


Figure 13.62
For Example 13.15.


① Trafo DC geçirmez. Bundan dolayı (12Vdc) yükte gerilim oluşmaz.

② 120 V (ac) : $R_s = 0$ alınıp ihmal etmiş. Yükte 40 V (ac) oluşur.

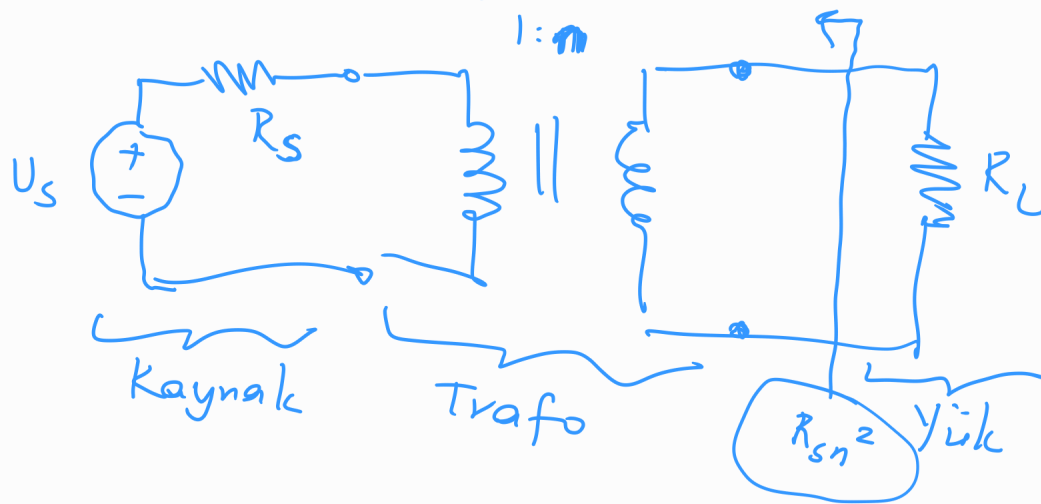- Empedans uyumuna oran olarak kullanımı.



• Maks. güç transfer etmek için.

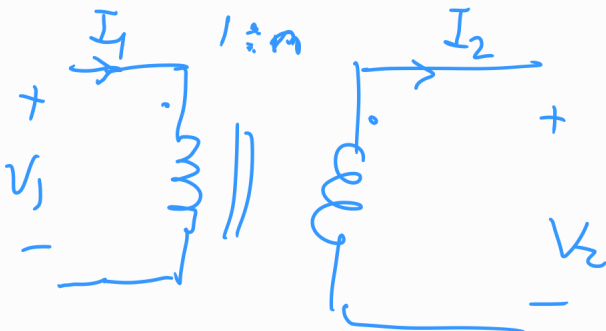

$$\Rightarrow \frac{V_2}{V_1} = n$$

$$\frac{I_2}{I_1} = \frac{1}{n}$$

$$Z_1 = \frac{V_1}{I_1} = \frac{V_2/n}{I_2/n} = \frac{V_2}{I_2} \frac{1}{n^2}$$

$$= Z_2 \frac{1}{n^2}$$

$$Z_2 = Z_1 n^2$$

Example 13.16

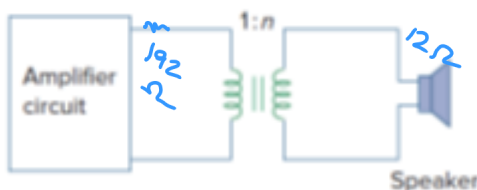


Figure 13.65

Using an ideal transformer to match the speaker to the amplifier; for Example 13.16.

The ideal transformer in Fig. 13.65 is used to match the amplifier circuit to the loudspeaker to achieve maximum power transfer. The Thevenin (or output) impedance of the amplifier is 192Ω , and the internal impedance of the speaker is 12Ω . Determine the required turns ratio.


Solution:

We replace the amplifier circuit with the Thevenin equivalent and reflect the impedance $Z_L = 12 \Omega$ of the speaker to the primary side of the ideal transformer. Figure 13.66 shows the result. For maximum power transfer,

$n = \sqrt{\frac{12}{192}} = \sqrt{\frac{1}{16}} = \frac{1}{4}$ olmalı

$n' = 1'$ den küçüğü olmalı.

• Güç dağıtımında kullanılır:

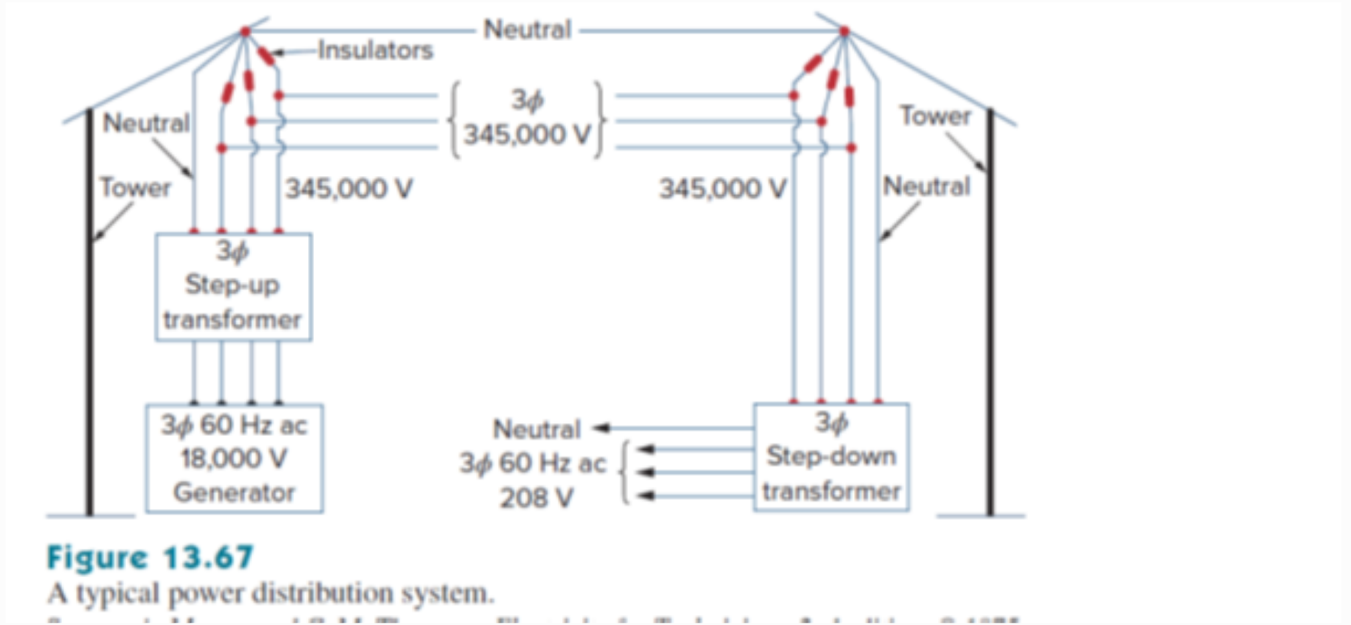

Güç dağıtım:

1) Üretim:

– Sonrasında : 100lerce Mega Volt - Amper Güç.

ör. 18 kV gerilim

o zaman $\sim 10^4$ A akım.

2) İletim:

– Step-up trafo : 154 kV veya 384 kV

– 100 kVA = 1000 V x 100 A

veya

= 10000 V x 10 A ✓ (daha ince kablo, daha az I^2R kaybı)

– Yüzlerce km iletiliyor-

(40 mm çapında kablo, 1000 Amper)

3) Dağıtım:

– 33 kV veya 15.8 kV'a indirilir.

buradanda 33 kV $\rightarrow$ 15.8 kV, 10 kV, 6.3 kV, 0.4 kV

— Evlere iş yerlerine dağıtılır (220V, 380V)

Example 13.17

A distribution transformer is used to supply a household as in Fig. 13.68. The load consists of eight 100-W bulbs, a 350-W TV, and a 15-kW kitchen range. If the secondary side of the transformer has 72 turns, calculate: (a) the number of turns of the primary winding, and (b) the current I_p in the primary winding.

$$\begin{array}{rcl}
 8 \times 100 \text{ W} & \text{Ampul} & \\
 350 \text{ W} & \text{TV} & \\
 + 15000 \text{ W} & \text{Mutfak} & \\
 \hline
 16150 \text{ W} & &
 \end{array}$$

gücün korunumu

birinci taraf da üretilen güç 16150 W

$$I_p = \frac{16150}{2400} = 6.729 \text{ A}$$

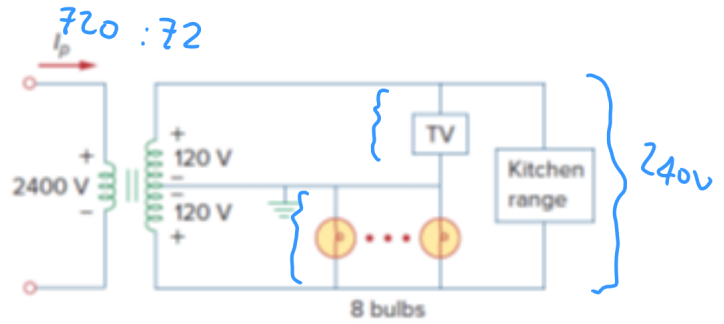


Figure 13.68
For Example 13.17.