

9.8 Calculate these complex numbers and express your results in rectangular form:

(a) $\frac{60/45^\circ}{7.5 - j10} + j2$

$$7.5 - j10 = 12.5 \angle -\tan^{-1}\left(\frac{10}{7.5}\right) = 12.5 \angle -53^\circ$$

(b) $\frac{32/-20^\circ}{(6 - j8)(4 + j2)} + \frac{20}{-10 + j24}$

(c) $20 + (16/-50^\circ)(5 + j12)$

a) $\frac{60 \angle 45^\circ}{12.5 \angle -53^\circ} + j2 = \frac{60}{12.5} \angle 98^\circ + j2$
 $= -0.67 + j4.75 + j2$
 $= -0.67 + j6.75$

b) $\frac{32 \angle -20^\circ}{24 + j12 - j32 + 16} + \frac{20}{-10 + j24}$

$$\frac{32 \angle -20^\circ}{40 - j20} - \frac{4}{5 - j12}$$

$$\frac{1.6 \angle -20^\circ (2 + j)}{(2 - j)(2 + j)}$$

$$\frac{4 (5 + j12)}{(5 - j12)(5 + j12)}$$

$$1.6 \angle -20^\circ \cdot 2.24 \angle 26.6^\circ - \frac{4 (5 + j12)}{169}$$

$$3.58 \angle -6.6^\circ - 0.12 - j0.28$$

$$3.56 - j0.41 - 0.12 - j0.28$$

$$3.44 - j0.69$$

9.9 Evaluate the following complex numbers and leave your results in polar form:

(a) $5/30^\circ \left(6 - j8 + \frac{3/60^\circ}{2 + j} \right)$

(b) $\frac{(10/60^\circ)(35/-50^\circ)}{(2 + j6) - (5 + j)}$

$$\begin{aligned}
 a) & 5 \angle 30^\circ \left(6 - j8 + \frac{3 \angle 60^\circ}{2.24 \angle 26^\circ} \right) \\
 & 5 \angle 30^\circ \left(6 - j8 + \underbrace{1.34 \angle 34^\circ}_{1.11 + j0.75} \right) \\
 & = 5 \angle 30^\circ (7.11 - j7.25) \\
 & = 10.15 \angle -45.5^\circ
 \end{aligned}$$


9.12 Let $X = 4 \angle 40^\circ$ and $Y = 20 \angle -30^\circ$. Evaluate the following quantities and express your results in polar form:

(a) $(X + Y)X^*$

(b) $(X - Y)^*$

(c) $(X + Y)/X$

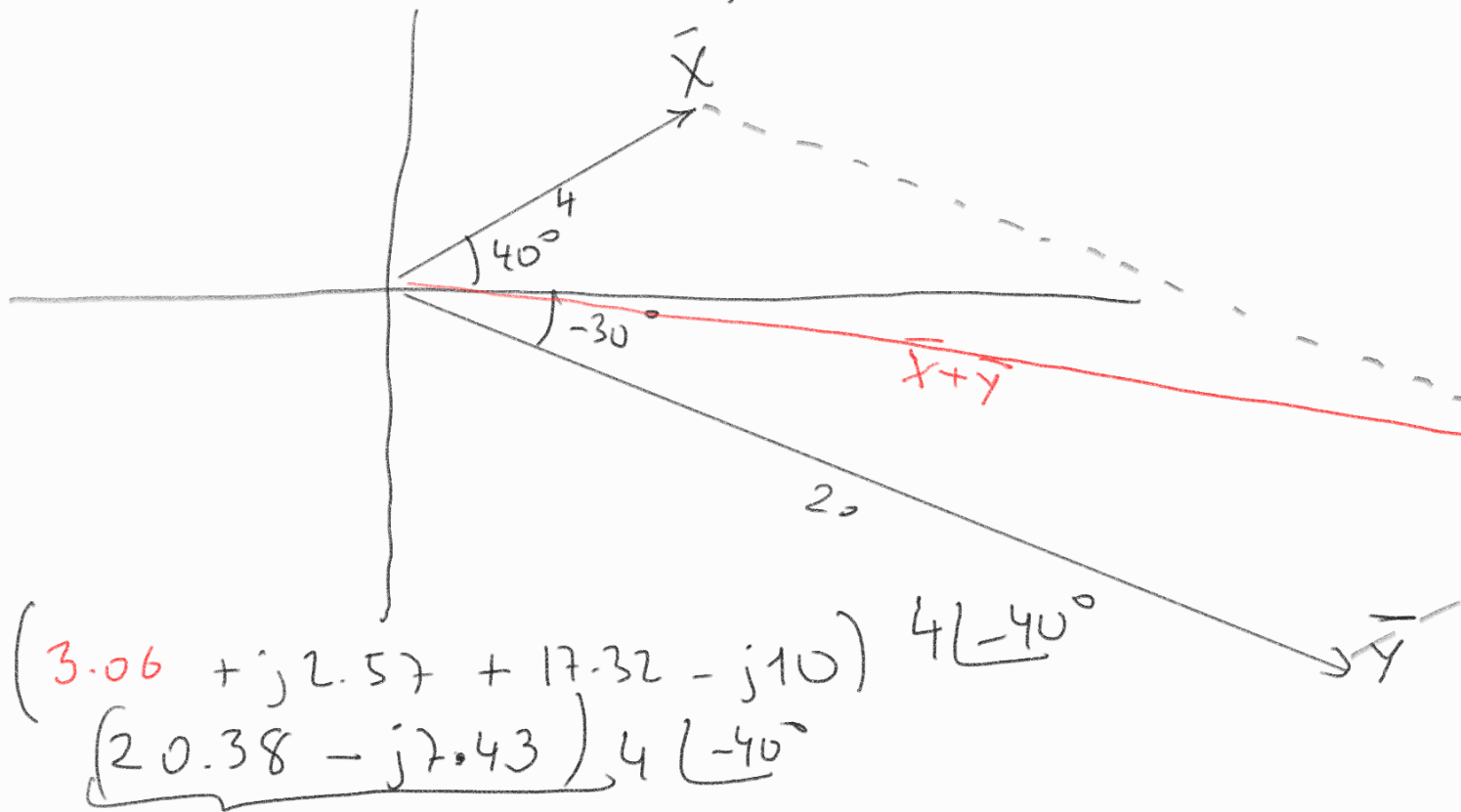a) $(4 \angle 40^\circ + 20 \angle -30^\circ) 4 \angle -40^\circ$



$$\begin{aligned}
 & (3.06 + j2.57 + 17.32 - j10) 4 \angle -40^\circ \\
 & (20.38 - j7.43) 4 \angle -40^\circ
 \end{aligned}$$

$$= 21.69 \angle -20^\circ \quad 4 \angle -40^\circ$$

$$= 86.76 \angle -60^\circ //$$



9.1) $\sqrt{14} 50 \cos(30t + 10^\circ) \text{ V}$

$$10^\circ = \frac{10}{180} \pi = \frac{\pi}{18}$$

• Genlik = 50 V


• açısal frekans = 30 rad/sn

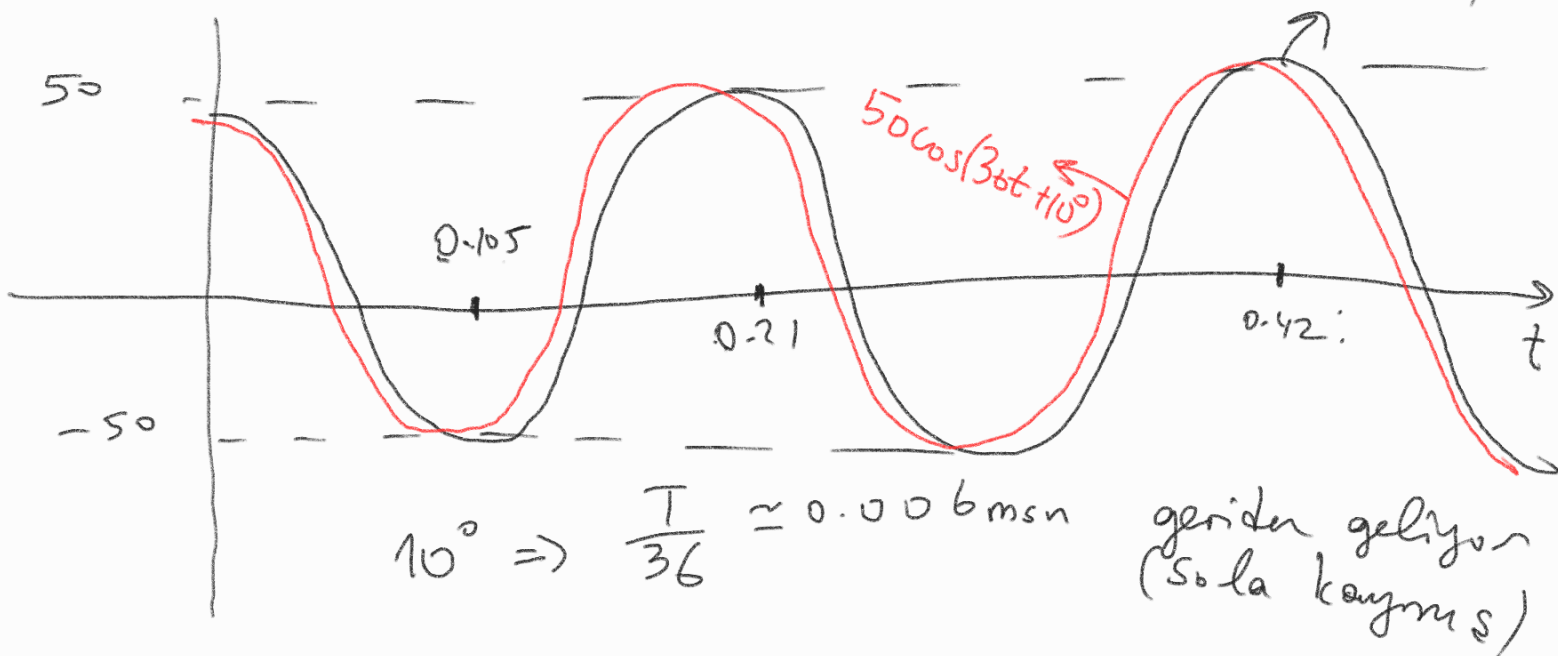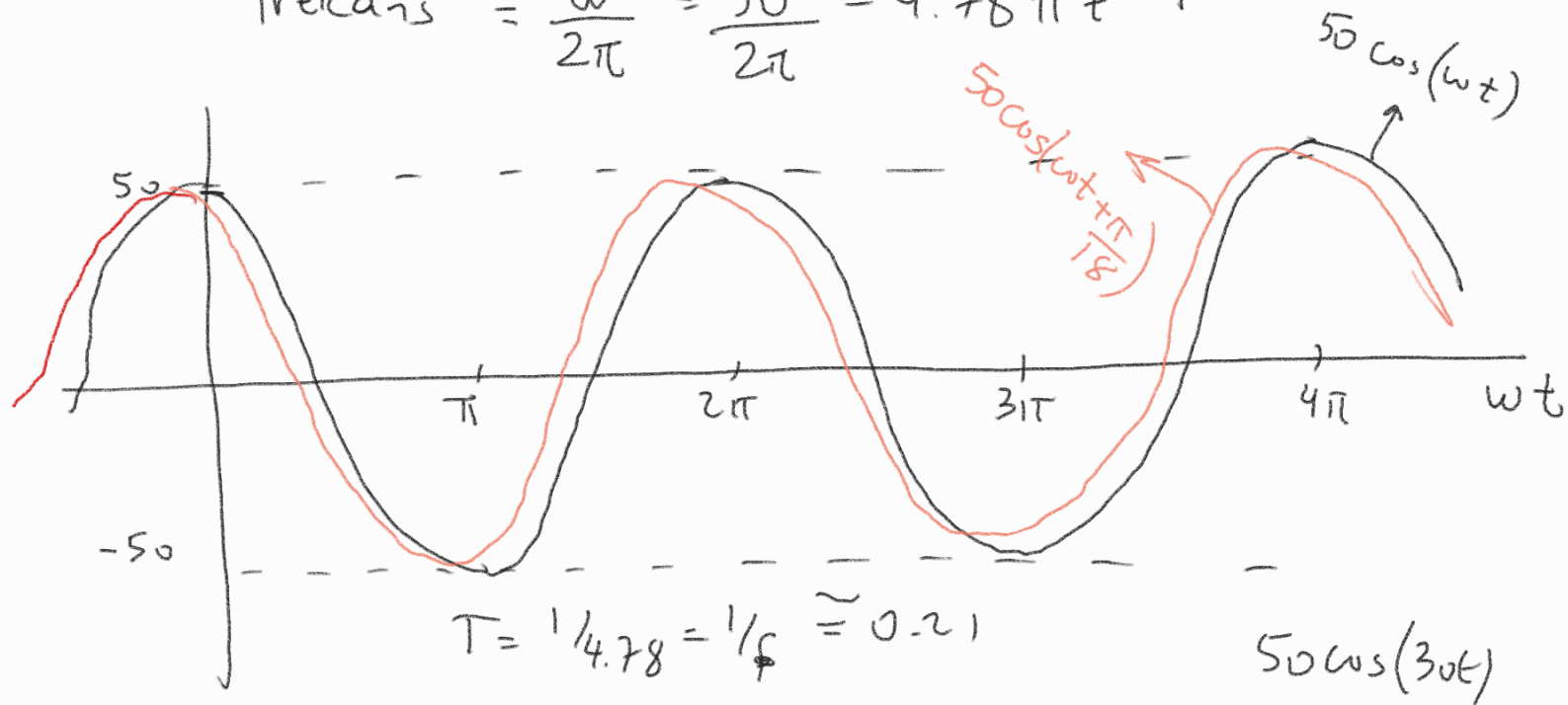• frekans = $\frac{\omega}{2\pi} = \frac{30}{2\pi} = 4.78 \text{ Hz} = f$



9.3

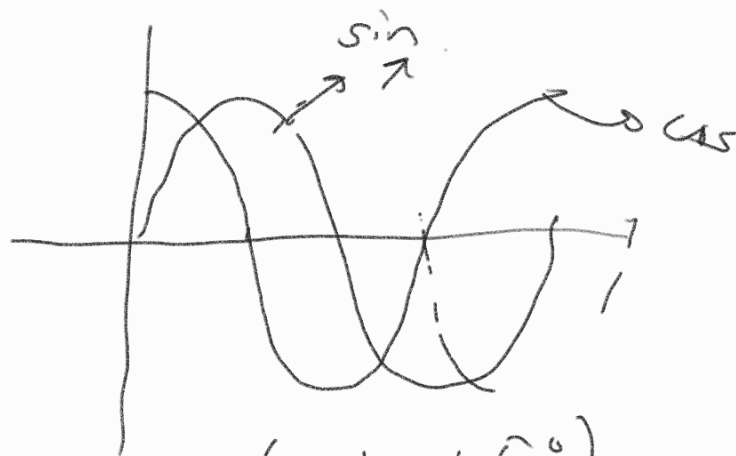a) $10 \sin(\omega t + 30^\circ) = 10 \cos(\omega t - 60^\circ)$



b) $-20 \sin(\omega t + 45^\circ)$
 $= -20 \cos(\omega t - 45^\circ)$

c) $-9 \sin(8t) = -9 \cos(8t - 90^\circ)$


$\cos(\omega t) = \sin(\omega t + 90^\circ)$

$\sin(\omega t) = \cos(\omega t - 90^\circ)$

9.5

$v_1 = 45 \sin(\omega t + 30^\circ)$
 $v_2 = 50 \cos(\omega t - 30^\circ)$
 $v_1 = 45 \cos(\omega t - 60^\circ)$

$60^\circ = \frac{T}{6}$

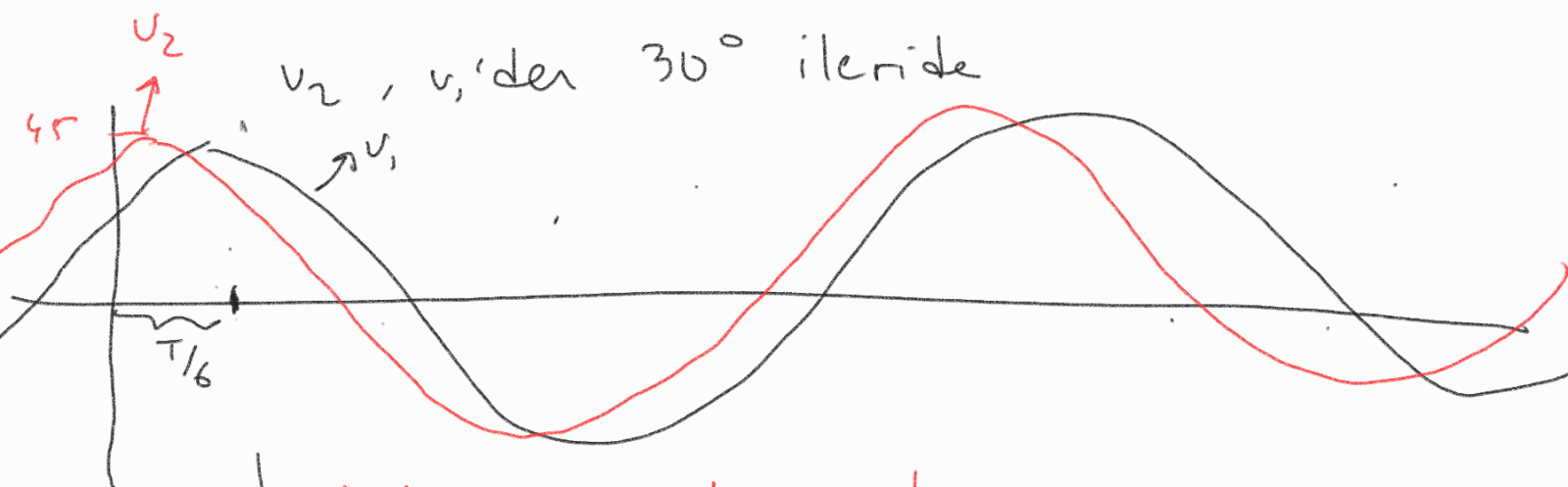

v_2 daha önce tepe değerine
ulaşıyor. O nedenle daha ileride.

13.6


c) $x(t) = 13 \cos(2t) + 5 \sin(2t)$
 $y(t) = 15 \cos(2t - 11.8^\circ)$

$$\cos(a+b) = \cos a \cos b - \sin a \sin b$$

$$\cos(a-b) = \cos a \cos b + \sin a \sin b$$

$$\sqrt{169 + 25} = \sqrt{194} \approx 13.82$$
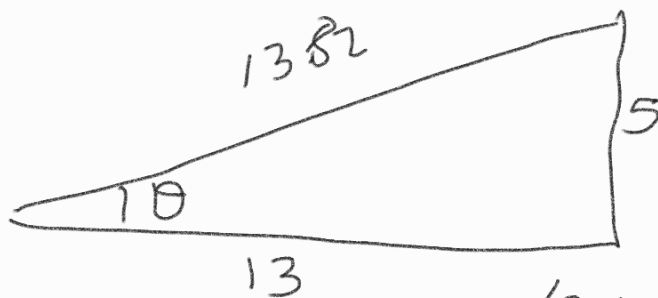
$$x(t) = 13.82 \times \left[\frac{13}{\underbrace{13.82}_{\cos \theta}} \cos(2t) + \frac{5}{\underbrace{13.8}_{\sin \theta}} \sin(2t) \right]$$



$$\theta \approx 21.04$$

$$x(t) = 13.82 \cos(2t - 21.04^\circ)$$

$$y(t) = 15 \cos(2t - 11.8^\circ) \rightarrow \text{daha ileride}$$

* sırasıyla, $x(t)$, $y(t)$ 'ye göre sağda

$y(t)$ solda
 $y(t)$ ileride.

9.11

a) $v(t) = 21 \cos(4t - 15^\circ)$

$$\overline{V} = 21 \angle -15^\circ$$

b) $i(t) = -8 \sin(10t + 70^\circ) \text{ mA}$

$$= -8 \cos(10t - 20^\circ) \text{ mA}$$

$$\overline{I} = -8 \angle -20^\circ \text{ mA}$$

$$= 8 \angle 160^\circ \text{ mA}$$

9.16 Transform the following sinusoids to phasors:

(a) $-20 \cos(4t + 135^\circ)$ (b) $8 \sin(20t + 30^\circ)$

(c) $20 \cos(2t) + 15 \sin(2t)$

12a, 17, 18a, 19a, 20, 22, 24a, 26, 27
30, 34, 39, 42, 43, 51, 55, 61, 62, 66, 72
80, 91, 93

9.18 Obtain the sinusoids corresponding to each of the following phasors:

→ (a) $V_1 = 60 \angle 15^\circ \text{ V}, \omega = 1$ $v_1 = 60 \cos(t + 15^\circ) \text{ V}$

(b) $V_2 = 6 + j8 \text{ V}, \omega = 40$ $v_2 = 10 \cos(40t + 53^\circ) \text{ V}$

(c) $I_1 = 2.8e^{-j\pi/3} \text{ A}, \omega = 377$ $i_1 = 2.8 \cos(377t - 60^\circ) \text{ A}$

(d) $I_2 = -0.5 - j1.2 \text{ A}, \omega = 10^3$ $i_2 = -1.3 \cos(1000t + 67.4^\circ) \text{ A}$
 $= 1.3 \cos(1000t - 112.6^\circ) \text{ A}$

9.17 Two voltages v_1 and v_2 appear in series so that their sum is $v = v_1 + v_2$. If $v_1 = 10 \cos(50t - \pi/3) \text{ V}$ and $v_2 = 12 \cos(50t + 30^\circ) \text{ V}$, find v .


$\bar{V}_1 = 10 \angle -60^\circ \text{ V}$ $\bar{V}_2 = 12 \angle 30^\circ \text{ V}$

$\bar{V} = \bar{V}_1 + \bar{V}_2 = 10 \cos(-60) + j 10 \sin(-60) + 12 \cos(30) + j 12 \sin(30)$

$(5 + 6\sqrt{3}) + j(-5\sqrt{3} + 6) = \bar{V}$
 $15.4 - j2.66$

$\bar{V} = 15.6 \angle -9.8^\circ \xrightarrow{\mathcal{P}^{-1}} v(t) = 15.6 \cos(50t - 9.8^\circ)$

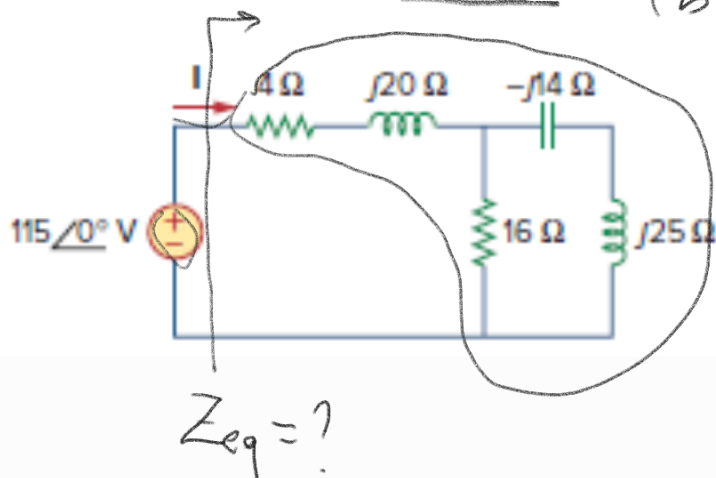9.39 For the circuit shown in Fig. 9.46, find Z_{eq} and use that to find current I . Let $\omega = 10$ rad/s.



(bu sonda derne
fazör alanında
verelimiz)

$$Z_{eq} = 4 + j20 + (16 \parallel j11)$$

$$= 4 + j20 + \frac{j176}{16 + j11}$$

$$= \frac{64 + j44 + j320 - 220 + j176}{16 + j11}$$

$$I_{eq} = \frac{-156 + j540}{16 + j11} = \frac{562 \angle 180 - 73.9^\circ}{19.4 \angle 34.5^\circ}$$

$\begin{matrix} 256 + 121 \\ 379 \end{matrix}$


$$= 29.0 \angle 71.6^\circ$$

$$I = \frac{115 \angle 0^\circ}{29 \angle 71.6^\circ} = 3.97 \angle -71.6^\circ$$

$$i(t) = 3.97 \cos(10t - 71.6^\circ) \text{ A}$$

9.42 Calculate $v_o(t)$ in the circuit of Fig. 9.49.

$$\omega = 200$$

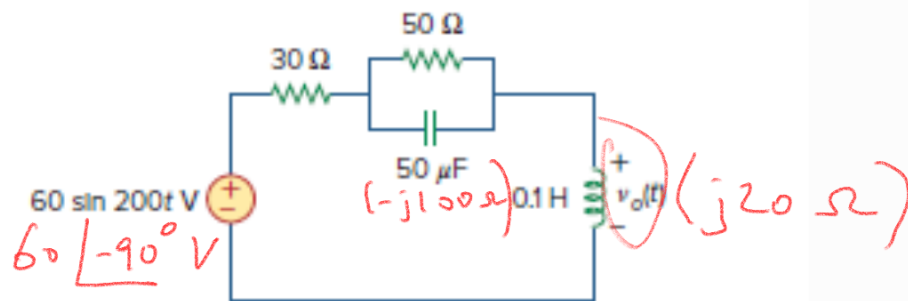

$$\frac{1}{j50 \times 10^{-6} \times 200}$$


$$\frac{100}{j}$$

$$-j100$$

Figure 9.49
For Prob. 9.42.

9.51 If the voltage v_o across the $2\text{-}\Omega$ resistor in the circuit of Fig. 9.58 is $90 \cos 2t$ V, obtain i_s .

$$\omega = 2$$

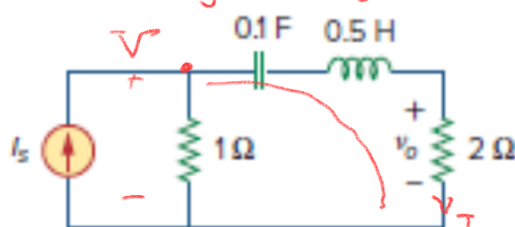

$$\bar{V}_o = 90 \text{ V}$$

Figure 9.58
For Prob. 9.51.

$$\bar{V} = 45 \angle 0^\circ (2 - j4)$$

$$\bar{I}_{1\Omega} = \frac{\bar{V}}{1\Omega} = 45 \angle 0^\circ (2 - j4)$$

$$\bar{I}_s = 45(2 - j4) + 45$$

$$= 90 - j180 + 45$$

$$= 135 - j180 = 225 \angle -53^\circ \text{ A}$$

$$i_s = 225 \cos(2t - 53^\circ) \text{ A}$$

9.43 Find current I_o in the circuit shown in Fig. 9.50.


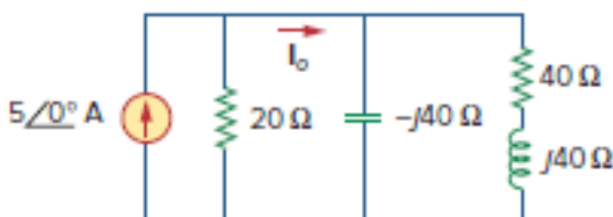


Figure 9.50
For Prob. 9.43.

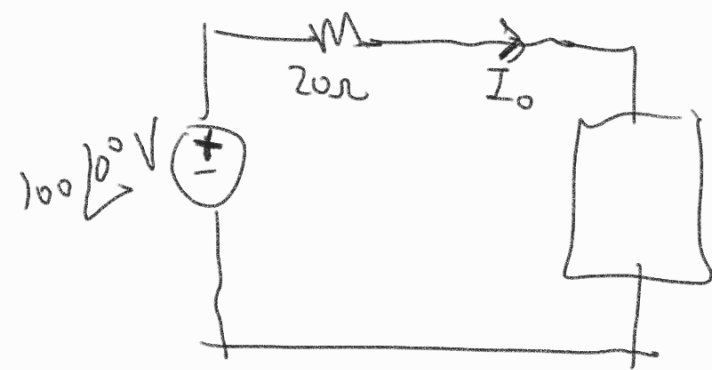

$$-j40 \parallel (40 + j40)$$

$$\frac{-j40(40 + j40)}{-j40 + 40 + j40}$$

$$= 40 - j40$$

$$I_0 = \frac{100 \angle 0^\circ}{20 + 40 - j40} = \frac{100 \angle 0^\circ}{60 - j40} = \frac{10}{\sqrt{52} \angle -\tan^{-1}(\frac{4}{6})}$$

$$I_0 = 13.9 \angle +33.7^\circ \text{ A}$$

9.55 Find Z in the network of Fig. 9.62, given that $V_o = 4 \angle 0^\circ \text{ V}$.

ML

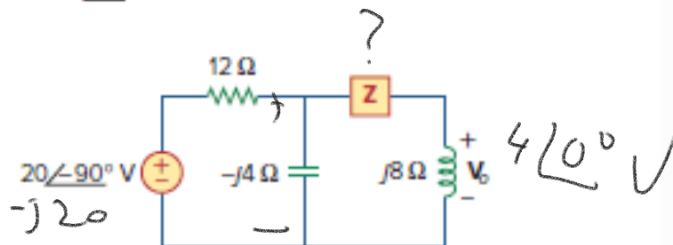


Figure 9.62
For Prob. 9.55.

$$\frac{-j20 (-j4 \parallel (Z + j8))}{12 + (-j4 \parallel (Z + j8))} \times \frac{j8}{Z + j8} = 4 \angle 0^\circ$$

$$j20 \frac{(-j4(Z + j8))}{-j4 + Z + j8}$$

$$\frac{12 + \frac{(-j4(Z + j8))}{-j4 + Z + j8}}{-j4 + Z + j8} \times \frac{j8}{Z + j8} = 4$$

$$j20 (-j4) (Z + j8)$$

$$\frac{Z + j8}{Z + j8}$$

$$12 + \frac{-j4(Z + j8)}{Z + j8}$$

$$\times \frac{j8}{Z + j8} = 4$$

$$\frac{80(\cancel{Z+j8})}{12Z+j48-j4Z+32} \times \frac{j8}{\cancel{Z+j8}} = 4$$

$$\frac{j640}{4} = (12-j4)Z + 32 + j48$$

$$\frac{j160 - 32 - j48}{12-j4} = Z$$

$$\boxed{\frac{-32 + j112}{12-j4} = Z}$$

9.61 Find Z_{eq} in the circuit of Fig. 9.68.

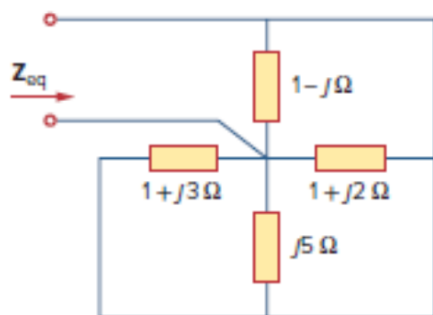


Figure 9.68
For Prob. 9.61.

$$Z_{eq} = (1-j) \parallel (1+j2) \parallel j5 \parallel (1+j3)$$

$$= \left(\frac{1}{1-j} + \frac{1}{1+j2} + \frac{1}{j5} + \frac{1}{1+j3} \right)^{-1}$$

$$= \left(\frac{1+j}{2} + \frac{1-j2}{5} - \frac{j}{5} + \frac{1-j3}{10} \right)^{-1}$$

$$= \left[\underbrace{5+j5} + \underbrace{2-j4} - \underbrace{j2} + \underbrace{1-j3} \right]^{-1}$$

$$= \left(\frac{8-j4}{10} \right)^{-1} = \frac{10}{8-j4} = \frac{10 \angle 0^\circ}{4\sqrt{5} \angle -26^\circ} = \frac{10}{4\sqrt{5}} \angle 26^\circ \Omega$$

9.91 Figure 9.91 shows a series combination of an inductance and a resistance. If it is desired to connect a capacitor in parallel with the series combination such that the net impedance is resistive at 10 kHz, what is the required value of C ?

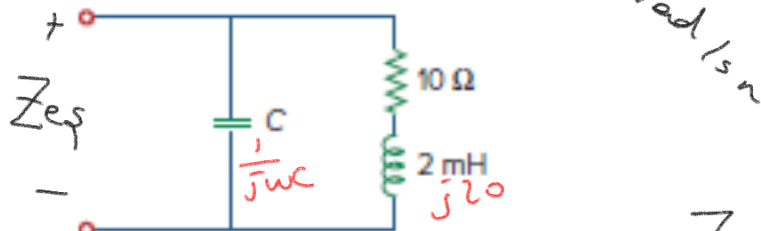


Figure 9.91
For Prob. 9.91.

$$Z_{es} \text{ resistive} \equiv Z_{es} \in \mathbb{R} \\ \text{Im}(Z_{es}) = 0$$

$$Z_{es} = \frac{1}{\frac{1}{j\omega C} + 10 + j20} = \frac{10 + j20}{1 + j10^5 C - 2 \times 10^5 C}$$

$$= \frac{(10 + j20)(1 - 2 \times 10^5 C - j10^5 C)}{(1 - 2 \times 10^5 C)^2 + (10^5 C)^2}$$

$$= \frac{-10 - 2 \times 10^6 C - j10^6 C + j20 - j4 \times 10^6 C + 2 \times 10^6 C}{\text{Payla}}$$

$$-10^6 C + 20 - 4 \times 10^6 C = 0$$

$$20 = 5 \times 10^6 C \Rightarrow C = \frac{20}{5 \times 10^6} = 4 \mu\text{F}$$

9.62 For the circuit in Fig. 9.69, find the input impedance Z_{in} at 10 krad/s.

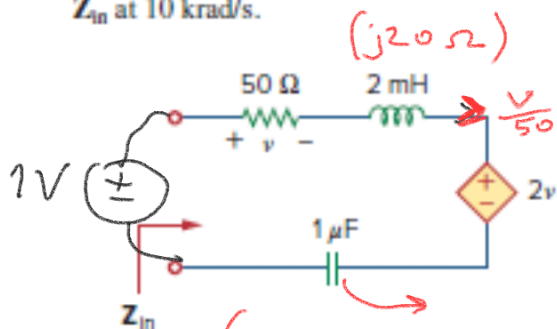


Figure 9.69
For Prob. 9.62.

$$\left(\frac{1}{j10^6 \times 10^{-6}} = -j100 \Omega \right)$$

$$1 = V + j20 \times \frac{V}{50} + 2V - j100 \times \frac{V}{50}$$

$$1 = V \left[1 + j0.4 + 2 - j2 \right]$$

$$V = \frac{1}{3-j1.6} \text{ Volt}$$

$$Z_{in} = \frac{1V}{I_{in}} = \frac{1}{\sqrt{150}} = \frac{50}{V} = 50(3-j1.6) = 150-j80 \Omega //$$

9.66 For the circuit in Fig. 9.73, calculate Z_T and V_{ab} .

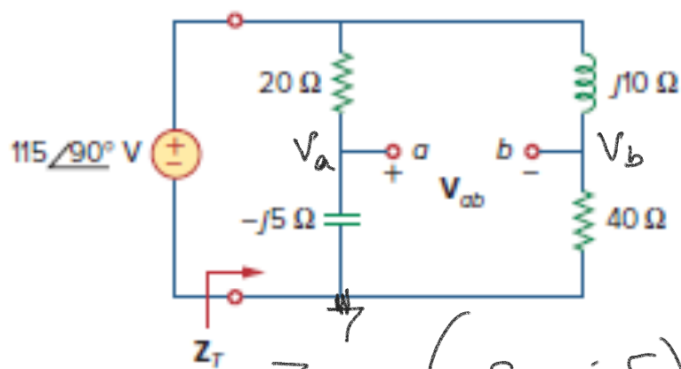



Figure 9.73
For Prob. 9.66.

$$\begin{aligned} Z_T &= (20-j5) // (40+j10) \\ &= \frac{(20-j5)(40+j10)}{60+j5} = \frac{(4-j)(40+j10)}{12+j1} \end{aligned}$$

$$\begin{aligned} \bar{V}_{ab} &= \bar{V}_a - \bar{V}_b \\ &= 115 \angle 90^\circ \left(\frac{-j5}{20-j5} - \frac{40}{40+j10} \right) \\ &= 115 \angle 90^\circ \frac{-j200 + 50 - 800 + j200}{(20-j5)(40+j10)} \\ &= 115 \angle 90^\circ \frac{-750}{800 + j200 - j200 + 50} = \frac{j115 \times (-750)}{850} \\ &= -j101.5 \text{ V} // \end{aligned}$$



For Prob. 9.72,

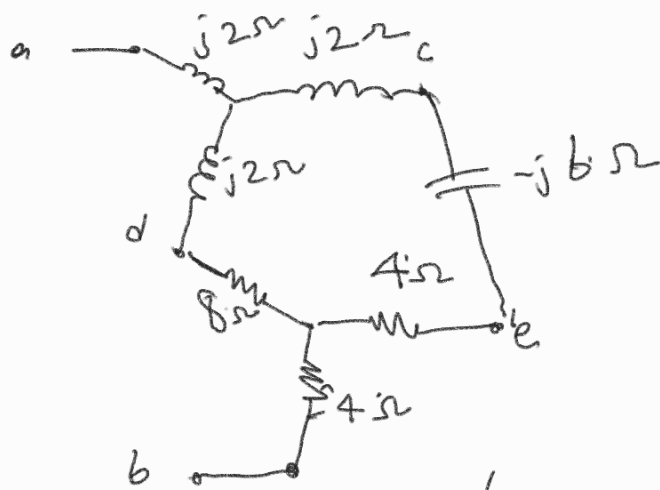

$$Z_{ab} = j^2 + 4 + \left((j^2 + 8) // (-j^4 + 4) \right)$$

$$= 4 + j2 + \frac{(8 + j2)(4 - j4)}{}$$

$$= 4 + j2 + \frac{3 \frac{12 - j2}{2 - j32 + j8} + 8}{12 - j2} = 4 + j2 + \frac{40 - j24}{12 - j2}$$

$$= \frac{48 + \cancel{j24} - j8 + 4 + 40 - \cancel{j24}}{12 - j2} = \frac{92 - j8}{12 - j2} = \frac{46 - j4}{6 - j}$$

$$\approx 46.2^\circ$$

6.08 | 9.5°

$$\approx 7.6 \text{ (4.5}^\circ \text{)} \sim$$

$$\frac{(-j9) \times (-j18)}{-j273} = -j6$$

$$\frac{j6 \times j6}{j18} = j2$$

$$\frac{20 \times 20}{20 + 20 + 10} = 8$$

$$\frac{20 \times 10}{50} = 4$$

9.80 Consider the phase-shifting circuit in Fig. 9.83. Let $V_i = 120$ V operating at 60 Hz. Find:

- V_o when R is maximum
- V_o when R is minimum
- the value of R that will produce a phase shift of 45°

$$f = 60 \text{ Hz}$$

$$\omega = 120\pi \text{ rad/s}$$

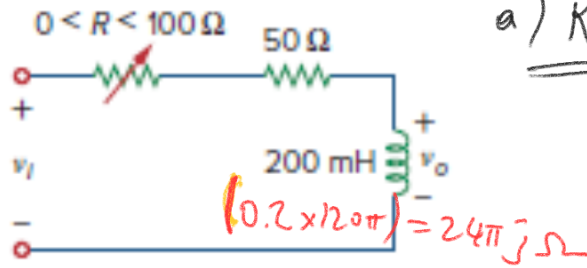


Figure 9.83

a) $R = 0$:

$$\bar{V}_o = \frac{j24\pi}{50 + j24\pi} \times 120$$

$$= \frac{j75 \times 120}{50 + j75}$$

$$= \frac{j360}{2 + j3} = \frac{360 \angle 90^\circ}{\sqrt{13} \angle 56.3^\circ}$$

$$\bar{V}_o = \frac{360}{\sqrt{13}} \angle 33.7^\circ \text{ V}$$

b) $R = 100$:

$$\bar{V}_o = 120 \times \frac{j75}{j75 + 150}$$

$$= 120 \times \frac{j}{2 + j}$$

$$\bar{V}_o = \frac{120 \angle 90^\circ}{\sqrt{5} \angle 26^\circ} = \frac{120}{\sqrt{5}} \angle 64^\circ \text{ V}$$

c) 45° için R ?

$$120 \frac{j75}{R + 50 + j75} = \bar{V}_o \rightarrow \text{fazının } 45^\circ \text{ olması}$$

$$R + 50 + j75 \rightarrow 45^\circ \text{ olması}$$

Yani, $R + 50 = 75$ olması

$$R = 25 \text{ olması}$$

9.93 A power transmission system is modeled as shown in Fig. 9.92. Given the source voltage and circuit elements

$V_s = 115 \angle 0^\circ \text{ V}$, source impedance

$Z_s = (1 + j0.5) \Omega$, line impedance

$Z_\ell = (0.4 + j0.3) \Omega$, and load impedance

$Z_L = (23.2 + j18.9) \Omega$, find the load current I_L .

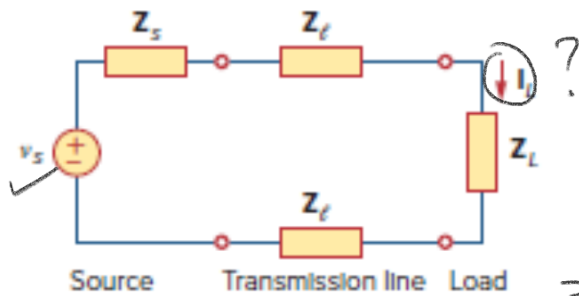


Figure 9.92
For Prob. 9.93.

$$\frac{115 \angle 0^\circ}{Z_s + 2Z_\ell + Z_L}$$

$$1 + j0.5 + 0.8 + j0.6 + 23.2 + j18.9$$

$$= \frac{115 \angle 0^\circ}{25 + j20} = \frac{23 \angle 0^\circ}{5 + j4} = \frac{23 \angle 0^\circ}{\sqrt{41} \angle 39^\circ}$$

$$\bar{I}_L = 3.6 \angle -39^\circ \text{ A}$$

Chapter 10: SINÜSOİDAL YATISKIN DURUM ANALİZİ

D.G.Y, Ç.A.Y, Süperpozisyon, Kaynak Dönüştürme, Thevenin, Norton, OP-AMP, Bazı uygulamalar.

10.7 Use nodal analysis to find V in the circuit of Fig. 10.56.

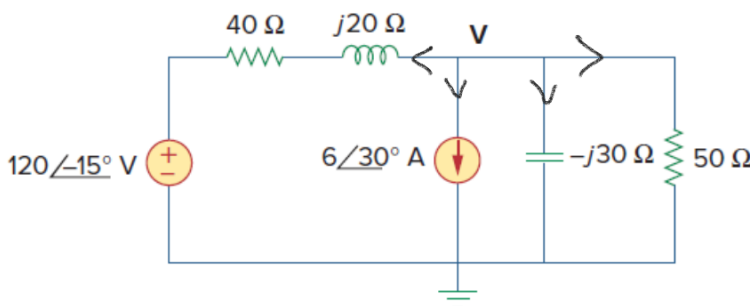


Figure 10.56
For Prob. 10.7.

$$\frac{V - 120 \angle -15^\circ}{40 + j20} + 6 \angle 30^\circ + \frac{V}{-j30} + \frac{V}{50} = 0$$

$$V \left(\frac{1}{40 + j20} + \frac{1}{-j30} + \frac{1}{50} \right) = \frac{6 \angle -15^\circ}{2 + j} - 6 \angle 30^\circ$$

$$\frac{V}{10} \left(\frac{1}{4+j2} + \frac{3+j5}{15} \right) = \frac{6 \angle -15^\circ}{\sqrt{5} \angle 26^\circ} - 6 \angle 30^\circ$$

$$V \frac{15+12+j20+j6-10}{(4+j2)150} = \frac{6}{\sqrt{5}} \angle -41^\circ - 6 \angle 30^\circ$$

10.10 Use nodal analysis to find v_o in the circuit of Fig. 10.59. Let $\omega = 2 \text{ krad/s}$.



ML

$$\frac{1}{j2 \times 10^{-6}} \times 2 \times 10^{-3} =$$

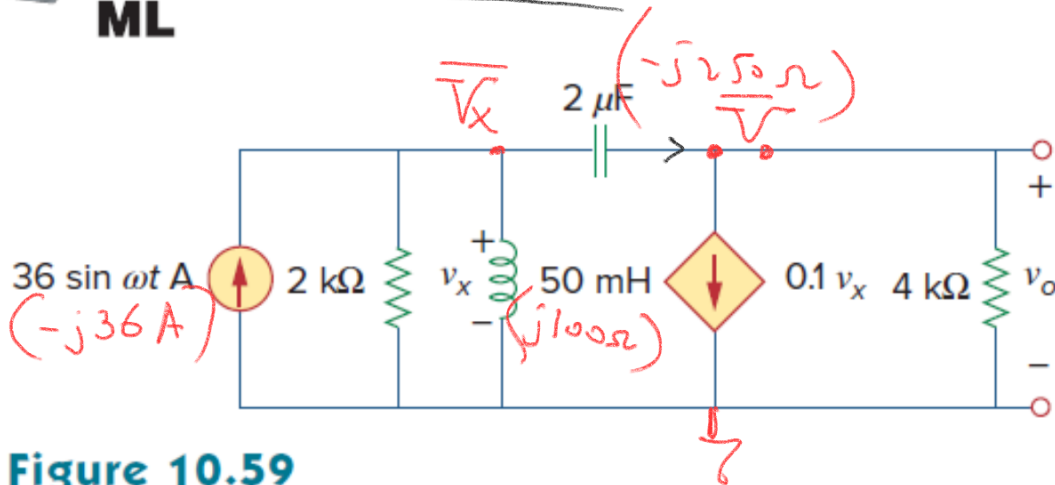


Figure 10.59

For Prob. 10.10.

$$-j36 = \frac{V_x}{2000} + \frac{V_x}{j100} + \frac{V_x - V_o}{-j250} \quad (1)$$

$$\frac{V_x - V_o}{-j250} = 0.1 V_x + \frac{V_o}{4000} \quad (2)$$

$$(1) -j36 = \frac{V_x}{2000} - \frac{jV_x}{2000} + \frac{j8V_x - j8V_o}{2000}$$

$$-j72000 = V_x(1+j7) - j8V_o \quad (1)$$

$$j16 V_x - j16 V_o = 400 V_x + V_o$$

$$(-400+j16) V_x = (1+j16) V_o \quad (2) \quad V_x = V_o \frac{1+j16}{-400+j16}$$


$$V_x \approx \frac{j16}{-400} V_o$$

$$-j72000 = \left(\frac{j16(1+j7)}{-400} - j8 \right) V_o$$

$$-j72000 = \frac{j16 - 112 + j3200}{-400} V_o$$

$$\frac{j72000 \times 400}{j3200} \approx V_o \quad V_o \approx 9000 V$$

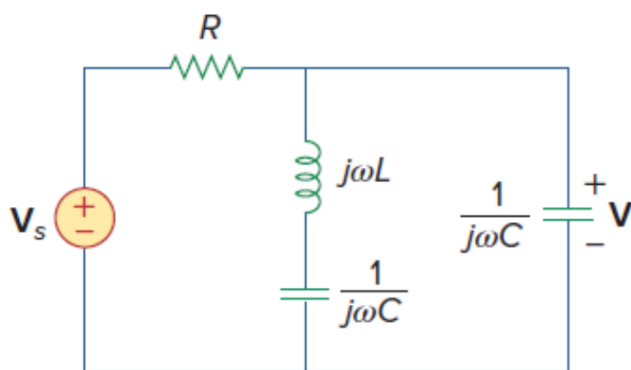10.23 Using nodal analysis obtain V in the circuit of Fig. 10.72.



$$V = \frac{V_s}{a + bj}$$

$a?$

$b?$

Figure 10.72

For Prob. 10.23.

10.39 Find I_1 , I_2 , I_3 , and I_x in the circuit of Fig. 10.84.



ML

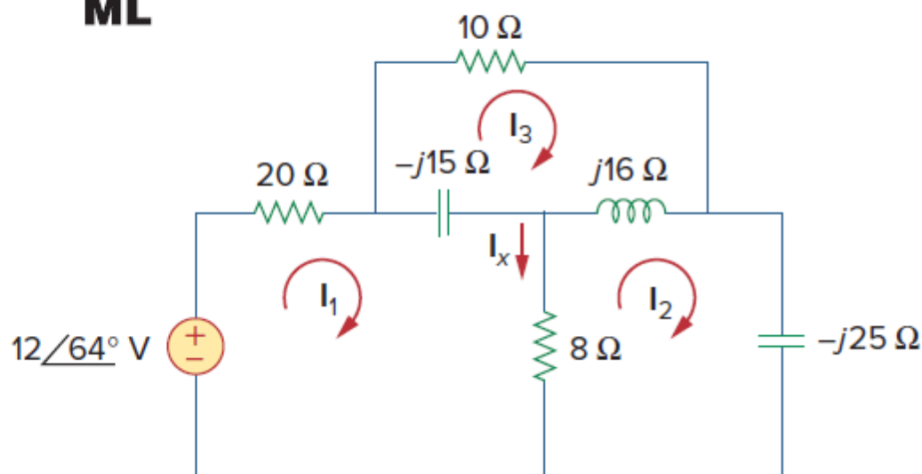


Figure 10.84

For Prob. 10.39.

$$(1) -12 \angle 64^\circ + 20 I_1 - j15(I_1 - I_3) + 8(I_1 - I_2) = 0$$


$$(2) 8(I_2 - I_1) + j16(I_2 - I_3) - j25 I_2 = 0$$

$$(3) 10 I_3 + j16(I_3 - I_2) - j15(I_3 - I_1) = 0$$

$$\underbrace{\begin{bmatrix} 28-j15 & -8 & j15 \\ -8 & 8-j9 & -j16 \\ j15 & -j16 & 10+j \end{bmatrix}}_{\bar{A}} \underbrace{\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}}_{\bar{I}} = \underbrace{\begin{bmatrix} 12 \angle 64^\circ \\ 0 \\ 0 \end{bmatrix}}_{\bar{b}}$$

$$\left. \begin{aligned} \bar{A} \times \bar{I} &= \bar{b} \Rightarrow \bar{I} = \text{inv}(\bar{A}) \times \bar{b} \\ \bar{I} &= \bar{A} \backslash \bar{b} \end{aligned} \right\} \text{Matlab}$$

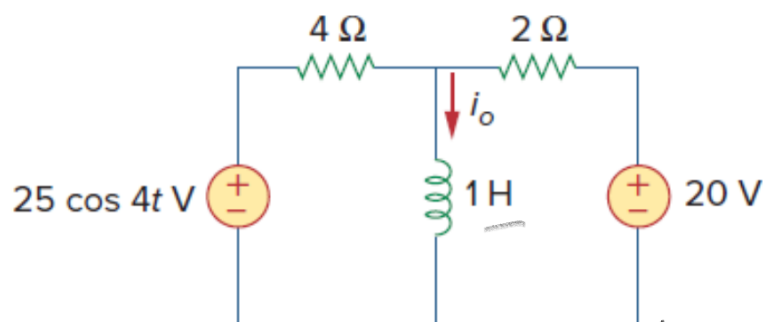
10.40 Find i_o in the circuit shown in Fig. 10.85 using superposition.



$$i_o = i_o' + i_o''$$

Figure 10.85
For Prob. 10.40.

i) i_o' ? ($25 \cos 4t$ is in)

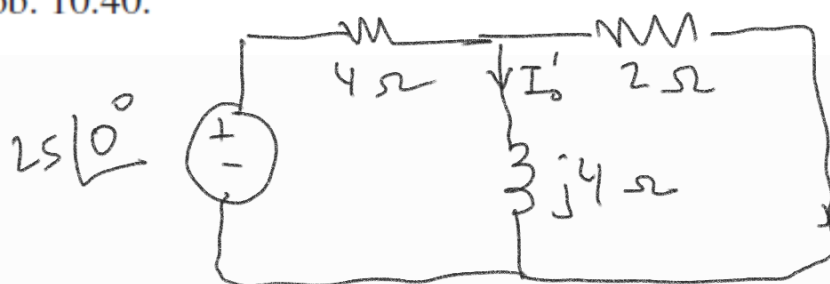

$$I_o' = \frac{25 \times (2 \parallel j4)}{4 + (2 \parallel j4)} \times \frac{2}{2 + j4}$$

$$= 25 \times \frac{j8}{2 + j4} \times \frac{2}{2 + j4}$$

$$= \frac{j200}{8 + j16 + j8} \times \frac{2}{2 + j4}$$


$$= \frac{j200}{8 + j24} \times \frac{2}{2 + j4} = \frac{j200}{(8 + j24)(1 + j2)} \times \frac{2}{(1 + j3)(1 + j2)}$$

$$= \frac{j25}{1 + j2 + j3 - 6} = \frac{25 \angle 90^\circ}{-5 + j5} = \frac{25 \angle 90^\circ}{5\sqrt{2} \angle 135^\circ}$$

$$I_o' = \frac{5}{\sqrt{2}} \angle -45^\circ$$

$$i_o'(t) = \frac{5}{\sqrt{2}} \cos(4t - 45^\circ) \text{ A}$$

ii) i_o'' ? (20 V DC)
 $\omega = 0$

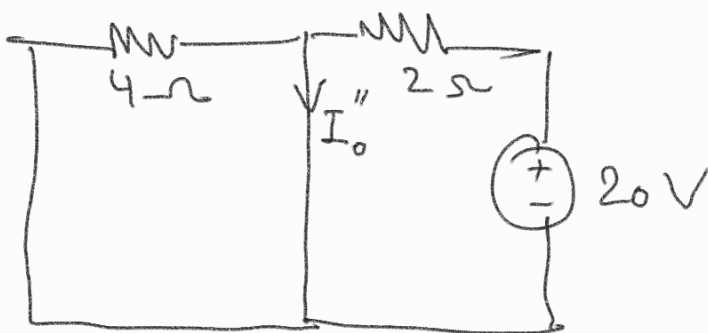


$$\Rightarrow I_o'' = \frac{20}{2} = 10 \text{ A DC}$$

$$i_o''(t) = 10 \text{ A}$$

$$i_o(t) = 10 + \frac{5}{\sqrt{2}} \cos(4t - 45^\circ) \text{ A}$$

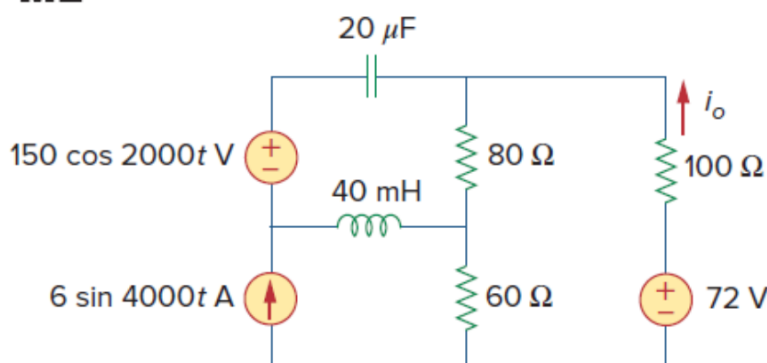10.48 Find i_o in the circuit of Fig. 10.93 using superposition.




$$\hat{i}_o = \hat{i}_o' + \hat{i}_o'' + \hat{i}_o'''$$

Figure 10.93

For Prob. 10.48.

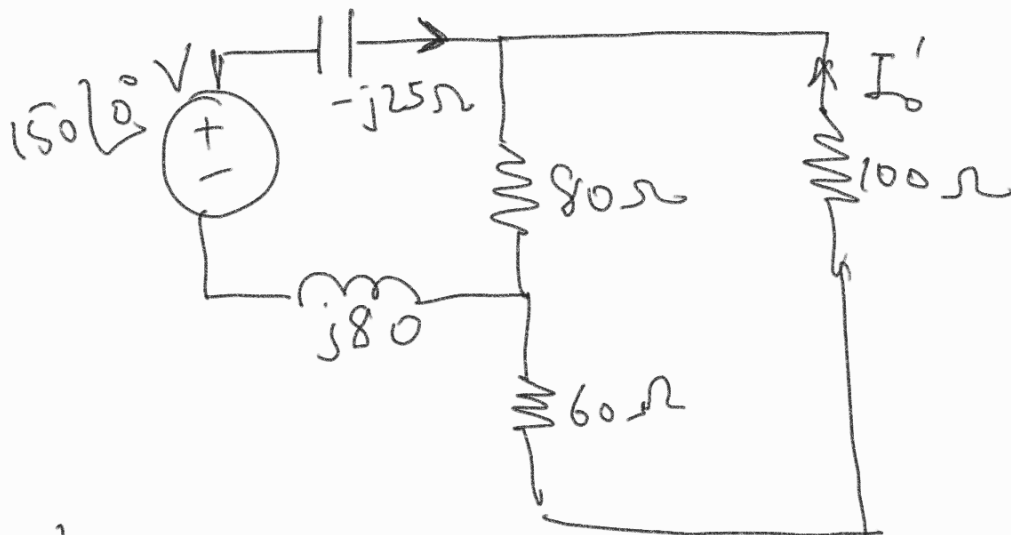i) $150 \cos 2000t$ V i.e. $\omega = 2000 \text{ rad/s}$




$$\frac{1}{j20 \times 10^3 \times 2 \times 10^3} = \frac{1000}{j40}$$

$$I_o' = \frac{150}{\frac{160}{3} + j55} \times \frac{-1}{3} = \frac{-50}{\frac{160}{3} + j55} = \frac{-10}{\frac{32}{3} + j11} \approx \frac{-10}{11\sqrt{2} \angle 45^\circ}$$

$$i_o'(t) = \frac{-10}{11\sqrt{2}} \cos(2000t - 45^\circ) \text{ A}$$

$$= \frac{10}{11\sqrt{2}} \cos(2000t + 135^\circ) \text{ A}$$

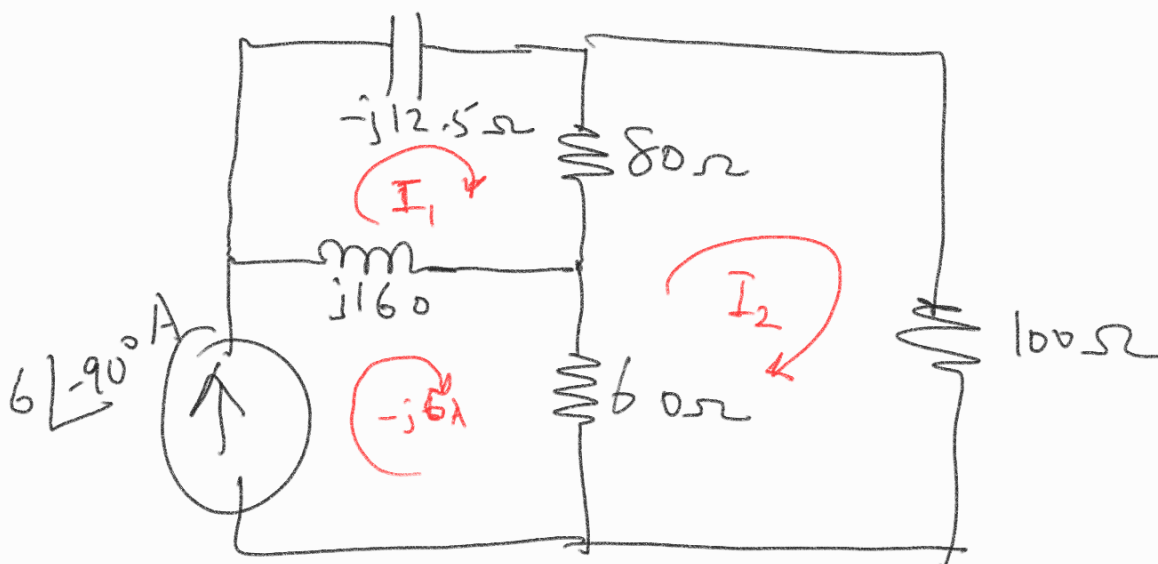ii) $6 \sin 4000t$ A i.e. $\omega = 4000 \text{ rad/s}$



$$\frac{1}{j4 \times 10^3 \times 20 \times 10^3} = \frac{1000}{80}$$

$$-j12.5 I_1 + 80(I_1 - I_2) + j160(I_1 + j6) = 0 \quad (1)$$

$$80(I_2 - I_1) + 100 I_2 + 60(I_2 + j6) = 0 \quad (2)$$


$$\begin{aligned}
 3 \times \left((80 + j147.5) I_1 - 80 I_2 = 960 \right) \\
 + \quad -80 I_1 + 240 I_2 = -j360
 \end{aligned}$$

$$(160 + j442.5) I_1 = 2880 - j360$$

buradan I_1 ve I_2 bulunur.

$$i_o'' = -I_2$$

ii) 72V DC için

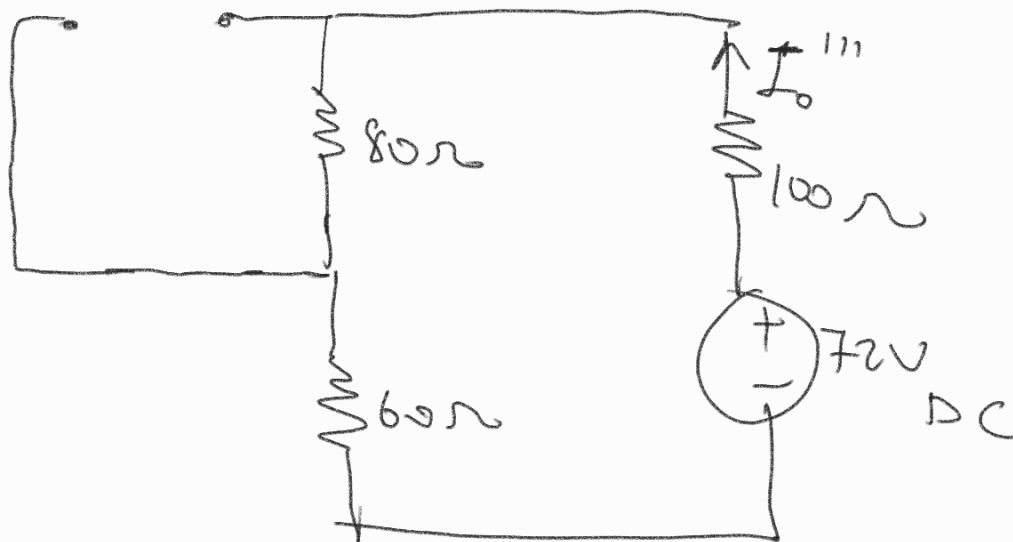

$$I_o''' = \frac{72}{740} = 0.3 \text{ A DC}$$

10.49 Using source transformation, find i in the circuit of Fig. 10.94.

$$\omega = 20 \text{ rad/s}$$


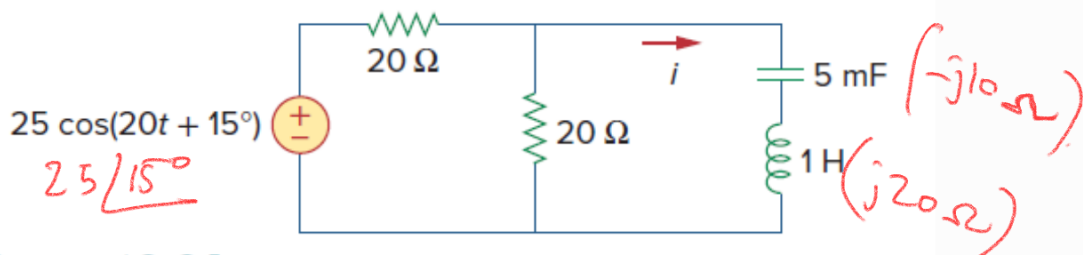


Figure 10.94

For Prob. 10.49.

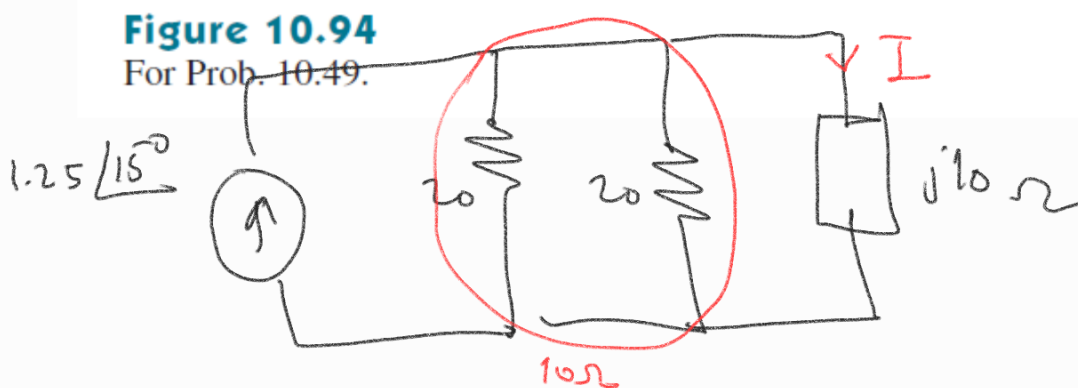

$$\frac{1}{j20 \times 5 \times 10^{-3}} = \frac{1}{100}$$

$$I = \frac{1.25 \angle 15^\circ \times 10}{10 + j10} = \frac{1.25 \angle 15^\circ}{\sqrt{2} \angle 45^\circ}$$

$$i(t) = \frac{1.25}{\sqrt{2}} \cos(20t - 30^\circ) \text{ A}$$

10.58 For the circuit depicted in Fig. 10.101, find the Thevenin equivalent circuit at terminals $a-b$.


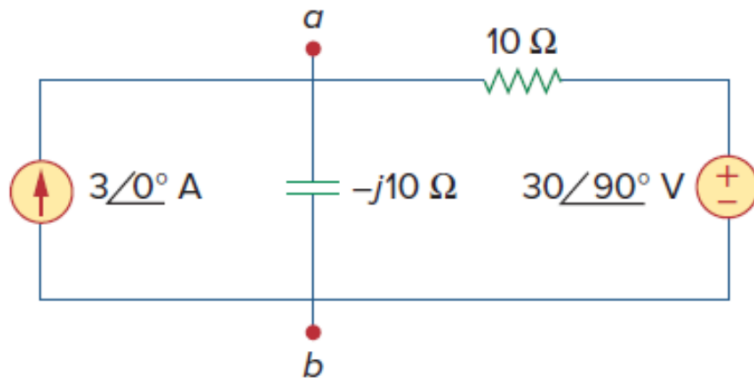


Figure 10.101

For Prob. 10.58.

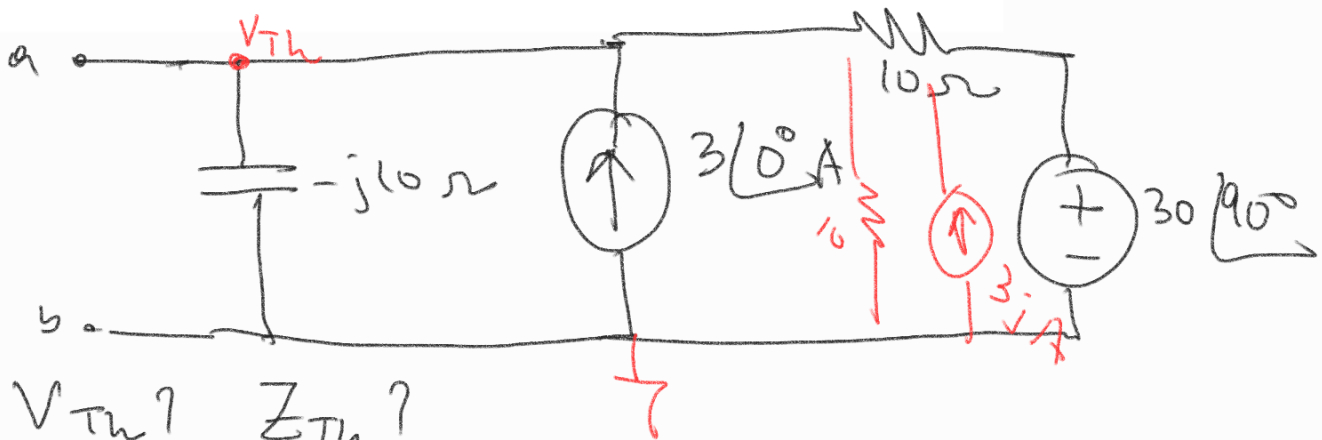

V_{Th} ? Z_{Th} ?


$$V_{Th} = V_{ad} = V_{ab}$$

Z_{Th} : kaynakları sıfırlayarak

$$Z_{Th} = -j10 // 10 = \frac{-j100}{10 - j10} = \frac{-j10}{1 - j} = \frac{10 \angle -90^\circ}{\sqrt{2} \angle -45^\circ} = 5\sqrt{2} \angle -45^\circ \Omega$$

$$Z_{Th} = 5 - j5 \Omega$$


V_{Th} : kaynak dönüşümü

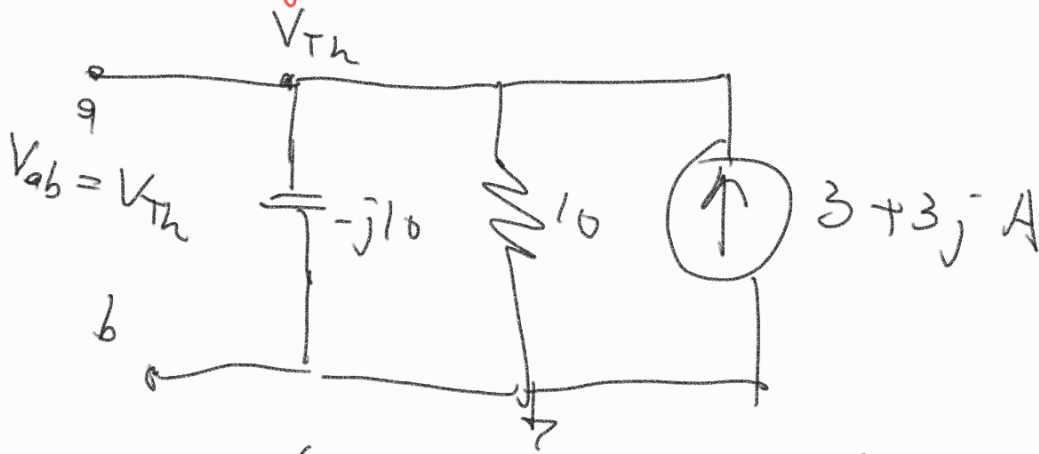

$$V_{Th} = (3 + 3j) \times (10 \parallel -j10)$$

$$= (3 + 3j) \times \frac{-j100}{10 - j10} = \frac{(3 + 3j)(-j10)}{1 - j}$$
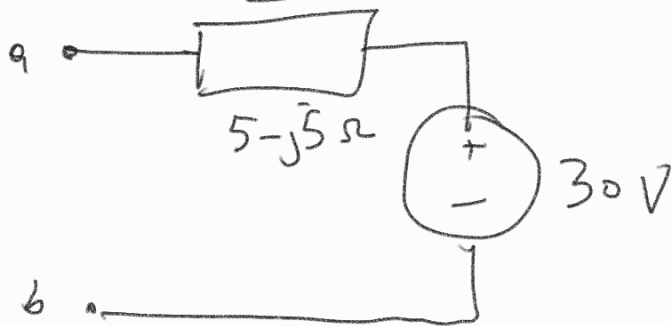
$$\frac{3\sqrt{2} \angle 45^\circ \times 10 \angle -90^\circ}{\sqrt{2} \angle -45^\circ} = 30 = V_{Th}$$



10.61 Find the Thevenin equivalent at terminals $a-b$ of the circuit in Fig. 10.104.



ML

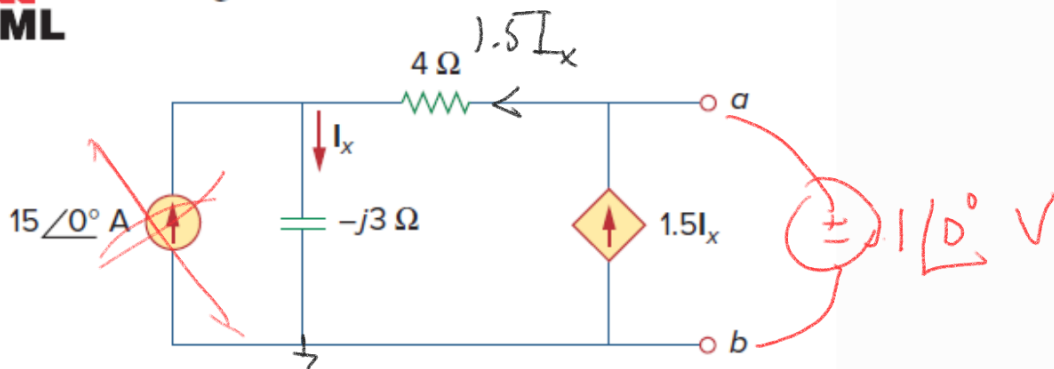


Figure 10.104

For Prob. 10.61.

$$V_{ab} = V_{Th}$$


$$15 + 1.5 I_x = I_x \Rightarrow$$

$$I_x = -30 \angle 0^\circ \text{ A}$$

$$V_{ab} = -j3 \times I_x + 4 \times 1.5 I_x = (6-j3) I_x = -30(6-j3)$$


$$V_{Th} = -90\sqrt{5} \angle -26^\circ \text{ V}$$
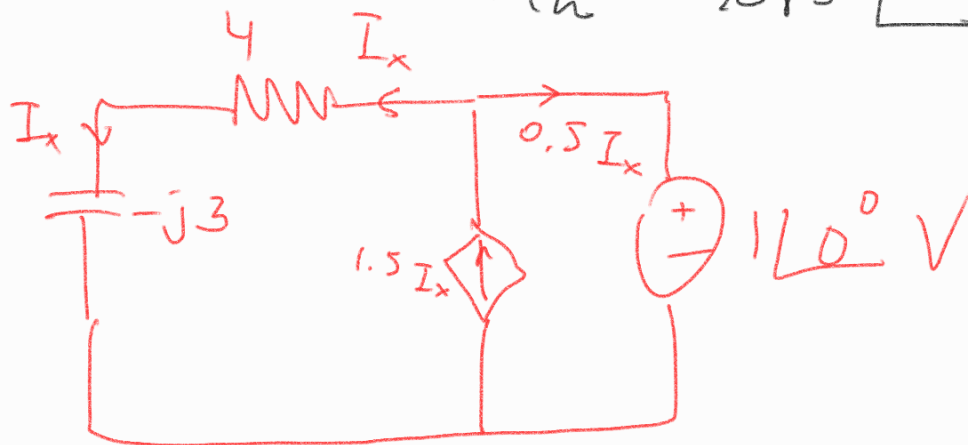
$$V_{Th} = 90\sqrt{5} \angle 154^\circ \text{ V}$$




$$(4-j3) I_x = 1$$
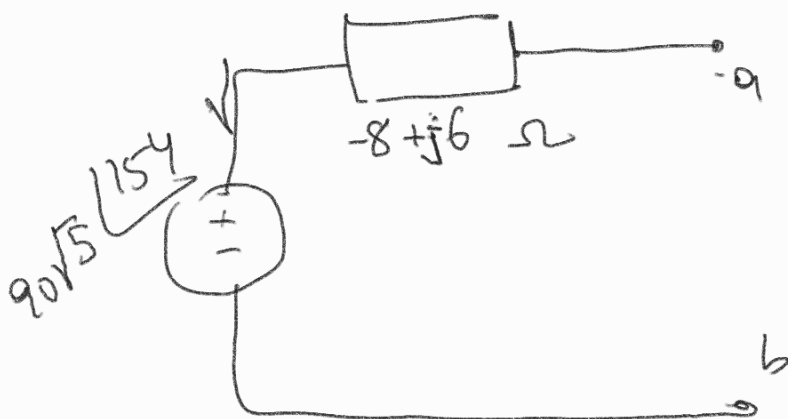
$$Z_{Th} = \frac{1 \angle 0^\circ}{-0.5 I_x} = \frac{(4-j3) I_x}{-0.5 I_x} = -8+j6 \Omega$$



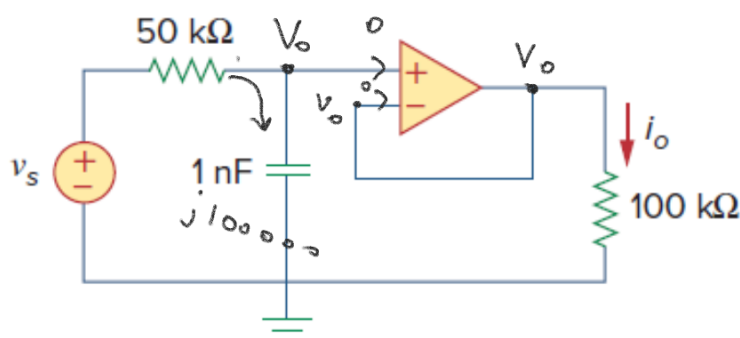10.72 Compute $i_o(t)$ in the op amp circuit in Fig. 10.115 if $v_s = 4 \cos(10^4 t) \text{ V}$. $\omega = 10000$



$$\frac{1}{j10^4 \times 10^{-9}}$$

Figure 10.115


For Prob. 10.72.

$$\begin{aligned}
 I_o &= 4 \angle 0^\circ \times \frac{-j100000}{50000 - j100000} \times \frac{1}{100000} \\
 &= \frac{4 \angle -90^\circ}{5 \times 10^4 \sqrt{5} \angle -64^\circ} = \frac{4}{5\sqrt{5}} \times 10^{-4} \angle -26^\circ \text{ A} \\
 &= 0.36 \times 10^{-4} \angle -26^\circ \text{ A} \\
 i_o(t) &= 36 \cos(10^4 t - 26^\circ) \mu\text{A}
 \end{aligned}$$

9.51 The circuit shown in Fig. P9.51 is operating at a frequency of 10 rad/s. Assume α is real and lies between -10 and $+10$, that is, $-10 \leq \alpha \leq 10$.

- Find the value of α so that the Thévenin impedance looking into the terminals a,b is purely resistive.
- What is the value of the Thévenin impedance for the α found in (a)? (I_m kism, sifir)
- Can α be adjusted so that the Thévenin impedance equals $500 - j500 \Omega$? If so, what is the value of α ?
- For what values of α will the Thévenin impedance be inductive? (I_m kism, positif)

Figure P9.51

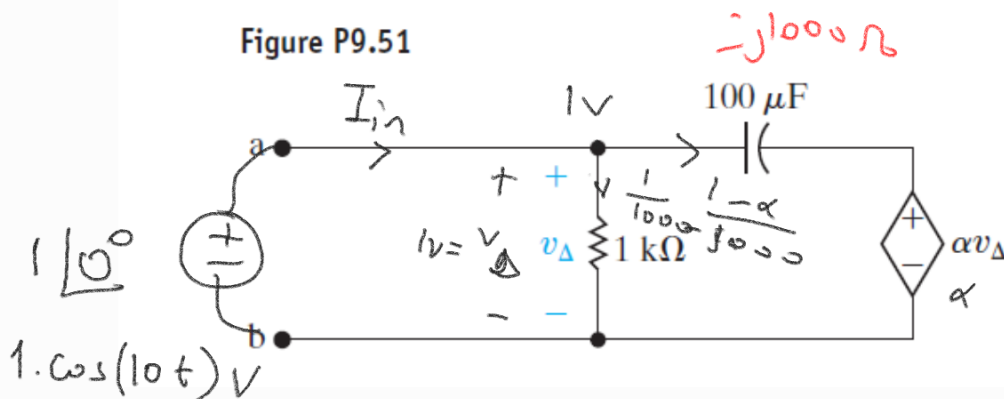

$$I_{in} = \frac{1}{1000} + \frac{1-\alpha}{j1000}$$

$$I_{in} = \frac{1 + j(1-\alpha)}{1000} \Rightarrow Z_{Th} = \frac{1}{I_{in}} = \frac{1000}{1 + j(1-\alpha)}$$

$\alpha = 1$ olursa $Z_{Th} \in \mathbb{R}$

b) bu durumda $Z_{Th} = 1000 \Omega$
 $(\alpha = 1)$

c) $500 - j500 = \frac{1000}{1 + j(1-\alpha)}$

$\alpha = 0$ olursa

$Z_{Th} = \frac{1000}{1 + j} = \frac{1000(1-j)}{2} = 500 - j500$

d) $\text{Im} \left\{ \frac{1000}{1 + j(1-\alpha)} \right\} > 0$ için

$\text{Im} \left\{ \frac{1000(1-j(1-\alpha))}{1 + (1-\alpha)^2} \right\} = \frac{-1000(1-\alpha)}{1 + (1-\alpha)^2}$

$\alpha > 1$ olmalı

> 0

10.75 In the op amp circuit of Fig. 10.118, find the closed-loop gain and phase shift of the output voltage with respect to the input voltage if $C_1 = C_2 = 1 \text{ nF}$, $R_1 = R_2 = 100 \text{ k}\Omega$, $R_3 = 20 \text{ k}\Omega$, $R_4 = 40 \text{ k}\Omega$, and $\omega = 2000 \text{ rad/s}$.

$C_1 = C_2 = 1 \text{ nF}$

$\frac{1}{j\omega C} = \frac{1}{j \times 2 \times 10^3 \times 10^{-9}}$
 $= -j 5 \times 10^5$

$\frac{\bar{V}_o}{\bar{V}_s} = ?$

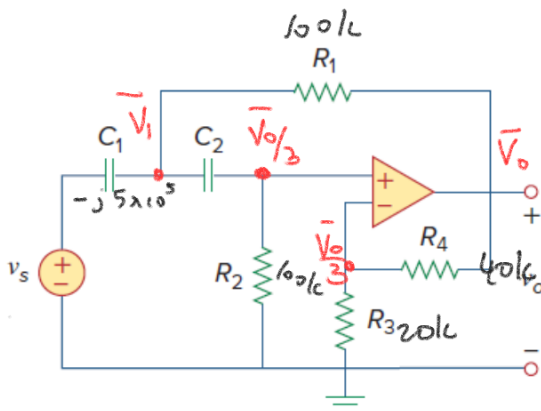


Figure 10.118
 For Prob. 10.75.

① $\frac{V_1 - V_s}{-j 500000} + \frac{V_1 - V_o}{100000} + \frac{V_1 - V_o/3}{-j 500000} = 0$

② $\frac{V_1 - V_o/3}{-j 500000} = \frac{V_o/3}{100000}$

$$(1) \quad jV_1 - jV_s + 5V_1 - 5V_o + jV_1 - j\frac{V_o}{3} = 0$$

$$(5+2j)V_1 - (5+j\frac{1}{3})V_o = jV_s \leftarrow$$

$$(2) \quad V_1 - \frac{V_o}{3} = -j\frac{5}{3}V_o \Rightarrow 3V_1 - V_o = -j5V_o$$

$$V_1 = \frac{1-j5}{3}V_o$$

$$(5+2j)\frac{(1-j5)}{3}V_o - (5+j\frac{1}{3})V_o = jV_s$$

$$\frac{(5+2j)(1-j5)}{3}V_o - 15-j V_o = jV_s$$

$$\frac{V_o}{V_s} = \frac{3j}{(5+2j)(1-j5)-15-j} = \frac{3j}{5-j15+2j+10-15-j} = \frac{3j}{-j24} = -1/8$$

$$\frac{V_o}{V_s} = -1/8$$


$$|Kazancı| = 1/8$$

Not: $\omega \rightarrow \infty : V_1 \rightarrow V_s : V_o \rightarrow 3V_s$

$$|Kazancı| \rightarrow 3$$

$\omega \rightarrow 0 : V \rightarrow 0 : V_o \rightarrow 0$

$$|Kazancı| \rightarrow 0$$

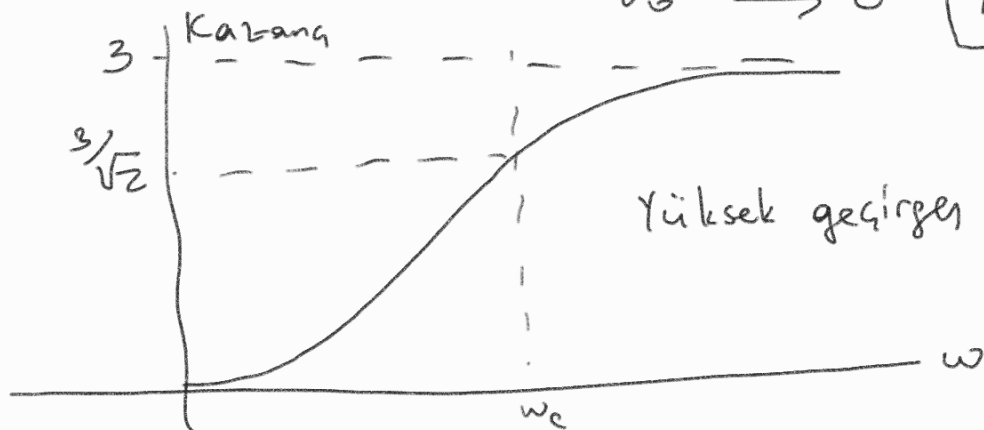

10.95 Figure 10.136 shows a Hartley oscillator. Show that the frequency of oscillation is

$$f_o = \frac{1}{2\pi \sqrt{C(L_1 + L_2)}}$$

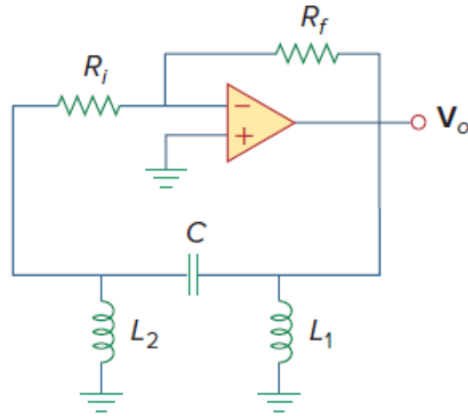



Figure 10.136

A Hartley oscillator; for Prob. 10.95.

CH 11 : AC (ALTERNATİF AKIM) GÜÇ ANALİZİ

$$p(t) = v(t) i(t)$$
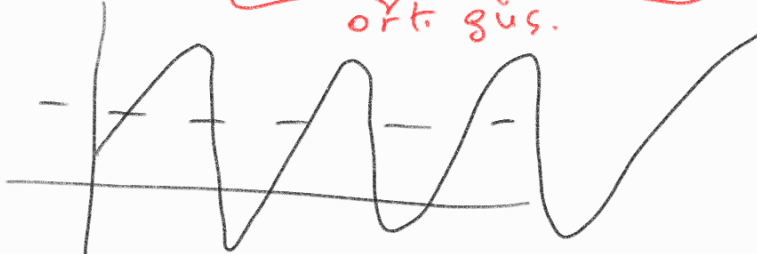
$$p(t) = \underbrace{\frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)}_{\text{ort. güç.}} + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$



$$\rightarrow P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) = \frac{1}{2} \text{Re} \{ \bar{V} \bar{I}^* \}$$

$$\text{Maks. ort. güç tr : } Z_L = Z_{Th}^* \Rightarrow P^{\max} = \frac{|V_{Th}|^2}{8 R_{Th}}$$


Yük tamamen resistif olacaksa : $R_L = |Z_{Th}|$

r.m.s değer :
etkin değer
efektif değer

$$I_{rms} = I_{eff} = \sqrt{\frac{1}{T} \int_0^T i(t)^2 dt}$$

$$P = \text{Re} \{ \bar{V}_{rms} \bar{I}_{rms}^* \} = V_{rms} I_{rms} \cos(\theta_v - \theta_i)$$

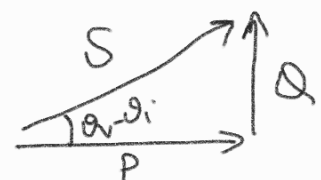$S = \bar{V}_{rms} \bar{I}_{rms}^*$ kompleks güç
güç faktörü $\cos(\theta_v - \theta_i)$



11.5 Assuming that $v_s = 8 \cos(2t - 40^\circ)$ V in the circuit of Fig. 11.37, find the average power delivered to each of the passive elements.

$$\frac{1}{\sqrt{2} \times 220}$$

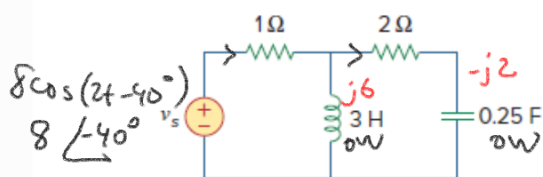


Figure 11.37
For Prob. 11.5.

$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$

$$= \frac{1}{2} \operatorname{Re} \{ \bar{V} \bar{I}^* \}$$

$$R: \theta_v - \theta_i$$

$$v = iR \rightarrow V = IR$$

$$L: V = I j\omega L$$

$$\frac{V}{I} = j\omega L$$

$$\theta_v - \theta_i = 90^\circ \rightarrow \cos(\theta_v - \theta_i) = 0 \Rightarrow P_L = 0$$

$$C: V = I / j\omega C \Rightarrow \frac{V}{I} = \frac{1}{j\omega C} \rightarrow \theta_v - \theta_i = -90^\circ$$

$$\rightarrow \cos(\theta_v - \theta_i) = 0 \Rightarrow P_C = 0$$

$$P_{1\Omega}: P_{1\Omega} = \frac{1}{2} \operatorname{Re} \{ \bar{V}_{1\Omega} \bar{I}_{1\Omega}^* \} = \frac{1}{2} \operatorname{Re} \{ \bar{I}_{1\Omega}^* 1\Omega \times \bar{I}_{1\Omega} \}$$

$$P_{2\Omega}: \frac{1}{2} |\bar{I}_{2\Omega}|^2 = \frac{1}{2} \operatorname{Re} \{ |\bar{I}_{1\Omega}|^2 \} = \frac{1}{2} |\bar{I}_{1\Omega}|^2$$

$$\bar{I}_{1\Omega} = \frac{8 \angle -40^\circ}{1 + (j6 \parallel (2 - j2))} = \frac{8 \angle -40^\circ}{1 + \frac{j6(2 - j2)}{2 + j4}} = \frac{8 \angle -40^\circ (2 + j4)}{2 + j4 + j12 + 12}$$

$$= \frac{8 \angle -40^\circ 2\sqrt{5} \angle 64^\circ}{14 + j16}$$

$$P_{1\Omega} = \frac{1}{2} \frac{8^2 \times (2\sqrt{5})^2}{14^2 + 16^2} = \frac{1}{2} \frac{64 \times 20}{452} \approx 1.42 \text{ Watt}$$

$$\bar{I}_{2\Omega} = \bar{I}_{1\Omega} \times \frac{j6}{2 + j4}$$

$$\frac{1}{2} |\bar{I}_{2\Omega}|^2 = \underbrace{\frac{1}{2} |\bar{I}_{1\Omega}|^2}_{1.42 \text{ W}} \times \frac{36}{2^2 + 4^2} = 1.42 \times \frac{36}{20} \approx 2.56 \text{ Watt}$$

11.7 Given the circuit of Fig. 11.39, find the average power absorbed by the 10-Ω resistor.

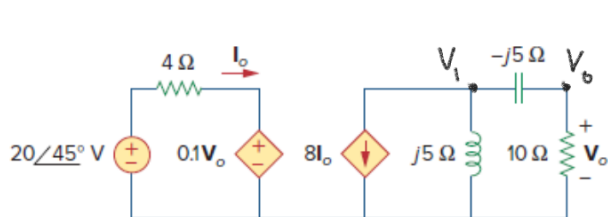


Figure 11.39
For Prob. 11.7.

$$P_{10\Omega} = ?$$

$$(1) \quad 20 \angle 45^\circ = 4 I_o + 0.1 V_o \quad \leftarrow$$

$$(2) \quad 8 I_o + \frac{V_1}{j5} + \frac{V_1 - V_o}{-j5} = 0 \Rightarrow j40 I_o + V_1 - V_1 + V_o = 0$$

$$\boxed{j40 I_o = -V_o}$$

$$(3) \quad \frac{V_1}{10 - j5} \times 10 = V_o$$

$$I_o = \frac{-V_o}{j40}$$

$$(1) \quad 20 \angle 45^\circ = \frac{-4 V_o}{j40} + 0.1 V_o = V_o \left(0.1 - \frac{1}{j10} \right)$$

$$V_o = \frac{20 \angle 45^\circ}{\frac{j-1}{j10}} = \frac{20 \angle 45^\circ}{j-1} j10 = \frac{20 \angle 45^\circ \cdot 10 \angle 90^\circ}{\sqrt{2} \angle 135^\circ}$$

$$\frac{1}{2} \operatorname{Re} \{ \bar{V} \bar{I}^* \} = \frac{1}{2} \operatorname{Re} \left\{ \bar{V} \frac{\bar{V}^*}{Z^*} \right\}$$

$$= \frac{1}{2} \operatorname{Re} \left\{ \frac{|\bar{V}|^2}{Z^*} \right\} \quad \xrightarrow{10}$$

$$V_o = \frac{200}{\sqrt{2}}$$

$$= \frac{1}{2} \frac{|\bar{V}|^2}{10} = \frac{1}{2} \frac{4 \times 10^4}{2 \times 10} = 1000 \text{ W}$$

11.17 Calculate the value of Z_L in the circuit of Fig. 11.48 in order for Z_L to receive maximum average power. What is the maximum average power received by Z_L ?


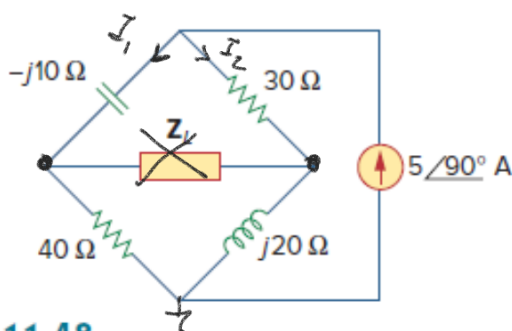


Figure 11.48
For Prob. 11.17.

$$Z_L = Z_{Th}^* \text{ olmalı}$$

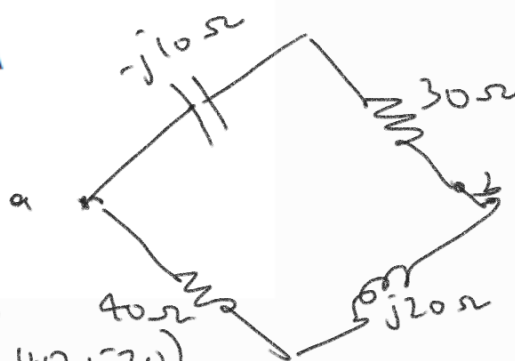

$$Z_{ab} = Z_{Th} = (-j10 + 30) \parallel (40 + j20)$$

$$= \frac{(30 - j10)(40 + j20)}{70 + j10} = \frac{1200 + j600 - j400 + 200}{70 + j10}$$

$$= \frac{1400 + j200}{70 + j10} = 20 \Omega$$

$$\boxed{Z_L = Z_{Th}^* = 20 \Omega} \quad \begin{cases} R_{Th} = 20 \\ X_{Th} = 0 \end{cases}$$

$$P^{max} = \frac{|V_{Th}|^2}{8 R_{Th}} = \frac{|V_{Th}|^2}{8 \times 20}$$

$$V_{Th} = ?$$

$$V_{Th} = V_{ad}$$

$$V_{ad} = 40 I_1 - j20 I_2$$

$$= 40 \cdot 5 \angle 90^\circ \frac{30+j20}{70+j10} - j20 \times 5 \angle 90^\circ \frac{40-j10}{70+j10}$$

$$= \frac{5 \angle 90^\circ}{70+j10} \left(\underbrace{1200 + j800 - j800 - 2000}_{1000} \right)$$

$$V_{ad} = \frac{5000 \angle 90^\circ}{70+j10} = \bar{V}_{Th}$$

$$P^{max} = \frac{|\bar{V}_{Th}|^2}{160} = \frac{(5000)^2}{5000 \times 160} = \frac{5000}{160} = 31.25 \text{ Watt}$$

11.20 The load resistance R_L in Fig. 11.51 is adjusted until it absorbs the maximum average power. Calculate the value of R_L and the maximum average power.

$$R \in \mathbb{R}$$

$$R_L = |Z_{Th}| \text{ olmalı}$$

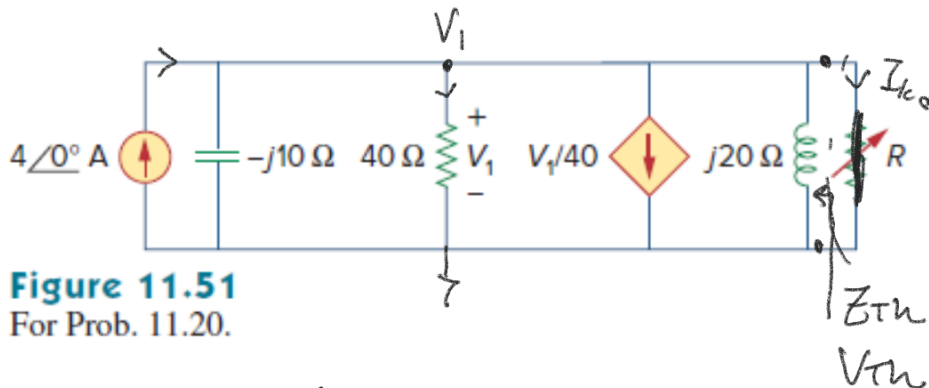


Figure 11.51
For Prob. 11.20.

$$\underline{V_{ad}}: 4 = \frac{V_1}{-j10} + \frac{V_1}{40} + \frac{V_1}{40} + \frac{V_1}{j20}$$

$$4 = V_1 (j4 + 1 + 1 - 2j) \Rightarrow V_1 = \frac{4}{2+j2} = V_{Th} = \frac{4}{2\sqrt{2} \angle 45^\circ} = \frac{2}{\sqrt{2}} \angle -45^\circ$$

I_{kd} : $V_1 = 0$ olur. $-j10\Omega$ ve 40Ω 'den akım geçmez
 $V_1/40$ akımı da sıfır olur.

0 kalan $I_{kd} = 4 \angle 0^\circ$ olur.

$$Z_{Th} = \frac{V_{ad}}{I_{kd}} = \frac{4}{(2+j2)4} = \frac{1}{2+j2} = \frac{1}{2\sqrt{2} \angle 45^\circ} = \frac{1}{2\sqrt{2}} \angle -45^\circ = Z_{Th}$$

$$R_L = |Z_{Th}| = \frac{1}{2\sqrt{2}} \Omega$$

$$P_{max} = \frac{|V_{Th}|^2}{8 R_L} = \frac{2}{8 \times \frac{1}{2\sqrt{2}}} = \frac{4\sqrt{2}}{8} = \frac{1}{\sqrt{2}} \text{ W}$$

11.30 Compute the rms value of the waveform depicted in Fig. 11.61.


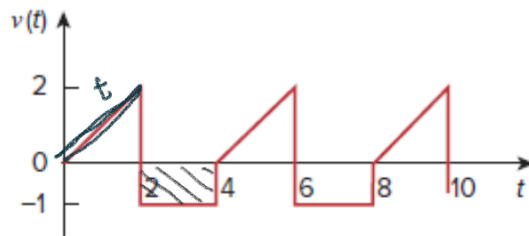


Figure 11.61
For Prob. 11.30.


$$V_{rms} = \sqrt{\frac{1}{4} \int_0^4 v^2(t) dt}$$

$$\begin{aligned} V_{rms} &= \sqrt{\frac{1}{4} \int_0^2 v^2(t) dt + \frac{1}{4} \int_2^4 v^2(t) dt} \\ &= \sqrt{\frac{1}{4} \int_0^2 v^2(t) dt + \frac{1}{2}} = \sqrt{\frac{1}{4} \int_0^2 t^2 dt + \frac{1}{2}} \\ &= \sqrt{\frac{1}{4} \left[\frac{t^3}{3} \right]_0^2 + \frac{1}{2}} = \sqrt{\frac{2}{3} + \frac{1}{2}} = \sqrt{\frac{7}{6}} \end{aligned}$$

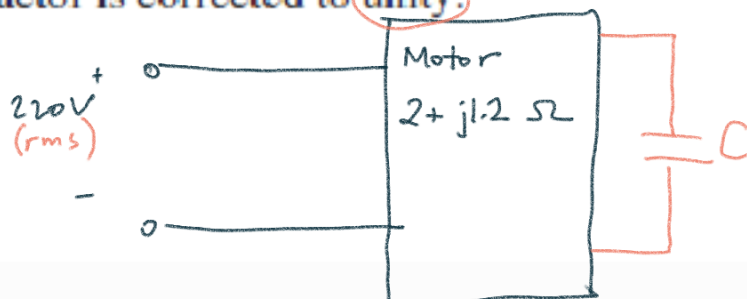11.39 An ac motor with impedance $Z_L = 2 + j1.2 \Omega$ is supplied by a 220-V, 60-Hz source. (a) Find pf, P, and Q. (b) Determine the capacitor required to be connected in parallel with the motor so that the power factor is corrected to unity.



$$\bar{S} = \bar{V} \bar{I}^* = \bar{I} Z \bar{I}^* = \bar{V} \frac{\bar{V}^*}{Z^*} = \frac{|\bar{V}|^2}{Z^*}$$

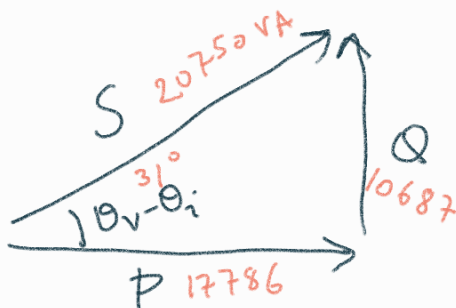

güç faktörü : $\cos(\theta_v - \theta_i) = \frac{P}{S}$

induktif lagging (takip eden) kapasitif leading (önde giden)

$$S = \frac{220^2}{2 - j1.2} = \frac{220^2}{\sqrt{5.44} \angle -31^\circ} = 20.75 \angle 31^\circ \text{ kVA}$$


a) $g.f. : 0.86$ takip eder.

$$P = 17786 \text{ Watt} \quad \bar{S} = 17786 + j10687 \text{ VA}$$

$$Q = 10687 \text{ VAR}$$

b) Kompanzasyon / Güç faktörü düzeltme.

$$\omega = 2\pi \times 60$$

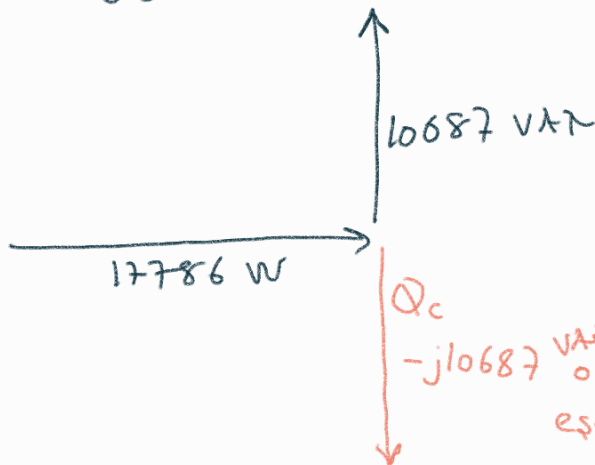

$$S_c = \frac{220^2}{(-j/\omega C)^*} = \frac{220^2 \omega C}{j}$$

$$= -j220^2 \omega C = -j10687$$

$$\Rightarrow 220^2 \times 120\pi \times C = 10687$$

$$C = \frac{10687}{220^2 \times 120\pi}$$

~ 50 μF

11.45 The voltage across a load and the current through it are given by

$$v(t) = 20 + 60 \cos 100t \text{ V}$$

$$i(t) = 1 - 0.5 \sin 100t \text{ A} = 1 - 0.5 \cos(100t - 90^\circ)$$

Find:

(a) the rms values of the voltage and of the current

(b) the average power dissipated in the load

a)
$$\sqrt{\frac{1}{T} \int_0^T (20 + 60 \cos 100t)^2 dt}$$

$$= \sqrt{\frac{1}{T} \int_0^T 400 + 2400 \cos 100t + 3600 \cos^2 100t dt}$$

($T = \frac{2\pi}{100}$)

$$V_{rms} = \sqrt{400 + 1800} = \sqrt{2200} = 46.9 \text{ V}$$

$$I_{rms} = \sqrt{1^2 + \frac{0.5^2}{2}} = \sqrt{1.125} \approx 1.061 \text{ A}$$

b) $p(t) = v(t) i(t)$

$$= (20 + 60 \cos 100t) (1 - 0.5 \sin 100t)$$

$$= 20 - 10 \sin 100t + 60 \cos 100t - 30 \cos(100t) \cos(100t - 90^\circ)$$

$$p(t) = 20 - 10 \cos(100t - 90^\circ) + 60 \cos(100t) - 15 \cos(200t - 90^\circ) - 15 \cos(90^\circ)$$

$$P = 20 \text{ Watt} \quad \text{ort. güç}$$

11.52 In the circuit of Fig. 11.71, device A receives 2 kW at 0.8 pf lagging, device B receives 3 kVA at 0.4 pf leading, while device C is inductive and consumes 1 kW and receives 500 VAR.

(a) Determine the power factor of the entire system.

(b) Find I given that $V_s = 120 \angle 45^\circ \text{ V rms}$.


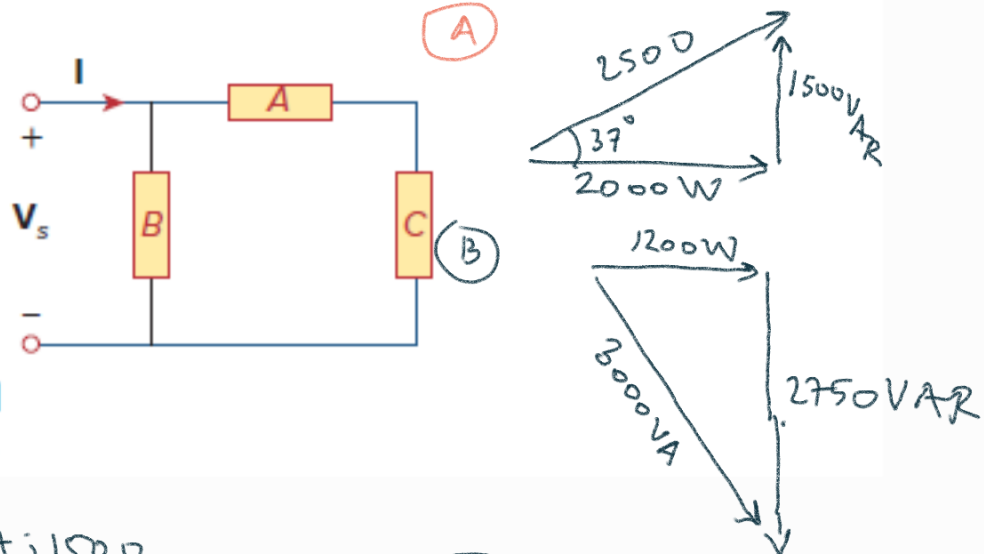


Figure 11.71
For Prob. 11.52.
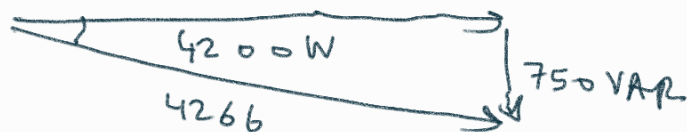
$$\begin{aligned} \bar{S}_{\text{eq}} &= 2000 + j1500 \\ &\quad + 1200 - j2750 \\ &\quad + 1000 + j500 \\ &= 4200 - j750 \end{aligned}$$



p.f. 0.985 önde gider (kapasitif)

$$b) \bar{S}_{\text{eq}} = \bar{V}_s \bar{I}^*$$

$$4266 \angle -9.78^\circ = 120 \angle 45^\circ \bar{I}^*$$

$$\bar{I}^* = 35.6 \angle -54.78^\circ \Rightarrow \bar{I} = 35.6 \angle 54.78^\circ \text{ A}$$

11.59 Calculate the reactive power in the inductor and capacitor in the circuit of Fig. 11.78.

ML

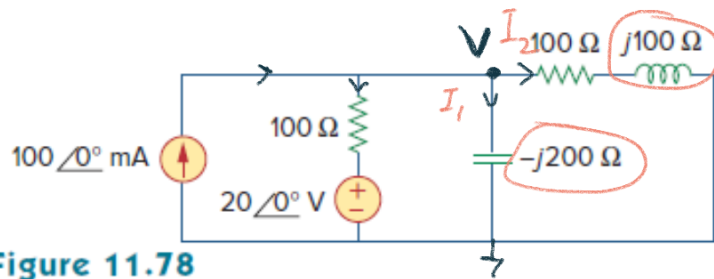


Figure 11.78
For Prob. 11.59.

$$0.1 = \frac{V-20}{100} + \frac{V}{-j200} + \frac{V}{100+j100}$$

$$10 = V-20 + \frac{V}{-j2} + \frac{V(1-j)}{(1+j)(1-j)}$$

$$10 = V-20 + \frac{V}{-j2} + \frac{V(1-j)}{2}$$

$$10 = \frac{-j2V + j40 + jV + V(1-j)}{2}$$

$$20 - j40 = V(-j2 + j + 1 - j)$$

$$V = \frac{20 - j40}{1 - j2} = 20 \text{ V}$$

$$I_1 = \frac{20}{-j200} \quad I_2 = \frac{20}{100+j100}$$

$$I_1 = 0.1 \angle 90^\circ \quad = \frac{20}{100\sqrt{2} \angle 45^\circ} = \frac{1}{5\sqrt{2}} \angle -45^\circ$$

$$\bar{S}_{-j200} = \frac{1}{2} |\bar{I}_1|^2 (-j200)$$

$$= -j \text{ VA}$$

0W ve -1VAR

$$\bar{S}_{j100} = \frac{1}{2} |\bar{I}_2|^2 j100$$

$$= \frac{1}{2} \frac{1}{50} j100 = j \text{ VA}$$

0W ve 1VAR

11.61 Given the circuit in Fig. 11.80, find I_o and the overall complex power supplied.


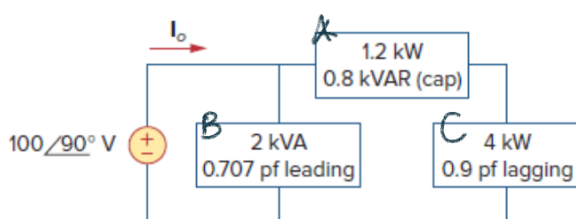


Figure 11.80
For Prob. 11.61.

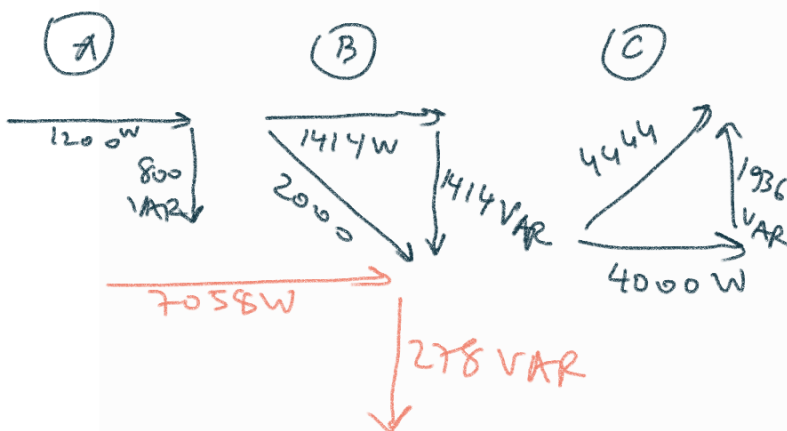

$$7058 - j278 = \frac{1100 \angle 90^\circ}{2} I_o^*$$

$$= j550 I_o^*$$

$$I_o = \left(\frac{7058 - j278}{j550} \right)^* = \frac{7058 - j278}{-j550} j$$

$$= \frac{278 + j7058}{550} \text{ A}$$

11.67 For the op amp circuit in Fig. 11.86, calculate:

- (a) the complex power delivered by the voltage source
- (b) the average power dissipated in the $10\text{-}\Omega$ resistor

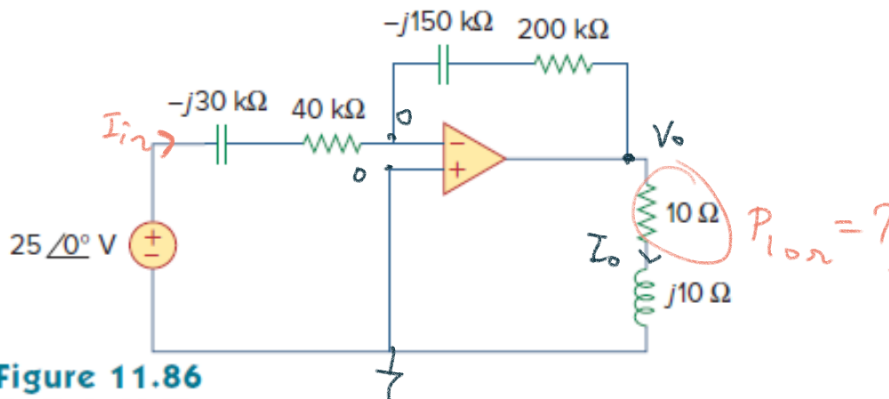


Figure 11.86
For Prob. 11.67.

$$V_o = -25 \times \frac{200000 - j150000}{40000 - j30000} = -125 \angle 0^\circ \text{ V}$$

$$I_o = \frac{-125}{10 + j10} \Rightarrow P_{10\Omega} = \frac{1}{2} |I_o|^2 10$$

$$= \frac{1}{2} \frac{125^2}{200} \times 10 = 390.6 \text{ W}$$


$$I_{in} = \frac{25}{40000 - j30000}$$

$$\bar{S}_s = \frac{1}{2} (-25) \times \bar{I}_{in}^* = \frac{-25}{2} \frac{25}{40000 + j30000}$$

$$\bar{S}_s = \frac{-625}{100000 \angle 37^\circ} = -625 \times 10^{-5} \angle -37^\circ \text{ VA}$$

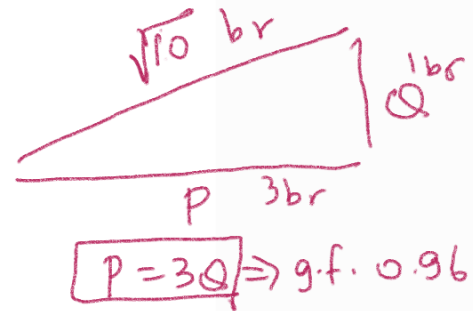11.73 A 240-V rms 60-Hz supply serves a load that is 10 kW (resistive), 15 kVAR (capacitive), and 22 kVAR (inductive). Find:


- the apparent power
- the current drawn from the supply
- the kVAR rating and capacitance required to improve the power factor to 0.96 lagging
- the current drawn from the supply under the new power-factor conditions



$$a) \bar{S} = 10000 + j7000 \text{ VA}$$


$$S = \sqrt{149} \text{ kVA}$$

$$b) \bar{I}_e = \frac{10000 - j7000}{240} \Rightarrow |I_e| = \frac{\sqrt{149} \times 1000}{240} \approx 50.83 \text{ A}$$

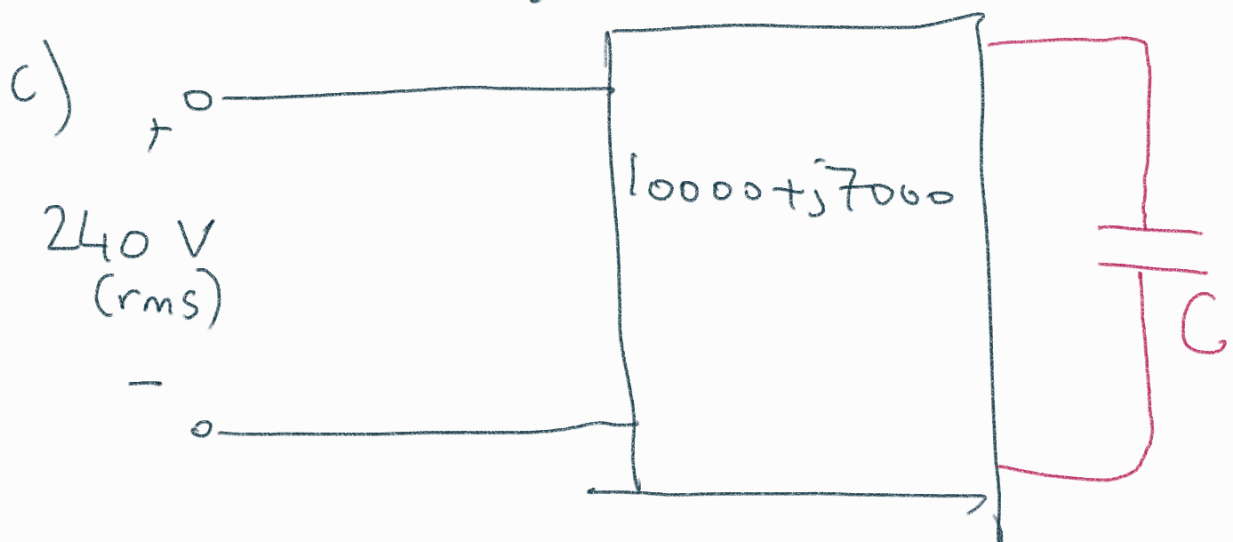

$$\cos^{-1}(0.96) = 16.3^\circ$$

$$\tan(16.3^\circ) = 0.29$$

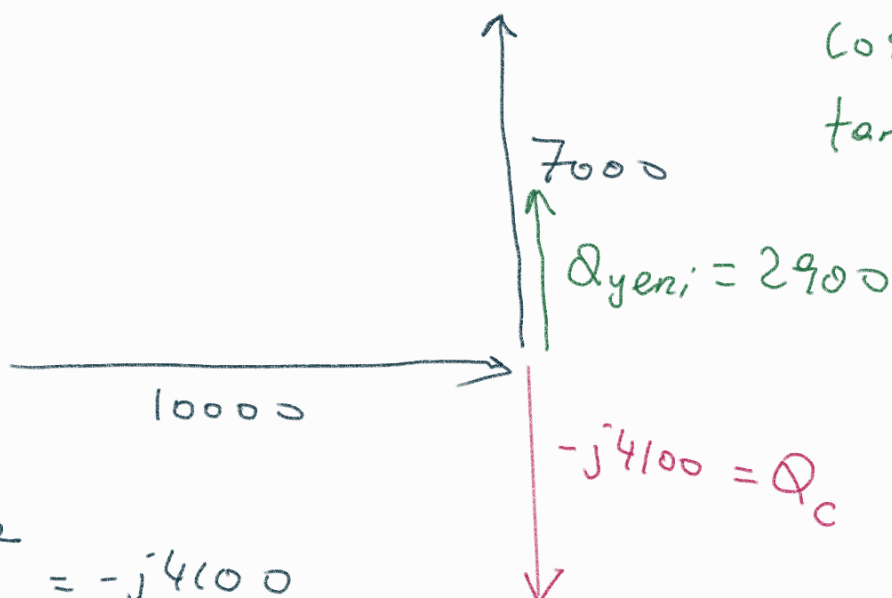

$$\frac{240^2}{Z_C^*} = -j4100$$

$$\rightarrow -j240^2 \times 120\pi \times C = 4100 \Rightarrow C = 188 \mu\text{F}$$

$$d) \bar{S}_{yeni} = 10000 + j2900 \text{ VA}$$

$$= 240 \bar{I}_{yeni}^*$$


$$\bar{I}_{yeni} = \frac{10000 - j2900}{240} \text{ A}$$

$$|\bar{I}_{yeni}| = \frac{10.41 \times 1000}{240} = 43.38$$

(Not: Itattaki kayıp $|\bar{I}_l|^2$ ile orantılı)
kayıptan kabaca %30 azalır.

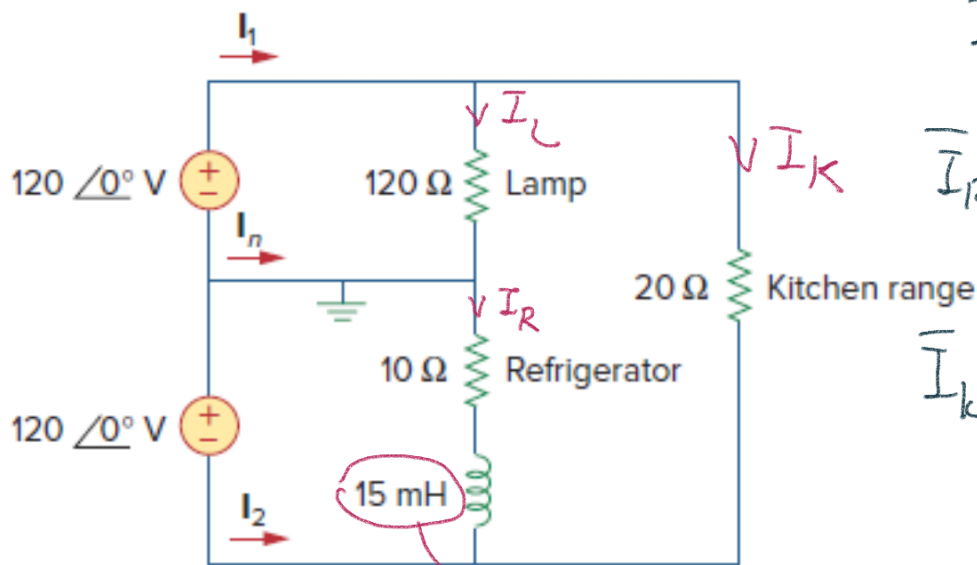11.85 A regular household system of a single-phase three-wire circuit allows the operation of both 120-V and 240-V, 60-Hz appliances. The household circuit is modeled as shown in Fig. 11.96. Calculate:

- the currents I_1 , I_2 , and I_n
- the total complex power supplied
- the overall power factor of the circuit



$$I_L = \frac{120}{120} = 1 \angle 0^\circ \text{ A}$$

$$\bar{I}_R = \frac{120}{10 + j5.65} = \frac{120}{11.5 \angle 29.5^\circ}$$

$$\bar{I}_K = \frac{240}{20} = 12 \angle 0^\circ \text{ A}$$

Figure 11.96

For Prob. 11.85.

$$\bar{I}_1 = \bar{I}_L + \bar{I}_K = 1 \angle 0^\circ + 12 \angle 0^\circ = 13 \angle 0^\circ$$

$$I_2 = -\bar{I}_R - \bar{I}_K = \frac{-120}{11.5 \angle 29.5^\circ} - 12$$

$$\bar{I}_n = \bar{I}_R - \bar{I}_L = \frac{120}{10+j5.65} - 1$$

$$b) \bar{S}_L = \frac{1}{2} |\bar{I}_L|^2 120 = 60 \text{ W} \quad \xrightarrow{60 \text{ W}}$$


$$\bar{S}_R = \frac{1}{2} |\bar{I}_R|^2 20 = \frac{1}{2} 12^2 \times 20 = 1440 \text{ W} \quad \xrightarrow{1440 \text{ W}}$$

$$\begin{aligned} \bar{S}_R &= \frac{1}{2} |\bar{I}_R|^2 (10+j5.65) = \frac{1}{2} \frac{120^2}{11.5^2} (10+j5.65) \\ &= 544.4 (10+j5.65) \\ &= 5444.4 + j307.6 \text{ VA} \end{aligned}$$

+

$2044.4 + j307.6 \text{ VA}$ sağlanmıştı
kaynak tarafından

c)

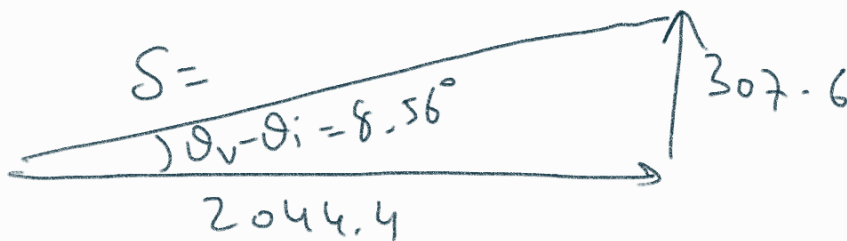

pf. 0.9888 (lagging)
takip eden

11.91 The nameplate of an electric motor has the following information:

Line voltage: 220 V rms

Line current: 15 A rms

Line frequency: 60 Hz


Power: 2700 W

Determine the power factor (lagging) of the motor.

Find the value of the capacitance C that must be connected across the motor to raise the pf to unity.

$$\bar{S} = V I^*$$

$$S = \underbrace{|V|}_{220} \underbrace{|I|}_{15}$$

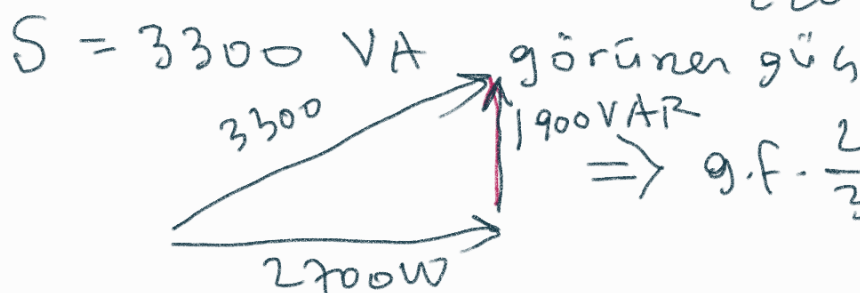


$$\Rightarrow \text{g.f.} = \frac{2700}{3300} = 0.81 \text{ (lagging)}$$

$$\downarrow -j1900 = Q_c = -j220^2 \times 120\pi \times C$$


$$\Rightarrow C \approx 104 \mu F \text{ or } 0.1 \text{ mF}$$

1.95 A coupling capacitor is used to block dc current from an amplifier as shown in Fig. 11.98(a). The amplifier and the capacitor act as the source, while the speaker is the load as in Fig. 11.98(b).

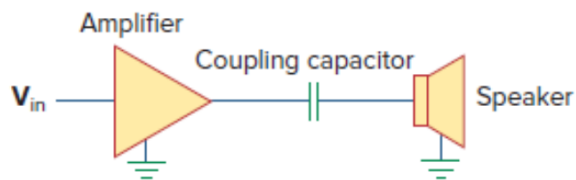- (a) At what frequency is maximum power transferred to the speaker?
- (b) If $V_s = 4.6 \text{ V rms}$, how much power is delivered to the speaker at that frequency?



(a)

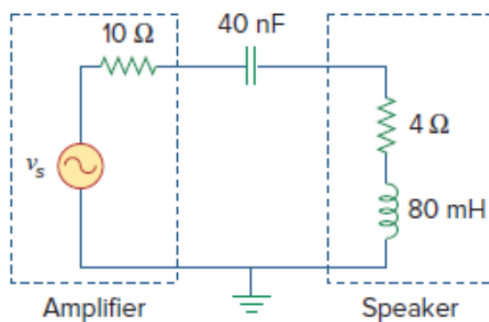


(b)

Figure 11.98
For Prob. 11.95.


10.6 Find the average power dissipated in the $30\ \Omega$ resistor in the circuit seen in Fig. P10.6 if $i_g = 6 \cos 20,000t\ \text{A}$.

PSPICE
MULTISIM

Figure P10.6

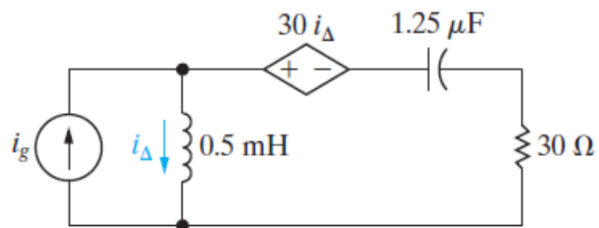

CHAPTER 12 : ÜÇ FAZLI DEVRELER

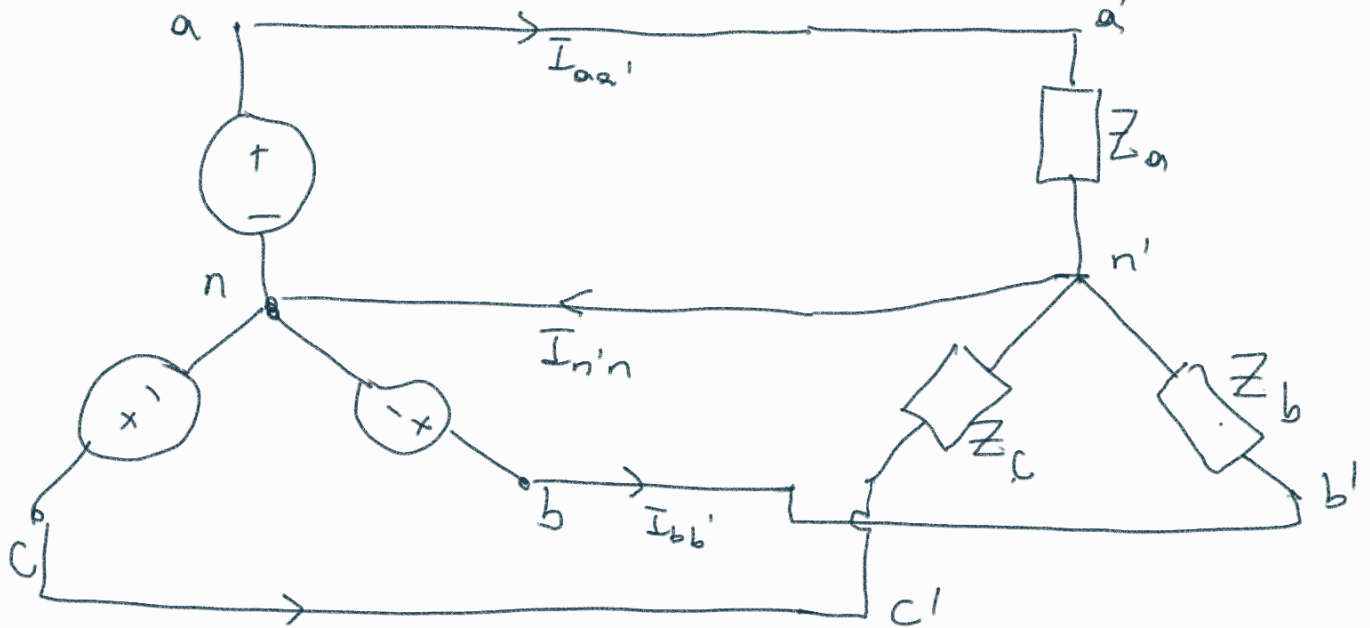

$$Z_a = Z_b = Z_c \text{ olursa}$$

$$I_{n'n} = 0 \text{ olur.}$$

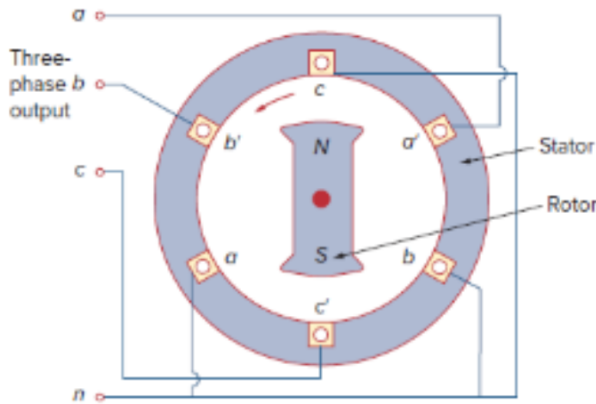


Figure 12.4
A three-phase generator.

Rotor ↺ Saat yönünün tersine dönerse

$$\bar{V}_a = V_p \angle 0^\circ \text{ V}$$


$$\bar{V}_b = V_p \angle -120^\circ \text{ V}$$

$$\bar{V}_c = V_p \angle -240^\circ \text{ V} = V_p \angle +120^\circ$$


buna abc dizisi denir.

(Not: Rotor ↻ dönerse o zaman acb dizisi olur. $\bar{V}_a = V_p \angle 0^\circ$ $\bar{V}_c = V_p \angle -120^\circ$ $\bar{V}_b = V_p \angle -240^\circ$)
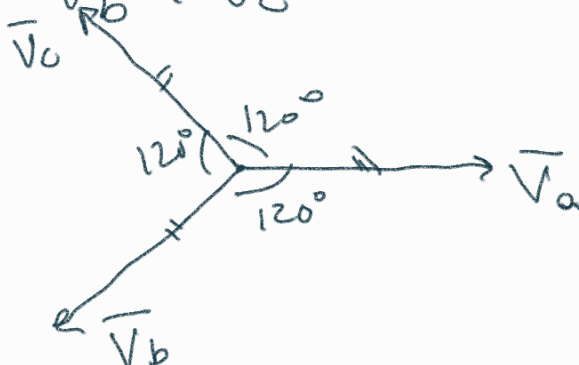
$$\bar{V}_a + \bar{V}_b + \bar{V}_c = 0$$



Dengeli 3 Faz: $Z_a = Z_b = Z_c$

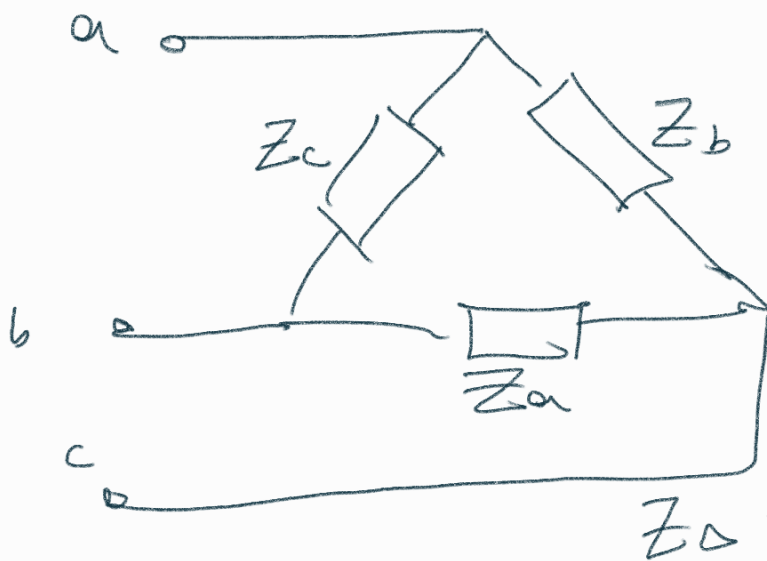

Y-Yük:

$$Z_1 = Z_2 = Z_3 = Z_Y \text{ ise}$$




Δ 'ya çevirirsek

$$Z_{\Delta} = Z_a = Z_b = Z_c = 3Z_Y \text{ olur}$$



$$Z_{\Delta} = 3Z_Y$$

Y- Δ

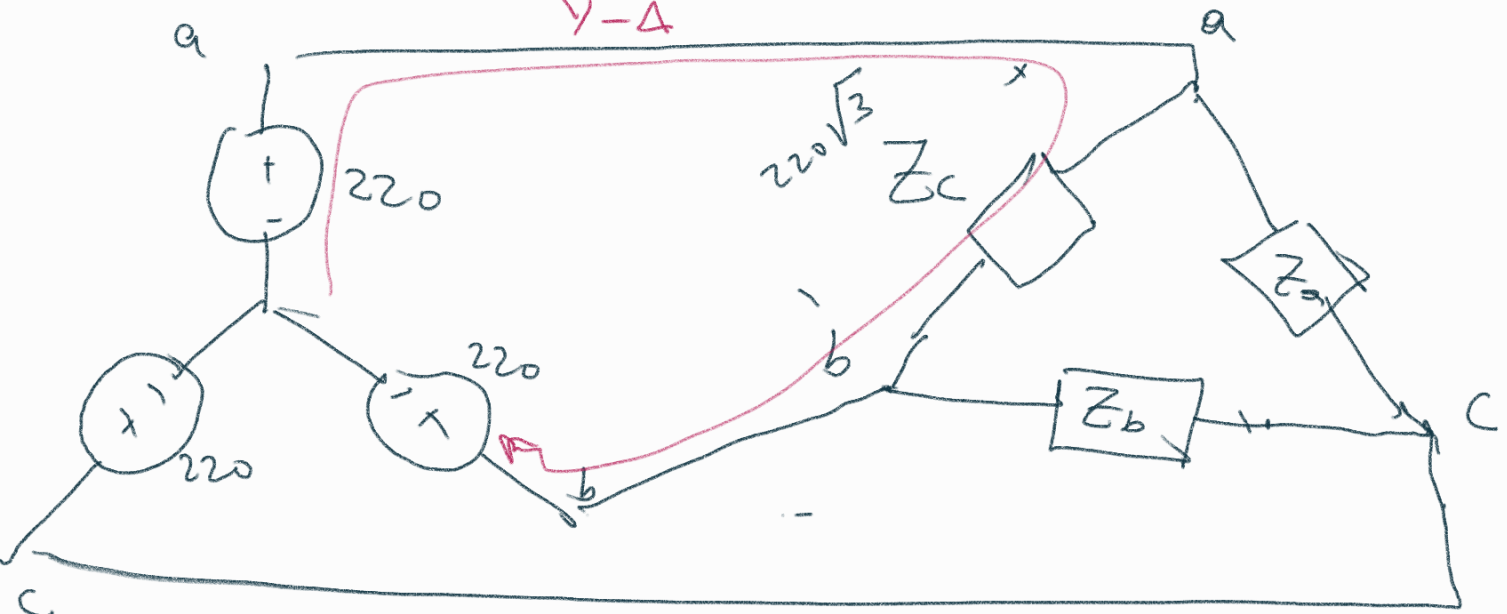

Y-Y ve Y- Δ

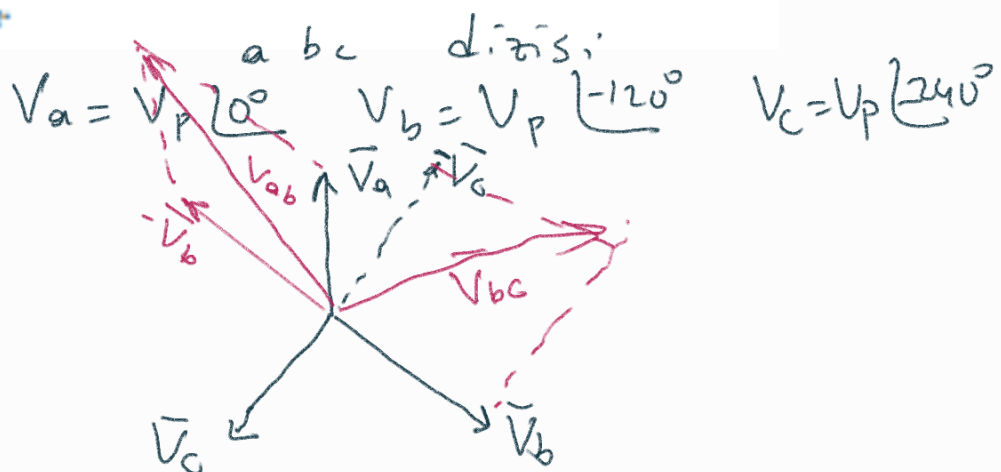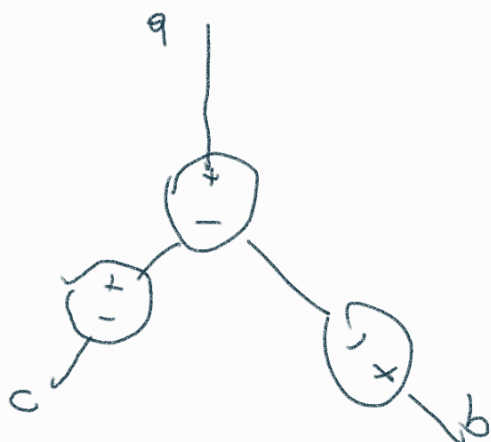12.3 Given a balanced Y-connected three-phase generator with a line-to-line voltage of $V_{ab} = 100/45^\circ$ V and $V_{bc} = 100/165^\circ$ V, determine the phase sequence and the value of V_{ca} .



$$\overline{V}_{ab} = \overline{V}_a - \overline{V}_b$$

$$\overline{V}_{bc} = \overline{V}_b - \overline{V}_c$$

abc dizisi olsaydı

$$V_a \rightarrow V_b \rightarrow V_c$$

$$V_{ab} \rightarrow V_{bc} \rightarrow V_{ca}$$

sıraları aynı olurdu.

Burada ise öyle değil

$\overline{V}_{bc}$, $\overline{V}_{ab}$ 'den 120° ileride

Özaman demek ki burada acb dizisi var.

$$\overline{V}_{ab} = 100 \angle 45^\circ$$

$$\overline{V}_{bc} = 100 \angle 165^\circ$$

$$\overline{V}_{ca} = 100 \angle -75^\circ$$


$\overline{V}_{ab} \rightarrow \overline{V}_{ca} \rightarrow \overline{V}_{bc}$ şeklinde.

12.8 In a balanced three-phase Y-Y system, the source is an acb sequence of voltages and $\overline{V}_{cn} = 120 \angle 35^\circ \text{ V rms}$. The line impedance per phase is $(1 + j2) \Omega$, while the per-phase impedance of the load is $(11 + j14) \Omega$. Calculate the line currents and the load voltages.

acb:

$$\overline{V}_{an} = 120 \angle 155^\circ \text{ V} \quad \overline{V}_{cn} = 120 \angle 35^\circ \text{ V}$$
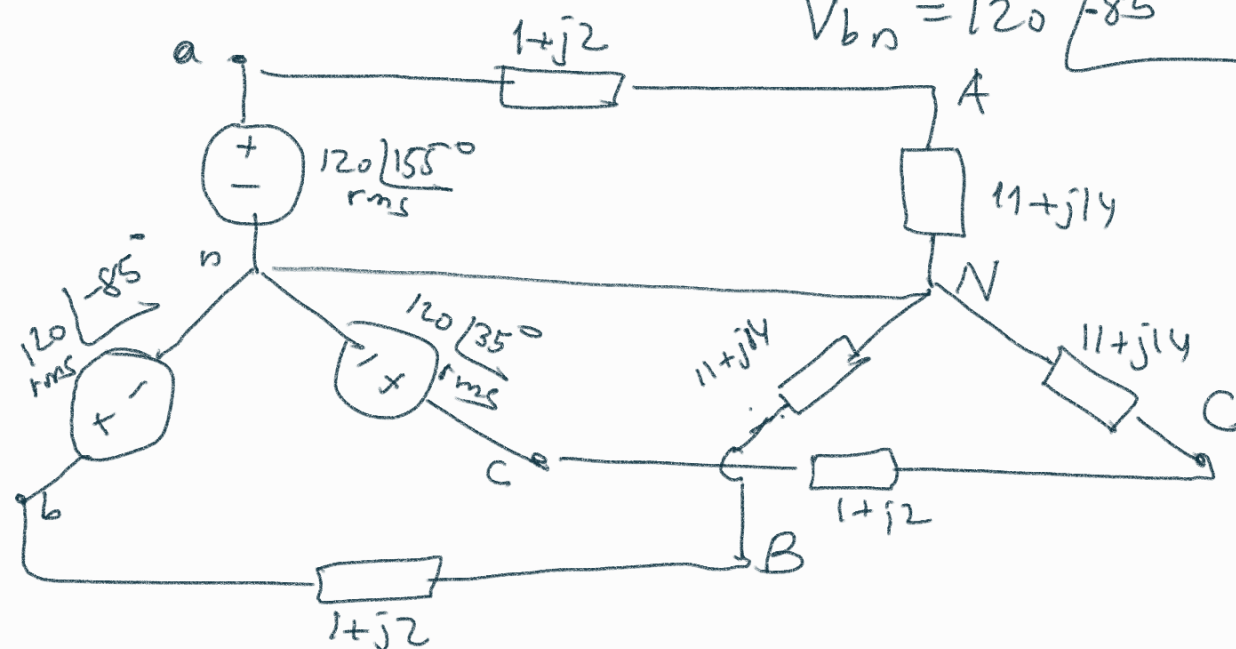
$$\overline{V}_{bn} = 120 \angle -85^\circ \text{ V}$$



Hat akımı , Faz akımı

Hat gerilimi , Faz gerilimi

Hatlar
arası gerilim

Y bağlantıda hat ve faz akımları aynı şey.
Dengeli olduğu için 3 ayrı devre var gibi.

$$\begin{cases} \bar{I}_{aA} = \frac{120 \angle 155^\circ}{12 + j16} = \frac{120 \angle 155^\circ}{20 \angle 53^\circ} = 6 \angle 102^\circ \text{ A} \\ \bar{I}_{cC} = 6 \angle -18^\circ \text{ A} \\ \bar{I}_{bB} = 6 \angle -138^\circ \text{ A} \end{cases}$$

$$\begin{cases} \bar{V}_{AN} = \bar{I}_{aA} (11 + j14) \\ \bar{V}_{CN} = \bar{I}_{cC} (11 + j14) \\ \bar{V}_{BN} = \bar{I}_{bB} (11 + j14) \end{cases} \quad \text{Yüklü faz gerilimleri}$$

12.13 In the balanced three-phase Y- Δ system in



Fig. 12.46, find the line current I_L and the average ML power delivered to the load.

abc varsayalım


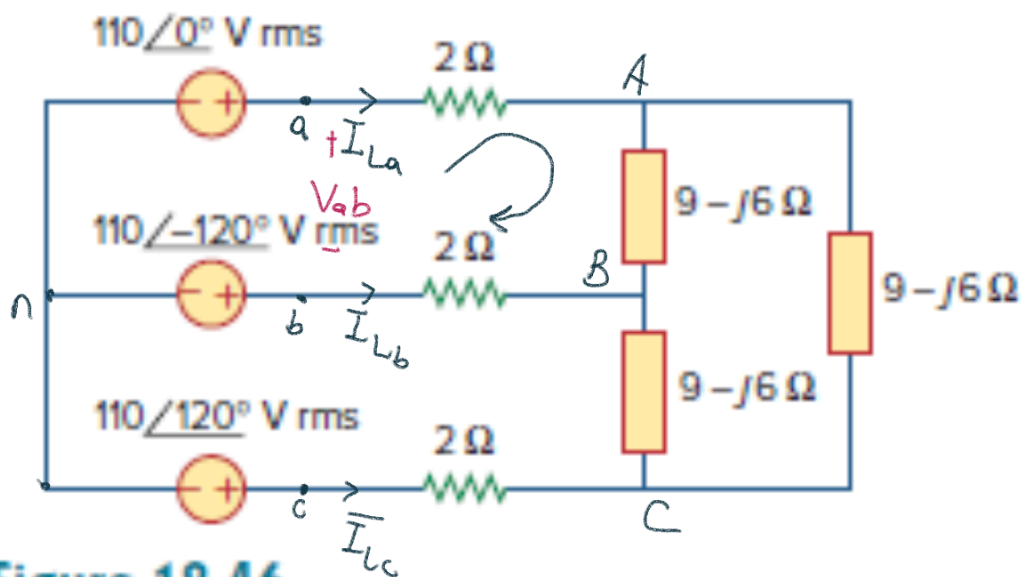


Figure 12.46
For Prob. 12.13.

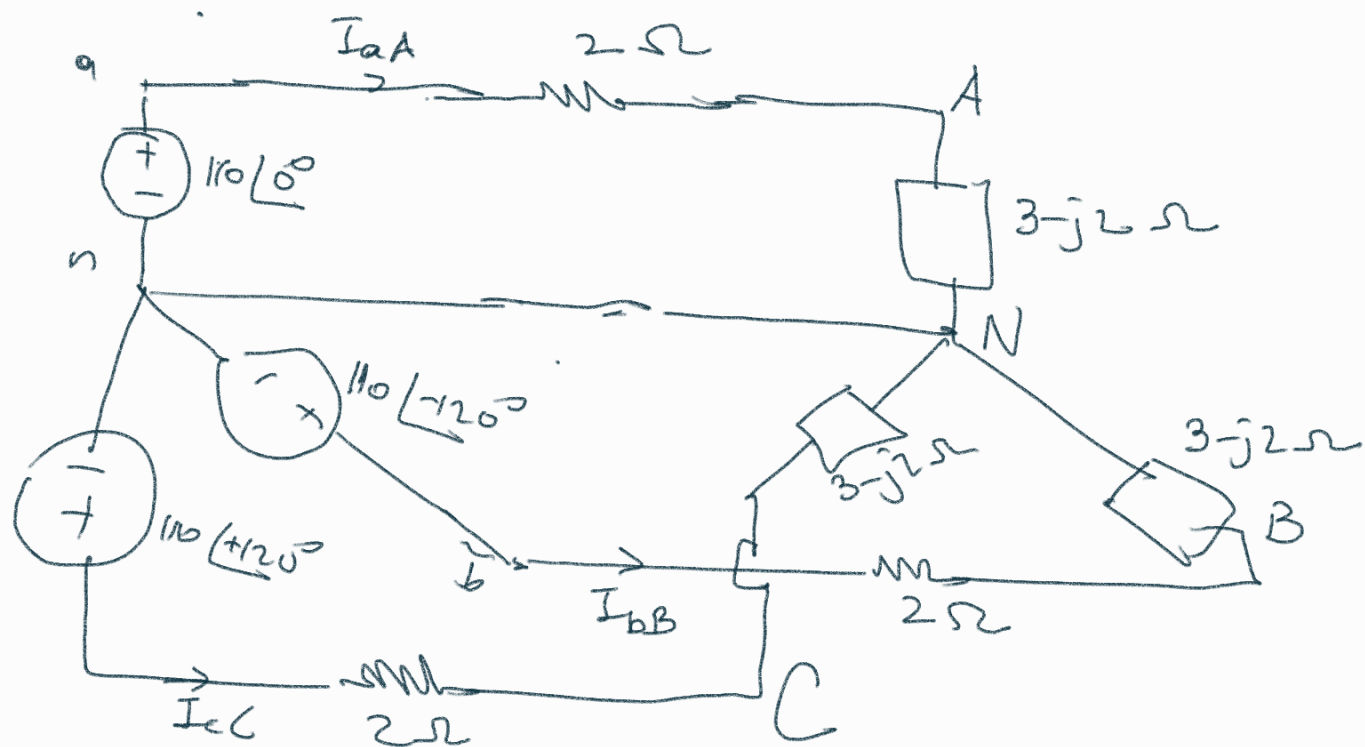

$$\bar{I}_{la} = \bar{I}_{aA} = \frac{110 \angle 0^\circ}{5-j2} = \frac{110 \angle 0^\circ}{\sqrt{29} \angle -4.8^\circ} = 20.4 \angle 21.8^\circ \text{ A}$$

$$\bar{I}_{lb} = \bar{I}_{bB} = 20.4 \angle -98.2^\circ \text{ A}$$

$$\bar{I}_{lc} = \bar{I}_{cC} = 20.4 \angle 141.8^\circ \text{ A}$$

$$I_L = 20.4$$


$$\sqrt{3} V_L I_L \cos \theta = P$$

$$\bar{V}_{AN} = \bar{I}_{aA} (3-j2) = 73.66 \angle -12.1^\circ$$

$$\bar{V}_{AB} = \sqrt{3} \bar{V}_{AN} \angle 30^\circ$$

$$= 127.58 \angle 17.9^\circ$$

$$V_L = 127.58$$

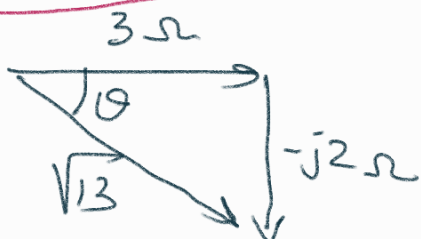

$$\theta = -33.7^\circ$$


$$\cos \theta = 0.83$$



$$P = \sqrt{3} \times 127.58 \times 20.4 \times 0.83 = \underline{\underline{3747 \text{ W}}}$$


$$V_{an} = 220 \angle 60^\circ$$

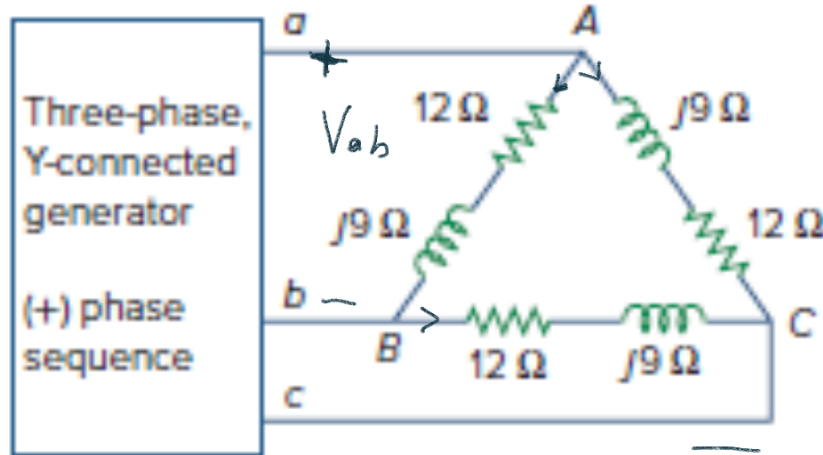12.18 If $V_{an} = 220 \angle 60^\circ \text{ V}$ in the network of Fig. 12.49, find the load phase currents I_{AB} , I_{BC} , and I_{CA} .



$V_{ab} = V_{AB}$
kaynak ve
yükteki hat
gerilimi.

Figure 12.49
For Prob. 12.18.

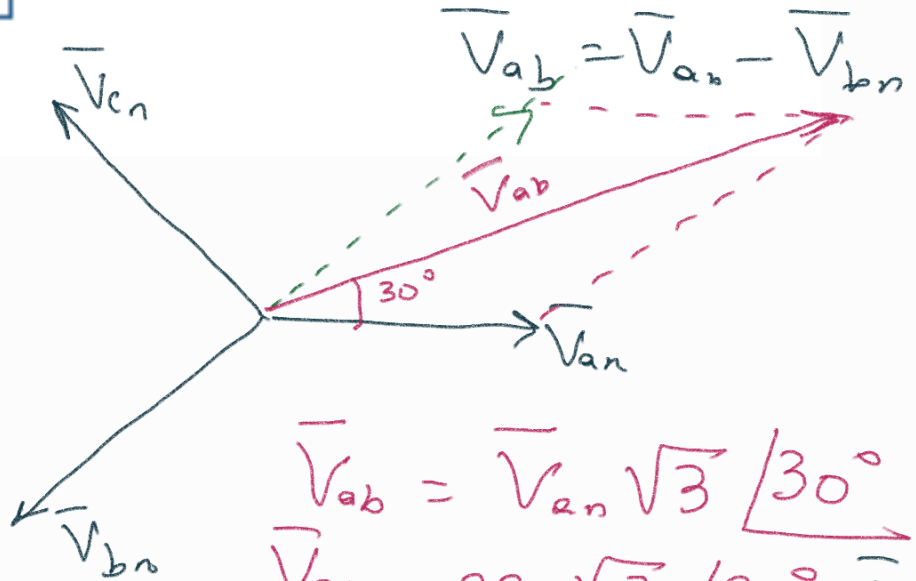

$$\bar{V}_{ab} = \bar{V}_{an} \sqrt{3} \angle 30^\circ$$

$$\bar{V}_{ab} = 220\sqrt{3} \angle 90^\circ = \bar{V}_{AB}$$

$$\bar{V}_{AB} = 220\sqrt{3} \angle 90^\circ \rightarrow \bar{I}_{AB} = \frac{220\sqrt{3} \angle 90^\circ}{15 \angle 37^\circ} = 25.4 \angle 53^\circ \text{ A}$$

$$\bar{V}_{BC} = 220\sqrt{3} \angle -30^\circ \rightarrow \bar{I}_{BC} = 25.4 \angle -67^\circ \text{ A}$$

$$\bar{V}_{CA} = 220\sqrt{3} \angle -150^\circ \rightarrow \bar{I}_{CA} = 25.4 \angle -187^\circ \text{ A}$$

$$= 25.4 \angle +173^\circ \text{ A}$$

12.30 In Fig. 12.56, the rms value of the line voltage is 208 V. Find the average power delivered to the load.

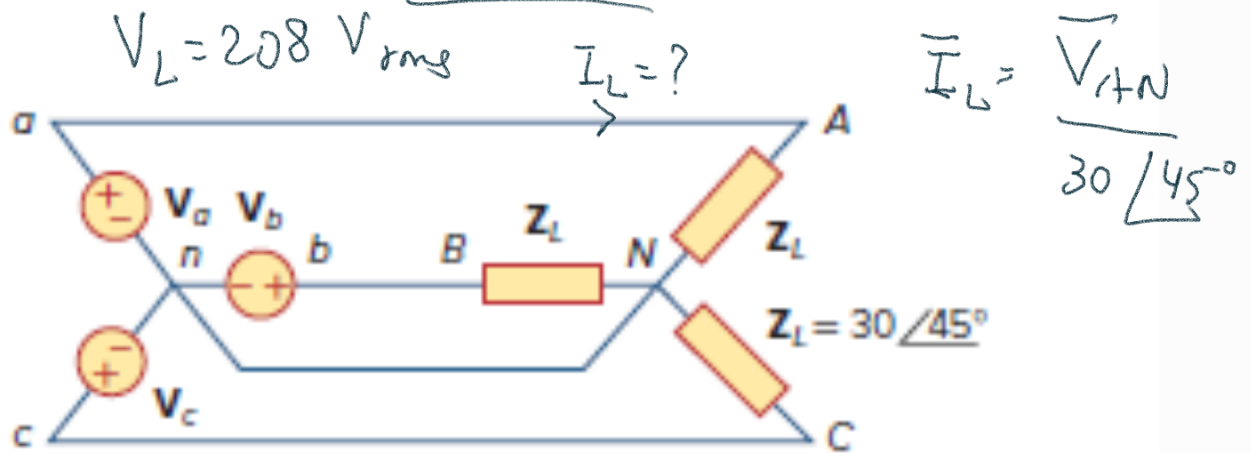


Figure 12.56
For Prob. 12.30.

Dengeli bir sistemde güç:

* Anlık güç sabittir (salınım yapmaz)

Hem Δ hem de Y bağlı yük için

$$P = \sqrt{3} V_L I_L \cos \theta$$

→ 3 fazın toplamı

↙ yük empedans açısı
↘ yükteki hat akımın büyüklüğü
↙ yükteki hat geriliminin büyüklüğü

$$Q = \sqrt{3} V_L I_L \sin \theta$$

$$\bar{S} = P + jQ$$

$$S = \sqrt{P^2 + Q^2}$$

$$\bar{V}_{AN} = \frac{\bar{V}_{AB}}{\sqrt{3}} \angle -30^\circ = \frac{208}{\sqrt{3}} \angle -30^\circ$$


$$\bar{I}_L = \frac{\bar{V}_{AN}}{30 \angle 45^\circ} = \frac{208}{30\sqrt{3}} \angle -75^\circ$$

$$I_L = \frac{208}{30\sqrt{3}}$$

$$P = \cancel{\sqrt{3}} \times 208 \times \frac{208}{\cancel{30\sqrt{3}}} \cos(45^\circ) = 1442 \cos(45^\circ) = 1000 \text{ Watt}$$

12.36 A 4200-V, three-phase transmission line has an impedance of $4 + j \Omega$ per phase. If it supplies a load of 1 MVA at 0.75 power factor (lagging), find:

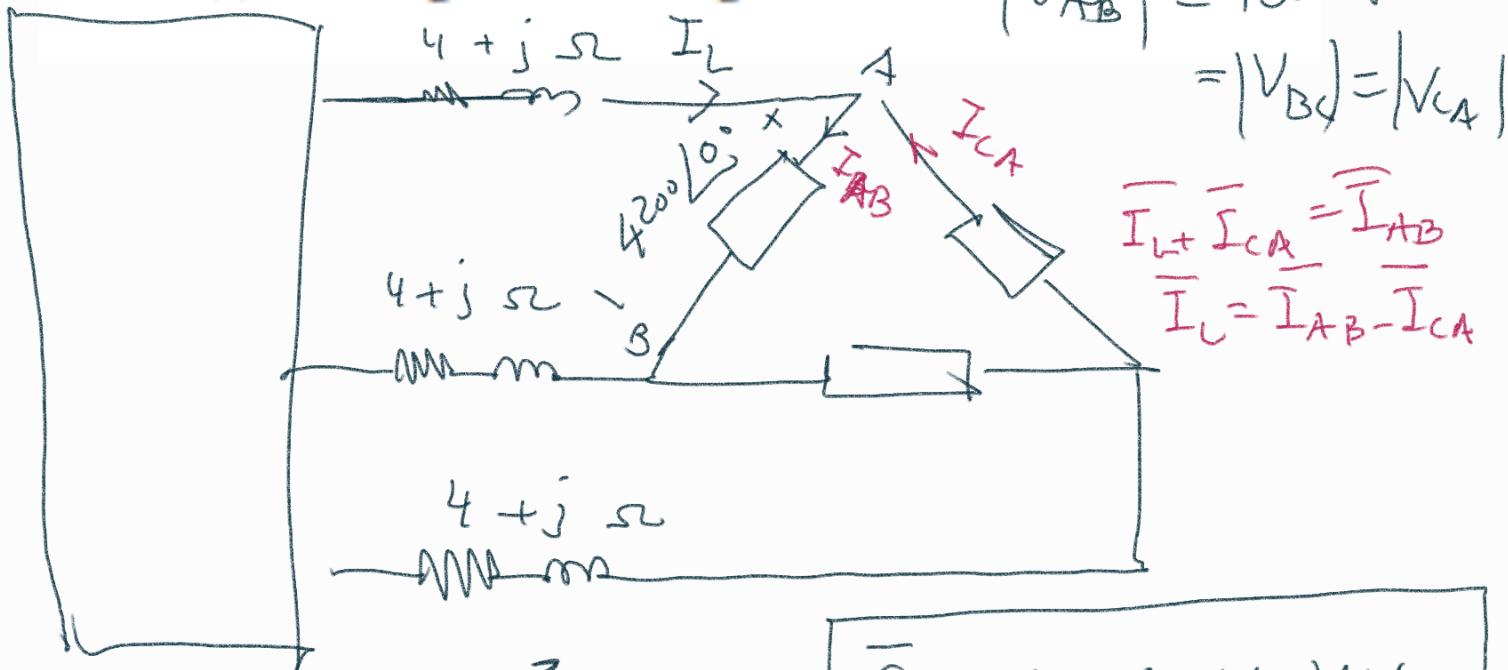- (a) the complex power
(b) the power loss in the line
(c) the voltage at the sending end



a)



$$\bar{S} = 0.75 + j0.66 \text{ MVA}$$

b) I_L 'ye ihtiyac var.

$$P_{\text{line}} = 3 \times 4 \times |I_L|^2$$

$$P = 0.75 \times 10^6 \text{ W} = \sqrt{3} \times 4200 \times I_L \times \cos \theta$$

$$I_L = \frac{10^6}{4200\sqrt{3}} \approx 137.5 \text{ A}_{\text{rms}}$$

$$P_{\text{line}} = 3 \times 4 \times 137.46^2 = 226.7 \text{ KW}$$


c) $\bar{V}_{ab} = (4 + j) \bar{I}_L + \bar{V}_{AB}$

$$\bar{V}_{AB} = 4200 \angle 0^\circ$$

$$\bar{S}_\phi = 0.25 + j0.22 \text{ MVA} = 4200 \angle 0^\circ \times \bar{I}_{AB}^*$$

yükteki faz akımı, $\rightarrow \bar{I}_{AB} = \frac{(0.25 - j0.22) \times 10^6}{4200} = 59.5 - j52.4 \text{ A}$

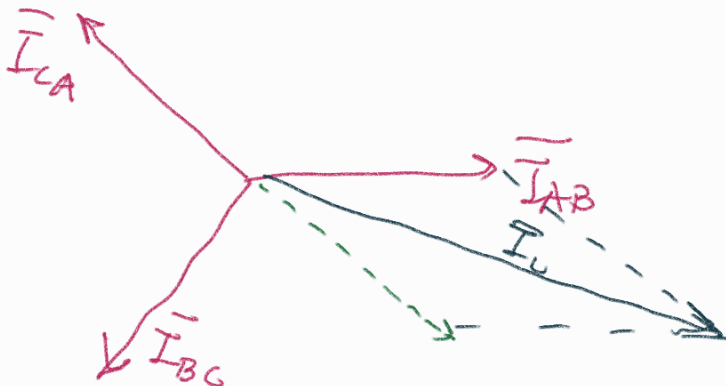hat akımı, $\bar{I}_L = \bar{I}_{AB} \sqrt{3} \angle -30^\circ \Rightarrow \bar{V}_{ab} = 4200 \angle 0^\circ + (4 + j) \bar{I}_L$



12.39 Find the real power absorbed by the load in Fig. 12.58.

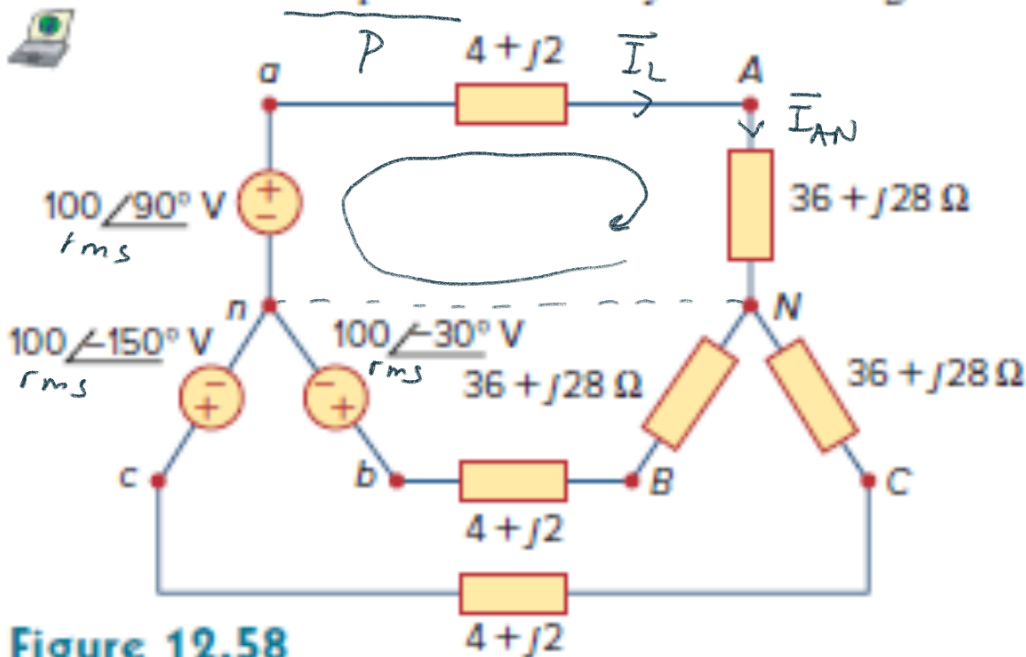


Figure 12.58
For Prob. 12.39.

$$100 \angle 90^\circ = \bar{I}_{AN} (4 + j2 + 36 + j28)$$

$$\bar{I}_{AN} = \frac{100 \angle 90^\circ}{40 + j30} = 2 \angle 53^\circ \text{ A}$$

$$P_A = |\bar{I}_{AN}|^2 \times 36 = 2^2 \times 36 = 144 \text{ W} \Rightarrow P = 3 P_A = 432 \text{ W}$$

$$\begin{aligned}
 V_{AN} : \text{Yükteki faz gerilimi} &: \bar{I}_{AN} \times (36 + j28) \\
 \text{Yükteki hat gerilimi} &: \bar{V}_{AB} = \bar{V}_{AN} \sqrt{3} \angle 30^\circ \\
 \text{Kaynaktaki faz gerilimi} &: V_{an} = 100 \angle 90^\circ \text{ V} \\
 \text{" hat gerilimi} &: \bar{V}_{ab} = \bar{V}_{an} \sqrt{3} \angle 30^\circ
 \end{aligned}$$


12.47 The following three parallel-connected three-phase loads are fed by a balanced three-phase source:

Load 1: 250 kVA, 0.8 pf lagging

Load 2: 300 kVA, 0.95 pf leading

Load 3: 450 kVA, unity pf

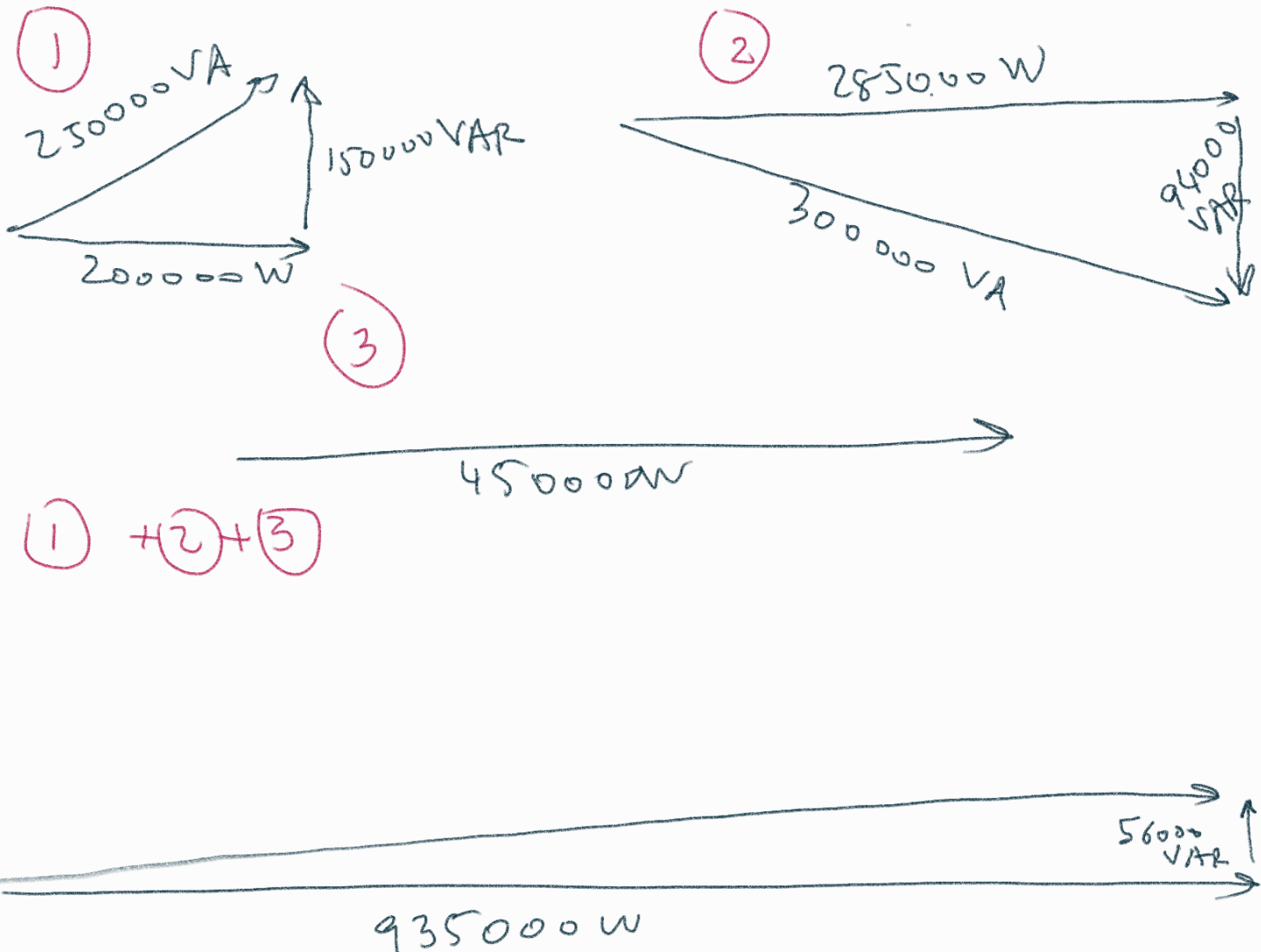If the line voltage is 13.8 kV, calculate the line current and the power factor of the source. Assume that the line impedance is zero.



$$S_{eq} = 935000 + j56000 \text{ VA}$$

$$= \sqrt{3} V_L I_L \cos \theta + j \sqrt{3} V_L I_L \sin \theta$$



$$\checkmark \theta = \tan^{-1} \left(\frac{56}{935} \right) \cong 3.43^\circ$$

$$p.f. = \cos \theta = 0.998 \text{ lagging}$$

$$935000 = \sqrt{3} \cdot 13800 \cdot I_L \cdot 0.998$$

$$I_L \cong 39.2 \text{ A (hat akımı büyüklüğü)}$$

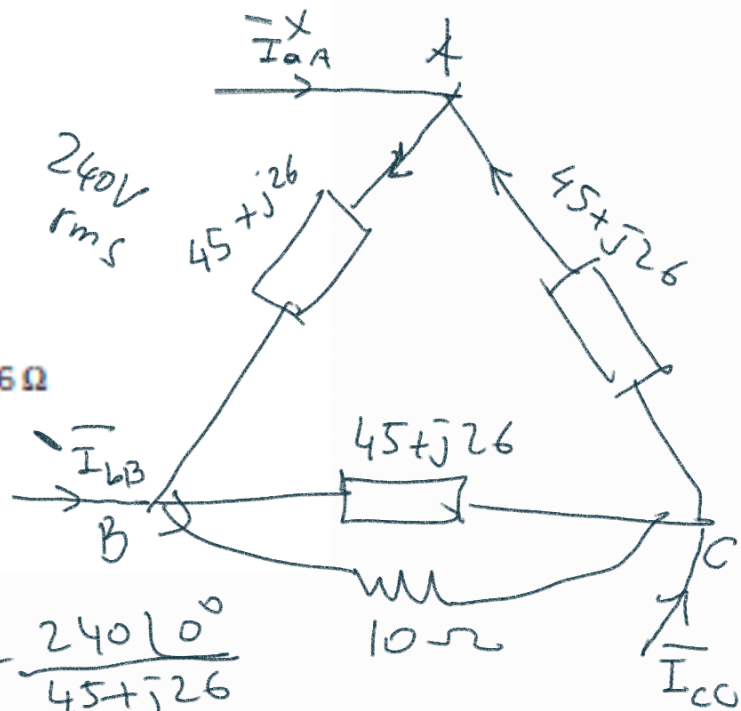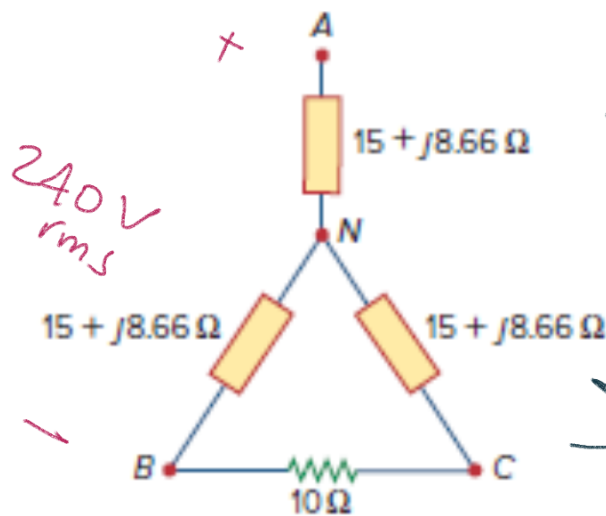12.55 A three-phase supply, with the line-to-line voltage of 240 V rms, has the unbalanced load as shown in Fig. 12.62. Find the line currents and the total complex power delivered to the load.



$$V_{AB} = 240 \angle 0^\circ \rightarrow I_{AB} = \frac{240 \angle 0^\circ}{45 + j26}$$

$$V_{BC} = 240 \angle -120^\circ \rightarrow I_{BC} = \frac{240 \angle -120^\circ}{(45 + j26) \parallel 10}$$

$$V_{CA} = 240 \angle +120^\circ \rightarrow I_{CA} = \frac{240 \angle +120^\circ}{45 + j26}$$

$$\bar{I}_{AB} - \bar{I}_{CA} = \bar{I}_{aA} \rightarrow \text{Line current a}$$

$$\bar{I}_{BC} - \bar{I}_{AB} = \bar{I}_{bB} \rightarrow \text{" " b}$$

$$\bar{I}_{CA} - \bar{I}_{BC} = \bar{I}_{cC} \rightarrow \text{" " c}$$



12.80 A balanced three-phase source furnishes power to the following three loads:

Load 1: 6 kVA at 0.83 pf lagging

Load 2: unknown

Load 3: 8 kW at 0.7071 pf leading

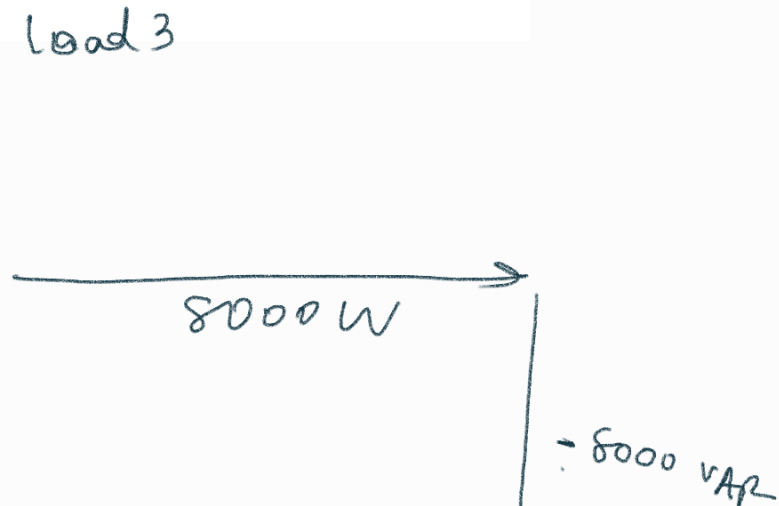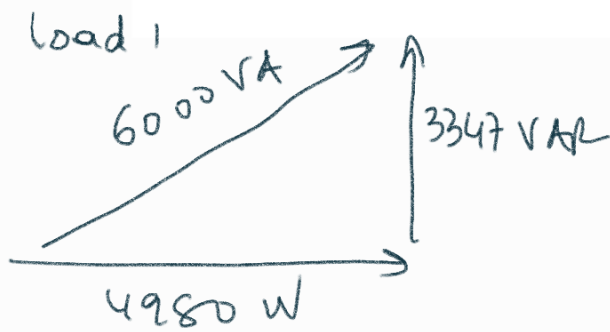If the line current is 84.6 A rms, the line voltage at the load is 208 V rms, and the combined load has a 0.8 pf lagging, determine the unknown load.



$$\begin{aligned}\bar{S}_{\text{eff}} &= \sqrt{3} \times 84.6 \times 208 \times 0.8 + j\sqrt{3} \times 84.6 \times 208 \times 0.6 \\ &= 24383 + j18287 \text{ VA}\end{aligned}$$


$$4980 + 8000 + P_2 = 24383 \Rightarrow P_2 = 11403 \text{ W}$$

$$3347 - 8000 + Q_2 = 18287 \Rightarrow Q_2 = 22940 \text{ VAR}$$

$$\bar{S}_2 = 11403 + j22940 \text{ VA}$$

11.35 A three-phase line has an impedance of $0.1 + j0.8 \Omega/\phi$. The line feeds two balanced three-phase loads connected in parallel. The first load is absorbing a total of 630 kW and absorbing 840 kVAR magnetizing vars. The second load is Y-connected and has an impedance of $15.36 - j4.48 \Omega/\phi$. The line-to-neutral voltage at the load end of the line is 4000 V. What is the magnitude of the line voltage at the source end of the line?

Load 1

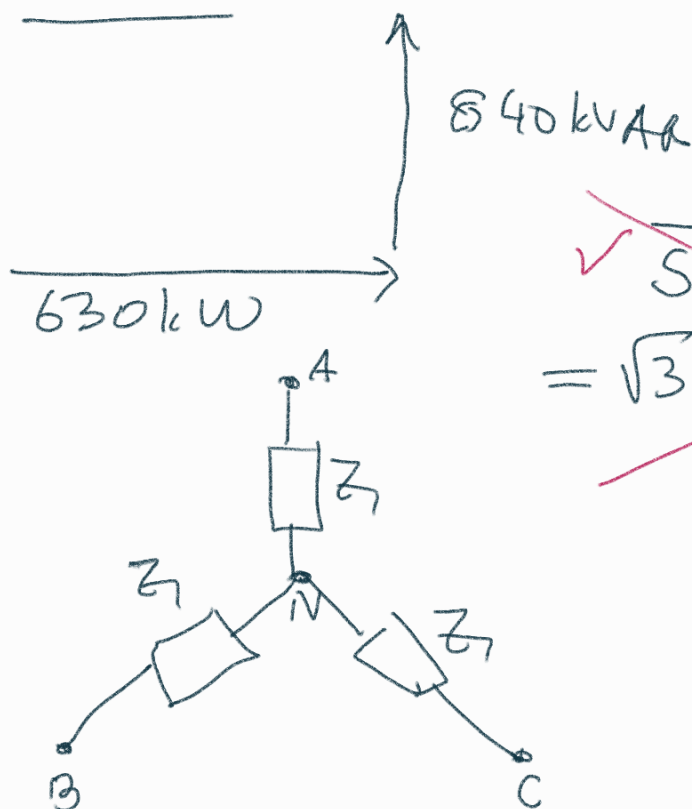

$$\checkmark \vec{S}_1 = 630000 + j840000 \text{ VA}$$

$$= \sqrt{3} V_L I_L \cos \theta + j \sqrt{3} V_L I_L \sin \theta$$

$\swarrow 4000\sqrt{3}$
 $\searrow 4000\sqrt{3}$


$$\vec{V}_{AN} = 4000 \angle 0^\circ$$

$$3 \times \frac{4000^2}{Z_1^*} = 630000 + j840000$$

$$\boxed{\frac{3 \times (4000)^2}{630000 - j840000} = Z_1}$$

$$Z_2 = 15.36 - j4.48$$
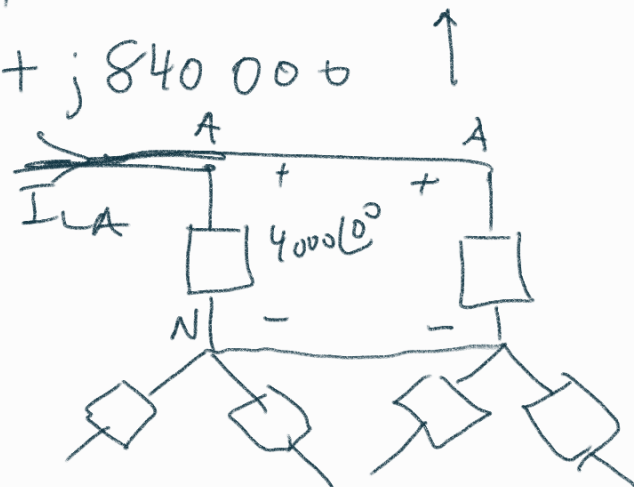
$$\vec{I}_{LA} = \frac{4000 \angle 0^\circ}{(Z_1)} + \frac{4000 \angle 0^\circ}{Z_2}$$



$$\bar{V}_{an} = (0.1 + j0.8) \bar{I}_L + 4000 \angle 0^\circ$$

$\underbrace{\hspace{10em}}_{V_{AN}}$


$$\bar{V}_{ab} = \sqrt{3} \bar{V}_{an} \angle 30^\circ$$

$(V_{ab}) \text{ bulunur} \Rightarrow \sqrt{3} |\bar{V}_{an}|$

11.37 The output of the balanced positive-sequence three-phase source in Fig. P11.37 is 41.6 kVA at a lagging power factor of 0.707. The line voltage at the source is 240 V.

- Find the magnitude of the line voltage at the load.
- Find the total complex power at the terminals of the load.

Figure P11.37

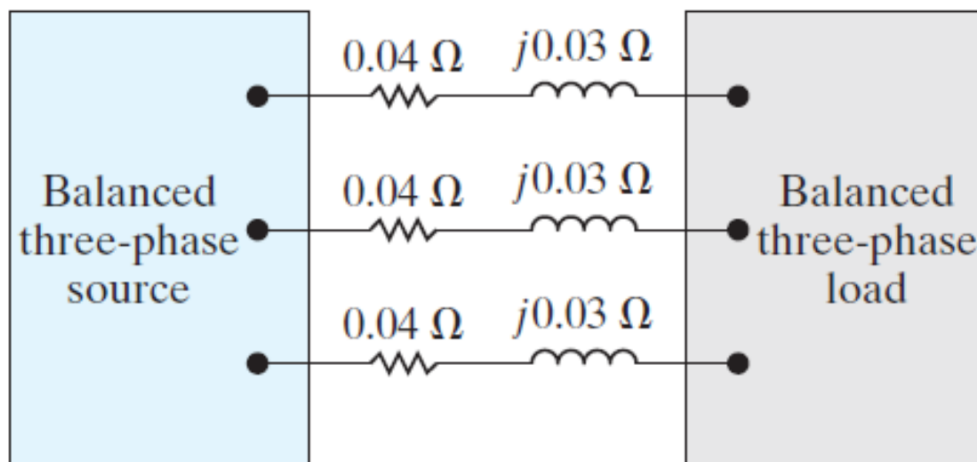

12.81 A professional center is supplied by a balanced three-phase source. The center has four balanced three-phase loads as follows:

Load 1: 150 kVA at 0.8 pf leading

Load 2: 100 kW at unity pf

Load 3: 200 kVA at 0.6 pf lagging

Load 4: 80 kW and 95 kVAR (inductive)

If the line impedance is $0.02 + j0.05 \, \Omega$ per phase and the line voltage at the loads is 480 V, find the magnitude of the line voltage at the source.

CHAPTER 13: MANYETİK BAĞLAŞIMLI DEVRELER (Coupled)

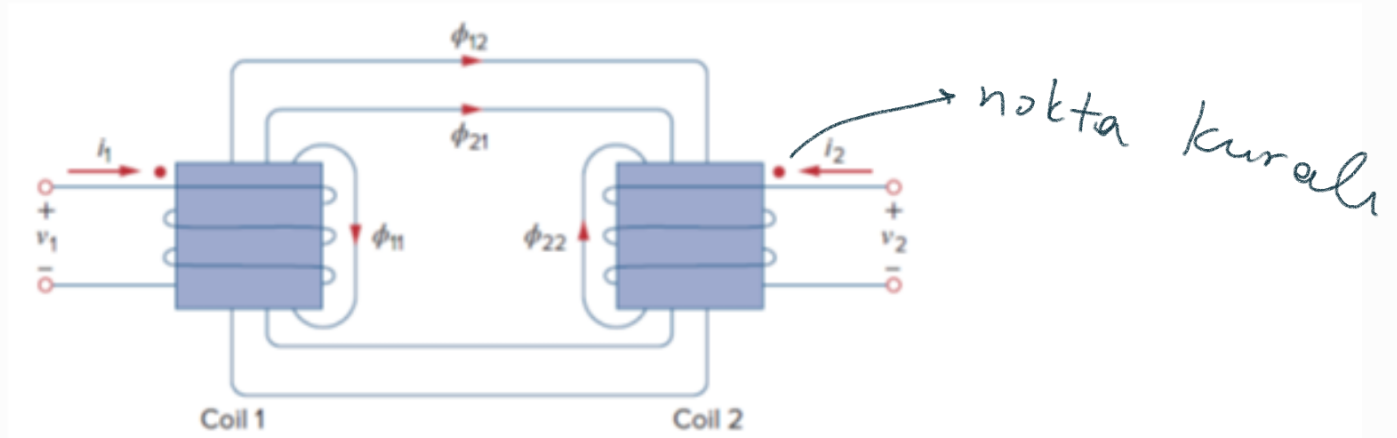


Figure 13.4
Illustration of the dot convention.



Figure 13.7

Time-domain analysis of a circuit containing coupled coils (a) and frequency-domain analysis of a circuit containing coupled coils (b).

Çevre akım yönünü kullanılır

ELE 201 :


$$w = \frac{1}{2} L_1 i_1^2 + \frac{1}{2} L_2 i_2^2 + M i_1 i_2$$

t anında

$M = k \sqrt{L_1 L_2}$

manyetik bağlaşım katsayısı
 $0 \leq k \leq 1$

$k \approx 1$: sıkı bağlaşım (geli) →

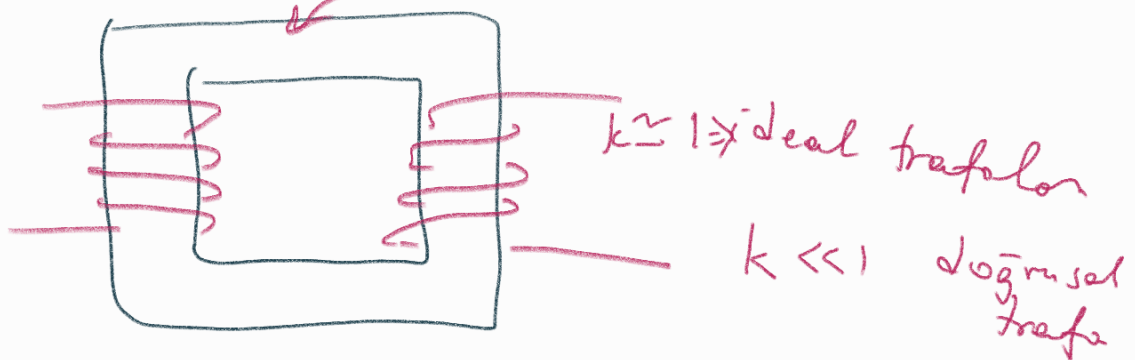

KAYNAK: TRAFO

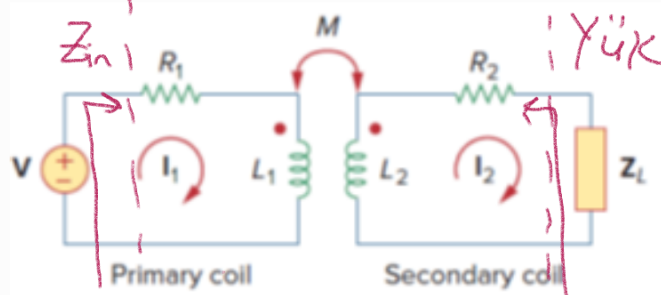


Figure 13.19

A linear transformer.

$$Z_{in} = R_1 + j\omega L_1 + Z_{reflected}$$

$$= R_1 + j\omega L_1 + \frac{\omega^2 M^2}{j\omega L_2 + R_2 + Z_L}$$

$$Z_{Th} = j\omega L_2 + R_2 + \frac{\omega^2 M^2}{j\omega L_1 + R_1}$$

13.4 (a) For the coupled coils in Fig. 13.74(a), show that

$$L_{eq} = L_1 + L_2 + 2M$$

(b) For the coupled coils in Fig. 13.74(b), show that

$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$

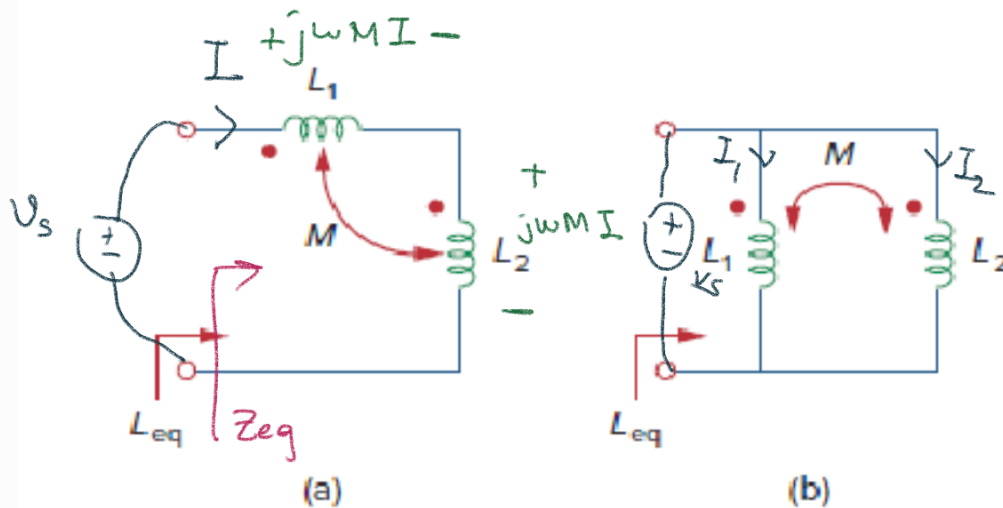


Figure 13.74

For Prob. 13.4.

a)

$$V_s = j\omega L_1 I + j\omega L_2 I + j\omega M I + j\omega M I$$

$$V_s = I j\omega (L_1 + L_2 + 2M)$$

$$Z_{eq} = \frac{V_s}{I} = j\omega \underbrace{(L_1 + L_2 + 2M)}_{L_{eq}}$$

$$b) \quad j\omega L_1 I_1 + j\omega M I_2 = j\omega L_2 I_2 + j\omega M I_1$$

$$\textcircled{1} j\omega (L_1 I_1 + M I_2) = j\omega (L_2 I_2 + M I_1) = V_s$$

$$Z_{eq} = \frac{V_s}{I_1 + I_2}$$

$$Z_{eq} = \frac{(L_1 I_1 + M I_2) j\omega}{I_1 + I_2}$$

$\textcircled{1}$

$$(L_1 - M) I_1 = (L_2 - M) I_2$$

$$I_2 = \frac{L_1 - M}{L_2 - M} I_1$$

$$= \frac{j\omega L_1 I_1 + M \frac{L_1 - M}{L_2 - M} I_1}{I_1 + \frac{L_1 - M}{L_2 - M} I_1}$$

$$= \frac{j\omega L_1 + M \frac{L_1 - M}{L_2 - M}}{1 + \frac{L_1 - M}{L_2 - M}}$$

$$= \frac{j\omega (L_1 L_2 - L_1 M + L_1 M - M^2)}{L_2 - M + L_1 - M}$$

$$Z_{eq} = \frac{j\omega (L_1 L_2 - M^2)}{L_1 + L_2 - 2M}$$

13.9 Find V_x in the network shown in Fig. 13.78.


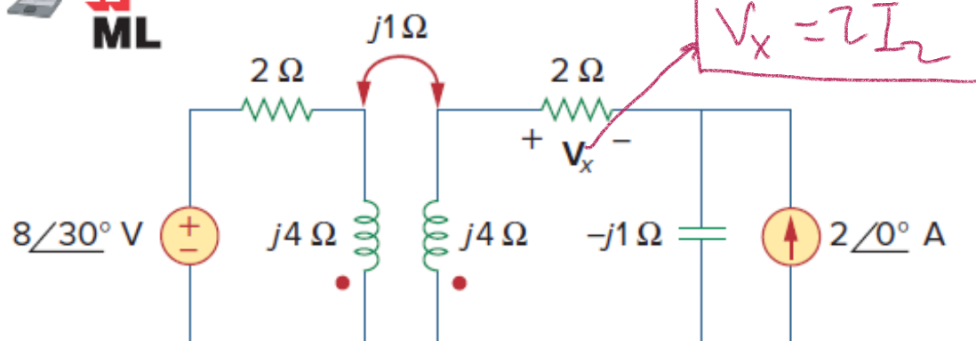


Figure 13.78

For Prob. 13.9.

Kaynak dö.,
 $V_x = 2I_2$

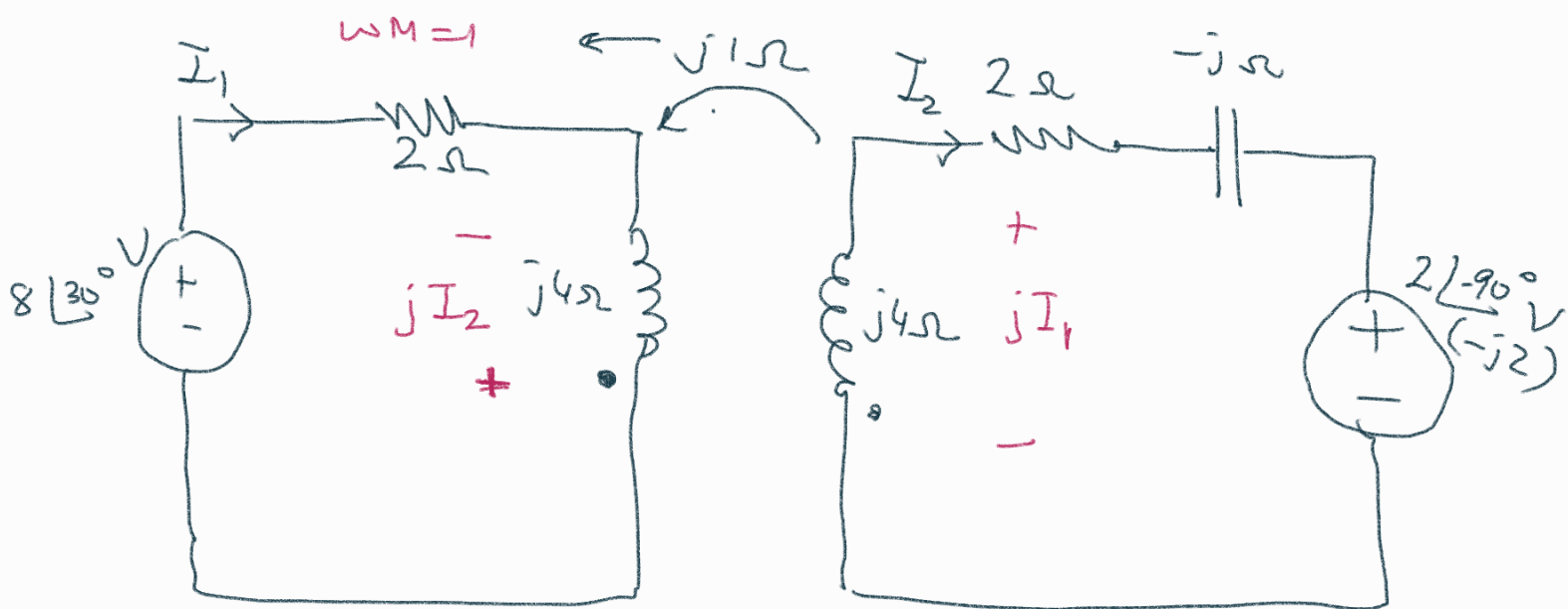

$$8 \angle 30^\circ = 2I_1 + j4I_1 - jI_2 \quad (1)$$

$$j4I_2 + 2I_2 - jI_2 - j2 - jI_1 = 0 \quad (2)$$

$$\begin{aligned} & \left((2+j4)I_1 - jI_2 = 8 \angle 30^\circ \right) \times j \\ & + \left(-jI_1 + (2+j3)I_2 = 2 \angle 90^\circ \right) \times (2+j4) \end{aligned}$$

$$I_2 + (2+j3)(2+j4)I_2 = 8 \angle 120^\circ + 2j(2+j4)$$

$$I_2 (1+4+j8+j6-12) = 8 \angle 120^\circ + 4j-8$$

$$I_2 = \frac{8 \angle 120^\circ + 4j-8}{-7+j14}$$

$$V_X = 2I_2 = \frac{16 \angle 120^\circ + 8j-16}{-7+j14} = \frac{-8+j13.86+8j-16}{-7+j14}$$

$$= \frac{-24+j21.86}{-7+j14}$$

$$V_X = \frac{24-j21.86}{7-j14} = \frac{32.46 \angle -42.3^\circ}{7\sqrt{2} \angle -64^\circ} = 2.07 \angle 21.7^\circ \checkmark$$

13.12 Determine the equivalent L_{eq} in the circuit of Fig. 13.81.

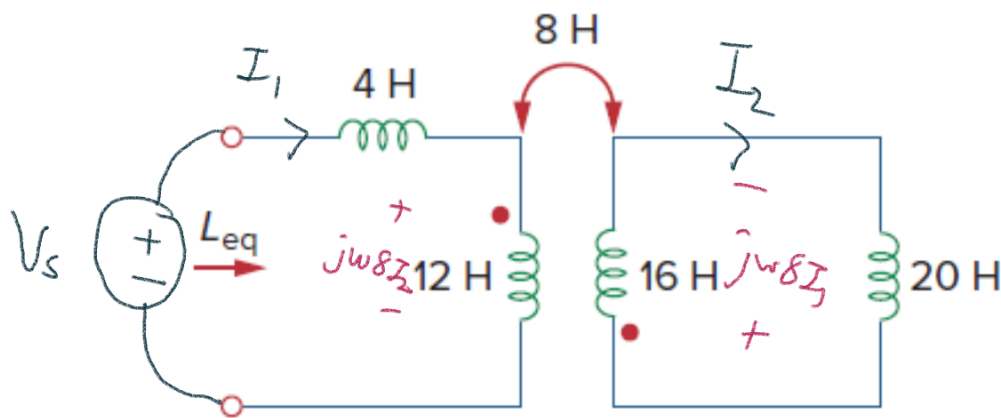


Figure 13.81

For Prob. 13.12.

$$(1) \quad V_s = j\omega 4 I_1 + j\omega 12 I_1 + j\omega 8 I_2$$

$$(2) \quad j\omega 20 I_2 + j\omega 16 I_2 + j\omega 8 I_1 = 0$$

$$\cancel{j\omega 36 I_2} = -\cancel{j\omega 8 I_1}$$

$$\boxed{9 I_2 = -2 I_1} \rightarrow \boxed{I_2 = -\frac{2}{9} I_1}$$

$$(1) \quad V_s = j\omega 4 I_1 + j\omega 12 I_1 - j\omega 8 \times \frac{2}{9} I_1$$

$$\frac{V_s}{I_1} = Z_{eq} = j\omega \left(4 + 12 - \frac{16}{9} \right)$$

$$L_{eq} = 16 - \frac{16}{9} = \frac{128}{9} \text{ H}$$

13.16 Obtain the Norton equivalent at terminals $a-b$ of the circuit in Fig. 13.85.



ML

$\omega M = j$

$I_N = I_k$

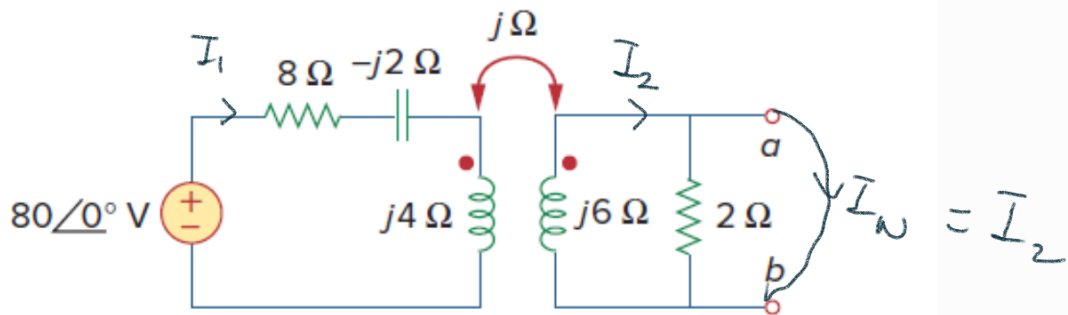


Figure 13.85

For Prob. 13.16.

$$(1) \quad 80 = (8 - j2) I_1 + j4 I_1 - j I_2$$

$$(2) \quad j6 I_2 - j I_1 = 0 \Rightarrow \boxed{6 I_2 = I_1}$$

$$(1) \quad 80 = (8 - j2) 6 I_2 + j24 I_2 - j I_2$$

$$I_2 = \boxed{\frac{80}{48 + j11}} = I_N$$

$$Z_{Th} = (Z_r + j6) \parallel 2$$

$$Z_r = \frac{(\omega M)^2}{8 + j2} = \frac{1}{8 + j2}$$

$$\boxed{Z_{Th} = \left(\frac{1}{8 + j2} + j6 \right) \parallel 2}$$

$$Z_{Th} = \frac{-12 + j48}{8 + j2} \parallel 2$$

13.24 In the circuit of Fig. 13.93,



(a) find the coupling coefficient,

(b) calculate v_o ,


(c) determine the energy stored in the coupled

inductors at $t = 2$ s. $w = \frac{1}{2} 4 i_1(2)^2 + \frac{1}{2} 2 i_2(2)^2 + 1 \times i_1(2) i_2(2)$

$$k = \frac{1}{2\sqrt{2}}$$

$$M = k\sqrt{L_1 L_2} \Rightarrow 1 = k\sqrt{4 \times 2}$$


$$\omega = 4$$

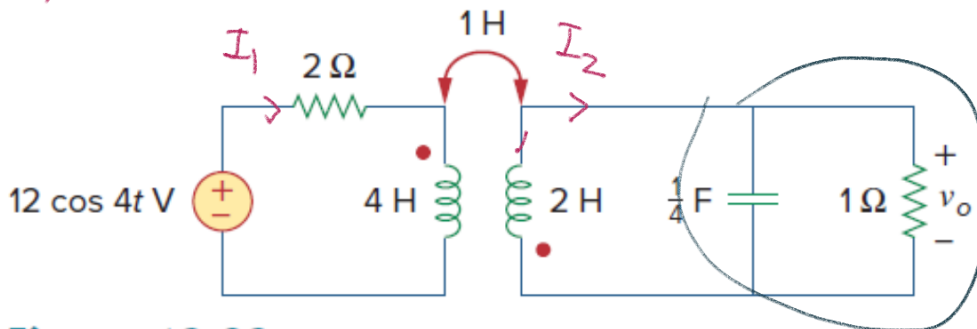

$$j \frac{1}{4} 4 = -j$$

Figure 13.93

For Prob. 13.24.

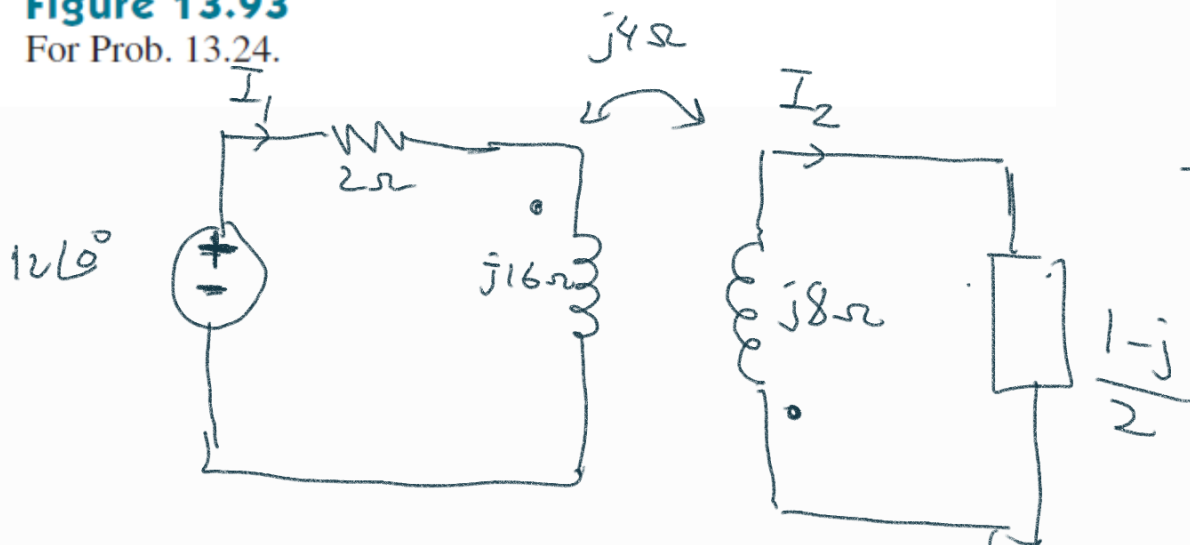

$$(1) \quad 12 = (2 + j16) I_1 + j4 I_2$$

$$(2) \quad j8 I_2 + \frac{1-j}{2} I_2 + j4 I_1 = 0$$

$$\boxed{\frac{1+j15}{2} I_2 = -j4 I_1}$$

$$\boxed{I_1 = \frac{1+j15}{-j8} I_2}$$

$$12 = \left[(2+j16) \frac{(1+j15)}{-j8} + j4 \right] I_2$$

$$12 = \frac{2+j30+j16-240+32}{-j8} I_2$$

$$\frac{-j96}{-206 + j46} = \bar{I}_2 = \frac{96 \angle -90^\circ}{211 \angle 180^\circ - 12.6^\circ} = 0.45 \angle -257.4^\circ \text{ A}$$

$$i_2(t) = 0.45 \cos(4t - 257.4^\circ) \text{ A}$$

$$I_1 = \frac{1 + j15}{-j8} \quad I_2 = \frac{-15}{8} I_2 = -0.84 \cos(4t - 257.4^\circ)$$

$$I_1 = 0.84 \cos(4t - 77.4^\circ) \text{ A}$$

8rad

$$t = 2 \sin 2e :$$

$$i_2(2) = 0.45 \cos\left(8 \times \frac{180}{\pi} - 257.4^\circ\right) = -0.45 \times 0.93 = -0.42$$

$$i_1(2) = 0.84 \cos\left(8 \times \frac{180}{\pi} - 77.4^\circ\right) = 0.93 \times 0.84 = 0.78$$

$$w = \frac{1}{2} \cdot 4 \cdot 0.78^2 + \frac{1}{2} \cdot 2 \cdot 0.42^2 - 1 \times 0.42 \times 0.78$$

***13.28** In the circuit of Fig. 13.97, find the value of X that will give maximum power transfer to the 20- Ω load.

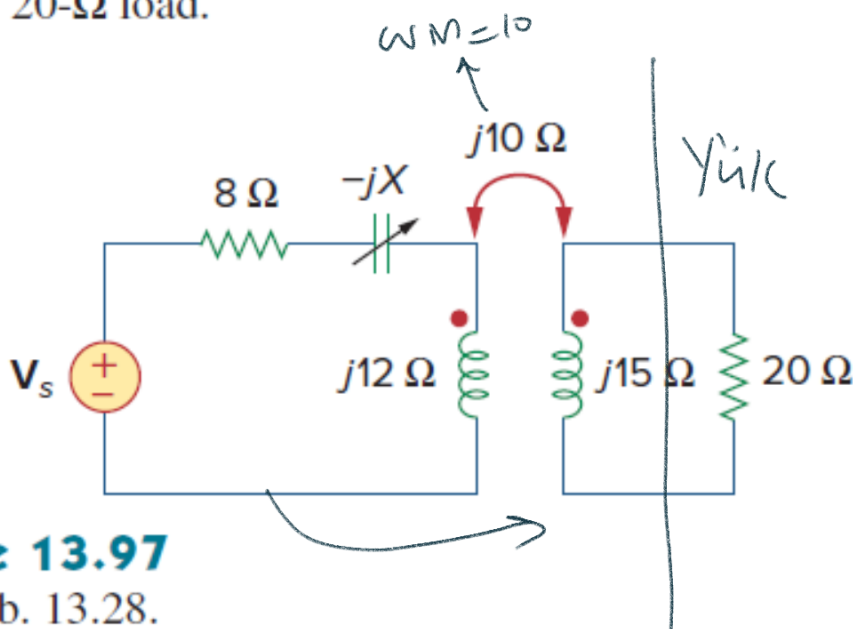


Figure 13.97

For Prob. 13.28.

maks güç aktarımı için $20 = |Z_{Th}| = 1 \text{ malı}$

$$Z_{Th} = j15 + \frac{100}{8 - jX + j12}$$

$$= \frac{j120 + 15X - 180 + 100}{8 + j(12 - X)} = \frac{(15X - 80) + j120}{8 + j(12 - X)}$$

$$\frac{(15X - 80)^2 + 120^2}{64 + (12 - X)^2} = 400$$

$$\frac{225X^2 - 2400 + 6400 + 14400}{64 + 144 - 24X + X^2} = 400$$

$$\underline{225X^2} + 18400 = 25600 + 57600 - \underline{9600X} + \underline{400X^2}$$

$$0 = 175X^2 - 9600X + 64800$$

$$X_{1,2} = \frac{9600 \mp \sqrt{9600^2 - 4 \cdot 175 \cdot 64800}}{350}$$

$$X_{1,2} = \frac{9600 \mp 6840}{350} = \left(\underset{?}{47}, \underset{?}{7.9} \right)$$

13.33 Determine the input impedance of the air-core transformer circuit of Fig. 13.102.

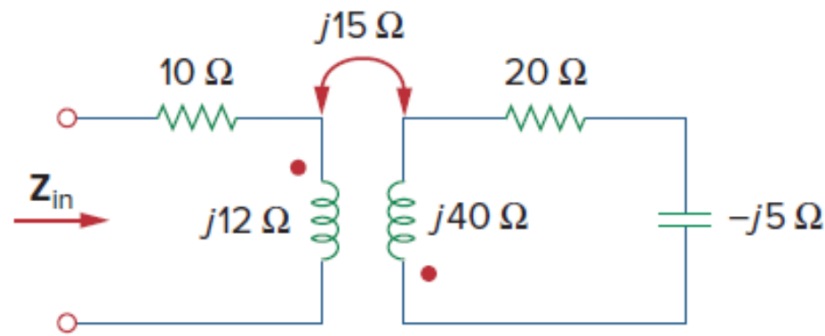


Figure 13.102

For Prob. 13.33.

$$Z_{in} = 10 + j12 + \frac{225}{20 + j35}$$

$$= \frac{200 + j350 + j240 - 420 + 225}{20 + j35}$$

$$= \frac{5 + j590}{20 + j35} = \frac{1 + j118}{4 + j7} \approx \frac{118 \angle 90^\circ}{\sqrt{65} \angle 60^\circ}$$

$$\approx 14.8 \angle 30^\circ$$

$$= 8 + j7.4 \Omega$$

13.39 A 1,200/240-V rms transformer has impedance $60 \angle -30^\circ \Omega$ on the high-voltage side. If the transformer is connected to a $0.8 \angle 10^\circ \Omega$ load on the low-voltage side, determine the primary and secondary currents when the transformer is connected to 1,200 V rms.