

13.39 A 1,200/240-V rms transformer has impedance $60 \angle -30^\circ \Omega$ on the high-voltage side. If the transformer is connected to a $0.8 \angle 10^\circ \Omega$ load on the low-voltage side, determine the primary and secondary currents when the transformer is connected to 1,200 V rms.

$$\left| \frac{V_2}{V_1} \right| = \left| \frac{N_2}{N_1} \right| = \left| \frac{I_1}{I_2} \right|$$

Nokta kuralı


1) Hen V_1 hen de V_2 noktalı tarafta pozitif ise gerilim ilişkisi pozitif. Aksi halde neg.

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$

2) Hen I_1 hen de I_2 noktalı taraftan giriyor veya çıkıyorsa, akım ilişkisi negatif

$$\frac{I_1}{I_2} = - \frac{N_2}{N_1}$$

aksi halde pozitif.

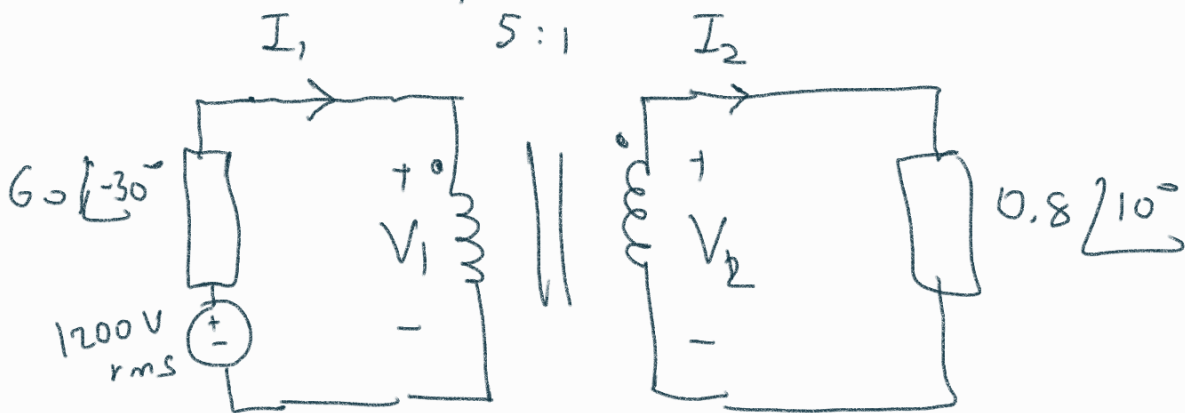

4 bilinmeyen, 4 denklem.

$$\textcircled{1} \quad 1200 = 60 \angle -30^\circ \bar{I}_1 + \bar{V}_1$$

$$\textcircled{2} \quad \bar{V}_2 = 0.8 \angle 10^\circ \bar{I}_2$$

$$\textcircled{3} \quad \bar{V}_1 = 5 \bar{V}_2$$

$$\textcircled{4} \quad \bar{I}_2 = 5 \bar{I}_1$$

$$\textcircled{1} \quad 1200 = 60 \angle -30^\circ \bar{I}_1 + 5 \bar{V}_2$$

$$\textcircled{2} \quad \bar{V}_2 = 4 \angle 10^\circ \bar{I}_1$$

$$1200 = 60 \angle -30^\circ \bar{I}_1 + 20 \angle 10^\circ \bar{I}_1$$

$$\bar{I}_1 = \frac{1200}{60 \angle -30^\circ + 20 \angle 10^\circ} = \frac{1200}{52 - j30 + 20 + j3.5}$$

$$\bar{I}_1 = \frac{1200}{72 - j26.5} = \frac{1200}{76.7 \angle -20.2^\circ}$$

$$\bar{I}_1 = 15.6 \angle 20.2^\circ \text{ A}_{\text{rms}}$$

$$\bar{I}_2 = 78 \angle 20.2^\circ \text{ A}_{\text{rms}}$$

***13.44** In the ideal transformer circuit of Fig. 13.109, find $i_1(t)$ and $i_2(t)$.


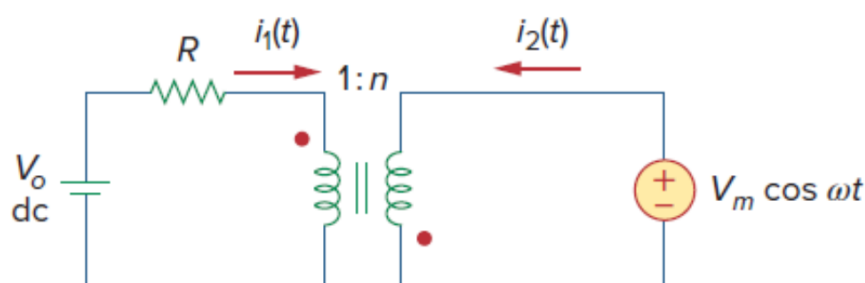


Figure 13.109

For Prob. 13.44.


DC:

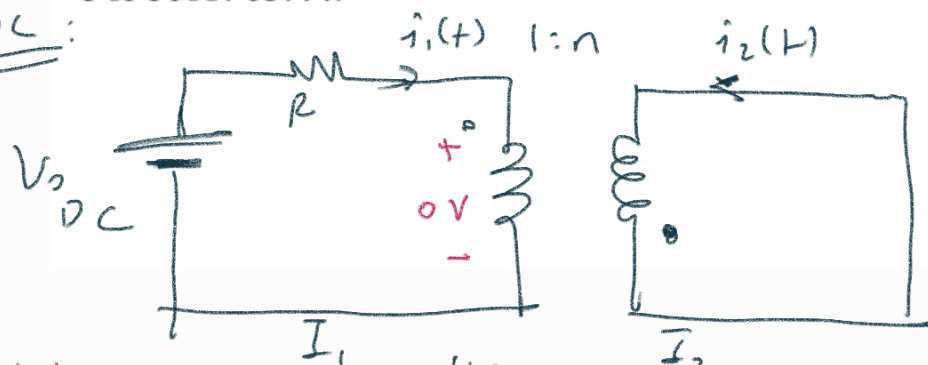

$$i_1 = \frac{V_o}{R} \text{ DC}$$

$$i_2 = 0 \text{ DC}$$

AC:

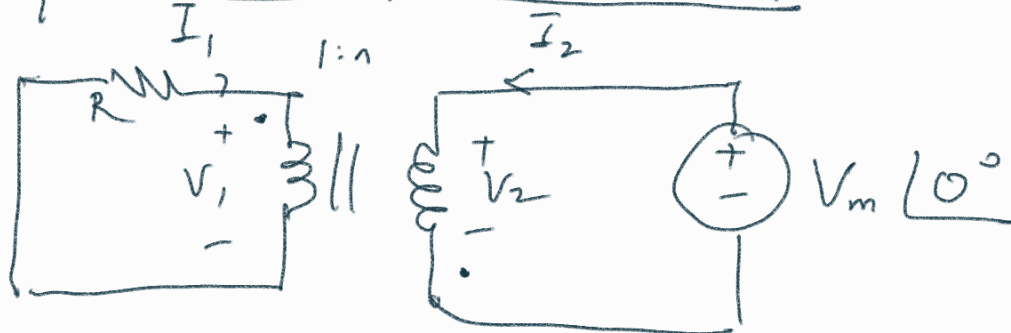

$$\overline{V}_2 = V_m \angle 0^\circ$$

$$\boxed{I_2 = \frac{I_1}{n}}$$

$$\overline{V}_1 = -\frac{V_m}{n} \angle 0^\circ$$

$$\overline{I}_1 R - \frac{V_m}{n} = 0 \Rightarrow \overline{I}_1 = \frac{V_m}{nR} \xrightarrow{\mathcal{P}^{-1}} i_1(t) = \frac{V_m}{nR} \cos(\omega t)$$

$$\overline{I}_2 = \frac{V_m}{n^2 R} \xrightarrow{\mathcal{P}^{-1}} i_2(t) = \frac{V_m}{n^2 R} \cos(\omega t)$$

Toplanda

$$i_1(t) = \frac{V_0}{R} + \frac{V_m}{nR} \cos(\omega t)$$

$$i_2(t) = \frac{V_m}{n^2 R} \cos(\omega t)$$

13.50 Calculate the input impedance for the network in Fig. 13.115.

ML

Figure 13.118

For Prob. 13.53.

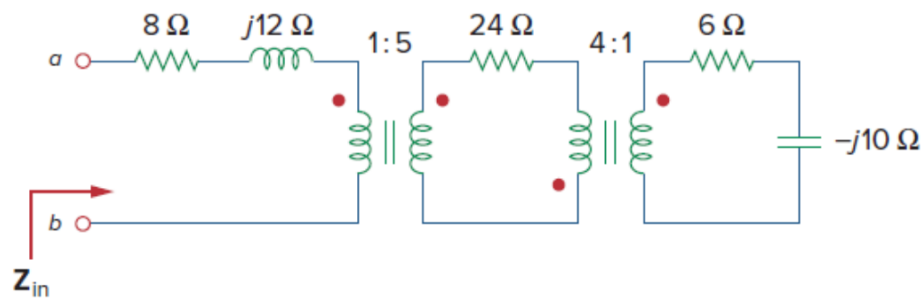


Figure 13.115

For Prob. 13.50.

$$\begin{aligned} Z_{in} &= \left((6 - j10) \times 16 + 24 \right) \frac{1}{25} + 8 + j12 \\ &= \frac{96 - j160 + 24}{25} + 8 + j12 = \frac{120 - j160}{25} + 8 + j12 \\ &= 4.8 - j6.4 + 8 + j12 \\ Z_{in} &= 12.8 + j5.6 \end{aligned}$$

- 13.51** Use the concept of reflected impedance to find the input impedance and current $\mathbf{I}_1$ in Fig. 13.116.

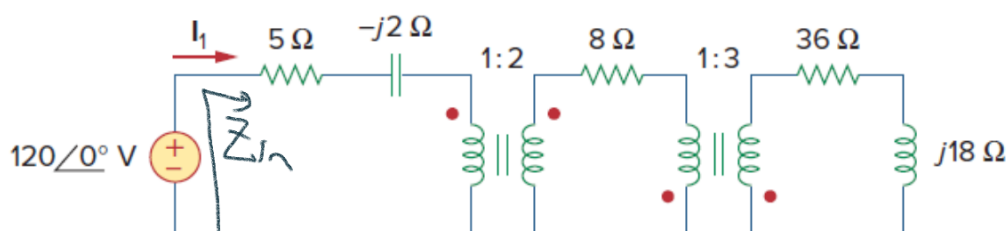


Figure 13.116
For Prob. 13.51.

$$Z_{in} = \left((36 + j18) \frac{1}{9} + 8 \right) \frac{1}{4} + 5 - j2$$

$$= (4 + j2 + 8) \frac{1}{4} + 5 - j2$$

$$= 3 + j0.5 + 5 - j2 = 8 - j1.5 \, \Omega$$

$$\mathbf{I}_1 = \frac{120 \angle 0^\circ}{8 - j1.5} = \frac{120 \angle 0^\circ}{8.14 \angle -10.6^\circ} = 14.7 \angle +10.6^\circ \text{ A}$$


- 13.58** Determine the average power absorbed by each resistor in the circuit of Fig. 13.123.



ML

$$P = \frac{1}{2} \times 20 \times 4.5^2 = 202.5 \text{ W}$$
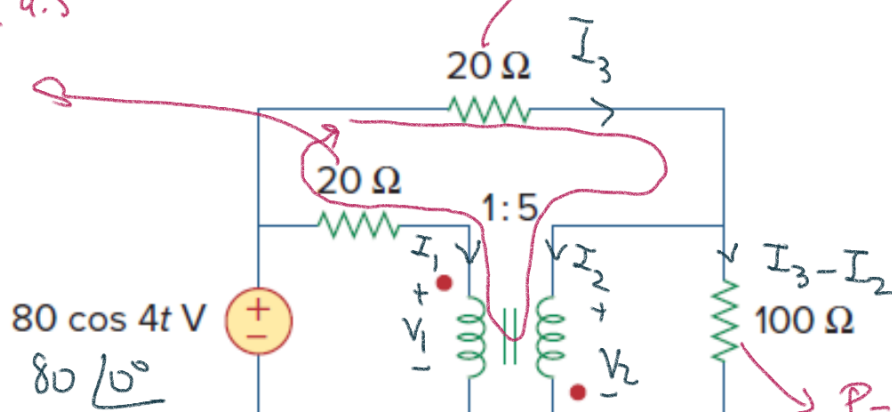
$$P = \frac{1}{2} \times 20 \times 1.4^2 = 19.6 \text{ W}$$



$$P = \frac{1}{2} \times 100 \times 0.5^2 = 12.5 \text{ W}$$

Figure 13.123
For Prob. 13.58.

$$\textcircled{1} \quad 80 = 20I_1 + V_1$$

$$100(I_3 - I_2) = V_2$$

$$\textcircled{3} \quad 20I_3 + V_2 - V_1 - 20I_1 = 0$$

$$V_2 = -5V_1$$

$$I_1 = 5I_2$$

$$\textcircled{1} \quad 80 = 100I_2 + V_1$$

$$\textcircled{2} \quad 100I_3 - 100I_2 = -5V_1$$

$$\textcircled{3} \quad 20I_3 - 5V_1 - V_1 - 100I_2 = 0 \Rightarrow 20I_3 - 6V_1 = 100I_2$$

$$\textcircled{3} \quad -100I_2 + 20I_3 = 6V_1$$

$$\textcircled{2} + \textcircled{3} \Rightarrow 80I_3 = -11V_1$$

$$\boxed{V_1 = -\frac{80}{11}I_3}$$

$$\textcircled{2} \quad 100I_3 - 100I_2 = \frac{400}{11}I_3 \Rightarrow 64I_3 = 100I_2$$

$$\boxed{I_3 = \frac{100}{64}I_2}$$

$$\textcircled{1} \quad 80 = 100I_2 - \frac{80}{11}I_3$$

$$80 = 100I_2 - \underbrace{\frac{80 \times 100}{11 \times 64}}_{11} I_2$$

$$80 = 89I_2 \rightarrow I_2 = 0.9A$$

$$I_3 = 1.4A$$

$$V_1 = -10.2V$$

$$I_1 = \frac{80 - V_1}{20} = \frac{90.2}{20} \approx 4.5A$$

$$I_3 - I_2 = 0.5A$$

13.63 Find the mesh currents in the circuit of Fig. 13.128


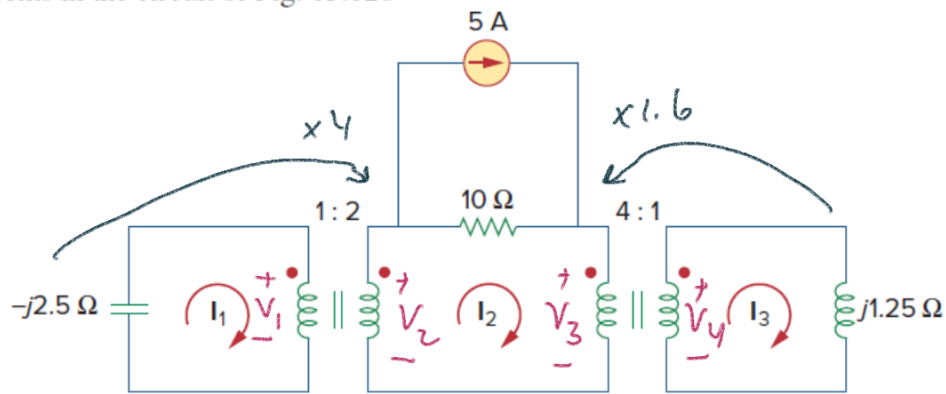


Figure 13.128

For Prob. 13.63.

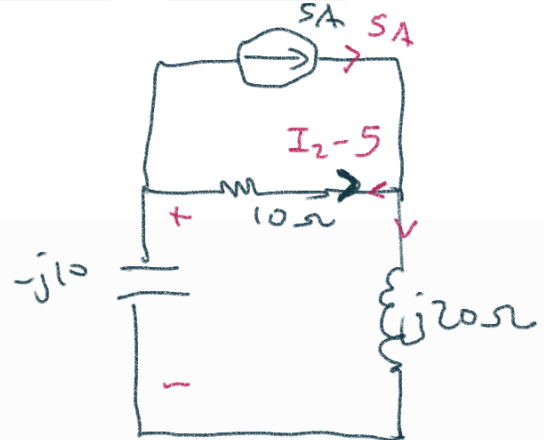- ① $V_1 = j2.5 I_1$
 - ② $V_2 = 2 V_1$
 - ③ $I_1 = 2 I_2$
 - ④ $-V_2 + 10(I_2 - 5) + V_3 = 0$
 - ⑤ $V_3 = 4 V_4$
 - ⑥ $I_3 = 4 I_2$
 - ⑦ $V_4 = j1.25 I_3$
-
- ③ $I_1 = 5 - 5j \approx 7 \angle -45^\circ$
 - ⑥ $I_3 = 10 - 10j \approx 14 \angle -45^\circ$



$$-5 \times \frac{j10}{10 + j10} = I_2 - 5$$

$$\frac{-50 \angle 90^\circ}{10\sqrt{2} \angle 45^\circ} = I_2 - 5$$

$$I_2 = 5 - \frac{5 \angle 45^\circ}{\sqrt{2}}$$

$$= 5 - 2.5 - 2.5j$$

$$I_2 = 2.5 - 2.5j$$

$$\approx 3.5 \angle -45^\circ$$

13.68 In the ideal autotransformer of Fig. 13.131, calculate I_1 , I_2 , and I_o . Find the average power delivered to the load.



ototrafo → tek sarım var.

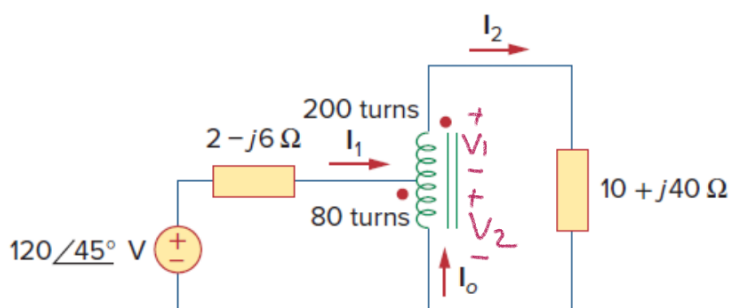


Figure 13.131

For Prob. 13.68.

$$(1) -120 \angle 45^\circ + (2-j6) I_1 + V_2 = 0$$

$$(2) -V_2 - V_1 + (10+j40) I_2 = 0$$

$$(3) V_1 = 2.5 V_2$$

$$(4) I_0 = -2.5 I_2$$

$$(5) I_1 + I_0 = I_2 \rightarrow I_1 = 3.5 I_2$$

$$(2) 3.5 V_2 = (10+j40) I_2$$

$$(1) 120 \angle 45^\circ = (2-j6) I_1 + \frac{10+j40}{3.5} I_2$$

$$120 \angle 45^\circ = I_2 \left[\frac{3.5(2-j6) + 10+j40}{3.5} \right]$$

$$= I_2 \left[\frac{24.5 - j73.5 + 10 + j40}{3.5} \right]$$

$$120 \angle 45^\circ = I_2 \left[\frac{34.5 - j23.5}{3.5} \right]$$

$$\frac{420 \angle 45^\circ}{34.5 - j23.5} = I_2 = \frac{420 \angle 45^\circ}{42 \angle -34^\circ} = 10 \angle 11^\circ \text{ A} //$$

$$I_1 = 3.5 I_2 = 35 \angle 11^\circ \text{ A} //$$

$$I_0 = -2.5 I_2 = -25 \angle 11^\circ$$

$$= 25 \angle -169^\circ \text{ A} //$$

13.77 The three-phase system of a town distributes power with a line voltage of 13.2 kV. A pole transformer connected to single wire and ground steps down the high-voltage wire to 120 V rms and serves a house as shown in Fig. 13.139.

- Calculate the turns ratio of the pole transformer to get 120 V.
- Determine how much current a 100-W lamp connected to the 120-V hot line draws from the high-voltage line.

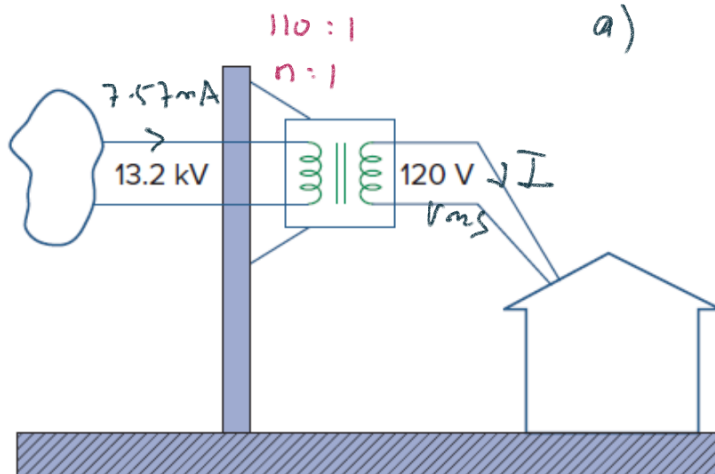


Figure 13.139
For Prob. 13.77.

$$a) \quad n = \frac{13200}{120}$$

$$n = 110 //$$

$$b) \quad 120 \bar{I}^* = 100$$

$$|I| = \frac{1}{1.2} \text{ A}$$

$$I_{\text{high voltage}} = \frac{I}{110}$$

$$= \frac{1}{132} \text{ A}$$

$$= 7.57 \text{ mA}$$

13.95 Ten bulbs in parallel are supplied by a 7,200/120-V transformer as shown in Fig. 13.147, where the bulbs are modeled by the 144-Ω resistors. Find:

- the turns ratio n ,
- the current through the primary winding.

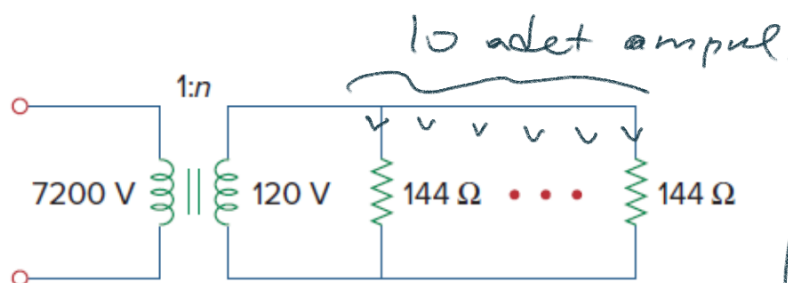


Figure 13.147


For Prob. 13.95

$$a) \quad n = \frac{1}{60} \text{ (malider)}$$

$$b) \quad \text{her bir akım} = \frac{120}{144} = \frac{100}{120} \text{ A}$$

$$\text{Toplam ikinci akım} = \frac{1000}{120}$$
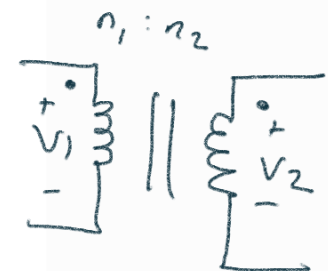
$$\text{Birinci akım} = \frac{1000}{120} \cdot \frac{1}{60} \text{ olur.}$$



$$\frac{V_2}{V_1} = \frac{n_2}{n_1}$$


notlata ters olsaydı

$$\frac{V_2}{V_1} = -\frac{n_2}{n_1}$$

13.91 A 25,000/240-V rms distribution transformer has a primary current rating of 75 A.


- (a) Find the transformer kVA rating.
(b) Calculate the secondary current.

$$25000 \times 75 = 1875 \text{ kVA}$$
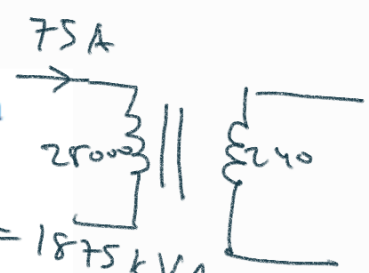
$$I_2 = \frac{25000}{240} \times 75 = 7812.5 \text{ A}$$


13.92 A 4,800-V rms transmission line feeds a distribution transformer with 1,200 turns on the primary and 28 turns on the secondary. When a 10-Ω load is connected across the secondary, find:

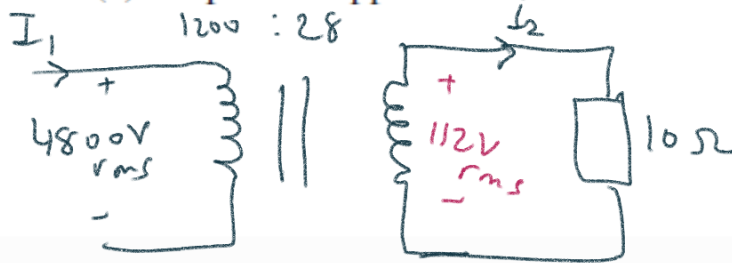- (a) the secondary voltage,
(b) the primary and secondary currents,
(c) the power supplied to the load.



a) $\frac{28}{1200} \times 4800 = 112 \text{ V}_{rms}$

b) $I_2 = 11.2 \text{ A}$ ikinci akım


$I_1 = \frac{28}{1200} \times 11.2 = 0.261 \text{ A}$ birinci akım

c) $P_{10\Omega} = \frac{112^2}{10} = 1264 \text{ W}$ güç verilir güç.

9.74 The value of k in the circuit in Fig. P9.74 is adjusted so that Z_{ab} is purely resistive when $\omega = 4 \text{ krad/s}$. Find Z_{ab} .

$$M = k\sqrt{L_1 L_2}$$

Figure P9.74

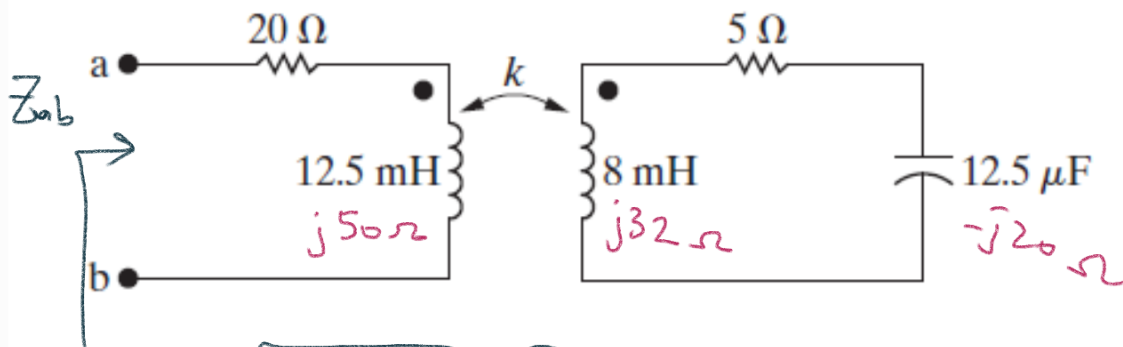

$$M = k\sqrt{12.5 \times 8 \times 10^{-6}} = k 10^{-2}$$

$$\omega M = 4000 \times k \times 10^{-2} = 40k$$

$$Z_{ab} = 20 + j50 + \frac{40^2 k^2}{5 + j12}$$

$$= 20 + j50 + \frac{1600k^2(5 - j12)}{169}$$

$Z_{ab} \in \mathbb{R}$ istiyorsa, 0 zaman

$$50 - \frac{1600k^2 \times 12}{169} = 0$$

$$k = \sqrt{\frac{50 \times 169}{1600 \times 12}} = 0.66 \text{ olmalıdır.}$$

9.77 The sinusoidal voltage source in the circuit seen in Fig. P9.77 is operating at a frequency of 200 krad/s. The coefficient of coupling is adjusted until the peak amplitude of i_1 is maximum.


PSPICE
MULTISIM

a) What is the value of k ?

b) What is the peak amplitude of i_1 if

→ $v_g = 560 \cos(2 \times 10^5 t) \text{ V}$
 $\omega M = 2 \times 10^5 k \sqrt{10^{-3} \times 4 \times 10^{-3}}$
 $= k 400$

Figure P9.77

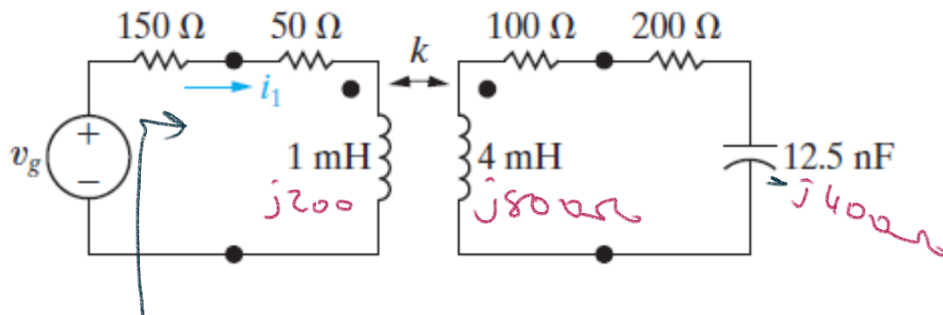

$$\frac{10^9}{j 12.5 \times 2 \times 10^5}$$

$$= \frac{10^4}{j 25} = -j 400$$

$|Z_{in}|$ minimize edilecek.

$$Z_{in} = 150 + 50 + j200 + \frac{k^2 160000}{300 + j400}$$

$$= 200 + j200 + \frac{k^2 1600 (3 - j4)}{(3 + j4)(3 - j4)}$$

$$= 200 + j200 + k^2 64 (3 - j4)$$

$$= (200 + 192k^2) + j(200 - 256k^2)$$

$$\arg \min_k \left\{ (200 + 192k^2)^2 + (200 - 256k^2)^2 \right\} = k^*$$

$$\arg \min_k \left\{ (25 + 24k^2)^2 + (25 - 32k^2)^2 \right\}$$

$$\cancel{2(25 + 24k^2) 48} = \cancel{2(25 - 32k^2) 64} = 0$$

$$\cancel{(25 + 24k^2) 48} = \cancel{(25 - 32k^2) 64}$$

$$75 + 72k^2 = 100 - 128k^2$$

$$200k^2 = 25$$

$$k = \sqrt{\frac{25}{200}} = \sqrt{\frac{1}{8}} = \frac{1}{2\sqrt{2}} \text{ olmalı.}$$

0 zaman:

$$Z_{in} = 200 + j200 + 8(3 - j4) \text{ olur.}$$


$$= 224 + j168$$

$$I_1 = \frac{560 \angle 0^\circ}{224 + j168}$$

$$\text{peak amplitude} = |I_1| = 2 \text{ A}$$

- 10.64** a) If N_1 equals 1000 turns, how many turns should be placed on the N_2 winding of the ideal transformer in the circuit seen in Fig. P10.64 so that maximum average power is delivered to the 6800Ω load?
- b) Find the average power delivered to the 6800Ω resistor.
- c) What percentage of the average power delivered by the ideal voltage source is dissipated in the linear transformer?

Figure P10.64

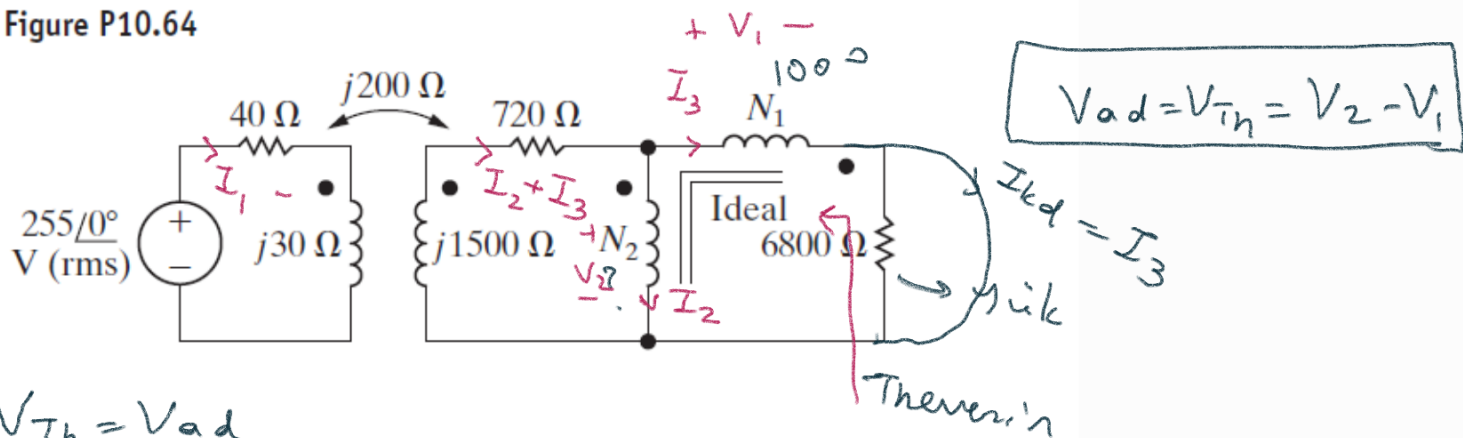

$$\underline{V_{Th} = V_{ad}}$$

$$(1) \quad 255 = 40I_1 + j30I_1 - j200(I_2 + I_3)$$

$$(2) \quad j1500(I_2 + I_3) + 720(I_2 + I_3) + V_2 - j200I_1 = 0$$

$$(3) \quad \frac{V_2}{V_1} = \frac{-N_2}{1000}$$

$$(4) \quad \frac{I_2}{I_3} = \frac{1000}{N_2}$$

$$(3) \quad 1000 V_2 = -N_2 V_1$$

örnek devre olduğundan $I_3 = 0 \rightarrow$ (4) $I_2 = 0$

$$(1) 255 = (40 + j30) I_1 \rightarrow I_1 = \frac{255}{50 \angle 37^\circ} \text{ A}$$

$$(2) V_2 = j200 I_1 \rightarrow V_2 = 200 \angle 90^\circ \frac{255}{50 \angle 37^\circ} = 1020 \angle 53^\circ \text{ V}$$

$$(3) V_1 = -\frac{1000 V_2}{N_2} \rightarrow -\frac{1000}{N_2} \times 1020 \angle 53^\circ \text{ V}$$

$$V_{Th} = V_2 - V_1 = 1020 \angle 53^\circ \left(1 + \frac{1000}{N_2} \right)$$

$I_{kd} = I_3$

$V_2 = V_1$ olmalı $\rightarrow 0$ zaman $V_2 = V_1 = 0$

Çünkü aynı zamanda

(3)'ü sağlanması lazım.

$$(1) 255 = (40 + j30) I_1 - j200 I_2 - j200 I_3$$

$$(2) (720 + j1500) I_2 + (720 + j1500) I_3 - j200 I_1 = 0$$

$$(4) \frac{I_2}{I_3} = \frac{1000}{N_2} \rightarrow \boxed{I_2 = \frac{1000}{N_2} I_3}$$

$$(1) 255 = (40 + j30) I_1 - j200 \left(1 + \frac{1000}{N_2} \right) I_3$$

$$(2) (720 + j1500) \left(1 + \frac{1000}{N_2} \right) I_3 = j200 I_1$$

$$(2) I_1 = \frac{720 + j1500}{j200} \left(1 + \frac{1000}{N_2} \right) I_3$$

$$(1) 255 = I_3 \left[(40 + j30) \left(\frac{720 + j1500}{j200} \right) \left(1 + \frac{1000}{N_2} \right) - j200 \left(1 + \frac{1000}{N_2} \right) \right]$$

$$255 = I_3 \left(1 + \frac{1000}{N_2} \right) \left[(40 + j30) \left(\frac{720 + j1500}{j200} \right) - j200 \right]$$

$$255 = I_3 \left(1 + \frac{1000}{N_2} \right) \left[\frac{28800 + j60000 + j21600 - 45000 + 40000}{j200} \right]$$

$$255 = I_3 \left(1 + \frac{1000}{N_2} \right) \frac{23800 + j81600}{j200}$$

$$I_3 = \frac{255 \cdot j200}{\left(1 + \frac{1000}{N_2} \right) (23800 + j81600)} = I_{kd}$$

$$Z_{Th} = \frac{V_{ad}}{I_{kd}} = \frac{1020 \angle 53^\circ}{j51000} \left(1 + \frac{1000}{N_2} \right)^2 (23800 + j81600)$$

$$|Z_{Th}| = 6800 \text{ ohms}$$

$$|Z_{Th}| = \frac{1020}{51000} 85000 \left(1 + \frac{1000}{N_2} \right)^2 = 6800$$

$$\left(1 + \frac{1000}{N_2} \right)^2 = 4 \Rightarrow 1 + \frac{1000}{N_2} = 2$$


$$2 = 1000$$

10.64 a) If N_1 equals 1000 turns, how many turns should be placed on the N_2 winding of the ideal transformer in the circuit seen in Fig. P10.64 so that maximum average power is delivered to the 6800Ω load?

b) Find the average power delivered to the 6800Ω resistor.

c) What percentage of the average power delivered by the ideal voltage source is dissipated in the linear transformer?

Figure P10.64

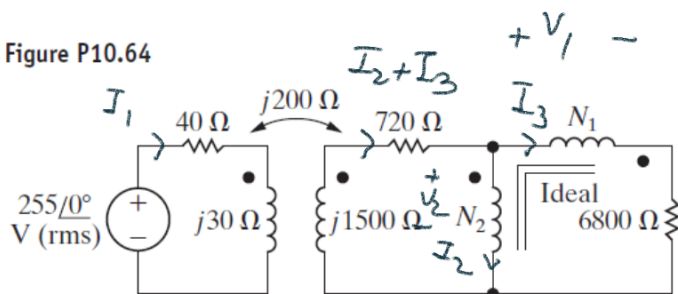

$$(1) 255 = (40 + j30) I_1 - j200(I_2 + I_3)$$

$$(2) (720 + j1500)(I_2 + I_3) + V_2 - j200 I_1 = 0$$

$$(3) V_2 = V_1 + 6800 I_3 \xrightarrow{(4)} \boxed{V_2 = 3400 I_3}$$

$$(4) \Rightarrow V_2 = -V_1$$

$$(5) I_2 = I_3$$

$$(1) 255 = (40 + j30) I_1 - j400 I_3$$

$$(2) (1440 + j3000) I_3 + 3400 I_3 = j200 I_1$$

$$\boxed{\frac{(4840 + j3000)}{j200} I_3 = I_1}$$

$$(1) 255 = \left((40 + j30) \frac{(4840 + j3000)}{j200} - j400 \right) I_3$$

$$255 = I_3 \frac{193600 + j120000 + j145200 - 90000 + 80000}{j200}$$

$$255 = \frac{183600 + j265200}{j200} I_3$$

$$\boxed{I_3 = \frac{j5100}{183600 + j265200}}$$

$$P_{6800\Omega} = |I_3|^2 6800 = \frac{510^2}{(1836^2 + 2652^2)} 6800 = \underline{\underline{170W}}$$

$$\overline{S}_{255V} = -255 \times I_1^*$$

$$I_1 = \frac{j510}{1836 + j2652} \frac{4840 + j3000}{j200}$$

$$I_1 = \frac{51 (242 + j150)}{1836 + j2652} = \frac{51 \times 284.7 \angle 31.8^\circ}{3225.5 \angle 55.3^\circ} = 4.5 \angle -13.5^\circ$$

$$\bar{S}_{255} = -255 \times 4.5 \angle 13.5^\circ$$

$$\bar{P}_{255} = -1116 \text{ W} \quad \text{Kaynakta sağlanan ort. güç.}$$

CHAPTER 14: FREKANS TEPKİSİ

$$\frac{V_o}{V_i} = H$$

$$\frac{V_o(j\omega)}{V_i(j\omega)} = H(j\omega) \quad \text{Transfer Fonksiyonu}$$

14.5 For the circuit shown in Fig. 14.72, find $H(s) = V_o/I_s$.

$$j\omega = s$$

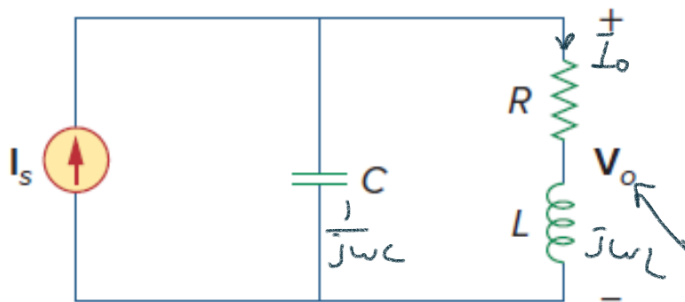


Figure 14.72

For Prob. 14.5.

$$V_o(j\omega) = I_s(j\omega) \frac{1}{j\omega C} \times \frac{(R + j\omega L)}{R + j\omega L + \frac{1}{j\omega C}}$$

$$H(j\omega) = \frac{V_o(j\omega)}{I_s(j\omega)} = \frac{R + j\omega L}{j\omega C (R + j\omega L + \frac{1}{j\omega C})} = \frac{R + j\omega L}{j\omega RC - \omega^2 LC + 1}$$

$$\omega \rightarrow 0 : H(j\omega) \rightarrow R$$

$$\omega \rightarrow \infty : H(j\omega) \rightarrow 0$$

$$\omega = \frac{1}{\sqrt{LC}} : \frac{R + j\sqrt{\frac{L}{C}}}{jR\sqrt{\frac{C}{L}}}$$

Section 14.3 The Decibel Scale

14.7 Calculate $|H(\omega)|$ if H_{dB} equals

- (a) 0.1 dB (b) -5 dB (c) 215 dB

$$X_{[dB]} = 20 \log_{10}(X) \xrightarrow{\text{Tersi}} 10^{\frac{X_{dB}}{20}} = X$$

↪ büyüklük.

$$X_{[dB]} = 10 \log_{10}(X)$$

↪ güç.

a) 0.1 dB $\Rightarrow 10^{\frac{0.1}{20}} = 10^{0.005} \approx 1.012$

b) -5 dB $\Rightarrow 10^{-\frac{5}{20}} = 0.56$

c) 215 dB $\Rightarrow 10^{\frac{215}{20}} = 56234132519$

2 $\xrightarrow{dB} 20 \times \log_{10} 2 \approx 6$ dB

4 $\xrightarrow{dB} 12$ dB

8 $\rightarrow 18$ dB

10 $\rightarrow 20$ dB

50 $\rightarrow 40 - 6 = 34$ dB

25 $\rightarrow 40 - 12 = 28$ dB

14.14 Draw the Bode plots for

$$\frac{(j\omega)^2}{s^2} = -\omega^2$$

$$H(\omega) = \frac{250(j\omega + 1)}{j\omega(-\omega^2 + 10j\omega + 25)}$$

$$1 + \frac{1}{s} = \frac{250(s+1)}{s(s^2 + 10s + 25)} = \frac{250(s+1)}{s(s+5)^2}$$

$$H_{dB} = 20 \log_{10} H$$

$$H(j\omega) = \frac{K (j\omega)^{\pm 1} \left(1 + \frac{j\omega}{Z_1}\right) \left[1 + \frac{j2p_1\omega}{\omega_k} + \left(\frac{j\omega}{\omega_k}\right)^2\right]}{\left(1 + \frac{j\omega}{p_1}\right) \left[1 + \frac{j2p_2\omega}{\omega_n} + \left(\frac{j\omega}{\omega_n}\right)^2\right]}$$

Zero Zero pole

1) Kazang : K

2) Orijinde bir kutup veya sifir. $(j\omega)^{\pm 1}$

3) Basit kutuplar veya sifirlar. $\left(1 + \frac{j\omega}{Z}\right) \frac{1}{1 + \frac{j\omega}{p}}$

4) Kuadratik kutuplar veya sifirlar.

$$\left[1 + \frac{j2p_1\omega}{\omega_k} + \left(\frac{j\omega}{\omega_k}\right)^2\right]$$


$$H(\omega) = \frac{250(1+j\omega)}{j\omega(-\omega^2 + 10j\omega + 25)} = \frac{10 \cancel{250}(1+j\omega)}{\cancel{25}(j\omega) \left(\left(\frac{j\omega}{5}\right)^2 + \frac{2j\omega}{5} + 1\right)}$$

(kuadratik : $\omega_k = 5$ $p_1 = 1$)
kutup

$$10 \rightarrow 20 \text{ dB}$$

$$\left|\frac{1}{j\omega}\right| \rightarrow -20 \log_{10}(\omega) \text{ dB}$$

$$|1+j\omega| \rightarrow$$

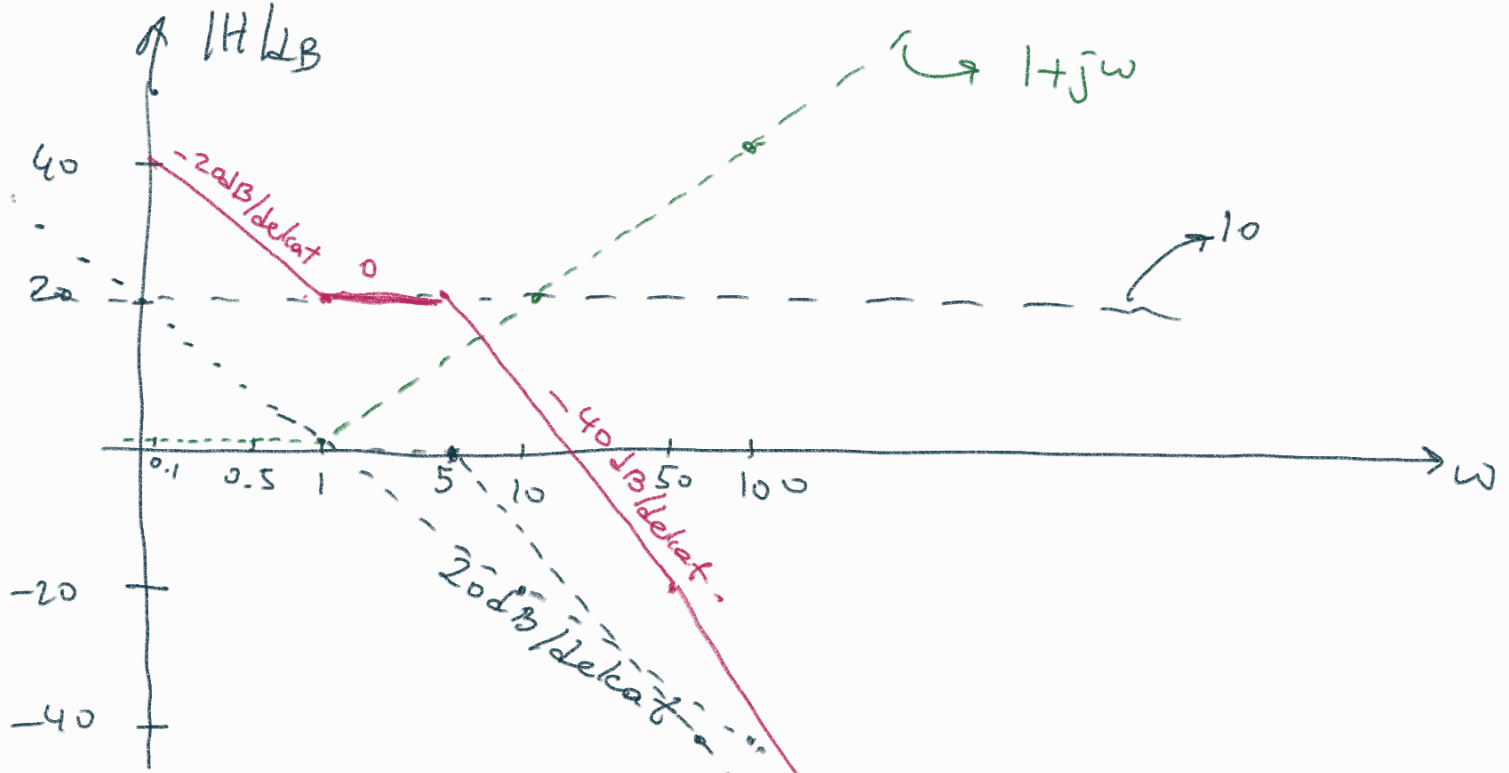

$$1 + j\frac{2\omega}{5} + \left(\frac{j\omega}{5}\right)^2 \xrightarrow{dB} 20 \log_{10} \left| 1 + j\frac{2\omega}{5} + \left(\frac{j\omega}{5}\right)^2 \right|$$

sıfır: 5'ten sonra 40dB/decade hızla yukarı

kutup: " " " " aşağı.

Afı grafiği:

1) Kazanç K: $\theta = 0$ sabit

2) Orijinde sıfır: $j\omega \Rightarrow \theta = 90^\circ$ sabit

" kutup: $(j\omega)^{-1} \Rightarrow \theta = -90^\circ$ sabit

3) Basit sıfır $1 + \frac{j\omega}{z} \Rightarrow \omega = z \Rightarrow \theta = 45^\circ$

$$\omega = \frac{z}{10} \Rightarrow \theta \approx 0^\circ$$

$$\omega = 10z \Rightarrow \theta \approx 90^\circ$$

$$\omega > 10z \Rightarrow \theta \approx 90^\circ$$

$$\omega < \frac{z}{10} \Rightarrow \theta \approx 0^\circ$$

Basit kutup

$$\frac{1}{1 + \frac{j\omega}{p}} \Rightarrow -45^\circ$$

$$-90^\circ$$

0°

$\frac{p}{10}$

?


10p

Tam ters.

Kuadratik sıfır:

$$1 + \frac{j2p_1 \omega}{z} + \left(\frac{j\omega}{z}\right)^2$$

büyük p_1 için

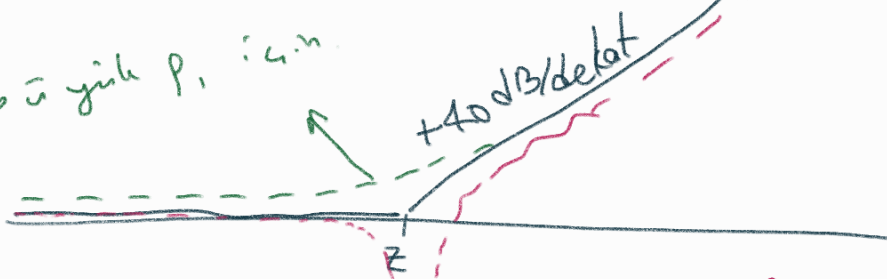


Kuadratik kutup: Tam tersi → küçük p_1 için

$$1 + \frac{j2\frac{\omega}{5}}{z} + \left(\frac{j\frac{\omega}{5}}{z}\right)^2 \Rightarrow \boxed{p=1}$$

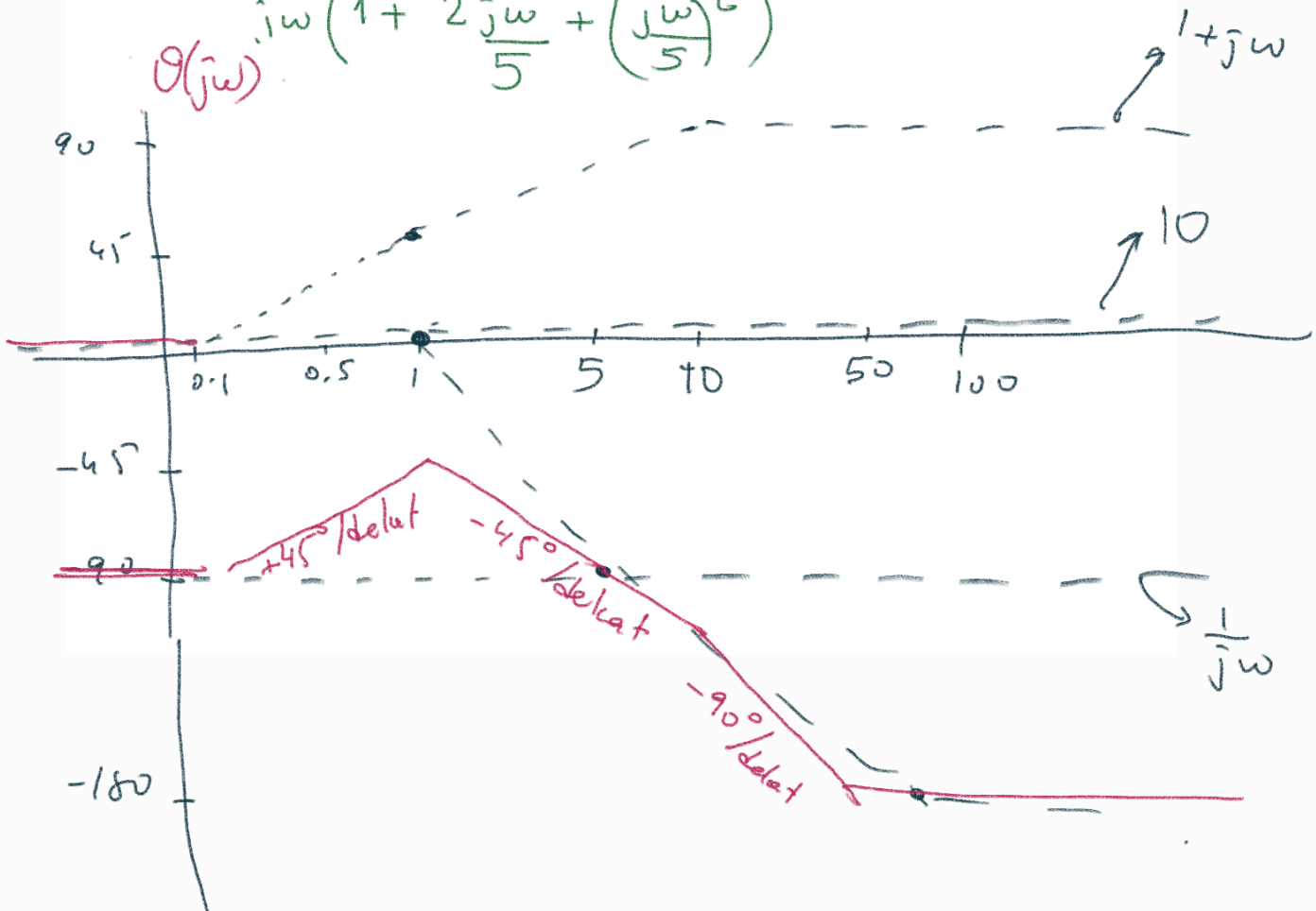14.14 Draw the Bode plots for

$$H(\omega) = \frac{250(j\omega + 1)}{j\omega(-\omega^2 + 10j\omega + 25)}$$


$$\frac{10(1+j\omega)}{j\omega \left(1 + 2\frac{j\omega}{5} + \left(\frac{j\omega}{5}\right)^2\right)}$$



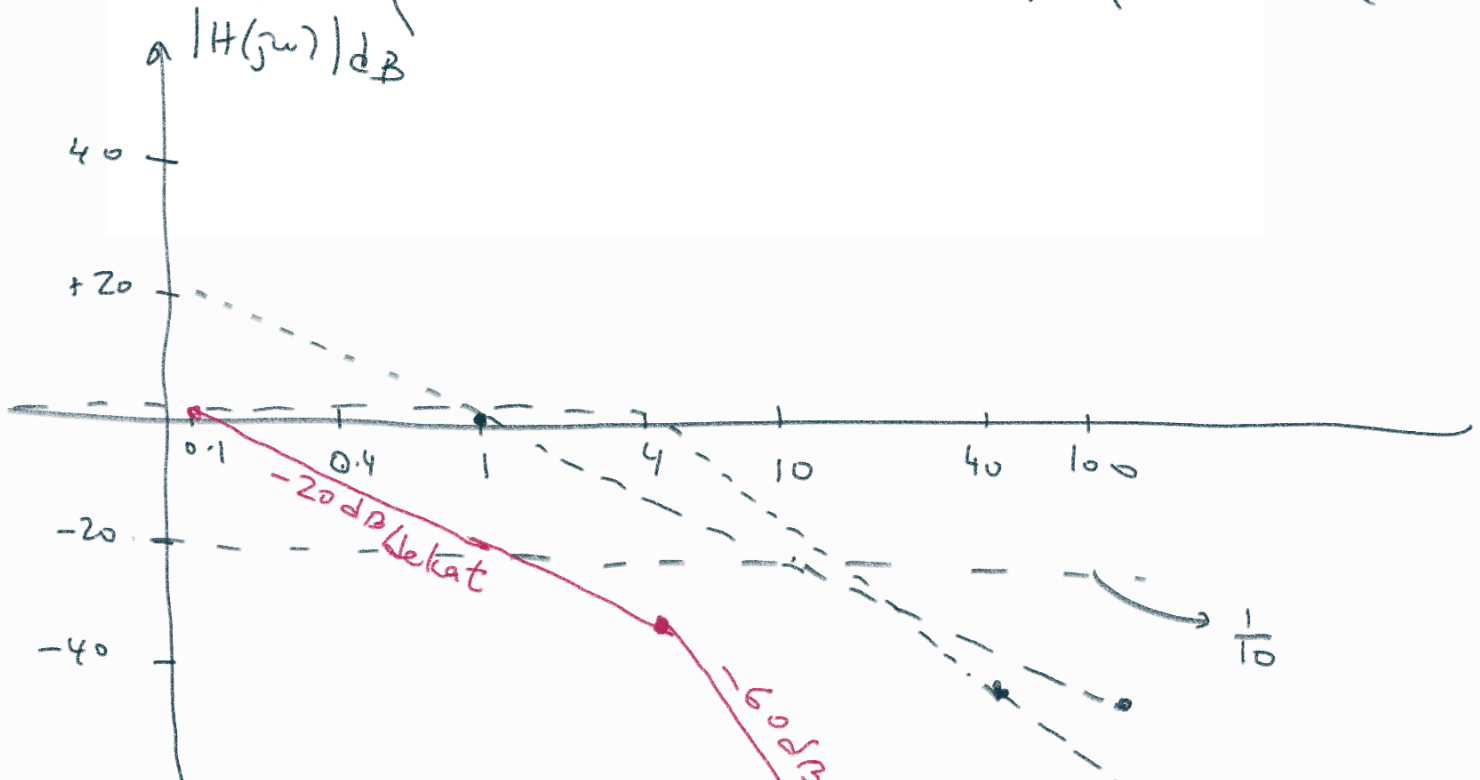14.16 Sketch Bode magnitude and phase plots for


$$H(s) = \frac{1.6}{s(s^2 + s + 16)}, \quad s = j\omega$$

$$H(j\omega) = \frac{1.6}{(j\omega)(16 + j\omega + (j\omega)^2)} = \frac{1.6}{j\omega \left(1 + \frac{j2\omega}{32} + \left(\frac{j\omega}{4}\right)^2 \right)}$$



özellik noktaları: $\omega = 0.1, 1, 10, 4, 0.4, 40$

$$\angle \theta(j\omega)$$

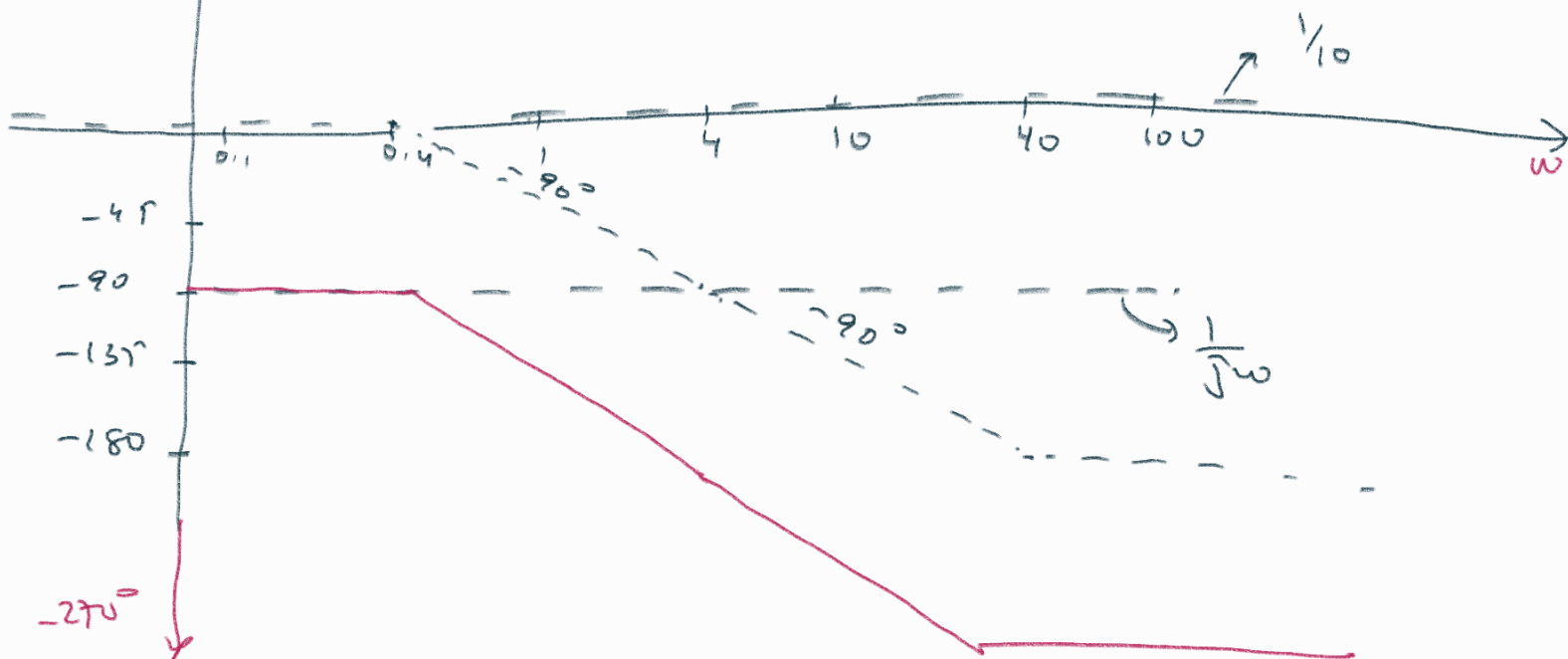


14.19 Sketch the asymptotic Bode plots of the magnitude and phase for

$$H(s) = \frac{80s}{(s+10)(s+20)(s+40)}, \quad s = j\omega$$


$$H(j\omega) = \frac{80j\omega}{(j\omega+10)(j\omega+20)(j\omega+40)}$$

$$= \frac{\cancel{80}j\omega}{\cancel{100}\cancel{10}(1+\frac{j\omega}{10})\cancel{20}(1+\frac{j\omega}{20})\cancel{40}(1+\frac{j\omega}{40})}$$
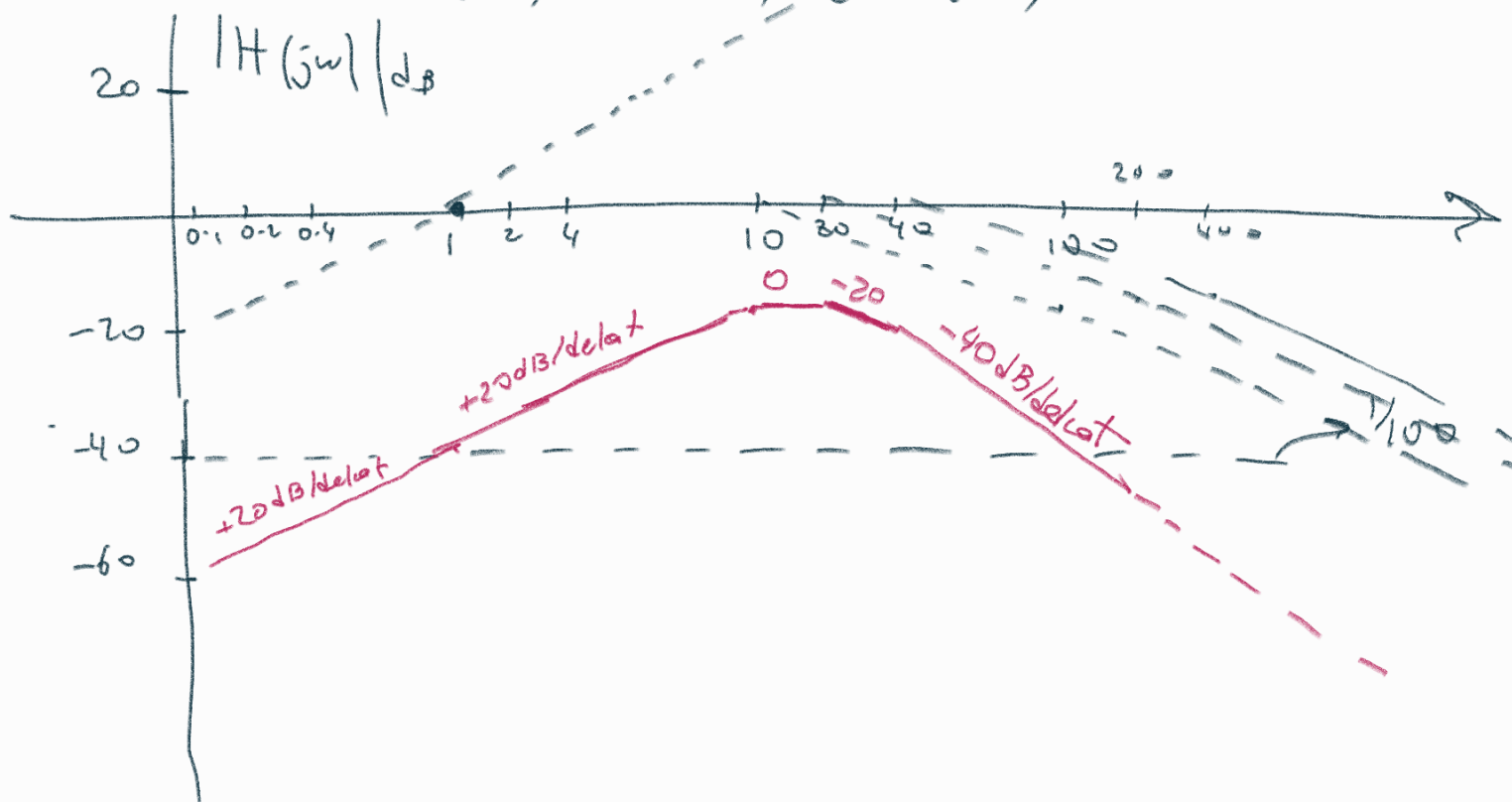
$$= \frac{j\omega}{100(1+\frac{j\omega}{10})(1+\frac{j\omega}{20})(1+\frac{j\omega}{40})}$$



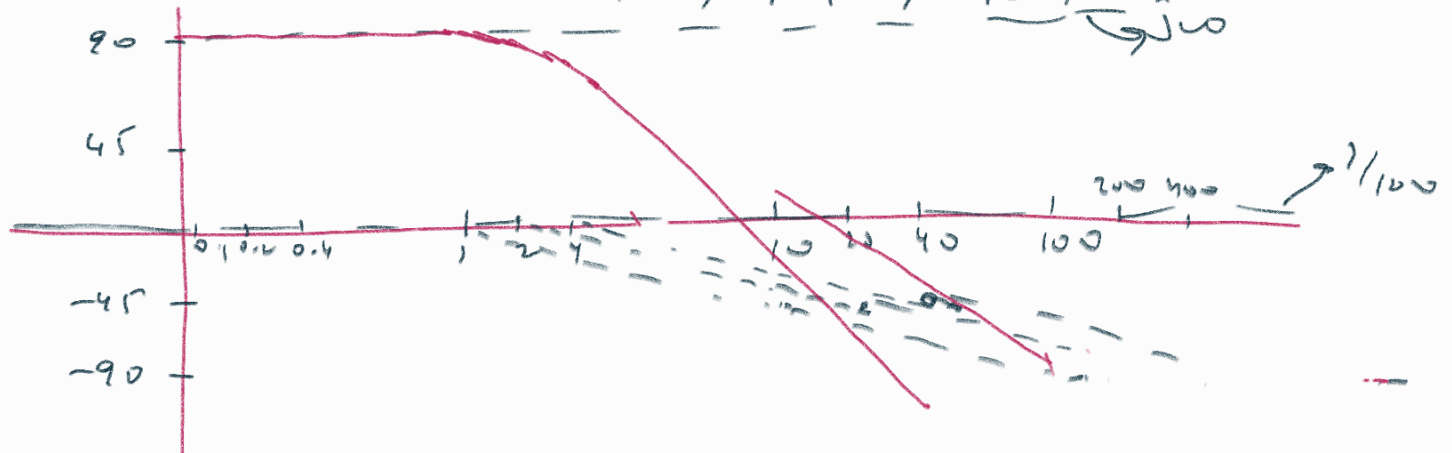Önemli noktalar: 0.1, 0.2, 0.4, 1, 2, 4, 10, 20, 40, $\frac{1}{100}$



-180

$$H(j\omega) = 10(j\omega) 20(1 + \frac{j\omega}{20})$$


14.21 Sketch the magnitude Bode plot for

$$H(s) = \frac{10s(s+20)}{(s+1)(s^2+60s+400)}, \quad s = j\omega$$

$$H(s) = \frac{10s(s+20)}{(s+1)(s+7.5)(s+52.5)}$$

$$\frac{60 \pm \sqrt{3600 - 1600}}{2} = -60 \pm \sqrt{2000} = -7.5, -52.5$$

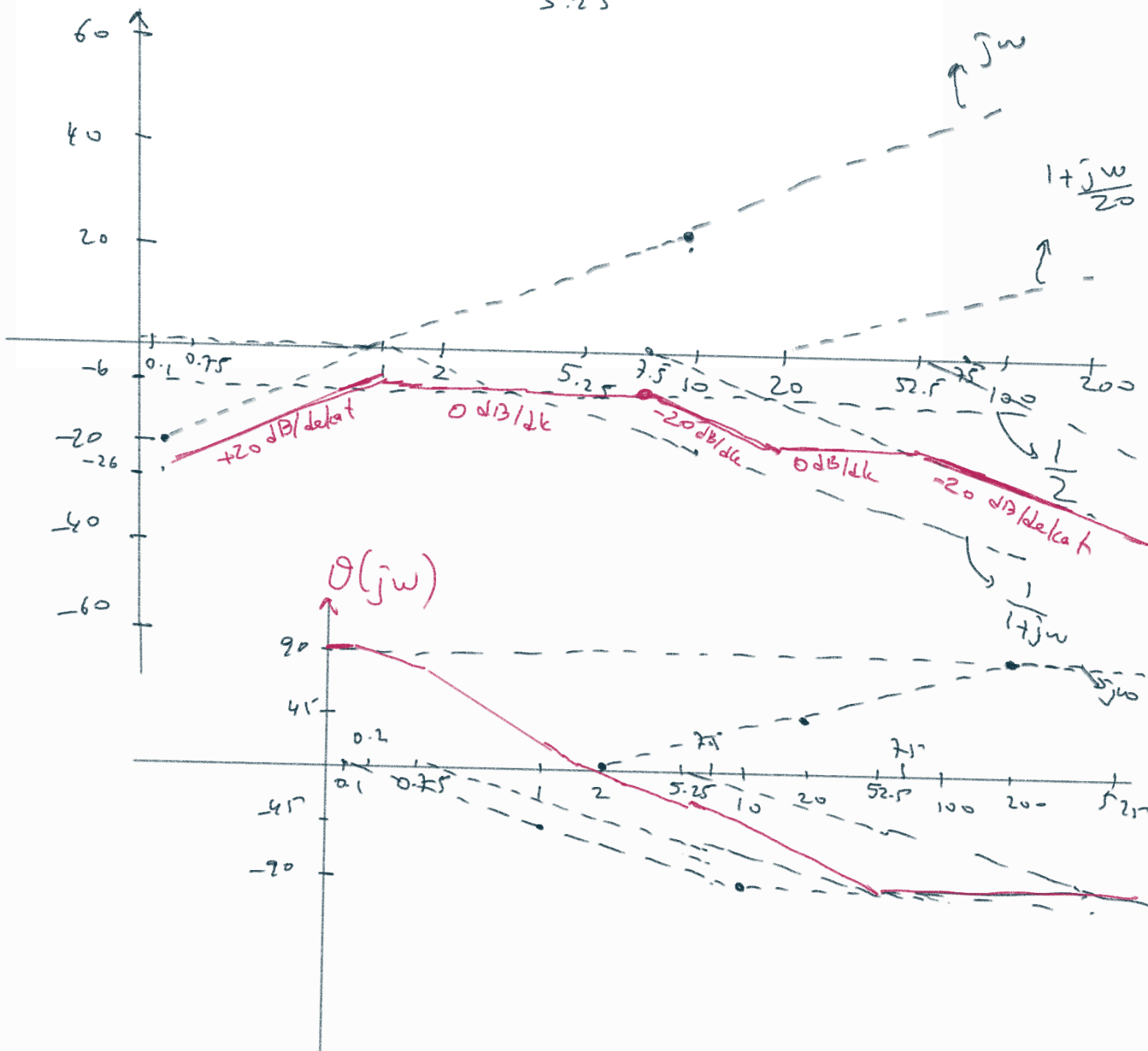Önemli noktalar: 0.1, 0.75, 1, 2, 7.5, 20, 52.5, 75, 200



14.22 Find the transfer function $\mathbf{H}(\omega)$ with the Bode magnitude plot shown in Fig. 14.74.


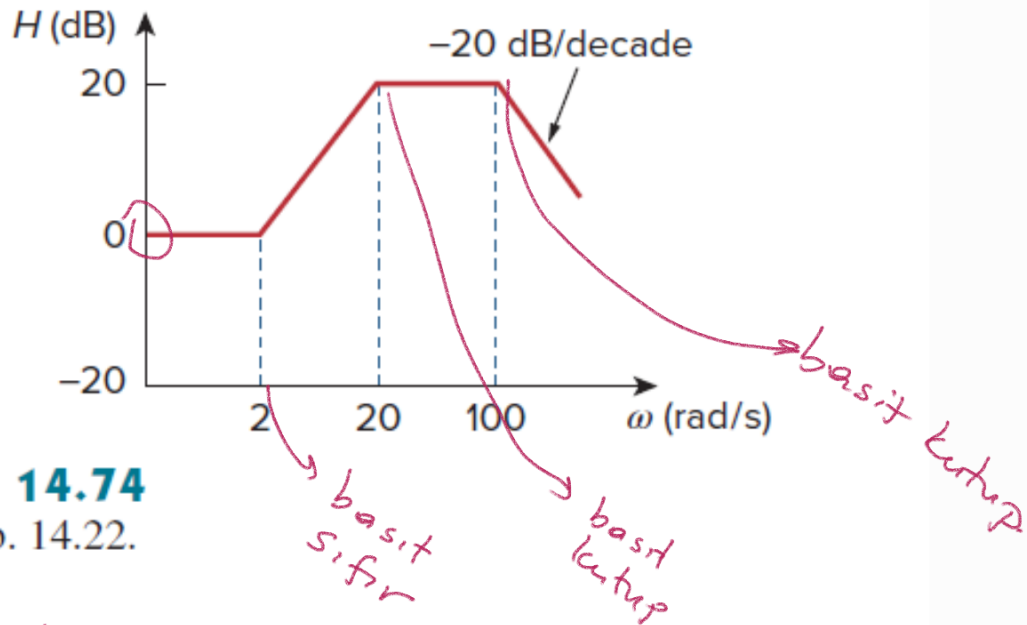


Figure 14.74
For Prob. 14.22.

$$H(j\omega) = \frac{(1 + j\frac{\omega}{2})}{(1 + j\frac{\omega}{20})(1 + j\frac{\omega}{100})}$$

$$H(s) = \frac{1 + \frac{s}{2}}{(1 + \frac{s}{20})(1 + \frac{s}{100})} = \frac{\frac{s+2}{2}}{(\frac{s+20}{20})(\frac{s+100}{100})} = \frac{1000(s+2)}{(s+20)(s+100)}$$

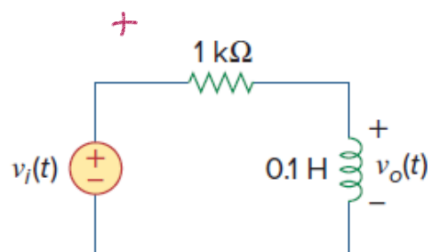14.50 Determine what type of filter is in Fig. 14.87.
Calculate the corner frequency f_c .



$$\omega \rightarrow \infty \Rightarrow V_o \rightarrow V_i$$

$$\omega \rightarrow 0 \Rightarrow V_o \rightarrow 0$$

HPF

Yüksek geçiren filtre.

Figure 14.87
For Prob. 14.50.

$$V_o = V_i$$

$$\frac{j\omega L}{R + j\omega L}$$

$$\frac{V_o}{V_i} = H(j\omega) = \frac{j\omega L}{R + j\omega L}$$

$$H_{\max} = \max_{\omega} |H(j\omega)| = 1$$

kesim frekans.
 ω_c


$$|H(j\omega_c)| = \frac{H_{\max}}{\sqrt{2}} = \frac{1}{\sqrt{2}}$$

$$\left| \frac{j\omega L}{R + j\omega L} \right| = \frac{1}{\sqrt{2}}$$

$$\frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}} = \frac{1}{\sqrt{2}} \Rightarrow \cancel{2\omega^2 L^2} = \cancel{R^2 + \omega^2 L^2}$$

$$\omega^2 L^2 = R^2$$

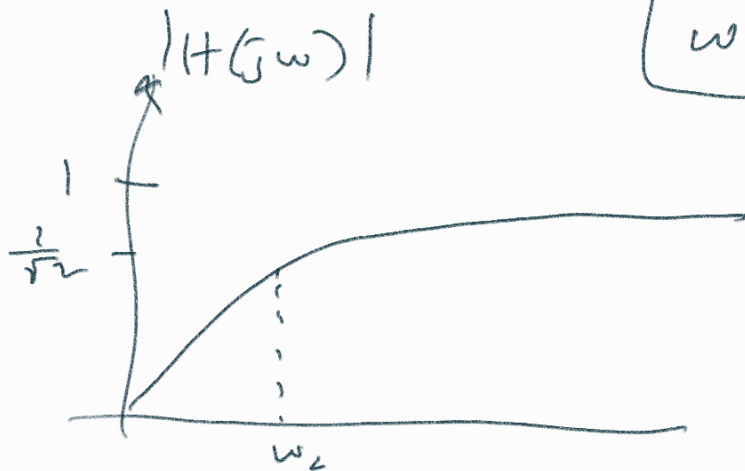
$$\boxed{\omega_c = \frac{R}{L}} = \frac{1k\Omega}{0.1H} = 10000 \text{ rad/s}$$




$$f_c = \frac{\omega_c}{2\pi} = \frac{5000}{\pi}$$

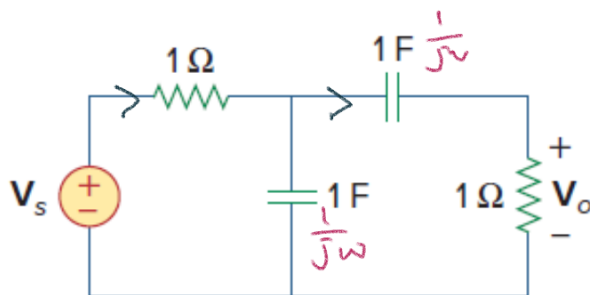14.57 Determine the center frequency and bandwidth of the band-pass filters in Fig. 14.88.

$$\frac{1}{j\omega C} = \frac{1}{j\omega}$$



(a)

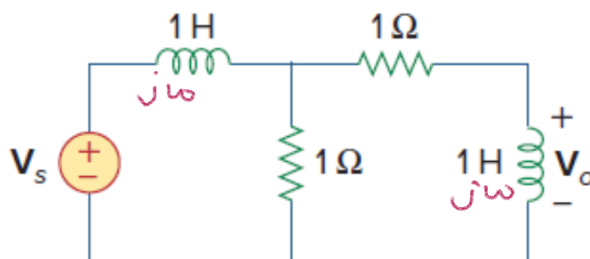

(b)

Figure 14.88

For Prob. 14.57.

$$(a) \quad V_o = 1 \times \frac{\frac{1}{j\omega}}{1 + \frac{2}{j\omega}} \times \frac{V_s}{1 + \left(\frac{1}{j\omega} \parallel \left(1 + \frac{1}{j\omega} \right) \right)}$$

$$\bar{V}_o = \frac{1}{2 + j\omega} \frac{\bar{V}_s}{1 + \frac{\frac{1}{j\omega} \left(1 + \frac{1}{j\omega} \right)}{\frac{2}{j\omega} + 1}}$$

$$= \frac{1}{2 + j\omega} \frac{V_s}{1 + \frac{1 + j\omega}{(j\omega)(j\omega) \frac{2 + j\omega}{j\omega}}} = \frac{V_s}{2 + j\omega} \frac{1}{1 + \frac{1 + j\omega}{(j\omega)(2 + j\omega)}}$$

$$V_o = \frac{V_s}{2 + j\omega} \frac{(j\omega)(2 + j\omega)}{j\omega(2 + j\omega) + 1 + j\omega}$$

$$\frac{V_o}{V_s} = \frac{j\omega}{j2\omega - \omega^2 + 1 + j\omega} = \frac{j\omega}{1 + j3\omega - \omega^2} = H(j\omega)$$

$$|H(j\omega)| = \frac{\omega}{\sqrt{(1 - \omega^2)^2 + 9\omega^2}}$$

$$H_{max} = \frac{1}{3}$$

$$\omega_0 = 1 \text{ Hz merkez frekans}$$

$$\frac{H_{max}}{\sqrt{2}} = \frac{1}{3\sqrt{2}} = \frac{\omega_c}{\sqrt{(1 - \omega_c^2)^2 + 9\omega_c^2}}$$


$$(1 - \omega_c^2)^2 + 9\omega_c^2 = 18\omega_c^2$$

$$1 - \omega_c^2 = \pm 3\omega_c$$

$$0 = \omega_c^2 \mp 3\omega_c - 1$$

$$\frac{\mp 3 \pm \sqrt{13}}{2} \rightarrow \text{olamaz}$$

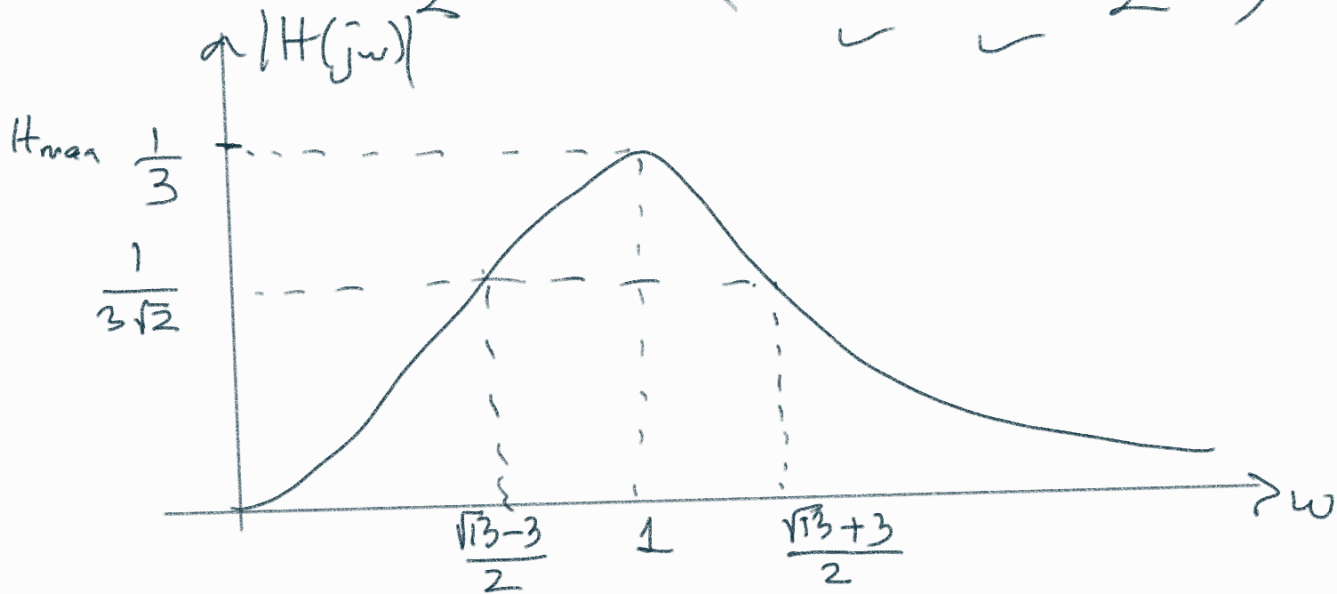
$$\omega_{c1,2} = \frac{-3 \pm \sqrt{13}}{2} = \left(\frac{\sqrt{13}-3}{2}, \frac{\sqrt{13}+3}{2} \right)$$



$$\omega_{c1}, \omega_{c2} = \frac{13-9}{4} = 1 = \omega_0^2$$

$$\boxed{\omega_{c1}, \omega_{c2} = \omega_0^2}$$

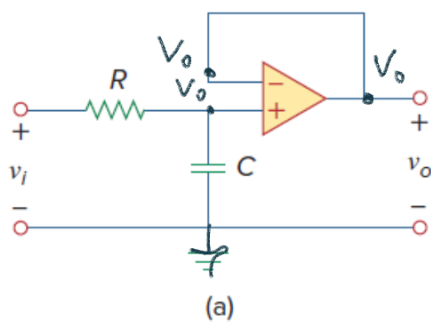
14.61 Find the transfer function for each of the active filters in Fig. 14.90.



$$V_o = V_i \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}}$$

$$H(j\omega) = \frac{1}{1 + j\omega RC}$$

$$|H| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

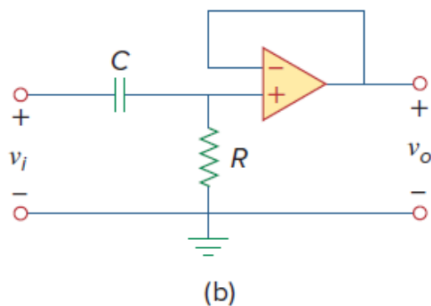

$$H(j\omega) = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC}$$

$$|H(j\omega)| = \frac{\omega RC}{\sqrt{1 + \omega^2 R^2 C^2}}$$



Figure 14.90

For Probs. 14.61 and 14.62.

14.69 Design the filter in Fig. 14.94 to meet the following requirements:



- (a) It must attenuate a signal at 2 kHz by 3 dB compared with its value at 10 MHz.
- (b) It must provide a steady-state output of $v_o(t) = 10 \sin(2\pi \times 10^8 t + 180^\circ)$ V for an input $v_s(t) = 4 \sin(2\pi \times 10^8 t)$ V.


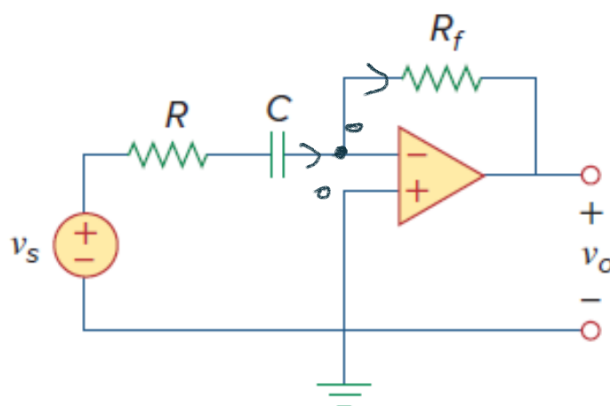


Figure 14.94

For Prob. 14.69.

a)

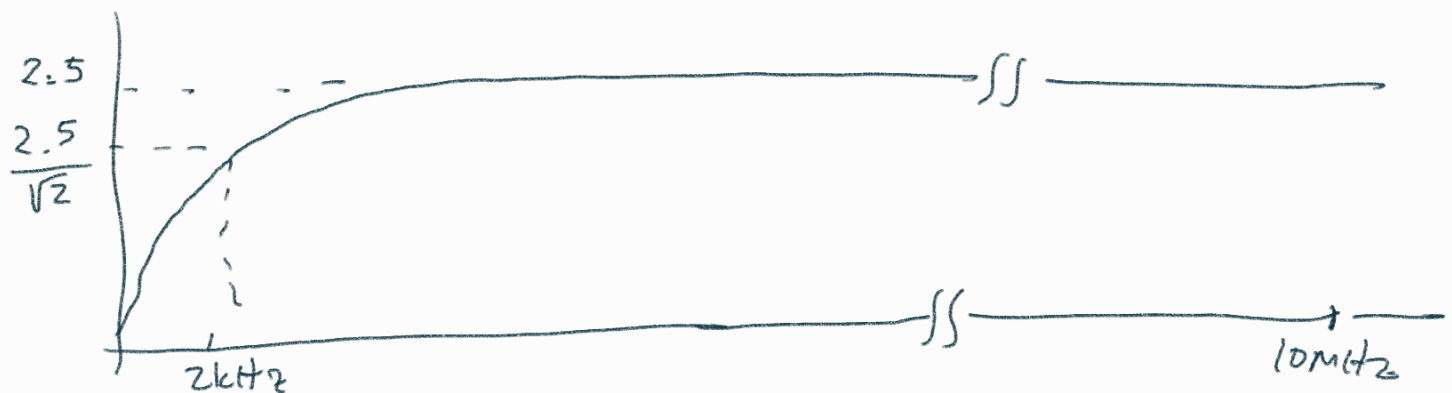

b)
$$\frac{-R_f}{R} = 2.5 \quad (1)$$

(2) kesin fr.

$$\frac{-R_f}{R + \frac{1}{j\omega C}} = \frac{-j\omega R_f C}{1 + j\omega R C}$$

$$= \frac{-j\omega R C}{1 + j\omega R C} \left(\frac{R_f}{R} \right)$$

$\omega_c = \frac{1}{RC} = 2\pi \times 2000$



$\frac{R_f}{R} = 2.5$

$$Q = \frac{\omega_0}{B} \quad \text{Quality factor}$$

14.18 For the bandpass filter shown in Fig. P14.18, find
 (a) ω_0 , (b) f_0 , (c) Q , (d) ω_{c1} , (e) f_{c1} , (f) ω_{c2} , (g) f_{c2} ,
 and (h) β . $\rightarrow \omega_{c2} - \omega_{c1}$

PSPICE
MULTISIM

Figure P14.18

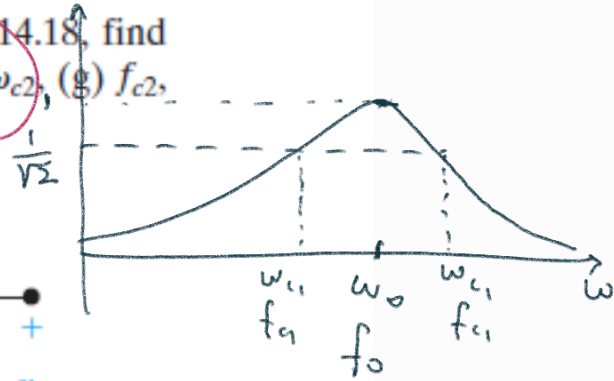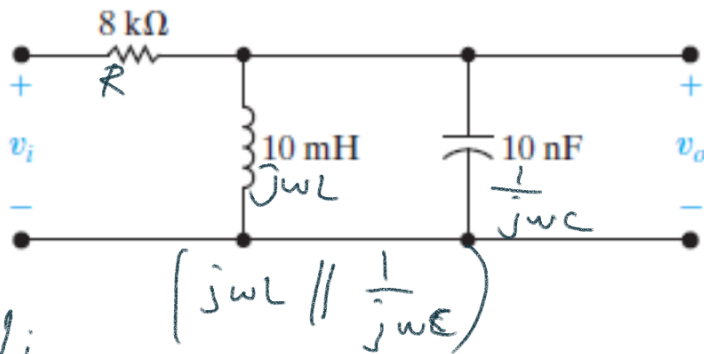

$$V_o = V_i$$

$$R + (j\omega L \parallel \frac{1}{j\omega C})$$

$$H(j\omega) = \frac{V_o}{V_i} = \frac{j\omega L}{j\omega L + \frac{1}{j\omega C}}$$

$$\frac{j\omega L}{1 - \omega^2 LC}$$

$$R + \frac{j\omega L}{j\omega C} = R + \frac{j\omega L}{1 - \omega^2 LC}$$

$$H(j\omega) = \frac{j\omega L}{R - \omega^2 LC + j\omega L} = \frac{j\omega \frac{L}{R}}{1 - \omega^2 LC + j\omega \frac{L}{R}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \text{merkez frekansı}$$

$$\omega_0 = \frac{1}{\sqrt{10^{-2} \times 10^{-8}}} = 10^5 \text{ rad/s}$$

$$f_0 = \frac{10^5}{2\pi} \approx 15900 \text{ Hz}$$

$$|H(j\omega)| = \frac{\omega \frac{L}{R}}{\sqrt{(1 - \omega^2 LC)^2 + \frac{\omega^2 L^2}{R^2}}}$$

$$H_{max} = 1 \Rightarrow |H(j\omega_c)| = \frac{1}{\sqrt{2}}$$

$$\frac{\omega_c \frac{L}{R}}{\sqrt{(1 - \omega_c^2 LC)^2 + \frac{\omega_c^2 L^2}{R^2}}} = \frac{1}{\sqrt{2}}$$

$$\cancel{2\omega_c^2 \frac{L^2}{R^2}} = 1 - 2\omega_c^2 LC + \omega_c^4 L^2 C^2 + \cancel{\omega_c^2 \frac{L^2}{R^2}}$$

$$0 = \omega_c^4 L^2 C^2 - 2\omega_c^2 LC - \omega_c^2 \frac{L^2}{R^2} + 1$$

$$0 = A^2 L^2 C^2 - A \left(2LC + \frac{L^2}{R^2} \right) + 1$$

$$\frac{2LC + \frac{L^2}{R^2} \mp \sqrt{\left(2LC + \frac{L^2}{R^2} \right)^2 - 4L^2 C^2}}{2L^2 C^2} = (\omega_{c1}, \omega_{c2})$$

$$\rightarrow 0 = \omega_c^4 10^{-20} - \omega_c^2 \left(2 \times 10^{-10} + \frac{10^{-4}}{64 \times 10^6} \right) + 1$$

$$= \omega_c^4 - \omega_c^2 \left(2.015625 \times 10^{-10} \right) + 10^{-20}$$

$$= A^2 - 2.015625 \times 10^{-10} A + 10^{-20}$$

$$= 2.015625 \times 10^{-10} \mp \sqrt{2.015625^2 \times 10^{-20} - 4 \times 10^{-20}}$$

$$= \frac{2.015625 \times 10^{-10} \pm \sqrt{0.06274} \times 10^{-10}}{2}$$

$$A_{1,2} = \left(\frac{1.75 \times 10^{-10}}{2}, \frac{2.25 \times 10^{-10}}{2} \right) = 0.875 \times 10^{-10}, 1.125 \times 10^{-10} \frac{\text{rad}}{\text{s}}$$

$$\omega_{c1,2} = (0.935 \times 10^5, 1.061 \times 10^5) \text{ rad/s}$$

$$f_{c1,2} = (14888, 16894) \text{ Hz}$$

$$\beta = \omega_{c2} - \omega_{c1} = 0.126 \times 10^5 \approx 12600 \text{ rad/s}$$

$$Q = \frac{\omega_0}{\beta} = \frac{10^5}{12600} \approx 7.94$$

14.27 Use a 5 nF capacitor to design a series RLC band-pass filter, as shown at the top of Fig. 14.27. The center frequency of the filter is 8 kHz, and the quality factor is 2.

DESIGN
PROBLEM
PSPICE
MULTISIM

- Specify the values of R and L .
- What is the lower cutoff frequency in kilohertz?
- What is the upper cutoff frequency in kilohertz?
- What is the bandwidth of the filter in kilohertz?



14.28 Design a series RLC band-pass filter using only



$$\omega_0 = \frac{1}{\sqrt{LC}} = 16000\pi$$

$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_{c2} = +\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\beta = \omega_{c2} - \omega_{c1} = \frac{R}{L}$$

$$Q = \frac{\omega_0}{\beta} = 2$$

$C = 5 \text{ nF}$ kullan.

$$2 = \frac{\frac{1}{\sqrt{LC}}}{\frac{R}{L}} = \frac{1}{\sqrt{LC}} \cdot \frac{L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}} = 2$$

$$\frac{1}{\sqrt{LC}} = 16000\pi$$

$$\frac{1}{L \times 5 \times 10^{-9}} = 256 \times 10^6 \pi^2$$

$$L = \frac{1000}{5 \times 256 \times \pi^2} = 79 \text{ mH}$$

$$\frac{1}{R} \sqrt{\frac{79 \times 10^{-3}}{5 \times 10^{-9}}} = 2$$

$$R \approx \frac{4 \times 10^3}{2} = 2 \text{ k}\Omega$$

$$d) \beta = \frac{R}{L} = \frac{2000}{79 \times 10^{-3}} = \frac{1}{40} \times 10^6 = 25000 \text{ rad/s}$$

$$\beta = \frac{25000}{2\pi} \text{ Hz}$$

$$b) \omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$= -12500 + \sqrt{12500^2 + 25 \times 10^6 \pi^2}$$

$$\omega_{c1} = -12500 + 51760 = 39260 \text{ rad/s} = 6252 \text{ Hz}$$



$$c) \omega_{c2} = +12500 + 51760 = 64260 \text{ rad/s} = 10232 \text{ Hz}$$

14.32 A block diagram of a system consisting of a sinusoidal voltage source, an *RLC* series bandpass filter, and a load is shown in Fig. P14.32. The internal impedance of the sinusoidal source is $80 + j0 \Omega$, and the impedance of the load is $480 + j0 \Omega$.

The *RLC* series bandpass filter has a 20 nF capacitor, a center frequency of 50 krad/s, and a quality factor of 6.25.

- Draw a circuit diagram of the system.
- Specify the numerical values of L and R for the filter section of the system.
- What is the quality factor of the interconnected system?
- What is the bandwidth (in hertz) of the interconnected system?

Figure P14.32

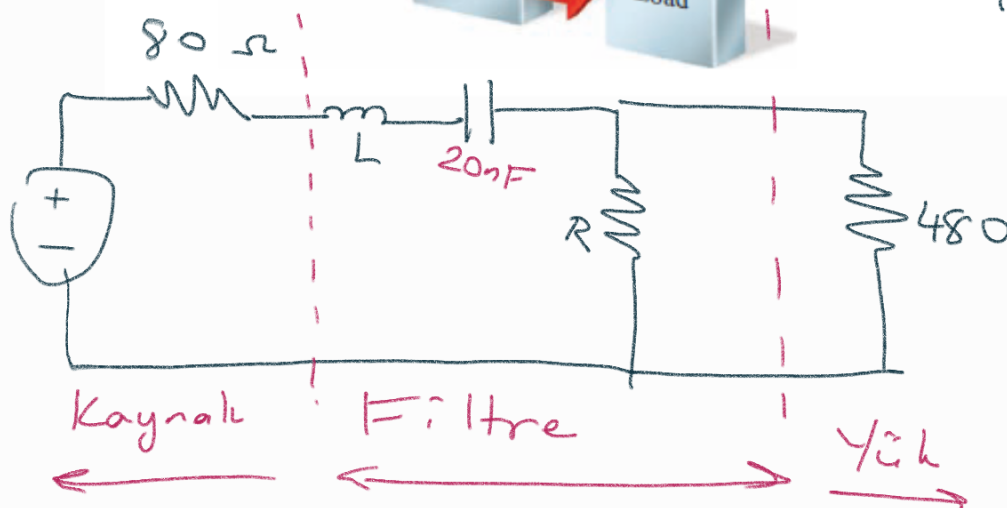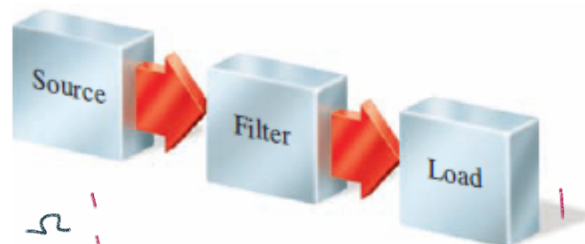

$$b) \omega_0 = \frac{1}{\sqrt{LC}} = 50000$$

$$Q = \frac{\omega_0}{\beta} = 6.25$$

$$\beta = \frac{50000}{6.25} = 8000 \text{ rad/s} = \frac{R}{L}$$


$$L = \frac{1}{50000^2 \times 20 \times 10^{-9}}$$

$$= \frac{1}{25 \times 20 \times 10^{-1}} = 0.02 \text{ H}$$

$$8000 = \frac{R}{0.02} \Rightarrow R = 160 \Omega$$

160 // 480

c) Inter-connected System

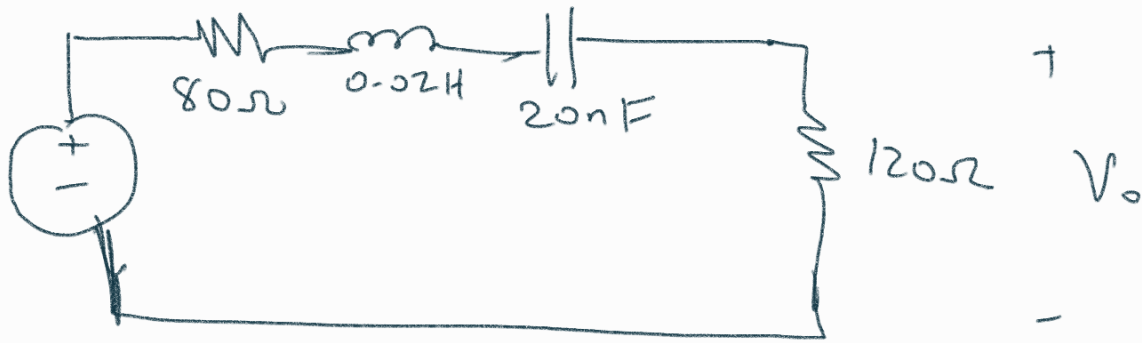

$$H(j\omega) = \frac{120}{200 + j0.02\omega + \frac{1}{j2 \times 10^{-8}\omega}}$$

$$H(j\omega) = \frac{120}{200 + j\left(0.02\omega - \frac{1}{2 \times 10^{-8}\omega}\right)}$$

Bunun sıfır olduğu yer merkez frekansıdır.


$$\omega_0 = \frac{1}{\sqrt{0.02 \times 2 \times 10^{-8}}} = \frac{1}{\sqrt{4 \times 10^{-10}}} = 5 \times 10^4 = 50000 \frac{\text{rad}}{\text{s}}$$

AYNI.

$$H_{\max} = 0.6$$

$$|H(j\omega_c)| = \frac{0.6}{\sqrt{2}}$$

$$|H(j\omega)| = \frac{120}{\sqrt{200^2 + \left(0.02\omega - \frac{1}{2 \times 10^{-8}\omega}\right)^2}}$$

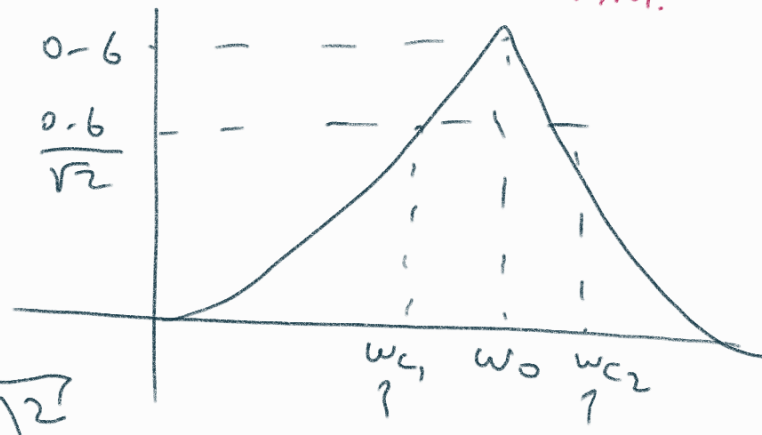

$$\frac{14400}{40000 + \left(0.02\omega - \frac{1}{2 \times 10^{-8}\omega}\right)^2} = \frac{0.36}{2}$$

$$\cancel{28800} = \cancel{14400} + 0.36 \left(4 \times 10^{-4} \omega^2 - \frac{0.04}{2 \times 10^{-8}} + \frac{1}{4 \times 10^{-16} \omega^2} \right)$$

14400

$$40000 = 4 \times 10^{-4} \omega^2 - 2 \times 10^6 + \frac{25 \times 10^{14}}{\omega^2}$$

$$40000 \omega^2 = 4 \times 10^{-4} \omega^4 - 2 \times 10^6 \omega^2 + 25 \times 10^{14}$$

$$0 = 4 \times 10^{-4} \omega^4 - (2 \times 10^6 + 40000) \omega^2 + 25 \times 10^{14}$$

$$= \omega^4 - (0.5 \times 10^{10} + 10^8) \omega^2 + 6.25 \times 10^{18}$$

$$= \omega^4 - 51 \times 10^8 \omega^2 + 6.25 \times 10^{18}$$

$$0 = A^2 - 51 \times 10^8 A + 6.25 \times 10^{18}$$

$$A = \frac{51 \times 10^8 \pm \sqrt{51^2 \times 10^{16} - 25 \times 10^{18}}}{2}$$

$$A_{1,2} = \frac{51 \times 10^8 \pm 10.5 \times 10^8}{2}$$

$$A_{1,2} = 20.25 \times 10^8, 30.75 \times 10^8$$

$$\omega_{c1,2} = (45000, 55452) \text{ rad/s}$$

$$\beta = 10452 \text{ rad/s} \Rightarrow 1664 \text{ Hz}$$


$$Q = \frac{\omega_0}{\beta} = \frac{50000}{10452} = \underline{\underline{4.78}} \text{ D\u00fc\u015ft\u00fc}$$

14.42 Use a 500 nF capacitor to design a bandreject filter, as shown in Fig. P14.42. The filter has a center frequency of 4 kHz and a quality factor of 5

DESIGN
PROBLEM
PSICE
MULTISIM

- Specify the numerical values of R and L .
- Calculate the upper and lower corner, or cutoff, frequencies in kilohertz.
- Calculate the filter bandwidth in kilohertz. 0.8 kHz


Figure P14.42

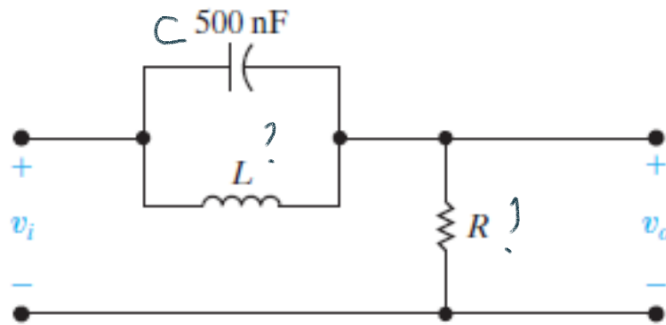

$$H(j\omega) = \frac{R}{R + \left(j\omega L \parallel \frac{1}{j\omega C} \right)}$$

$$= \frac{R}{R + \frac{j\omega L}{j\omega C}} = \frac{R}{R + \frac{j\omega L}{1 - \omega^2 LC}}$$
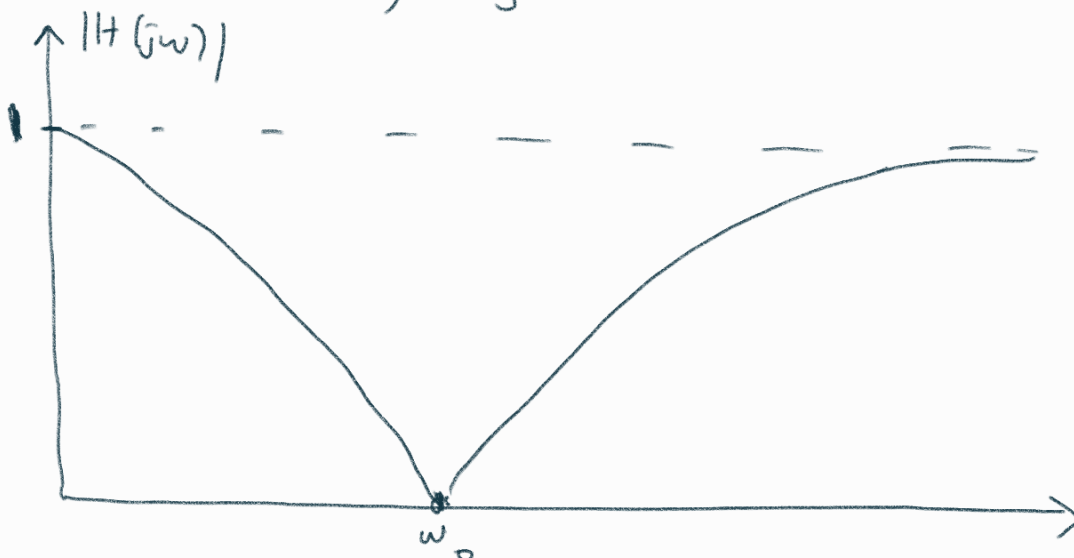
$$H(j\omega) = \frac{R(1 - \omega^2 LC)}{R(1 - \omega^2 LC) + j\omega L} = \frac{1 - \omega^2 LC}{1 - \omega^2 LC + j\omega \frac{L}{R}}$$



$$\omega_0 = \frac{1}{\sqrt{LC}} = 8000\pi \rightarrow 4\text{kHz}$$

$$Q = \frac{\omega_0}{\beta} = 5$$

$$\beta = \frac{\omega_0}{5} = 1600\pi \text{ rad/s}$$

$$8000\pi = \frac{1}{\sqrt{5 \times 10^{-7} L}}$$

$$L = \frac{1}{64\pi^2 \times 10^6 \times 5 \times 10^{-7}} \approx 3.2 \text{ mH}$$

small

$$\frac{1}{\sqrt{2}} = \frac{1 - \omega^2 LC}{\sqrt{(1 - \omega^2 LC)^2 + \frac{\omega^2 L^2}{R^2}}}$$

$$(1 - \omega^2 LC)^2 + \frac{\omega^2 L^2}{R^2} = 2(1 - \omega^2 LC)^2$$

$$\frac{\omega^2 L^2}{R^2} = 1 + \omega^4 L^2 C^2 - 2\omega^2 LC$$

$$\omega^4 L^2 C^2 - \omega^2 \left(\frac{L^2}{R^2} + 2LC \right) + 1 = 0$$

$$\omega^4 - \omega^2 \left(\frac{1}{R^2 C^2} + \frac{2}{LC} \right) + \frac{1}{L^2 C^2} = 0$$

$$A^2 - A \left(\frac{1}{R^2 C^2} + \frac{2}{LC} \right) + \frac{1}{L^2 C^2} = 0$$

$$A = \frac{\frac{1}{R^2 C^2} + \frac{2}{LC} \pm \sqrt{\left(\frac{1}{R^2 C^2} + \frac{2}{LC} \right)^2 - \frac{4}{L^2 C^2}}}{2}$$

$$\omega_{c1,2} = \frac{\frac{1}{R^2 C^2} + \frac{2}{LC} \pm \sqrt{\frac{1}{R^4 C^4} + \frac{4}{LC}}}{2} = 7240\pi$$

$$\omega_0 = 8000\pi = \sqrt{\omega_{c1} \omega_{c2}}$$

$$\omega_{c2} - \omega_{c1} = 1600\pi$$

$$64 \times 10^6 \pi^2 = \omega_{c1} (1600\pi + \omega_{c1})$$

$$0 = \omega_{c1}^2 + 1600\pi \omega_{c1} - 64 \times 10^6 \pi^2$$

$$\omega_{c1} = \frac{-1600\pi \pm \sqrt{(1600\pi)^2 + 256 \times 10^6 \pi^2}}{2}$$

$$\omega_{c1} = \frac{\sqrt{256 + 2.56 \times 10^3} \pi - 1.6 \times 10^3 \pi}{2}$$

$$\omega_{c1} \approx \frac{14.48 \times 10^3 \pi}{2} = 7.24 \times 10^3 \pi$$

$$\omega_{c2} = 1600\pi + 7240\pi = 8840\pi$$

c) $\beta = 1600\pi \text{ rad/s} \Rightarrow 800 \text{ Hz}$

14.48 Given the following voltage transfer function:

$$H(s) = \frac{V_o}{V_i} = \frac{25 \times 10^6}{s^2 + 1000s + 25 \times 10^6}$$

a) At what frequencies (in radians per second) is the magnitude of the transfer function equal to unity?

→ b) At what frequency is the magnitude of the transfer function maximum?

→ c) What is the maximum value of the transfer function magnitude? → 1

a) $H(j\omega) = \frac{25 \times 10^6}{j1000\omega + 25 \times 10^6 - \omega^2}$

→ $|H(j\omega)| = \frac{25 \times 10^6}{\sqrt{(25 \times 10^6 - \omega^2)^2 + 10^6 \omega^2}} = 1$

$$\omega = 0 \text{ olduğunda } |H(j\omega)| = 1$$


$$(25 \times 10^6)^2 = (25 \times 10^6 - \omega^2)^2 + 10^6 \omega^2$$

$$(\cancel{25 \times 10^6})^2 = (\cancel{25 \times 10^6})^2 - 50 \times 10^6 \omega^2 + \omega^4 + 10^6 \omega^2$$

$$0 = \omega^4 - 49 \times 10^6 \omega^2$$

$$0 = \omega^2 (\omega^2 - 49 \times 10^6)$$

$\omega = 0$
 $\omega = 7 \times 10^3$ } Bu iki frekansta $|H| = 1$ olur.

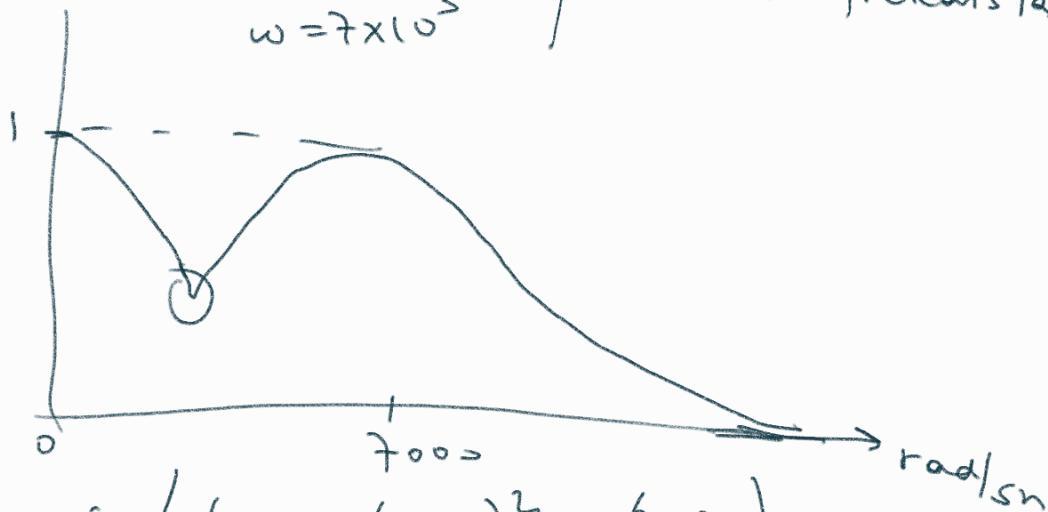

$$b) \min (25 \times 10^6 - \omega^2)^2 + 10^6 \omega^2$$

$$\Rightarrow 2(25 \times 10^6 - \omega^2)(-2\omega) + 2 \times 10^6 \omega = 0$$

$$\omega [-4(25 \times 10^6 - \omega^2) + 2 \times 10^6] = 0$$

$$-98 \times 10^6 + 4\omega^2 = 0$$

$$\frac{49}{2} \times 10^6 = \omega^2$$

15.44 a) Design a broadband Butterworth bandpass filter with a lower cutoff frequency of 200 Hz and an upper cutoff frequency of 2500 Hz. The pass-band gain of the filter is 40 dB. The gain should be down at least 40 dB at 40 Hz and 12.5 kHz. Use 1 μ F capacitors in the high-pass circuit and 2.5 k Ω resistors in the low-pass circuit.

b) Draw a circuit diagram of the filter and label all the components.

AKTIF FILTRELER

1. DERECE ALGAK GEÇİREN;


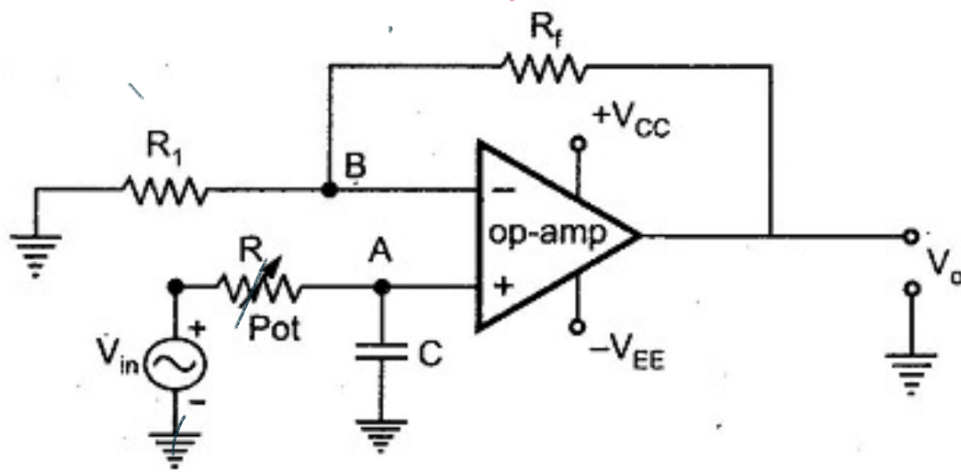


Fig. 2.74 First order low pass butterworth filter

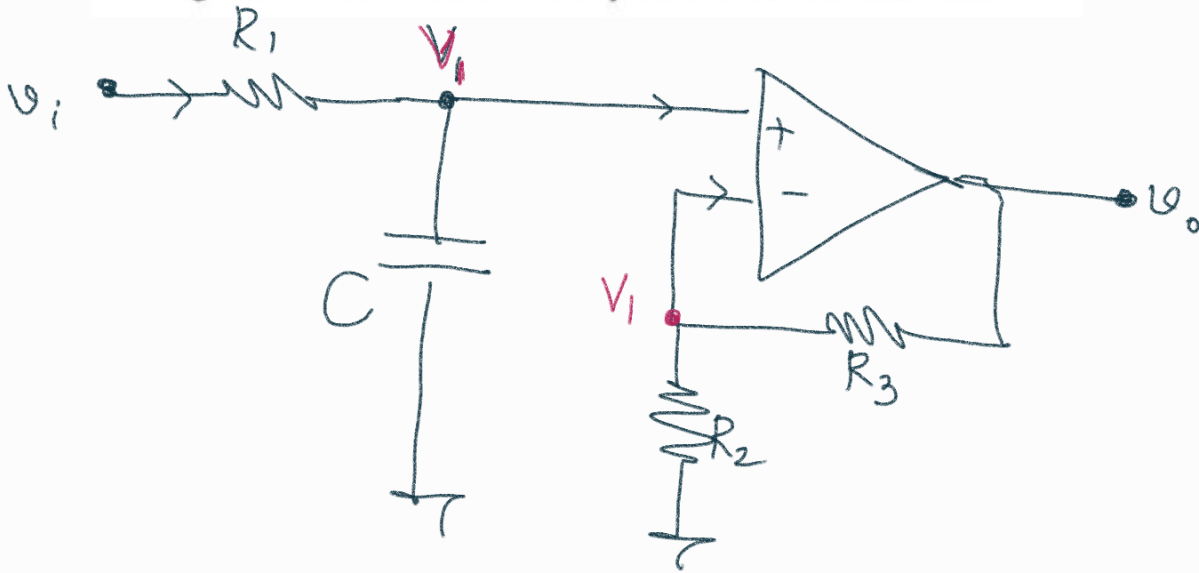

$$\textcircled{1} \frac{V_i - V_1}{R_1} = \frac{V_1}{1/j\omega C}$$

$$\textcircled{2} \frac{V_1}{R_2} = \frac{V_o}{R_2 + R_3}$$

$$\textcircled{1} \frac{V_i}{R_1} = \frac{V_1}{R_1} + V_1 j\omega C \Rightarrow \frac{V_i}{R_1} = V_1 \left(\frac{1}{R_1} + j\omega C \right)$$

$$V_1 = \frac{V_i}{R_1 \left(\frac{1}{R_1} + j\omega C \right)}$$

$$\textcircled{2} \frac{V_i}{R_2 R_1 \left(\frac{1}{R_1} + j\omega C \right)} = \frac{V_o}{R_2 + R_3}$$

$$V_o = \frac{R_2 + R_3}{R_2} \times \frac{1}{1 + j\omega R_1 C} \times V_i$$

$$H(j\omega) = \frac{R_2 + R_3}{R_2} \times \frac{1}{1 + j\omega R_1 C} = \frac{R_2 + R_3}{R_2} \times \frac{\frac{1}{R_1 C}}{\frac{1}{R_1 C} + j\omega}$$

Genel Form: $H = K \frac{b \omega_c}{s + b \omega_c}$

$$\left[\omega_c = \frac{1}{R_1 C} \right] \left[K = \frac{R_2 + R_3}{R_2} \right] \left[b = 1 \right]$$

1. DEREĞİ YÜKSEK GEÇİRGEN :

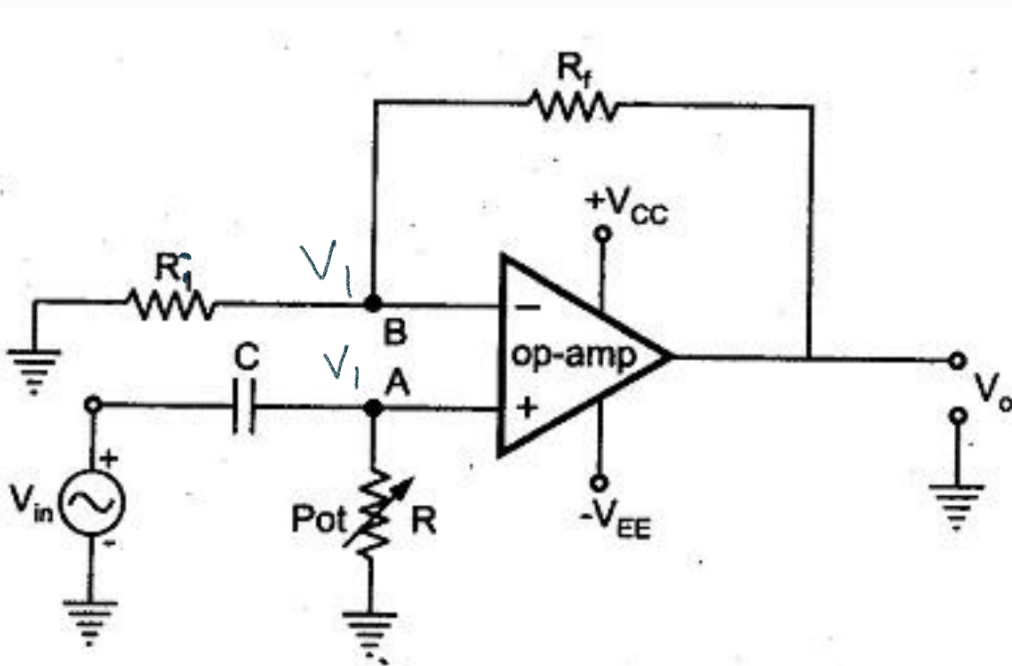


Fig. 2.79 First order high pass Butterworth filter

$$\textcircled{1} \quad \frac{V_{in} - V_1}{\frac{1}{j\omega C}} = \frac{V_1}{R} \Rightarrow V_{in} j\omega C = V_1 \left(j\omega C + \frac{1}{R} \right)$$

$$V_1 = \frac{j\omega C}{j\omega C + \frac{1}{R}} \times V_{in}$$

$$\textcircled{2} \quad \frac{V_1}{R_i} = \frac{V_o}{R_i + R_f} \Rightarrow V_o = V_1 \frac{R_i + R_f}{R_i}$$


$$(1) + (2) \Rightarrow V_o = V_{in} \frac{j\omega C}{j\omega C + \frac{1}{R}} \cdot \frac{R_i + R_f}{R_i}$$

$$H(j\omega) = \frac{j\omega RC}{j\omega RC + 1} \times \frac{R_i + R_f}{R_i}$$

$$= \frac{j\omega}{\underbrace{j\omega + \frac{1}{RC}}_{s + \underbrace{\frac{1}{RC}}_{\omega_c/b}}} \cdot \underbrace{\frac{R_i + R_f}{R_i}}_K$$


(b=1) Genel form: $H(s) = K \frac{s}{s + \frac{\omega_c}{b}}$

n. derece Bant Geçirgen Filtre

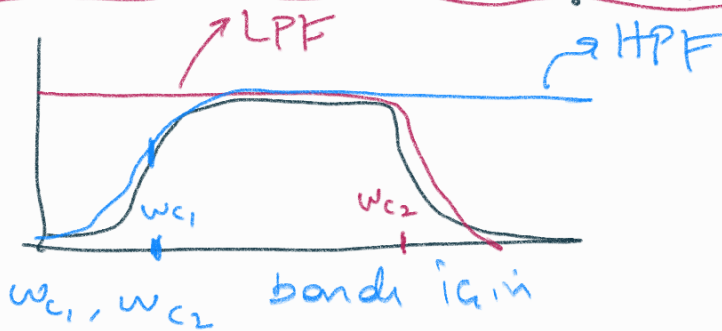

BPF (ω_{c1}, ω_{c2})

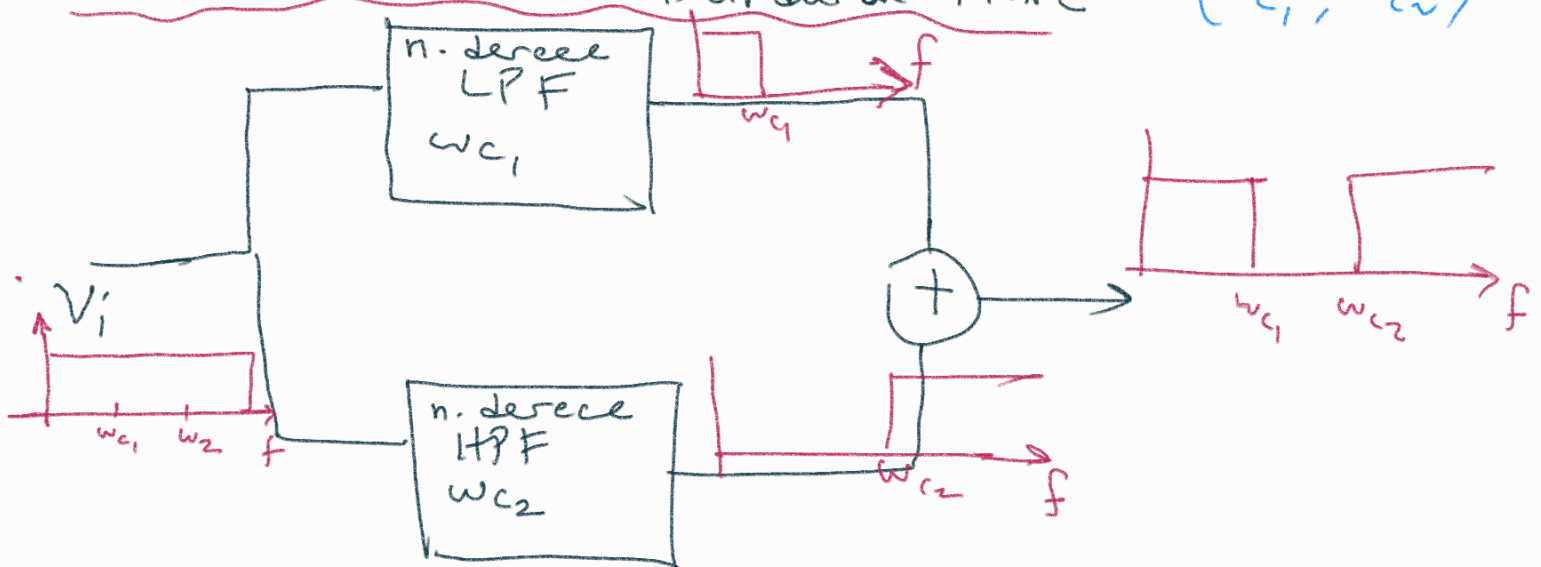n'inci Derece Bant Durduran Filtre (ω_{c1}, ω_{c2})



2. Derece Aktıf Geçiren Filtre

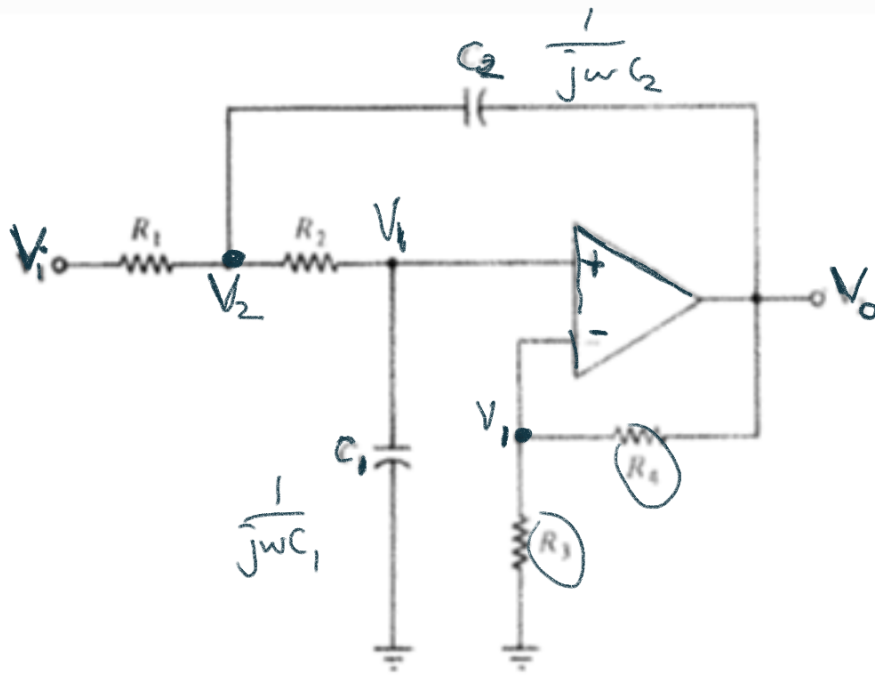


FIGURE 5.12 Second-order VCVS low-pass filter circuit.

$$(1) \quad \frac{V_i - V_2}{R_1} = \frac{V_2 - V_o}{1/j\omega C_2} + \frac{V_2 - V_1}{R_2}$$

$$(2) \quad \frac{V_2 - V_1}{R_2} = \frac{V_1}{1/j\omega C_1} \Rightarrow V_2 = V_1 \left(\frac{1}{R_2} + j\omega C_1 \right)$$

$$(3) \quad \frac{V_1}{R_3} = \frac{V_o}{R_3 + R_4} \Rightarrow V_1 = V_o \frac{R_3}{R_3 + R_4}$$

$$(2) \vee (3)'den : V_2 = V_o \left(\frac{R_3}{R_3 + R_4} \right) \left(\frac{1}{R_2} + j\omega C_1 \right)$$

$$(1) \quad \frac{V_i}{R_1} = V_2 \left(\frac{1}{R_1} + j\omega C_2 + \frac{1}{R_2} \right) - \frac{V_1}{R_2} - V_o j\omega C_2$$

$$\frac{V_i}{R_1} = V_o \underbrace{\left(\frac{R_3}{R_3 + R_4} \right)}_{\frac{1}{K}} \left(\frac{1}{R_2} + j\omega C_1 \right) \left(\frac{1}{R_1} + \frac{1}{R_2} + j\omega C_2 \right) - \frac{V_o}{R_2} \underbrace{\frac{R_3}{R_3 + R_4}}_{\frac{1}{K}} - V_o j\omega C_2 \frac{1}{K}$$

$$\frac{V_i}{R_1} = V_o \left[\frac{1}{K} \quad \frac{1}{R_1 R_2} + \frac{1}{K R_2^2} + \frac{j\omega C_2}{K R_2} + \frac{j\omega C_1}{K R_1} + \frac{j\omega C_1}{K R_2} - \frac{\omega^2 C_1 C_2}{K} - \frac{1}{R_2} \frac{1}{K} - \frac{j\omega C_2 K}{K} \right]$$

$$V_i = V_o \left[\frac{1}{K} \quad \frac{1}{R_2} + \frac{R_1}{K R_2^2} + \frac{j\omega C_2 R_1}{K R_2} + \frac{j\omega C_1}{K} + \frac{j\omega C_1 R_1}{K R_2} - \frac{\omega^2 C_1 C_2 R_1}{K} - \frac{R_1}{R_2} \frac{1}{K} - \frac{j\omega C_2 R_1 K}{K} \right]$$

$$\frac{V_o}{V_i} = \frac{1}{\frac{1}{K} \frac{1}{R_1} + \frac{R_1}{K R_2^2} - \frac{R_1}{R_2} \frac{1}{K} + j\omega \left(\frac{C_2 R_1}{K R_2} + \frac{C_1}{K} + \frac{C_1 R_1}{K R_2} - \frac{C_2 R_1 K}{K} \right) - \frac{\omega^2 C_1 C_2 R_1}{K}}$$

$$= \frac{K}{\frac{1}{R_1} + \frac{R_1}{R_2^2} - \frac{R_1}{R_2} + j\omega \left((C_2 + C_1) \frac{R_1}{R_2} + C_1 - C_2 R_1 K \right) - \omega^2 C_1 C_2 R_1}$$

General Form

$$H(s) = \frac{K b \omega_c^2}{s^2 + a \omega_c s + b \omega_c^2}$$

$$\omega_c = \sqrt{\frac{1}{C_1 C_2 R_1 R_2}} \quad b = 1$$

$$H(s) = \frac{K \times \frac{1}{C_1 C_2 R_1 R_2} b \omega_c^2}{s^2 + s \underbrace{\frac{(R_1 + R_2)}{C_1 R_1 R_2}}_{a \omega_c} + \frac{1}{C_1 C_2 R_1 R_2} b \omega_c^2}$$

2. Derece Yüksek Geçiren

(R ve C yer değiştirmiş)

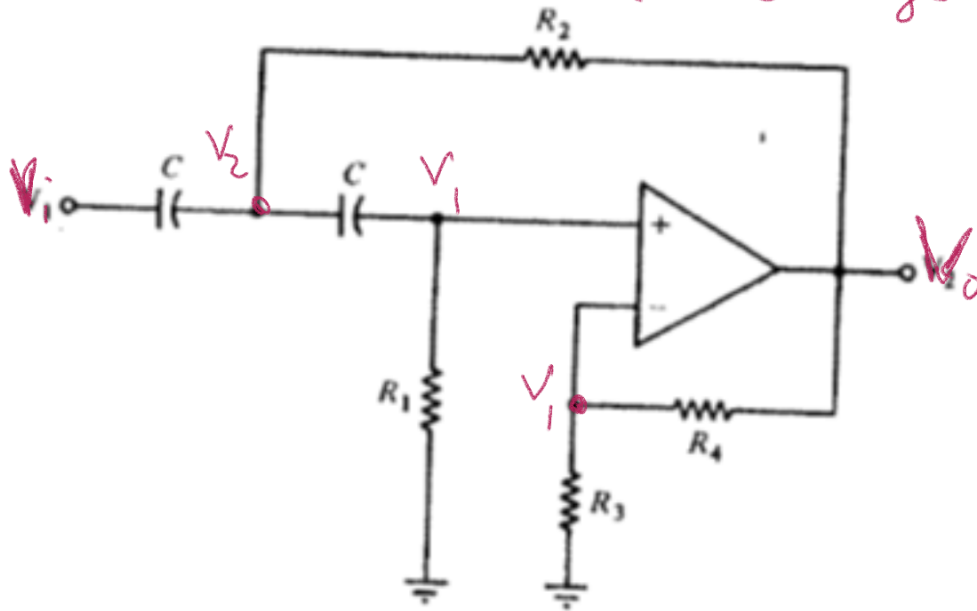


FIGURE 6.4 Second-order VCVS high-pass filter circuit.

$$(1) (V_i - V_2)j\omega C = \frac{V_2 - V_o}{R_2} + (V_2 - V_1)j\omega C$$

$$(2) (V_2 - V_1)j\omega C = \frac{V_1}{R_1}$$

$$(3) \frac{V_1}{R_3} = \frac{V_o}{R_4 + R_3}$$

$$(1) V_i j\omega C = V_2 \left(2j\omega C + \frac{1}{R_2} \right) - V_1 j\omega C - \frac{V_o}{R_2}$$

$$(2) V_2 j\omega C = V_1 \left(j\omega C + \frac{1}{R_1} \right) \Rightarrow V_2 = \frac{R_3}{R_4 + R_3} V_o \left(1 + \frac{1}{j\omega C R_1} \right)$$

$$(3) V_1 = \frac{R_3}{R_4 + R_3} V_o$$

$$V_i j\omega C = V_o \left[\frac{1}{K} \left(1 + \frac{1}{j\omega C R_1} \right) \left(2j\omega C + \frac{1}{R_2} \right) - \frac{1}{K} j\omega C - \frac{1}{R_2} \right]$$

$$V_i j\omega C = V_o \left[\frac{1}{K} \left(j^2 \omega^2 C + \frac{1}{R_2} + \frac{2}{R_1} - \frac{1}{j\omega C R_1 R_2} - j\omega C \right) - \frac{1}{R_2} \right]$$

$$V_i j\omega C = V_o \left[\frac{1}{K} \left(j\omega C + \frac{1}{R_2} + \frac{2}{R_1} - \frac{1}{j\omega C R_1 R_2} \right) - \frac{1}{R_2} \right]$$

$$\boxed{K=1}$$

$$V_i j\omega C = V_o \left[j\omega C + \frac{2}{R_1} - \frac{1}{j\omega C R_1 R_2} \right]$$

$$\frac{V_o}{V_i} = \frac{j\omega C}{j\omega C + \frac{2}{R_1} - \frac{1}{j\omega C R_1 R_2}}$$

$$\frac{V_o}{V_i} = \frac{-\omega^2 C^2 R_1 R_2}{-\omega^2 C^2 R_1 R_2 + 2j\omega C R_2 - 1}$$

$$H(s) = \frac{s^2 C^2 R_1 R_2}{s^2 C^2 R_1 R_2 + 2s C R_2 - 1}$$

$$H(s) = \frac{s^2}{s^2 + \frac{s}{R_1} \frac{C_1 + C_2}{C_1 C_2} + \frac{1}{C_1 C_2 R_1 R_2}}$$

General form :

$$\frac{K s^2}{s^2 + \frac{a \omega_c}{b} s + \frac{\omega_c^2}{b}}$$

(Butterworth: $b=1$)

$$\omega_c = \sqrt{\frac{1}{C_1 C_2 R_1 R_2}}$$

$$\frac{a \omega_c}{b} = \frac{1}{R_1} \frac{C_1 + C_2}{C_1 C_2}$$

n	a	b
1	-	1
2	1.414214	1
3	1.000000	1 → 2. derece 1 → 1. derece
4	0.765367 1.847759	1 → 2. derece 1 → 2. derece
5	- 0.618 1.618	1 → 1. derece 1 → 2. 1 → 2.
6		
7		
8		

2. derece :
LPF

$$H(s) = \frac{\frac{1}{C_1 C_2 R_1 R_2} + s \frac{R_1 + R_2}{C_1 R_1 R_2} + s^2}{b \omega_c^2 + s a \omega_c + s^2}$$

Annotations: ω_c^2 points to the constant term in the numerator; $\sqrt{2} \omega_c$ points to the coefficient of s in the numerator; ω_c^2 points to the constant term in the denominator; ω_c points to the coefficient of s in the denominator.

2. derece
HPF

$$H(s) = \frac{\frac{1}{C_1 C_2 R_1 R_2} + s \frac{1}{R_1} \left(\frac{C_1 + C_2}{C_1 C_2} \right) + s^2}{s^2 + \frac{a \omega_c}{b} s + \frac{\omega_c^2}{b}}$$

Annotations: ω_c^2 points to the constant term in the numerator; $\sqrt{2} \omega_c$ points to the coefficient of s in the numerator.

$b = 1$

$|H(j\omega)| =$

$$\frac{A_{LP}}{\sqrt{1 + (\omega/\omega_c)^{2n}}}$$

$n = 1, 2, 3, \dots$

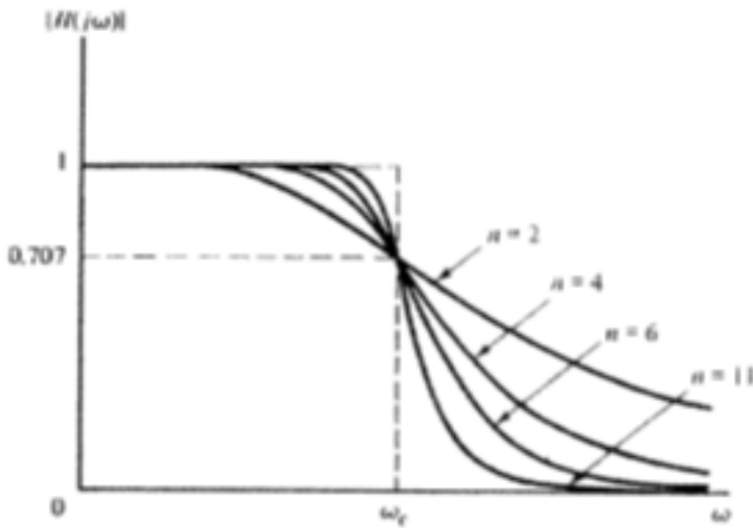


FIGURE 5.5 Low-pass Butterworth magnitudes.

Örnek: First order LPF $K=4$


$$\omega_c = 1000 \text{ Hz}$$

$$H(s) = K \frac{b \omega_c}{s + \omega_c b}$$

$$(b=1)$$

$$\omega_c = \frac{1}{RC} = 2000\pi$$

$$\frac{R_3 + R_2}{R_2} = 4$$

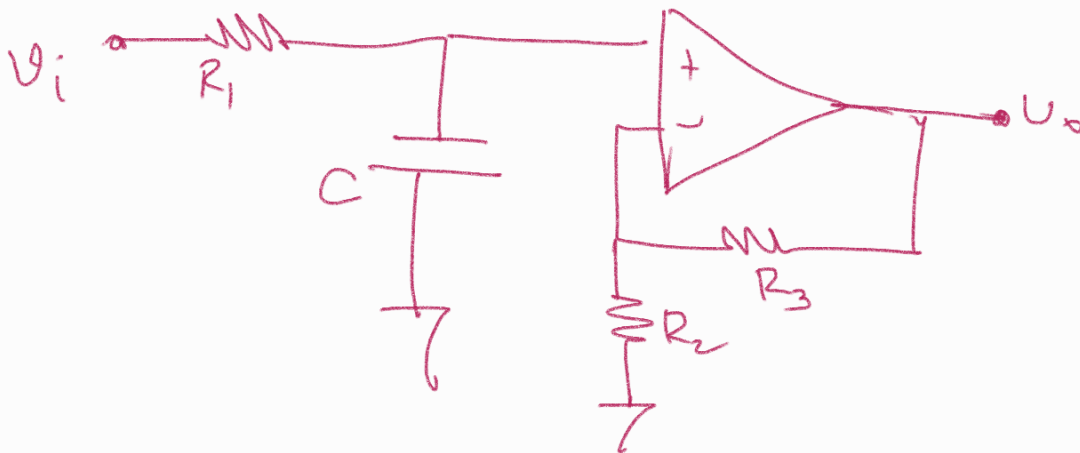

$$R_1 = 1 \text{ k}\Omega$$

$$C = \frac{1}{2\pi \cdot 10^6} = \frac{1}{2\pi} \mu\text{F}$$

$$R_2 = 1 \text{ k}\Omega \text{ olursa}$$

$$R_3 = 3 \text{ k}\Omega \text{ olur.}$$

2. derece LPF

$$H(s) = K \frac{b \omega_c^2}{s^2 + a \omega_c s + b \omega_c^2}$$

$$H(s) = \frac{K \frac{1}{C_1 C_2 R_1 R_2}}{\frac{1}{C_1 C_2 R_1 R_2} + \frac{s}{C_1} \frac{R_1 + R_2}{R_1 R_2} + s^2}$$

Örnek: 2nd order LPF Butterworth

$$K=2, \quad \omega_c = 1000 \text{ Hz}$$

$$(a = \sqrt{2}, \quad b = 1)$$

$$R_1, R_2, R_3, R_4, C_1, C_2 ?$$

CHAPTER 15: LAPLACE DÖNÜŞÜMÜ:

TABLE 15.1

Properties of the Laplace transform.

Property	$f(t)$	$F(s)$
Linearity	$a_1 f_1(t) + a_2 f_2(t)$	$a_1 F_1(s) + a_2 F_2(s)$
Scaling	$f(at)$	$\frac{1}{a} F\left(\frac{s}{a}\right)$
Time shift	$f(t-a)u(t-a)$	$e^{-as} F(s)$
Frequency shift	$e^{-at} f(t)$	$F(s+a)$
Time differentiation	$\frac{df}{dt}$	$sF(s) - f(0^-)$
	$\frac{d^2 f}{dt^2}$	$s^2 F(s) - sf(0^-) - f'(0^-)$
	$\frac{d^3 f}{dt^3}$	$s^3 F(s) - s^2 f(0^-) - sf'(0^-) - f''(0^-)$
	$\frac{d^4 f}{dt^4}$	$s^4 F(s) - s^3 f(0^-) - s^2 f'(0^-) - sf''(0^-) - f'''(0^-)$
Time integration	$\int_0^t f(x) dx$	$\frac{1}{s} F(s)$
Frequency differentiation	$tf(t) \rightarrow$	$-\frac{d}{ds} F(s)$
Frequency integration	$\frac{f(t)}{t}$	$\int_s^\infty F(x) dx$
Time periodicity	$f(t) = f(t+nT)$	$\frac{F_1(s)}{1 - e^{-sT}}$
Initial value	$f(0)$	$\lim_{s \rightarrow \infty} sF(s)$
Final value	$f(\infty)$	$\lim_{s \rightarrow 0} sF(s)$
Convolution	$f_1(t) * f_2(t)$	$F_1(s) F_2(s)$

TABLE 15.2

Laplace transform pairs.*

$f(t)$	$F(s)$
$\delta(t)$	1
$u(t)$	$\frac{1}{s}$
e^{-at}	$\frac{1}{s+a}$
t	$\frac{1}{s^2}$
t^n	$\frac{n!}{s^{n+1}}$
te^{-at}	$\frac{1}{(s+a)^2}$
$t^n e^{-at}$	$\frac{n!}{(s+a)^{n+1}}$
$\sin at$	$\frac{a}{s^2 + a^2}$
$\cos at$	$\frac{s}{s^2 + a^2}$
$\sin(at + \theta)$	$\frac{s \sin \theta + a \cos \theta}{s^2 + a^2}$
$\cos(at + \theta)$	$\frac{s \cos \theta - a \sin \theta}{s^2 + a^2}$
$e^{-at} \sin at$	$\frac{a}{(s+a)^2 + a^2}$
$e^{-at} \cos at$	$\frac{s+a}{(s+a)^2 + a^2}$

*Defined for $t \geq 0$; $f(t) = 0$, for $t < 0$.

15.5 Find the Laplace transform of each of the following functions:

(a) $t^2 \cos(2t + 30^\circ) u(t)$

(b) $3t^4 e^{-2t} u(t)$

(c) $2tu(t) - 4 \frac{d}{dt} \delta(t)$

(d) $2e^{-(t-1)} u(t)$

(e) $5u(t/2)$

(f) $6e^{-t/3} u(t)$

(g) $\frac{d^n}{dt^n} \delta(t)$

a) $\cos(2t) \xrightarrow{\mathcal{L}} \frac{s}{s^2+4}$

$$\cos(2t+30^\circ) = \cos(2t)\cos 30^\circ - \sin(2t)\sin 30^\circ$$

$$\xrightarrow{\mathcal{L}} \frac{s \cos 30^\circ}{s^2+4} - \frac{2 \sin 30^\circ}{s^2+4}$$

$$+ \cos(2t+30^\circ)$$

$$\xrightarrow{\mathcal{L}} \frac{d^2}{ds^2} \left[\frac{s \cos(30^\circ)}{s^2+4} - \frac{2 \sin 30^\circ}{s^2+4} \right]$$

b) $e^{-2t} u(t) \xrightarrow{\mathcal{L}} \frac{1}{s+2}$

$3t^4 e^{-2t} u(t) \xrightarrow{\mathcal{L}} \frac{d^4}{ds^4} \left(\frac{1}{s+2} \right) = 3 \frac{24}{(s+2)^5}$

$$\frac{1}{s+2} \rightarrow \frac{-1}{(s+2)^2} \rightarrow \frac{2}{(s+2)^3} \rightarrow \frac{-6}{(s+2)^4} \rightarrow \frac{+24}{(s+2)^5}$$

c) $2t u(t) - 4 \frac{d}{dt} \delta(t) \xrightarrow{\mathcal{L}} \frac{-2}{s^2} - 4s$

d) $2e^{-(t-1)} u(t) = 2e e^{-t} u(t) \xrightarrow{\mathcal{L}} \frac{2e}{s+1}$

e) $5u(t/2) \xrightarrow{\mathcal{L}} 5 \times 2$

$$u(t) \xrightarrow{\mathcal{L}} \frac{1}{s} \quad 5u\left(\frac{t}{2}\right) \rightarrow 2 \frac{1}{s} = \frac{5}{s}$$

f) $6e^{-t/3} u(t) = 6e^{-t/3} u\left(\frac{t}{3}\right)$

$$6e^{-t}u(t+1) \xrightarrow{\mathcal{L}} \frac{6}{s+1}$$

$$6e^{-t/3}u\left(\frac{t}{3}\right) \rightarrow \frac{6 \times 3}{3s+1}$$

$$g) \frac{d^n \delta(t)}{dt^n} = s^n$$

15.10 In two different ways, find the Laplace transform of

(I)

$$\cos t \xrightarrow{\mathcal{L}} \frac{s}{s^2+1}$$

$$e^{-t} \cos t \xrightarrow{\mathcal{L}} \frac{s+1}{(s+1)^2+1} \Rightarrow te^{-t} \cos t \xrightarrow{\mathcal{L}} \frac{d}{ds} \left[\frac{s+1}{(s+1)^2+1} \right]$$

$$\frac{d}{dt} (te^{-t} \cos t) \xrightarrow{\mathcal{L}} s \frac{d}{ds} \left[\frac{s+1}{(s+1)^2+1} \right]$$

(II)

$$e^{-t} \cos t + t(-e^{-t} \cos t - e^{-t} \sin t)$$

$$\underbrace{e^{-t} \cos t} - \underbrace{te^{-t} \cos t} - te^{-t} \sin t$$

$$\frac{s+1}{(s+1)^2+1} - \frac{d}{ds} \left[\frac{s+1}{(s+1)^2+1} \right] - \frac{d}{ds} \left[\frac{1}{(s+1)^2+1} \right]$$

15.14 Find the Laplace transform of the signal in Fig. 15.26.

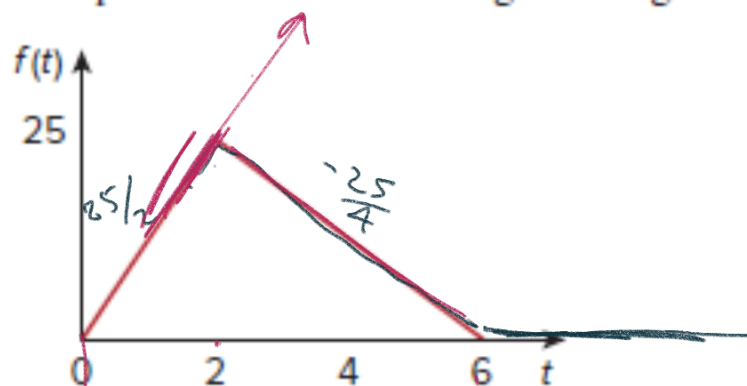


Figure 15.26
For Prob. 15.14.

$$f(t) = \frac{25}{2} t \underbrace{u(t)}_{\frac{1}{s}} - \boxed{\frac{75}{4} (t-2) u(t-2)} + \frac{25}{4} (t-6) u(t-6)$$

$$F(s) = \frac{25}{2} \frac{d}{ds} \left(\frac{1}{s} \right) - \frac{75}{4} e^{-2s} \frac{d}{ds} \left(\frac{1}{s} \right) + \frac{25}{4} e^{-6s} \frac{d}{ds} \left(\frac{1}{s} \right)$$

$$F(s) = -\frac{1}{s^2} \left[\frac{25}{2} - \frac{75}{4} e^{-2s} + \frac{25}{4} e^{-6s} \right]$$

15.19 Calculate the Laplace transform of the infinite train of unit impulses in Fig. 15.31.

dürtü treni

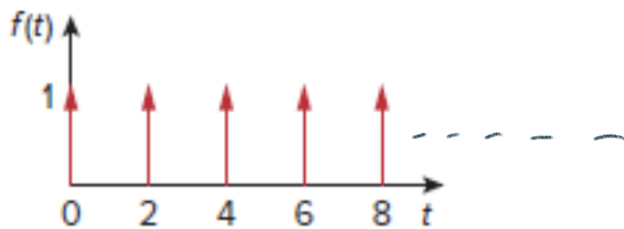


Figure 15.31
For Prob. 15.19.

Not: $\delta(t) \xrightarrow{\mathcal{L}} 1$
 $\delta(t-a) \xrightarrow{\mathcal{L}} e^{-as}$

$$\delta(t) + \delta(t-2) + \delta(t-4) + \dots$$

$$\sum_{i=0}^{\infty} \delta(t-2i) \xrightarrow{\mathcal{L}} \sum_{i=0}^{\infty} e^{-2is}$$

$$= \sum_{i=0}^{\infty} (e^{-2s})^i$$

$$\boxed{F(s) = \frac{1}{1-e^{-2s}}}$$

15.26 Determine the initial and final values of $f(t)$, if they exist, given that:

(a) $F(s) = \frac{5s^2 + 3}{s^3 + 4s^2 + 6}$

(b) $F(s) = \frac{s^2 - 2s + 1}{4(s-2)(s^2 + 2s + 4)}$

$$\lim_{t \rightarrow 0} f(t) = \lim_{s \rightarrow \infty} s F(s)$$

$$\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} s F(s)$$

a) $\frac{s(5s^2 + 3)}{s^3 + 4s^2 + 6} \Big|_{s=\infty} = 5 = f(0)$


$\frac{s(5s^2 + 3)}{s^3 + 4s^2 + 6} \Big|_{s=0} = 0 \Rightarrow f(\infty)$

b) $\frac{s(s^2 - 2s + 1)}{4(s-2)(s^2 + 2s + 4)} \Big|_{s=\infty} = \frac{1}{4} = f(0)$

$\frac{s(s^2 - 2s + 1)}{4(s-2)(s^2 + 2s + 4)} \Big|_{s=0} = 0 = f(\infty)$

$2, -1 + \sqrt{3}j, -1 - \sqrt{3}j$

Dolayısıyla bu kural kullanılmaz

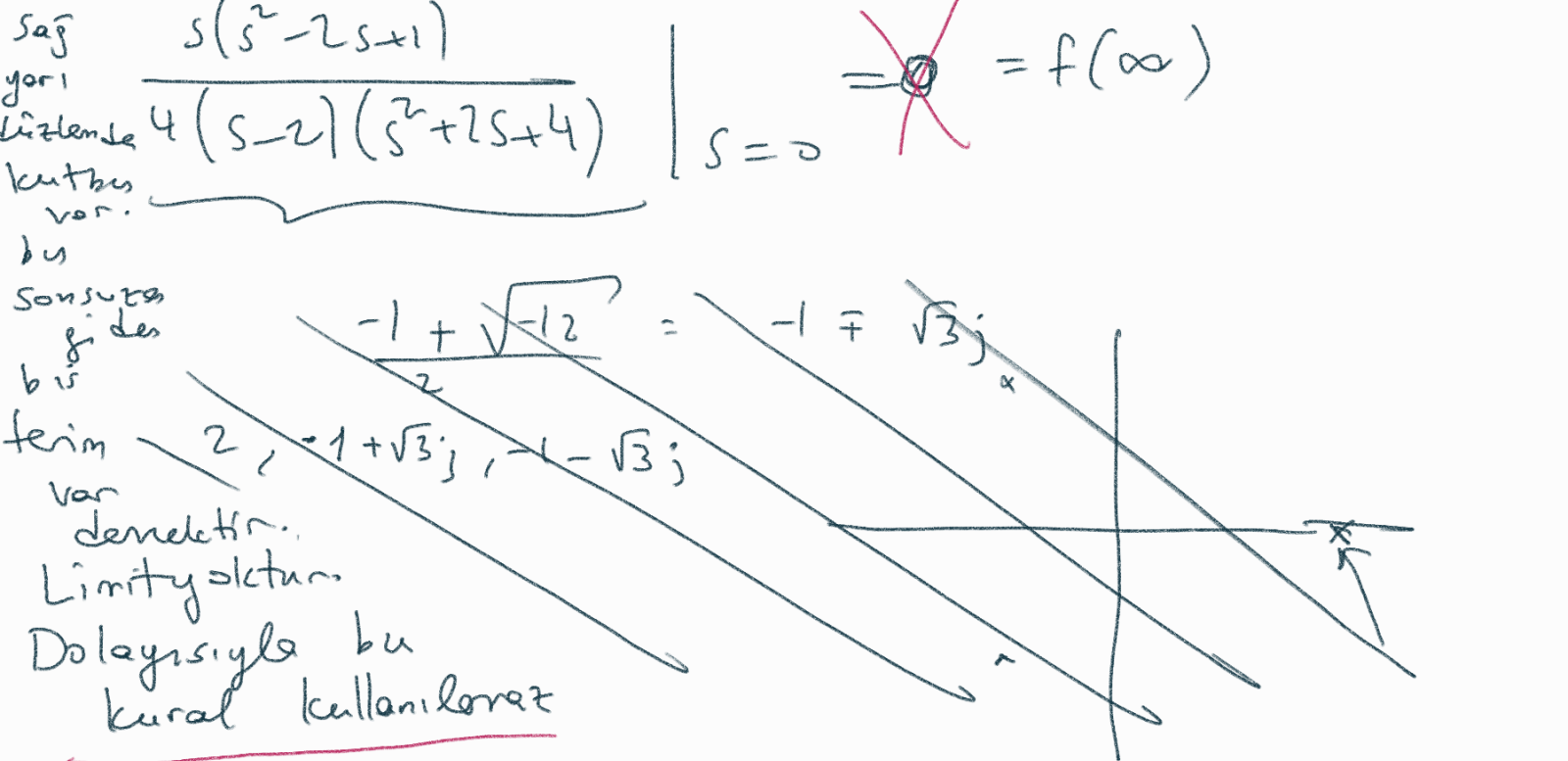

15.32 Determine the inverse Laplace transform of each of the following functions:

✓ (a) $\frac{8(s+1)(s+3)}{s(s+2)(s+4)}$

✓ (b) $\frac{s^2 - 2s + 4}{(s+1)(s+2)^2}$

✓ (c) $\frac{s^2 + 1}{(s+3)(s^2 + 4s + 5)}$

a) $F(s) = \frac{K_1 \xrightarrow{3}}{s} + \frac{K_2 \xrightarrow{2}}{s+2} + \frac{K_3 \xrightarrow{3}}{s+4}$

$$K_1 = \frac{8 \times 1 \times 3}{2 \times 4} = 3$$

$$K_2 = \frac{8 \times (-1) \times (1)}{(-2) \times (2)} = 2$$

$$K_3 = \frac{8 \times (-3) \times (-1)}{(-4) \times (-2)} = 3$$


$$f(t) = (3 + 2e^{-2t} + 3e^{-4t}) u(t)$$

15.26

$$s^3 + 4s^2 + 6$$

$$\frac{d}{dt} \rightarrow 3s^2 + 8s = s(3s+8)$$

	-8/3 0		
s	-	-	+
3s+8	-	+	+

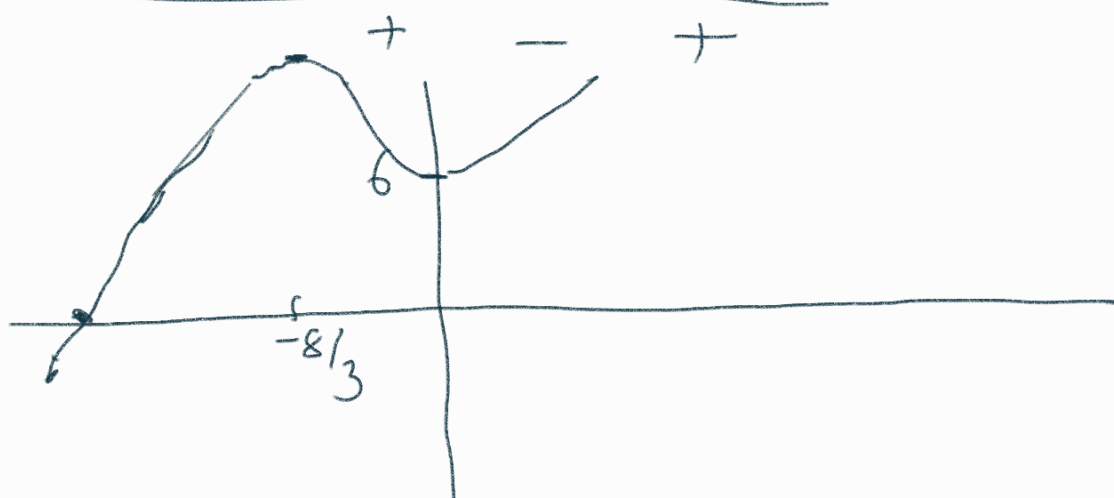

$$b) \quad \frac{s^2 - 2s + 4}{(s+1)(s+2)^2} = \frac{k_1 \rightarrow 7}{s+1} + \frac{k_2 \rightarrow -12}{(s+2)^2} + \frac{k_3 \rightarrow -6}{s+2}$$

$$k_3 = \left(\frac{d}{ds} \left\{ (s+2)^2 F(s) \right\} \right) \bigg|_{s=-2}$$

$$\left\{ \frac{d}{ds} \frac{s^2 - 2s + 4}{s+1} \right\} \bigg|_{s=-2} = \frac{(2s-2)(s+1) - (s^2 - 2s + 4)}{(s+1)^2} \bigg|_{s=-2}$$

$$= \frac{(-6)(-1) - (4 + 4 + 4)}{(-1)^2}$$

$$= \frac{6 - 12}{1} = -6$$

$$\boxed{\frac{7}{s+1} - \frac{12}{(s+2)^2} - \frac{6}{s+2}}$$

$$\frac{7(s+2)^2 - 12(s+1) - 6(s+1)(s+2)}{(s+1)(s+2)^2}$$

$$= \frac{7s^2 + 28s + 28 - 12s - 12 - 6s^2 - 18s - 12}{(s+1)^2(s+2)^2}$$

$$s^2 - 2s + 4 \quad \checkmark$$

$$f(t) = \left(7e^{-t} - 12te^{-2t} - 6e^{-2t} \right) u(t)$$

$$c) \quad \frac{s^2 + 1}{(s+3)(s^2 + 4s + 5)}$$

$$s_{1,2} = \frac{-4 \mp \sqrt{16 - 20}}{2}$$

$$= -2 \mp j$$

$$\frac{\overset{\rightarrow 5}{K_1}}{s+3} + \frac{\overset{\rightarrow -2}{K_2}}{\underbrace{s+2-j}_{\text{L-1}}} + \frac{\overset{\rightarrow -2}{K_2^*}}{s+2+j} \quad 2|K|e^{-\alpha t} \cos(\omega t + \theta_K)$$

$$K_1 = \frac{9+1}{9-12+5} = 5 \quad \rightarrow 4e^{-2t} \cos(2t + 180^\circ)$$

$$K_2 = \frac{(-2+j)^2 + 1}{(-2+j+3)(2j)} = \frac{+4 - 4j - 1 + 1}{(1+j)(2j)}$$

$$= \frac{4\sqrt{2} \angle -45^\circ}{\sqrt{2} \angle 45^\circ \cdot 2 \angle 90^\circ}$$

$$= 2 \angle -180^\circ = -2$$

$$K_2^* = -2$$

$$f(t) = 5e^{-3t} + 4e^{-2t} \cos(t + 180^\circ)$$

$$F(s) = \frac{s^2+1}{(s+3)(s^2+4s+5)} = \frac{\overset{\rightarrow 5}{K_1}}{s+3} + \frac{\overset{\rightarrow -4}{K_2}s + \overset{\rightarrow -8}{K_3}}{s^2+4s+5}$$

$$\underbrace{5s^2 + 20s + 25}_{\text{red}} + \underbrace{K_2 s^2}_{\text{red}} + K_3 s + 3K_2 s + 3K_3 = s^2 + 1 \quad \uparrow$$

$$K_2 = -4$$

$$20 + K_3 + 3K_2 = 0 \Rightarrow K_3 = -8$$

$$25 + 3K_3 = 1 \quad \checkmark$$

$$F(s) = \frac{5}{s+3} - \frac{4s+8}{\underbrace{s^2+4s+5}_{(s+2)^2+1}}$$

$$\frac{5}{s+3} - \frac{4(s+2)}{(s+2)^2+1}$$

$$5e^{-3t} - 4e^{-2t} \cos(t) \quad \underline{A \rightarrow N1}$$

15.40 Show that

$$\mathcal{L}^{-1} \left[\frac{4s^2 + 7s + 13}{(s+2)(s^2 + 2s + 5)} \right] =$$

$$[\sqrt{2}e^{-t} \cos(2t + 45^\circ) + 3e^{-2t}]u(t)$$

$$s_{1,2} = \frac{-2 \pm \sqrt{4 - 20}}{2} = -1 \pm 2j$$

$$F(s) = \frac{K_1}{s+2} + \frac{K_2 \frac{1}{\sqrt{2}} \angle 45^\circ}{s+1-2j} + \frac{K_2^* \frac{1}{\sqrt{2}} \angle -45^\circ}{s+1+2j}$$

$$K_1 = \frac{16 - 14 + 13}{4 - 4 + 5} = 3$$

$$K_2 = \frac{4(-1+2j)^2 + 7(-1+2j) + 13}{(-1+2j+2)(4j)}$$

$$= \frac{(4 + 16j - 16) - 7 + 14j + 13}{(1+2j)(4j)} = \frac{-6 - 2j}{(1+2j)(4j)}$$

$$K_2 = \frac{-3-j}{(1+2j)4j(-j)} = \frac{-1+3j}{2(1+2j)}$$

$$|K_2| = \frac{\sqrt{10}}{2\sqrt{5}} = \frac{1}{\sqrt{2}}$$


$$\frac{(-1+3j)(1-2j)}{2 \times 5} = \frac{-1+2j+3j+6}{2 \times 5} = \frac{5+5j}{10} = \frac{5\sqrt{2} \angle 45^\circ}{10} = \frac{1}{\sqrt{2}} \angle 45^\circ$$

$$f(t) = \left[3e^{-2t} + 2 \frac{1}{\sqrt{2}} e^{-t} \cos(2t + 45^\circ) \right] u(t)$$

$$(c) Z(s) = \frac{5}{s(s+1)(s^2+6s+10)}$$

*15.41 Let $x(t)$ and $y(t)$ be as shown in Fig. 15.36. Find $z(t) = x(t) * y(t)$.

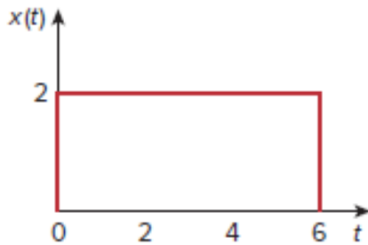
15.42 Design a problem to help other students better understand how to convolve two functions together.



$$2u(t) - 2u(t-6)$$

$$\frac{2}{s} + \frac{2e^{-6s}}{s}$$

Figure 15.36
For Prob. 15.41.

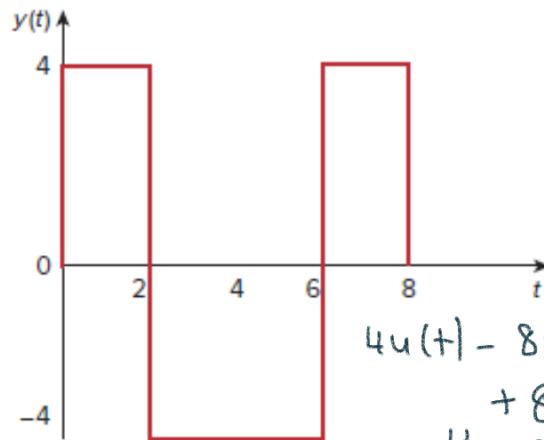

$$4u(t) - 8u(t-2) + 8u(t-6) - 4u(t-8)$$

$$\frac{4}{s} - \frac{8}{s}e^{-2s} + \frac{8}{s}e^{-6s} - \frac{4}{s}e^{-8s}$$



$$x(t) * y(t) \xrightarrow{\mathcal{L}} X(s) Y(s)$$

$$x(t) * y(t) = \int_{-\infty}^{\infty} x(\tau) y(t-\tau) d\tau$$

$$= \int_{-\infty}^{\infty} y(\tau) x(t-\tau) d\tau$$

$$8-t + t-6$$

$$\textcircled{2}$$

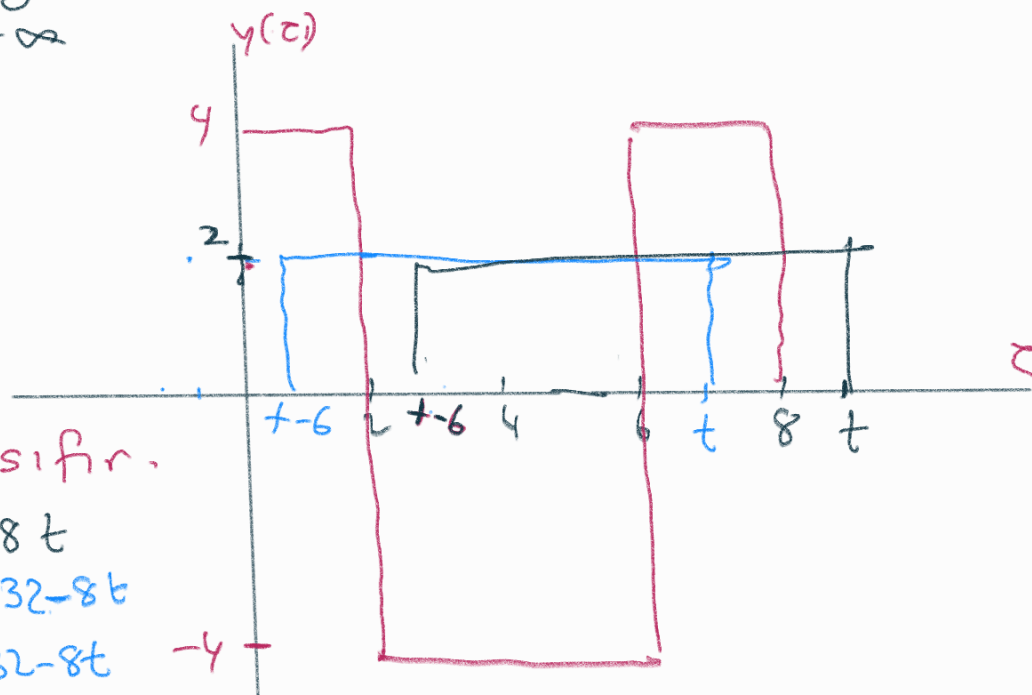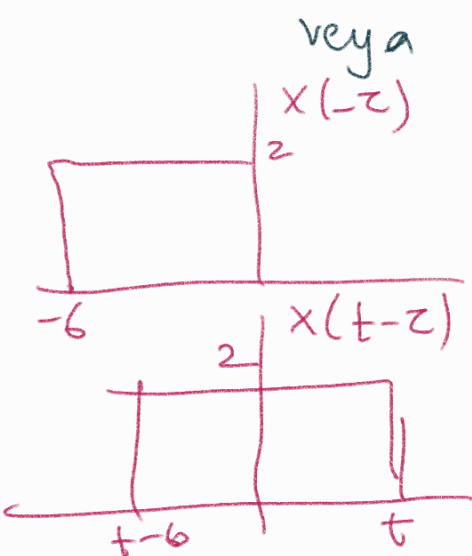

$$t < 0 \rightarrow \text{similar}$$

$$0 < t < 2 \rightarrow 8t$$

$$2 < t < 4 \rightarrow 32-8t$$

$$4 < t < 6 \rightarrow 32-8t$$

$$6 < t < 8 \rightarrow -16$$

$$8 < t < 12 \rightarrow 8t-80$$


$$16 + (t-2)(-8)$$

$$16 + 16 - 8t$$

$$12 < t < 14 \rightarrow 12-8t$$

$$14 < t \rightarrow 0$$


$$x(t) * y(t)$$

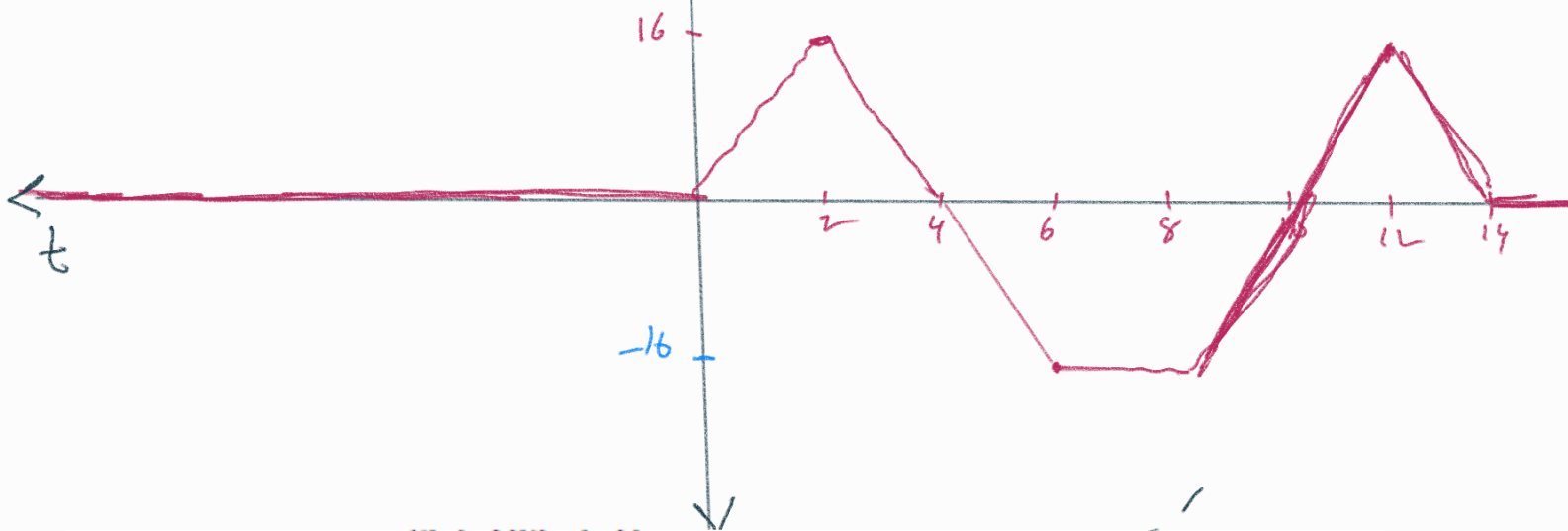

*15.49 Use the convolution integral to find:

(a) $t * e^{at}u(t)$

(b) $\cos(t) * \cos(t)u(t)$

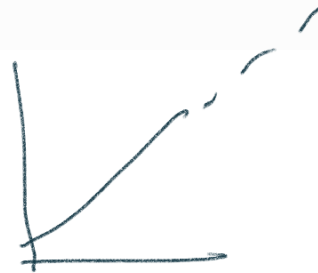

$$x(t) * y(t) = \int_{-\infty}^{\infty} x(\tau) y(t-\tau) d\tau$$

$$= \int_{-\infty}^{\infty} \underbrace{\tau u(\tau) e^{a(t-\tau)} u(t-\tau)}_{\tau < 0 \text{ ve } \tau > t \text{ iken sifir}} d\tau$$

$$= \int_0^t \tau e^{at} e^{-a\tau} d\tau$$

$$= e^{at} \int_0^t \tau e^{-a\tau} d\tau$$

$$\begin{aligned} \tau &= u \\ d\tau &= du \\ e^{-a\tau} d\tau &= du \\ -\frac{1}{a} e^{-a\tau} &= v \end{aligned}$$

Not $\int u dv = uv - \int v du$

$$= e^{at} \left[-\frac{\tau}{a} e^{-a\tau} \Big|_0^t - \int_0^t -\frac{1}{a} e^{-a\tau} d\tau \right]$$

$$= e^{at} \left[-\frac{t}{a} e^{-at} + \int_0^t \frac{1}{a} e^{-az} dz \right]$$

$$= e^{at} \left[-\frac{t}{a} e^{-at} + \left. -\frac{1}{a^2} e^{-az} \right|_0^t \right]$$

$$= e^{at} \left[-\frac{t}{a} e^{-at} + \frac{1}{a^2} - \frac{1}{a^2} e^{-at} \right] = -\frac{t}{a} - \frac{1}{a^2} + \frac{e^{at}}{a^2}$$

b) $\cos(t)u(t) * \cos(t)u(t)$ t

$$= \int_{-\infty}^{\infty} \cos(\tau) u(\tau) \cos(t-\tau) u(t-\tau) d\tau$$

$$= \int_0^t \cos(\tau) \cos(t-\tau) d\tau$$

$$= \int_0^t \frac{1}{2} \cos(t) + \frac{1}{2} \cos(2\tau-t) d\tau$$

$$= \left. \frac{1}{2} \cos(t) \tau \right|_0^t + \left. \frac{1}{4} \sin(2\tau-t) \right|_0^t$$

$$= \frac{t}{2} \cos(t) + \frac{1}{4} \sin(t) - \frac{1}{4} \sin(-t)$$

$$= \frac{t}{2} \cos(t) + \frac{1}{2} \sin(t)$$

15.52 Use the Laplace transform to find $i(t)$ for $t > 0$ if

$$\frac{d^2 i}{dt^2} + 3 \frac{di}{dt} + 2i + \delta(t) = 0,$$

$$i(0) = 0, \quad i'(0) = 3$$

$$i \rightarrow I$$

$$\frac{di}{dt} \rightarrow sI - i(0)$$

$$\frac{d^2 i}{dt^2} \rightarrow s(sI - i(0)) - i'(0)$$

$$= s^2 I - si(0) - i'(0)$$

$$s^2 I - \cancel{si(0)} - \cancel{i'(0)} + 3sI - \cancel{3i(0)} + 2I + 1 = 0$$

$$I(s^2 + 3s + 2) - 3 + 1 = 0$$

$$I = \frac{2}{s^2 + 3s + 2} = \frac{K_1}{s+1} + \frac{K_2}{s+2}$$

$$i(t) = (2e^{-t} - 2e^{-2t}) u(t)$$

15.60 Solve the following integrodifferential equation

$$2\frac{dx}{dt} + 5x + 3 \int_0^t x dt + 4 \overset{4u(t)}{=} \sin 4t, \quad x(0) = 1$$

$$\frac{dx}{dt} \rightarrow sX - x(0)$$

$$\int_0^t x dt \rightarrow \frac{X}{s}$$

$$\frac{4}{s^2 + 16}$$

$$2sX - 2 + 5X + 3\frac{X}{s} + \frac{4}{s} = \frac{4}{s^2 + 16}$$

$$\left(2s + 5 + \frac{3}{s}\right)X = \frac{4}{s^2 + 16} - \frac{4}{s} + 2$$

$$\frac{2s^2 + 5s + 3}{\cancel{s}} X = \frac{4s - 4s^2 - 64 + 2s(s^2 + 16)}{(s^2 + 16)\cancel{s}}$$

$$X = \frac{+2s^3 - 4s^2 + 4s + 32s - 64}{(s^2 + 16)(2s^2 + 5s + 3)}$$

$$X = \frac{+2(s^3 - 2s^2 + 18s - 32)}{(s^2 + 16) \cdot 2(s^2 + 2.5s + 1.5)}$$

$$= \frac{s^3 - 2s^2 + 18s - 32}{(s - 4j)(s + 4j)(s + 1)(s + 1.5)}$$

$\frac{-2.5 \pm \sqrt{6.25 - 6}}{2}$
 $\frac{-2.5 \pm 0.5}{2}$
 $-1, -1.5$

$$= \frac{K_1}{s+1} + \frac{K_2}{s+1.5} + \frac{K_3}{s-4j} + \frac{K_3^*}{s+4j}$$

$$K_1 = \frac{-1 - 2 - 18 - 32}{17 \times 0.5} = -\frac{106}{17}$$

$$K_2 = \frac{(-1.5)^3 - 4.5 - 27 - 32}{18.25(-0.5)} = 7.329$$

$$x(t) = \left[K_1 e^{-t} + K_2 e^{-1.5t} + 2|K_3| \cos(4t + \theta_K) \right] u(t)$$

$$K_3 = \left. X(s)(s - 4j) \right|_{s=4j}$$

CHAPTER 16: LAPLACE DÖNÜŞÜMÜ İLE DEVRE ANALİZİ




$R: \quad v = i R$



$V = I R$

$L: \quad v = L \frac{di}{dt} \xrightarrow{\mathcal{L}} V = L [s I - i(0^-)]$


$V = sL I - L i(0^-)$

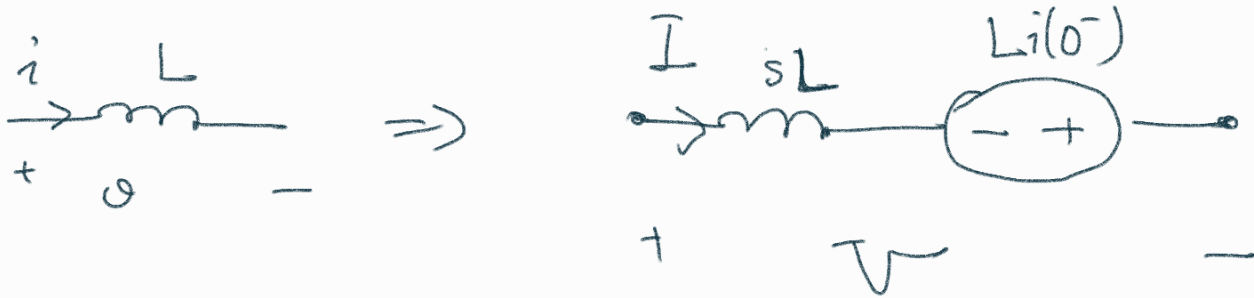


$I = \frac{V + Li(0^-)}{sL}$

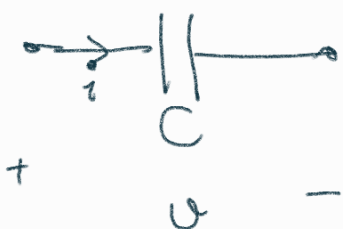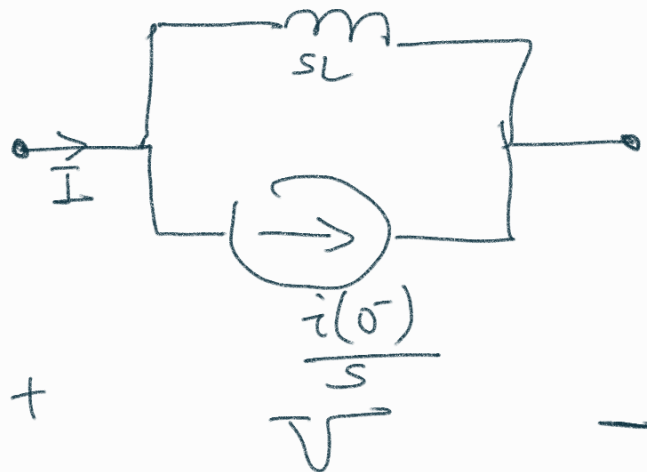

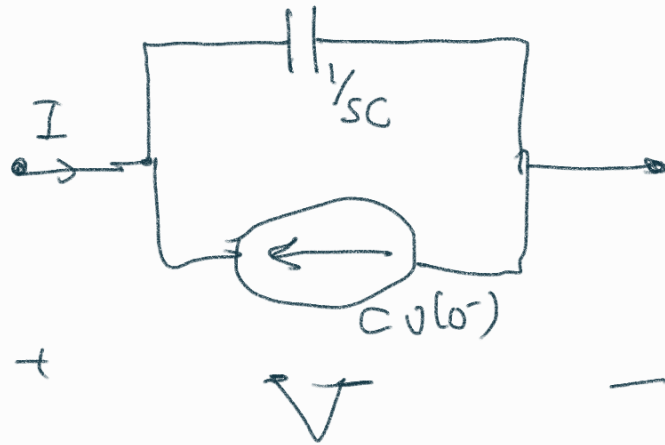$i = C \frac{dv}{dt} \xrightarrow{\mathcal{L}} I = sC V - C v(0^-)$


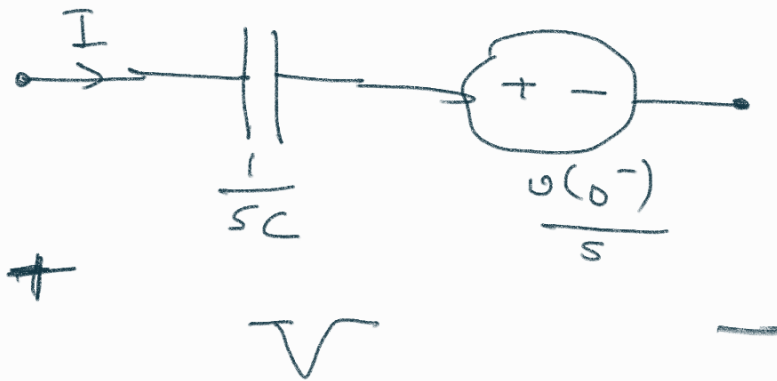
$$V = \frac{I + C v(0^-)}{sC} = \frac{I}{sC} + \frac{v(0^-)}{s}$$



16.10 The step responses of a series *RLC* circuit are

$$V_c = 40 - 10e^{-2000t} - 10e^{-4000t} \text{ V}, t > 0 \quad t=0 \rightarrow V_c(0^-) = 20$$

$$i_L(t) = 3e^{-2000t} + 6e^{-4000t} \text{ mA}, t > 0 \quad t=0 \rightarrow i_L(0^-) = 9 \text{ mA}$$

(a) Find C .

(b) Determine what type of damping is exhibited by the circuit.


overdamped / aşırı sönümlü



$$C \left(+200000e^{-2000t} + 400000e^{-4000t} \right) = (3e^{-2000t} + 6e^{-4000t}) \times 10^{-3}$$

$$C \times 200000 = 3 \times 10^{-3}$$

$$C = 0.15 \mu\text{F}$$

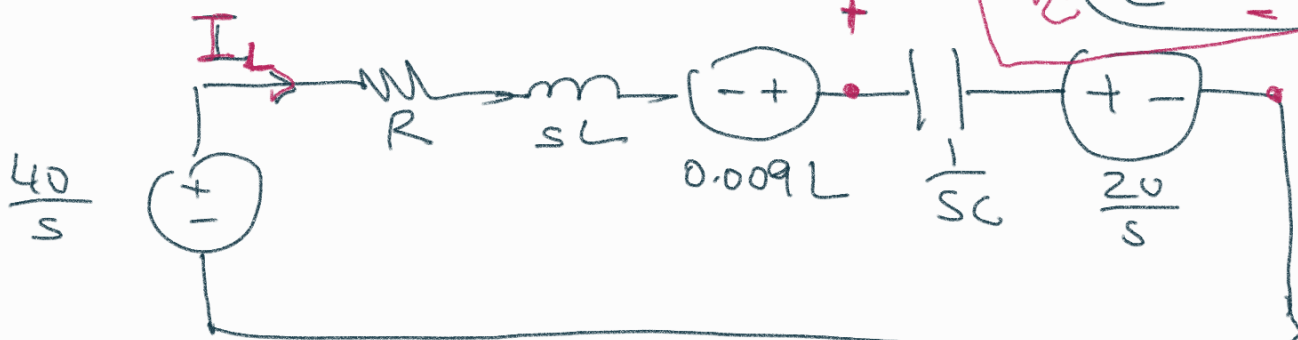

DOĞRU YÖNTEM

$$I_L = \frac{\frac{40}{s} + 0.009L - \frac{20}{s}}{R + sL + \frac{1}{sC}}$$

$$= \frac{0.009Ls + 20}{s^2L + sR + \frac{1}{C}}$$

$$I_L = \frac{0.009s + \frac{20}{L}}{s^2 + s\frac{R}{L} + \frac{1}{LC}} \text{ mA}$$

Kökler -2000, -4000

$$\frac{-\frac{R}{L} \pm \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}}}{2}$$

$$V_C = \frac{1}{sC} I_L + \frac{20}{s}$$

$$V_C = \frac{\frac{0.009}{C}s + \frac{20}{LC}}{s(s^2 + s\frac{R}{L} + \frac{1}{LC})} + \frac{20}{s}$$

40uH

$$\frac{-R}{L} = -6000 \text{ bulunur}$$

$$\frac{-6000 + \sqrt{6000^2 - \frac{4}{LC}}}{2} = -2000$$

$$\sqrt{6000^2 - \frac{4}{LC}} = 2000$$

$$36 \cdot 10^6 - 4 \cdot 10^6 = \frac{4}{LC}$$

$$8 \cdot 10^6 = \frac{1}{LC}$$

$$I_L = \frac{K_1}{s+2000} + \frac{K_2}{s+4000} = \frac{0.009s + \frac{20}{L}}{(s+2000)(s+4000)}$$

$$K_1 = \frac{-18 + \frac{20}{L}}{2000} = 3 \times 10^{-3}$$

$$-18 + \frac{20}{L} = 6$$

$$\frac{20}{L} = 24$$

$$L = \frac{20}{24} \text{ H}$$

$$V_C = \frac{K_1}{s} + \frac{K_2}{s+2000} + \frac{K_3}{s+4000} + \frac{20}{s}$$

$$= (K_1 + 20) + K_2 e^{-2000t} + K_3 e^{-4000t}$$

$$= 40 - 10e^{-2000t} - 10e^{-4000t}$$

$$V_C = \frac{\frac{0.009s}{C} + \frac{20}{LC}}{s(s+2000)(s+4000)} + \frac{20}{s}$$

$$\left[\frac{20}{LC} = 20 \right] \Rightarrow LC = 1 \Rightarrow C = \frac{24}{20}$$

$$\frac{-\frac{18}{C} + \frac{20}{LC}}{2000(-2000)} = -10$$

$$\frac{-\frac{18}{24} \times 20 + 20}{-4 \times 10^6} = -10$$

16.19 The switch in Fig. 16.42 moves from position A to position B at $t = 0$ (please note that the switch must connect to point B before it breaks the connection at A, a make before break switch). Find $v(t)$ for $t > 0$.


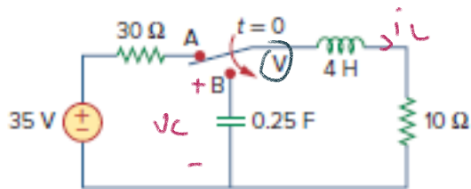
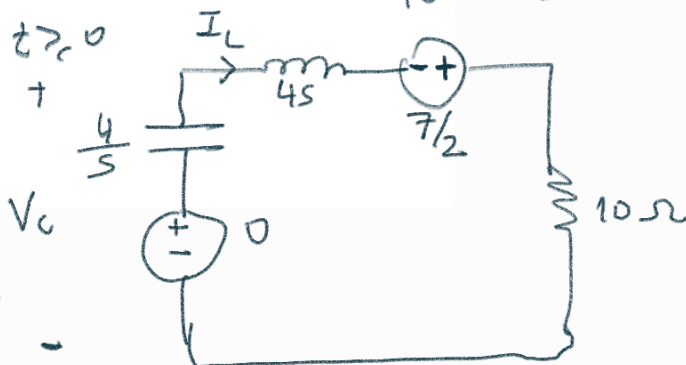


Figure 16.42
For Prob. 16.19.

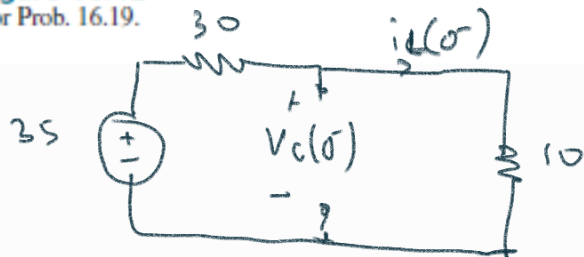

$$\rightarrow v_L = L \frac{di_L}{dt}$$

$$\rightarrow V_L = sL \bar{I}_L - L i_L(0^-)$$

$$i_C = C \frac{dv_C}{dt}$$

$$I_C = sC V_C - C v_C(0^-)$$

$$V_C = \frac{I_C + C v_C(0^-)}{sC} = \frac{I_C}{sC} + \frac{v_C(0^-)}{sC}$$

$$I_L \left(\frac{4}{s} + 4s + 10 \right) - \frac{7}{2} = 0$$

$$I_L = \frac{\frac{7}{2}}{4s + 10 + \frac{4}{s}}$$

$$I_L = \frac{\frac{7s}{2}}{4s^2 + 10s + 4}$$

$$I_L = \frac{7s}{8 \left(s^2 + \frac{5}{2}s + 1 \right)}$$

$$\frac{-\frac{5}{2} \pm \sqrt{\frac{25}{4} - 4}}{2} = \frac{-\frac{5}{2} \pm \frac{3}{2}}{2}$$

$$= -\frac{4}{2}, -\frac{1}{2} = (-2, -0.5)$$

$$I_L = \frac{K_1}{s+2} + \frac{K_2}{s+0.5}$$

$$K_1 = \frac{7(-2)}{8(-1.5)} = +\frac{7}{6}$$

$$K_2 = \frac{7(-0.5)}{8(1.5)} = -\frac{3.5}{12}$$

$$V_C = -\frac{4}{s} I_L = -\frac{7}{2 \left(s^2 + \frac{5}{2}s + 1 \right)} = \frac{K_1}{s+2} + \frac{K_2}{s+0.5}$$

=

$$K_1 = \frac{-7}{2(-1.5)} = 7/3$$

$$K_2 = \frac{-7}{2(1.5)} = -7/3$$

$$v_c(t) = \left(\frac{7}{3} e^{-2t} - \frac{7}{3} e^{-0.5t} \right) u(t) //$$

16.23 Obtain $v(t)$ for $t > 0$ in the circuit of Fig. 16.46.



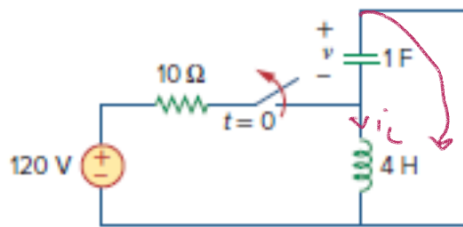
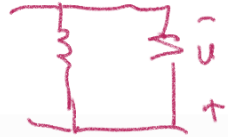


Figure 16.46
For Prob. 16.23.

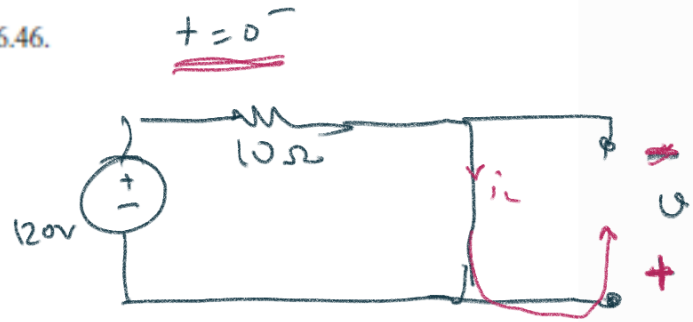

$$v(0^-) = 0$$

$$i_L(0^-) = 12 \text{ A}$$

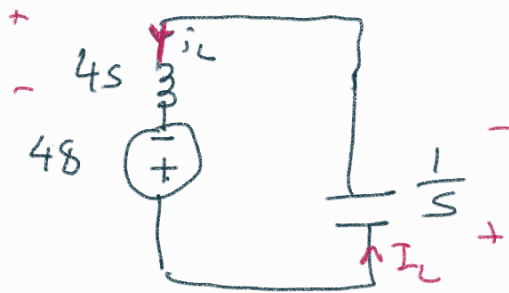

$$(4s + \frac{1}{s}) I_L = 48$$

$$I_L = \frac{48s}{4s^2 + 1}$$

$$= \frac{12s}{s^2 + 1/4}$$

$$V = \frac{1}{s} I_L$$

$$= \frac{12}{s^2 + 1/4}$$

$$\xrightarrow{\mathcal{L}^{-1}} \left\{ 24 \cdot \frac{\frac{1}{2}}{s^2 + 1/4} \right\}$$

$$= 24 \sin\left(\frac{1}{2}t\right)$$

$$= 24 \cos\left(\frac{1}{2}t - 90^\circ\right) //$$

16.25 Calculate $v(t)$ for $t > 0$ in the circuit of Fig. 16.48.



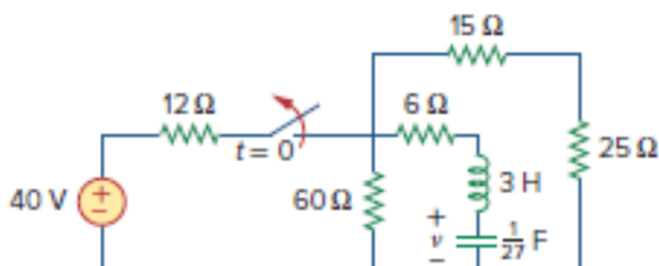
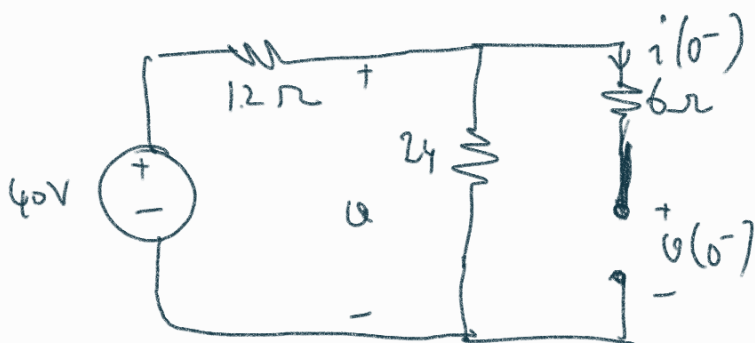


Figure 16.48
For Prob. 16.25.

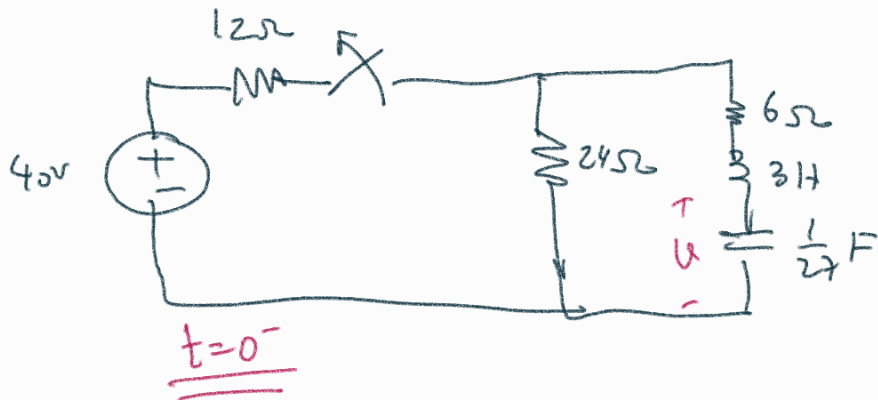

$$v(0^-) = 80/3 \checkmark$$

$$i(0^-) = 0$$

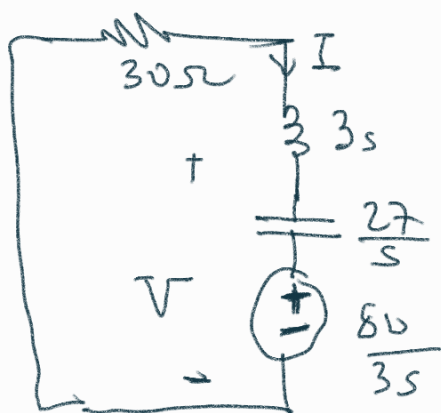

$$i_c = C \frac{dv_c}{dt}$$

$$I_c = s(C v_c - C v_c(0^-))$$

$$\frac{I_c + C v_c(0^-)}{sC} = v_c$$

$\frac{v_c(0^-)}{s}$

$$I \left(3s + 30 + \frac{27}{s} \right) + \frac{80}{3s} = 0$$

$$I = \frac{-\frac{80}{3s}}{\frac{3s^2 + 30s + 27}{s}}$$

$$= \frac{-80}{9(s^2 + 10s + 9)}$$

$$= \frac{-80}{9(s+1)(s+9)} = \frac{K_1}{s+1} + \frac{K_2}{s+9}$$

$$V = \frac{27}{s} I + \frac{80}{3s}$$

$$= \frac{-240}{s(s+1)(s+9)} + \frac{80}{3s}$$

$$V = \frac{K_1}{s} + \frac{K_2}{s+1} + \frac{K_3}{s+9} + \frac{80/3}{s}$$

$$K_1 = -\frac{240}{9} = -\frac{80}{3} \quad K_2 = \frac{-240}{(-1)(8)} = 30 \quad K_3 = \frac{-240}{(-9)(-8)} = -\frac{10}{3}$$

$$v(t) = \left(-\frac{80}{3} + 30e^{-t} - \frac{10}{3}e^{-9t} + \frac{80}{3} \right) u(t)$$

$$v(t) = \left(30e^{-t} - \frac{10}{3}e^{-9t} \right) u(t)$$

16.28 For the circuit in Fig. 16.51, find $v(t)$ for $t > 0$.


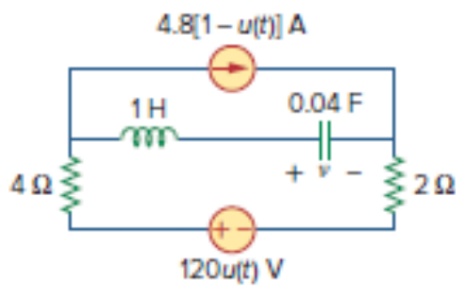



Figure 16.51
For Prob. 16.28.

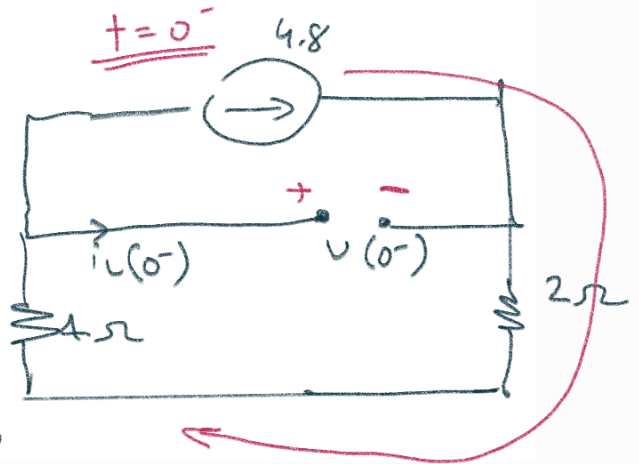

$$i_L(0^-) = 0$$

$$v(0^-) = -6 \times 4.8 =$$

$$-\frac{4.8 \times 6}{28.8}$$

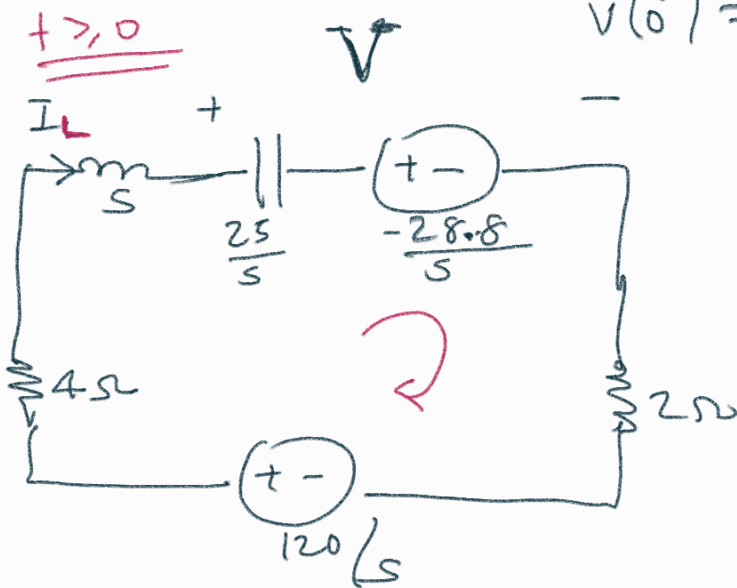

$$I_L \left(s + \frac{25}{s} + 6 \right) - \frac{28.8}{s} - \frac{120}{s} = 0$$

$$I_L = \frac{148.8}{s^2 + 6s + 25} = \frac{148.8}{(s+3-4j)(s+3+4j)}$$

$$-6 \pm \sqrt{36-100} = \frac{-6 \pm 8j}{2} = -3 \pm 4j$$

$$= \frac{148.8 \cdot \frac{1}{4} \cdot 4}{(s+3)^2 + 4^2} \xrightarrow{\mathcal{L}^{-1}} 37.2 e^{-3t} \sin(4t) u(t)$$

$$V = \frac{25}{s} I_L - \frac{28.8}{s}$$

$$= \frac{25 \times 148.8}{s(s^2 + 6s + 25)} - \frac{28.8}{s}$$

$$\frac{14880}{4} = 3720$$

$$= \frac{3720}{s(s+3-4j)(s+3+4j)} - \frac{28.8}{s}$$

$$= \frac{K_1}{s} + \frac{K_2}{s+3-4j} + \frac{K_2^*}{s+3+4j} - \frac{28.8}{s}$$


$$K_1 = \frac{3720}{25}, \quad K_2 = \frac{3720}{(-3+4j)8j} = \frac{3720}{5/127^\circ} 8/90^\circ$$

$$= 148.8$$

$$= \frac{148.8}{s} + \frac{93 \angle 143^\circ}{s+3-4j} + \frac{93 \angle -143^\circ}{s+3+4j} - \frac{28.8}{s} = 93 \angle 217^\circ = 93 \angle 143^\circ$$


$$v(t) = (120 + 186 e^{-3t} \cos(4t + 143^\circ)) u(t)$$

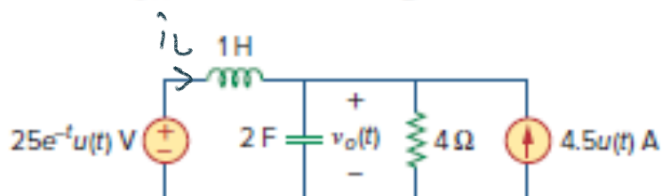16.35 Find $v_o(t)$ in the circuit of Fig. 16.58.



$$t \leq 0^- \\ v_o(0^-) = 0 \\ i_L(0^-) = 0$$

Figure 16.58
For Prob. 16.35.

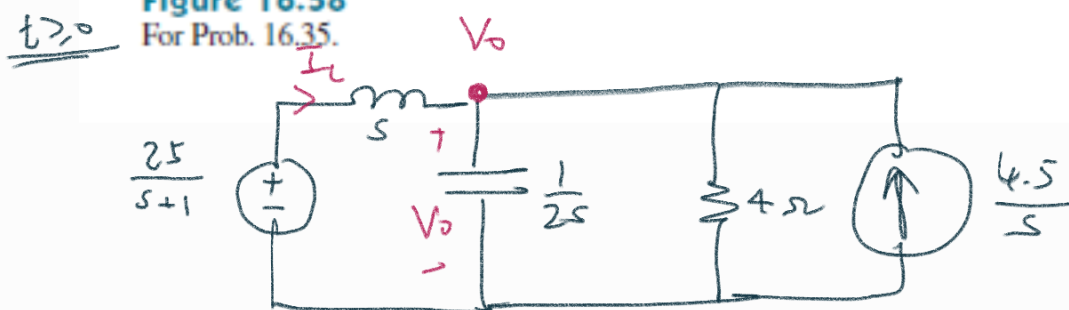

D.G.V.

$$\frac{V_o - \frac{25}{s+1}}{s} + V_o 2s + \frac{V_o}{4} = \frac{4.5}{s}$$

$$V_o \left(\frac{1}{s} + 2s + \frac{1}{4} \right) = \frac{25}{s(s+1)} + \frac{4.5}{s}$$

$$V_o \left(\frac{8s^2 + s + 4}{4s} \right) = \frac{25 + 4.5s + 4.5}{s(s+1)}$$

$$V_0 = \frac{18s + 118}{(s+1)(8s^2 + s + 4)} = \frac{18s + 118}{8(s+1)\left(s^2 + \frac{1}{8}s + \frac{1}{2}\right)}$$

$$\frac{-\frac{1}{8} \pm \sqrt{\frac{1}{64} - 2}}{2} \approx \frac{-\frac{1}{16} \pm \frac{\sqrt{2}j}{2}}$$

$$= \frac{K_1}{s+1} + \frac{K_2s + K_3}{s^2 + \frac{s}{8} + \frac{1}{2}}$$

$$\rightarrow K_1 = \frac{100}{8\left(1 - \frac{1}{8} + \frac{1}{2}\right)} = \frac{100}{11} \checkmark = 9.1$$

$$K_1s^2 + \frac{K_1}{8}s + \frac{K_1}{2} + K_2s^2 + K_3s + K_2s + K_3 = \frac{18s + 118}{8}$$

$$K_1 + K_2 = 0 \rightarrow K_2 = \frac{-100}{11} \checkmark = -9.1$$

$$\frac{100}{88} - \frac{100}{11} + K_3 = \frac{18}{8} \Rightarrow K_3 = \frac{18}{8} + \frac{700}{88} = 10.2$$

$$\frac{K_1}{2} + K_3 = \frac{55}{11} + 10.2 = \frac{118}{8}$$

$$\frac{9.1}{s+1} + \frac{-9.1s + 10.2}{\left(s + \frac{1}{16}\right)^2 + \frac{1}{2}}$$

$$\frac{9.1}{s+1} + \frac{-9.1\left(s + \frac{1}{16}\right) + 10.77}{\left(s + \frac{1}{16}\right)^2 + \frac{1}{2}} \rightarrow 10.77\sqrt{2} \frac{1}{\sqrt{2}}$$

$$\mathcal{L}^{-1} \rightarrow 9.1e^{-t} - 9.1e^{-\frac{t}{16}} \cos\left(\frac{1}{\sqrt{2}}t\right) + 10.77\sqrt{2}e^{-\frac{t}{16}} \sin\left(\frac{1}{\sqrt{2}}t\right)$$

16.42 Given the circuit in Fig. 16.65, find $i(t)$ and $v(t)$ for $t > 0$.


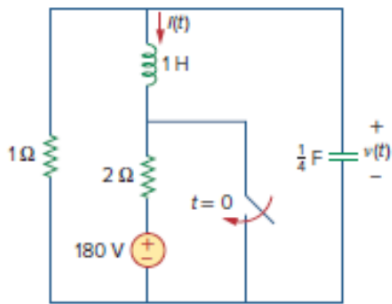



Figure 16.65
For Prob. 16.42.

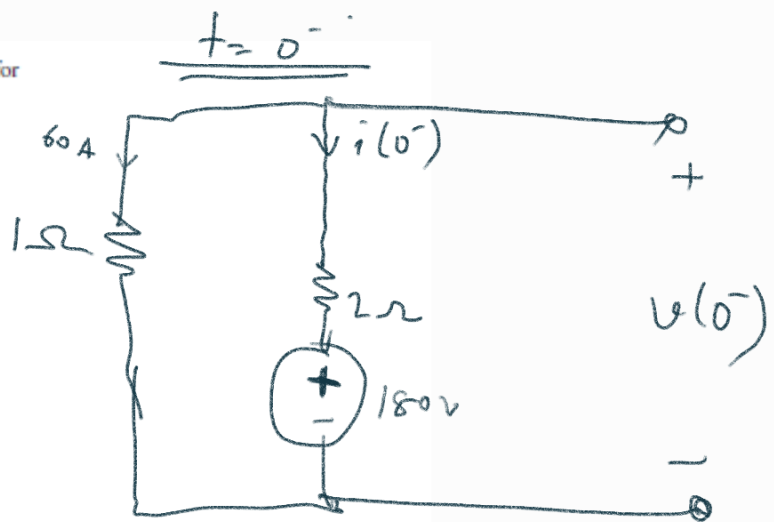

$$i(0^-) = -60 \text{ A}$$

$$v(0^-) = 60 \text{ V}$$

$t \geq 0$:

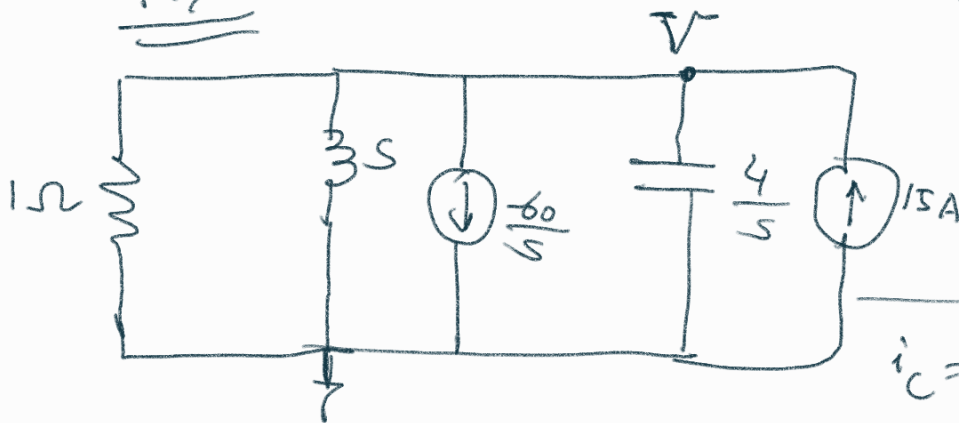

$$v_L = L \frac{di_L}{dt} \xrightarrow{\mathcal{L}} V_L = sLI_L - Li_0$$

$$I_L = \frac{V_L + Li_0}{sL}$$

$$I_L = \frac{V_L}{sL} + \frac{i_0}{s}$$

$$i_C = C \frac{dv_C}{dt} \xrightarrow{\mathcal{L}} I_C = sCV_C - Cv_0$$

$$\frac{V}{1} + \frac{V}{s} - \frac{60}{s} + \frac{Vs}{4} = 15$$

$$V \left(1 + \frac{1}{s} + \frac{s}{4} \right) = \frac{60}{s} + 15$$

$$V \cdot \frac{s^2 + 4s + 4}{4s} = \frac{15s + 60}{s}$$

$$V = \frac{60(s+4)}{(s+2)^2} = \frac{K_1}{(s+2)^2} + \frac{K_2}{s+2}$$

$$K_2 = 60(-2+4) = 120$$

$$K_2 = \left\{ \frac{d}{ds} 60(s+4) \right\} \bigg|_{s=-2} = 60$$

$$v(t) = (120te^{-2t} + 60e^{-2t})u(t)$$

16.48 Find $V_x(s)$ in the circuit shown in Fig. 16.71.

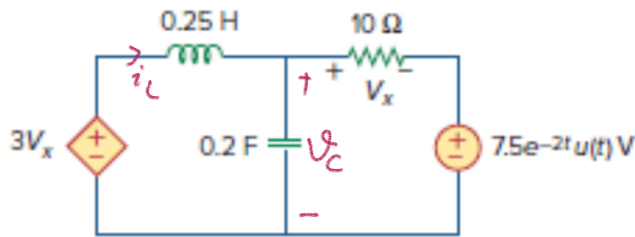



Figure 16.71

For Prob. 16.48.

$t = 0^-$

$$V_c(0^-) = 0$$

$$i_L(0^-) = 0$$

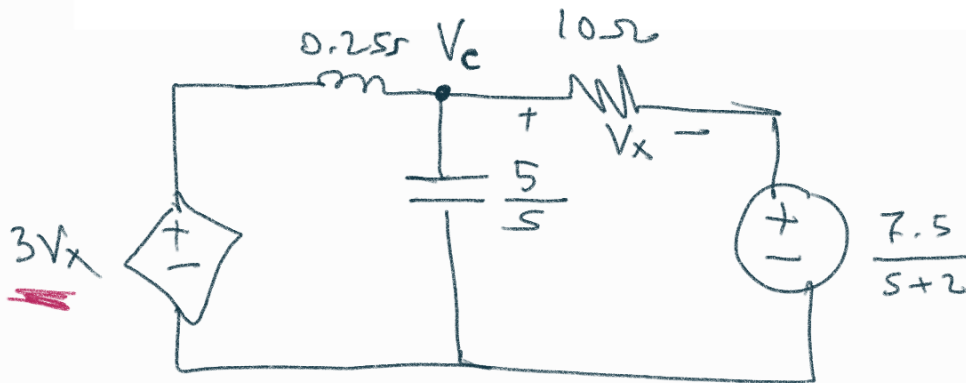

$$(1) \quad \frac{V_c - 3V_x}{0.25s} + \frac{V_c}{5} + \frac{V_c - \frac{7.5}{s+2}}{10} = 0$$

$$(2) \quad V_x = V_c - \frac{7.5}{s+2}$$

$$40V_c - 120V_x + 2s^2V_c + sV_c - \frac{7.5s}{s+2} = 0$$

$$V_c(2s^2 + s + 40) = 120V_x + \frac{7.5s}{s+2}$$

$$V_c(2s^2 + s + 40) = 120V_c - \frac{120 \times 7.5}{s+2} + \frac{7.5s}{s+2}$$

$$V_c(2s^2 + s - 80) = \frac{7.5}{s+2}(s - 120)$$

$$V_c = \frac{7.5(s - 120)}{2(s+2)(s^2 + \frac{s}{2} - 40)}$$

bir kök pozitif olduğundan
 V_c sonsuza gider.

$$\frac{-\frac{1}{2} \mp \sqrt{\frac{1}{4} + 160}}{2}$$

$$-\frac{1}{4} \mp 2\sqrt{10}$$

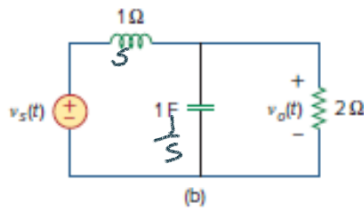
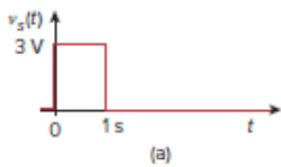


Figure 16.80
For Prob. 16.57.

$$3u(t) - 3u(t-1) \xrightarrow{\mathcal{L}} \frac{3}{s} - \frac{3e^{-s}}{s}$$

$$\frac{3}{s}(1-e^{-s}) \cdot \frac{2 // \frac{1}{s}}{s + (2 // \frac{1}{s})} = V_o(s)$$

$$= \frac{3}{s}(1-e^{-s}) \frac{\frac{2}{s}}{s + \frac{2}{s}} = \frac{3}{s}(1-e^{-s}) \frac{2}{s^2 + 2}$$

$$= \frac{3}{s}(1-e^{-s}) \frac{2}{2s^2 + s + 2} = \frac{6(1-e^{-s})}{s(2s^2 + s + 2)} = \frac{3(1-e^{-s})}{s(\tilde{s}^2 + \frac{1}{2}\tilde{s} + 1)}$$

$$\left(s_{1,2} = \frac{-\frac{1}{2} \pm \sqrt{\frac{1}{4} - 4}}{2} \right)$$

$$= \frac{-\frac{1}{4} \pm \sqrt{\frac{1}{16} - 1}}{2} = \frac{-\frac{1}{4} \pm \sqrt{\frac{-15}{16}}}{2}$$

$$= -0.25 \pm j0.97$$

$$\approx -0.25 \pm j$$

$$\frac{3}{s(s+0.25-j)(s+0.25+j)} - \frac{3e^{-s}}{s(s+0.25-j)(s+0.25+j)}$$

$$\frac{K_1}{s} + \frac{K_2}{s+0.25-j} + \frac{K_2^*}{s+0.25+j}$$

$$K_1 = \frac{3}{0.25^2 + 1^2} = 2.82$$

$$K_2 = \frac{3}{(-0.25+j)(2j)} = \frac{-3}{+2 + 0.5j} = 1.46 \angle 14^\circ = 1.46 \angle -166^\circ$$

$$(2.82 + 2.92e^{-0.25t} \cos(t-166^\circ))u(t)$$

$$- (2.82 + 2.92e^{-0.25(t-1)} \cos((t-1)-166^\circ))u(t-1)$$

16.66 For the op amp circuit in Fig. 16.89, find $v_o(t)$ for $t > 0$. Take $v_s = 12 e^{-5t} u(t)$ V. $\rightarrow V_s = \frac{12}{s+5}$

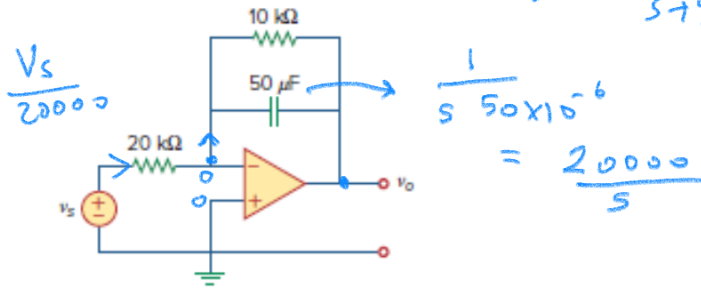


Figure 16.89
For Prob. 16.66.

$$V_o = -\frac{V_s}{20000} \times \left(10000 \parallel \frac{20000}{s} \right)$$

$$= \frac{-12}{20000(s+5)} \times \frac{\frac{2 \times 10^8}{s}}{10000 + \frac{20000}{s}}$$

$$= \frac{-12 \times 2}{s} \times \frac{1}{2(s+5) \left(1 + \frac{2}{s} \right)} = \frac{-24}{2(s+5) \left(\frac{s+2}{s} \right)}$$

$$V_o(s) = \frac{-12}{(s+2)(s+5)}$$

$$V_o(s) = \frac{K_1}{s+2} + \frac{K_2}{s+5}$$

$$K_1 = -4 \quad K_2 = +4$$

$$v_o(t) = (-4e^{-2t} + 4e^{-5t})u(t)$$

$$\frac{V_o}{V_s} = H(s) \xrightarrow{\mathcal{L}^{-1}} h(t) \text{ dürtü tepkisi}$$

$$\delta(t) * \underbrace{h(t)}_{\text{dürtü tepkisi}} \xrightarrow{\mathcal{L}} \underbrace{\mathcal{L}\{\delta(t)\}}_1 H(s) = 1+Ls$$

16.69 Find $I_1(s)$ and $I_2(s)$ in the circuit of Fig. 16.92.


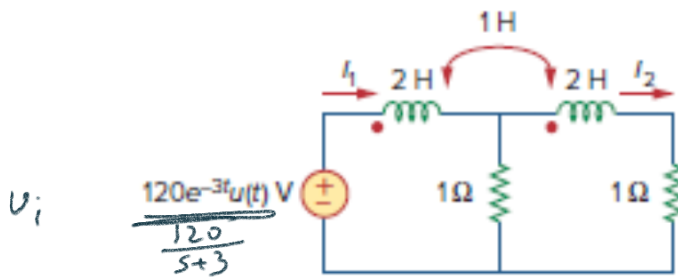


Figure 16.92
For Prob. 16.69.

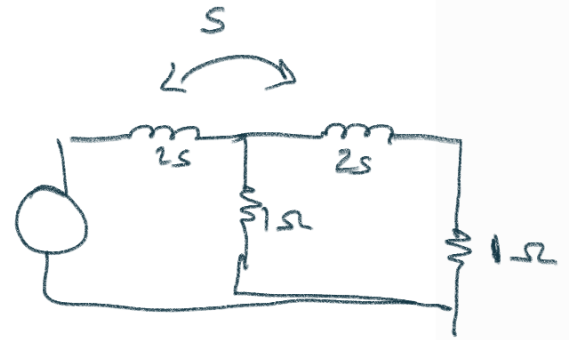

$$(1) -v_i + 2i_1' + 1i_2' + 1(i_1 - i_2) = 0$$

$$(2) 1(i_2 - i_1) + 2i_2' + 1i_1' + 1i_2 = 0$$

s-domain:

$$(1) -\frac{120}{s+3} + 2sI_1 + sI_2 + I_1 - I_2 = 0$$

$$(2) I_2 - I_1 + 2sI_2 + sI_1 + I_2 = 0$$

$$(1) (2s+1)I_1 + (s-1)I_2 = \frac{120}{s+3}$$

$$(2) (s-1)I_1 + (2s+2)I_2 = 0 \Rightarrow I_2 = \frac{-(s-1)}{2s+2} I_1$$

$$(1) \left[2s+1 - \frac{(s-1)^2}{2s+2} \right] I_1 = \frac{120}{s+3}$$

$$\frac{4s^2 + 4s + 2s + 2 - s^2 + 2s - 1}{2(s+1)} I_1 = \frac{120}{s+3}$$

$$= I_1 = \frac{240(s+1)}{(s+3)(3s^2 + 8s + 1)}$$

$$= \frac{80(s+1)}{(s+3)\left(s^2 + \frac{8}{3}s + \frac{1}{3}\right)}$$


$$s_{1,2} = \frac{-\frac{8}{3} \mp \sqrt{\left(\frac{64}{9} - \frac{4}{3}\right)}}{2} = \frac{-\frac{8}{3} \mp \sqrt{\frac{52}{9}}}{2}$$

$$= \frac{-2.7 \mp 2.4}{2}$$

$$= -0.15, -2.55$$

$$i_1(t) = \frac{K_1}{s+3} + \frac{K_2}{s+0.15} + \frac{K_3}{s+2.55}$$

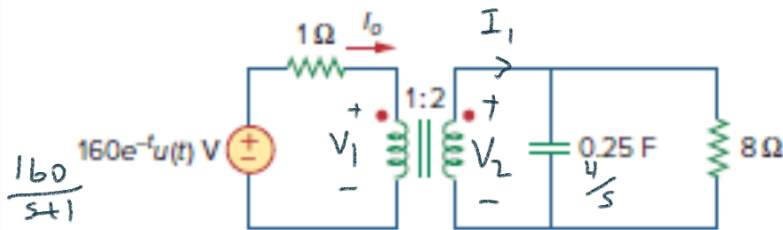16.71 For the ideal transformer circuit in Fig. 16.94, determine $i_o(t)$.



$$V_2 = 2V_1$$

$$I_0 = 2I_1$$

Figure 16.94
For Prob. 16.71.

$$\rightarrow \frac{160}{s+1} = 1 \cdot I_0 + V_1$$

$$V_2 = I_1 \left(\frac{4}{s} \parallel 8 \right) \Rightarrow 2V_1 = \frac{I_0}{2} \left(\frac{4}{s} \parallel 8 \right)$$

$$\frac{160}{s+1} = I_0 + \frac{I_0}{4} \left(\frac{4}{s} \parallel 8 \right)$$

$$= I_0 \left[1 + \frac{1}{4} \frac{\frac{32}{s}}{\frac{4}{s} + 8} \right] = I_0 \left[1 + \frac{1}{4} \frac{\cancel{32}^8}{8s+4} \right]$$

$$I_0 = \frac{\frac{160}{s+1}}{\frac{8s+4+8}{8s+4}} = \frac{160}{s+1} \frac{8s+4}{8s+12}$$

$$I_0 = \frac{80(2s+1)}{(s+1)(s+1.5)}$$

$$K_1 = -160$$

$$K_2 = +320$$

$$i_o(t) = (-160e^{-t} + 320e^{-1.5t})u(t)$$

(Not: yansıyan empedans ile daha hızlı yapılabilirdi)

16.77 Obtain the transfer function $H(s) = V_o/V_s$ for the circuit of Fig. 16.96.

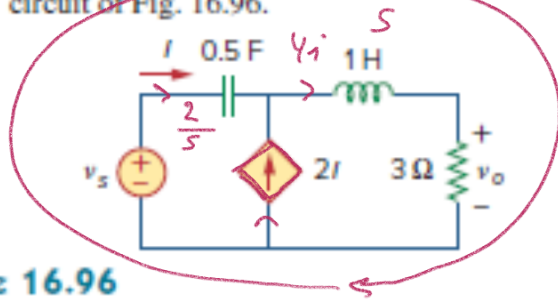


Figure 16.96
For Prob. 16.77.

$$-V_s + \frac{2}{s} I + s 4 I + 3 I = 0$$

$$I = \frac{V_s}{\frac{2}{s} + 4s + 3}$$

$$V_o = 3 I = \frac{3s V_s}{4s^2 + 3s + 2} \Rightarrow H(s) = \frac{V_o}{V_s} = \frac{3s}{4s^2 + 3s + 2}$$

16.85 A circuit has a transfer function

$$H(s) = \frac{3(s+4)}{(s+1)(s+2)^2}$$

$$h(t) = ?$$

Find the impulse response.

$$x(t) \rightarrow \boxed{h(t)} \rightarrow y(t)$$

$$y(t) = x(t) * h(t)$$

$$\frac{K_1}{s+1} + \frac{K_2}{(s+2)^2} + \frac{K_3}{s+2}$$

$$Y(s) = X(s) H(s)$$

$$K_1 = \frac{3 \times 3}{1} = 9$$

$$K_2 = \frac{3 \times 2}{-1} = -6$$

$$K_3 = \left(\frac{d}{ds} (s+2)^2 H(s) \right) \bigg|_{s=-2} = \left[\frac{d}{ds} \frac{3(s+4)}{s+1} \right]_{s=-2}$$

$$= \frac{3(s+1) - 3(s+4)}{(s+1)^2} \bigg|_{s=-2}$$

$$= \frac{-3 - 6}{1} = -9$$

$$h(t) = (9e^{-t} - 6te^{-2t} - 9e^{-2t})u(t)$$

16.90 Develop the state equations for the circuit shown in Fig. 16.104.

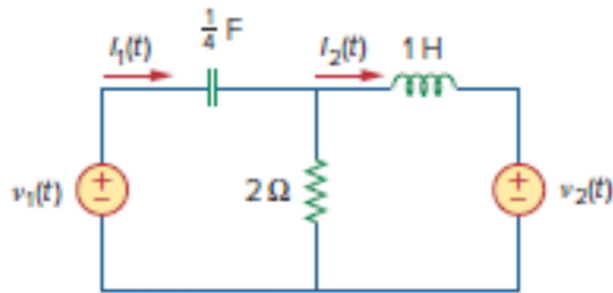


Figure 16.104
For Prob. 16.90.

$$\begin{aligned}\bar{X}' &= A\bar{X} + B\bar{u} \\ \bar{y} &= C\bar{X} + D\bar{u}\end{aligned}$$

16.97 A system is formed by cascading two systems as shown in Fig. 16.106. Given that the impulse responses of the systems are

$$h_1(t) = 21e^{-t}u(t), \quad h_2(t) = e^{-4t}u(t)$$

- (a) Obtain the impulse response of the overall system.
(b) Check if the overall system is stable.

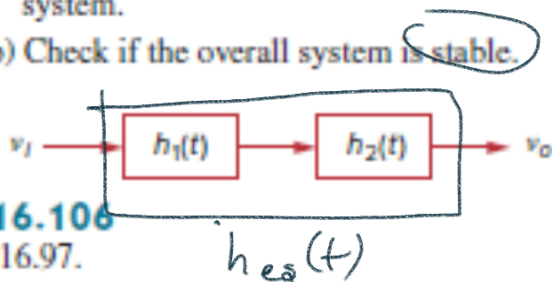


Figure 16.106
For Prob. 16.97.

$$H_{cs}(s) = H_1(s) H_2(s)$$

$$= \frac{21}{s+1} \cdot \frac{1}{s+4}$$

Transfer fonksiyonu

$$h_{cs}(t) = \mathcal{L}^{-1} \{ H_{cs}(s) \}$$

$$H_{cs}(s) = \frac{K_1}{s+1} + \frac{K_2}{s+4} \xrightarrow{\mathcal{L}} h_{cs}(t) = (7e^{-t} - 7e^{-4t})u(t)$$

b) T.F. kutupları sol yarı düzlemde olduğundan sistem karardır