

13.33 Determine the input impedance of the air-core transformer circuit of Fig. 13.102.

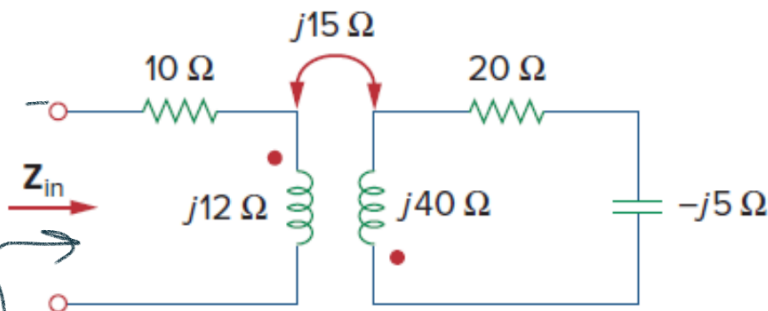


Figure 13.102

For Prob. 13.33.


$$Z_{in} = 10 + j12 + \frac{15^2}{20 + j35}$$

$$= \frac{200 + j350 + j240 - 420 + 225}{20 + j35}$$

$$= \frac{5 + j590}{20 + j35} = \frac{1 + j118}{4 + j7} = \frac{118 \angle 90^\circ}{\sqrt{65} \angle 60.25^\circ}$$

$$Z_{in} = 14.64 \angle 29.75^\circ \Omega$$

Ideal Trafo lar

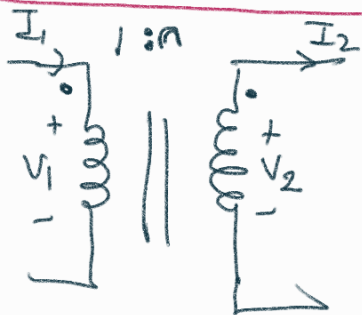

$$V_1, V_2$$


$$I_1, I_2$$

$$\frac{|V_2|}{|V_1|} = n \quad \frac{|I_1|}{|I_2|} = n$$

Nokta kuralı:

- Hen $\overline{V_1}$ hen de $\overline{V_2}$ noktalı tarafta aynı işaretli ise $\frac{V_2}{V_1} = n$, değilse $\frac{V_2}{V_1} = -n$
- Hen $\overline{I_1}$ hen de $\overline{I_2}$ noktalı taraftan giriyorsa veya çıkıyorsa $\frac{I_1}{I_2} = n$, değilse $\frac{I_1}{I_2} = -n$

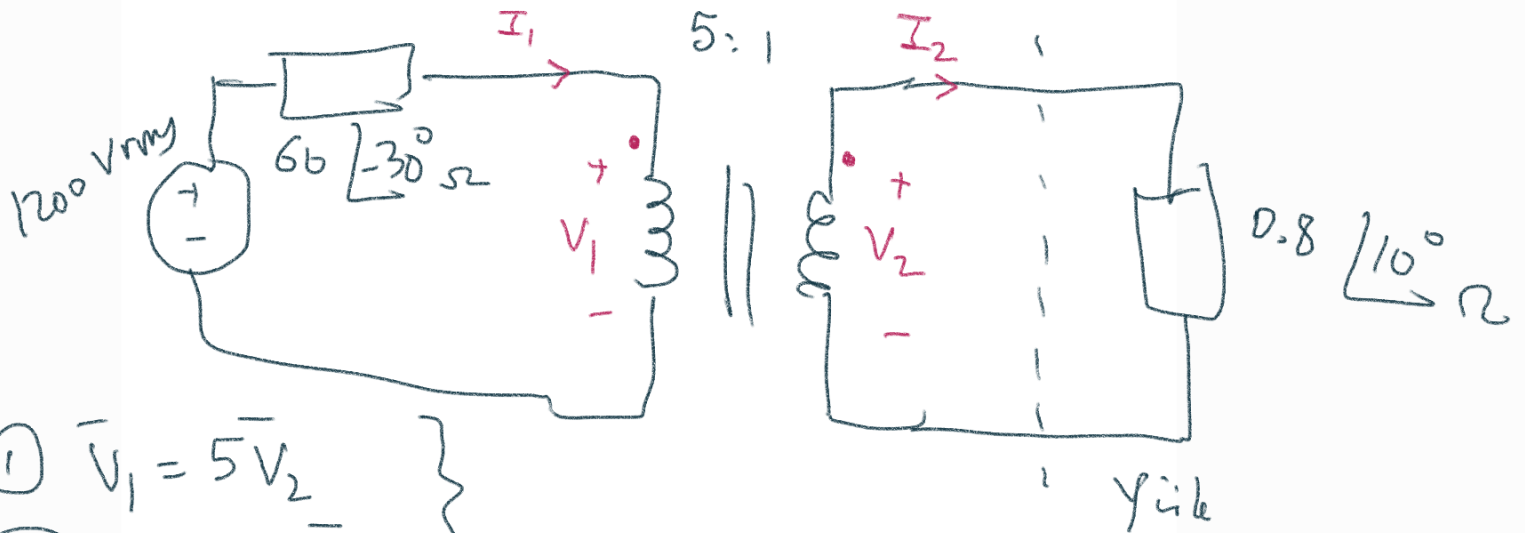13.39 A 1,200/240-V rms transformer has impedance $60 \angle -30^\circ \Omega$ on the high-voltage side. If the transformer is connected to a $0.8 \angle 10^\circ \Omega$ load on the low-voltage side, determine the primary and secondary currents when the transformer is connected to 1,200 V rms. $\bar{I}_1, \bar{I}_2 = ?$



$$\begin{aligned} (1) \quad \bar{V}_1 &= 5 \bar{V}_2 \\ (2) \quad \bar{I}_2 &= 5 \bar{I}_1 \end{aligned}$$

$$(3) \quad 1200 = 60 \angle -30^\circ \bar{I}_1 + \bar{V}_1$$

$$(4) \quad \bar{V}_2 = 0.8 \angle 10^\circ \bar{I}_2$$

$$(4) \quad \frac{\bar{V}_1}{5} = 4 \angle 10^\circ \bar{I}_1 \Rightarrow \bar{V}_1 = 20 \angle 10^\circ \bar{I}_1$$

$$(3) \quad 1200 = 60 \angle -30^\circ \bar{I}_1 + 20 \angle 10^\circ \bar{I}_1$$

$$\bar{I}_1 = \frac{1200}{60 \angle -30^\circ + 20 \angle 10^\circ}$$

$$= \frac{1200}{52 - j30 + 19.7 + j3.5} = \frac{1200}{71.7 - j26.5}$$


$$= \frac{1200}{76.4 \angle -20.3^\circ}$$

$$\bar{I}_2 = 78.53 \angle 20.3^\circ \text{ A}$$

(2)

$$\bar{I}_1 = 15.7 \angle 20.3^\circ \text{ A}$$

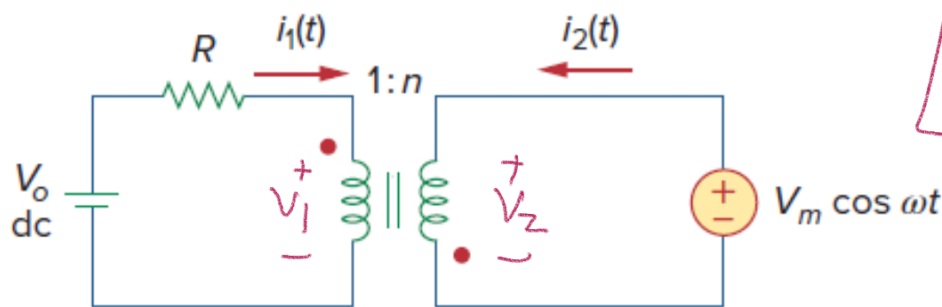*13.44 In the ideal transformer circuit of Fig. 13.109, find $i_1(t)$ and $i_2(t)$.



$$\frac{\bar{I}_1}{\bar{I}_2} = n$$



$$\frac{\bar{V}_2}{\bar{V}_1} = -n$$

Figure 13.109

For Prob. 13.44.


Superposition uygulanabilir

DC
ω = 0

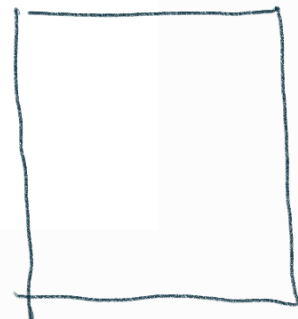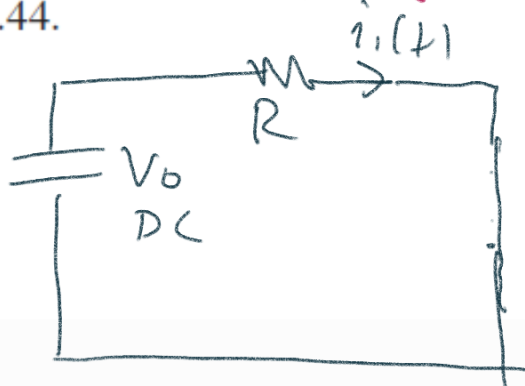

$$i_1(t) = \frac{V_0}{R} \text{ A} \quad i_2(t) = 0$$

AC

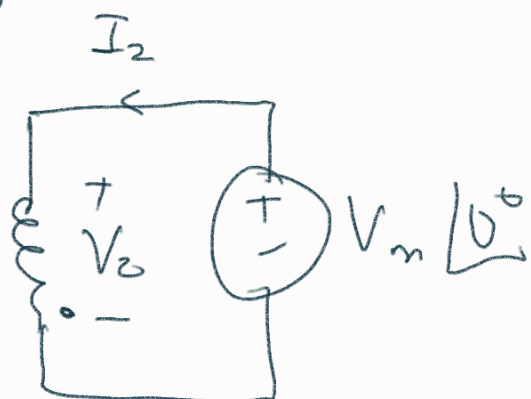

$$\bar{V}_2 = V_m \angle 0^\circ$$

$$\bar{V}_1 = -\frac{V_m}{n} \angle 0^\circ$$

$$(1) \quad R \bar{I}_1 + \bar{V}_1 = 0 \Rightarrow R \bar{I}_1 = \frac{V_m}{n} \angle 0^\circ$$

$$\bar{I}_1 = \frac{V_m}{nR} \angle 0^\circ \xrightarrow{\bar{P}^{-1}} \frac{V_m}{nR} \cos(\omega t)$$

$$\bar{I}_2 = \frac{V_m}{n^2 R} \angle 0^\circ \xrightarrow{\bar{P}^{-1}} \frac{V_m}{n^2 R} \cos(\omega t)$$

TOPLAMDA: $i_1(t) = \frac{V_0}{R} + \frac{V_m}{nR} \cos(\omega t)$

$$i_2(t) = \frac{V_m}{n^2 R} \cos(\omega t)$$

13.50 Calculate the input impedance for the network in Fig. 13.115.

ML

empedans yansıması
sarımlar oranının karesi
ile olur ve
noktalardan
bağımsızdır.


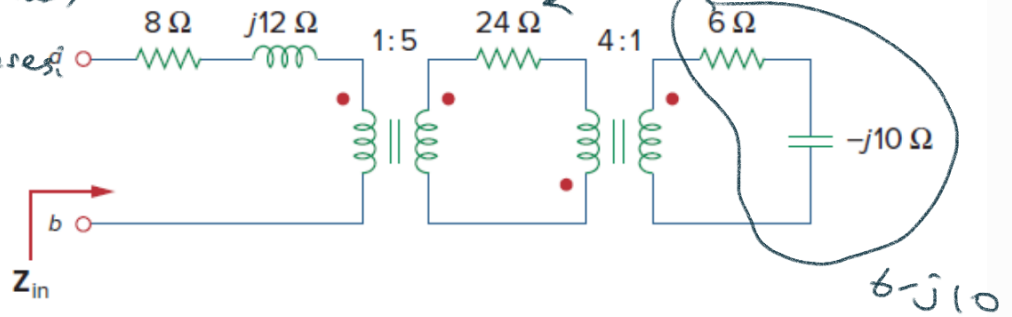


Figure 13.118
For Prob. 13.53.

Figure 13.115
For Prob. 13.50.

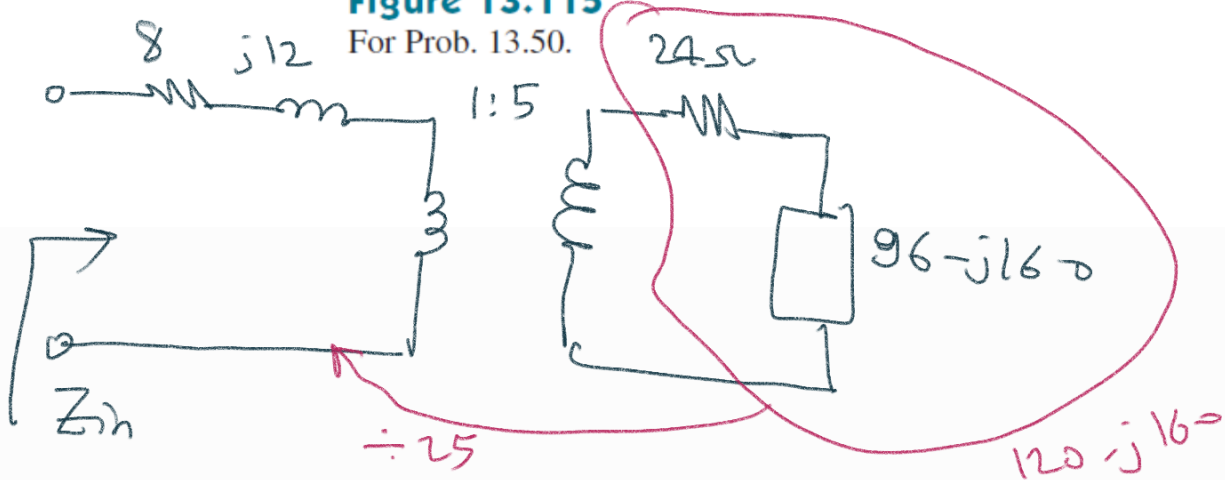

$$Z_{in} = 8 + j12 + \frac{120 - j160}{25}$$

$$= 8 + j12 + 4.8 - j6.4$$

$$Z_{in} = 12.8 + j5.6 \Omega$$

13.51 Use the concept of reflected impedance to find the input impedance and current I_1 in Fig. 13.116.

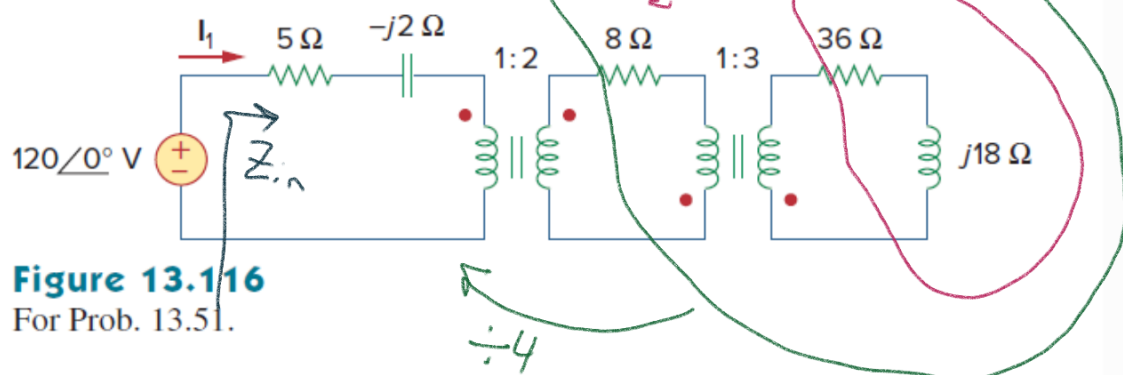


Figure 13.116
For Prob. 13.51.

$$Z_{in} = \left(\frac{36 + j18}{9} + 8 \right) \frac{1}{4} + 5 - j2$$

$$= \left(\frac{4 + j2 + 8}{4} \right) + 5 - j2$$

$$= 3 + j0.5 + 5 - j2 = 8 - j1.5 \Omega //$$

$$\bar{I}_1 = \frac{120}{Z_{in}} = \frac{120}{8 - j1.5} = \frac{120 \angle 0^\circ}{8.14 \angle -10.6^\circ}$$

$$\bar{I}_1 = 14.7 \angle +10.6^\circ \text{ A} //$$

13.58 Determine the average power absorbed by each




resistor in the circuit of Fig. 13.123.

3 gevre var

$$P = \frac{1}{2} \times 20 \times 4.5^2 = 202.5 \text{ W}$$
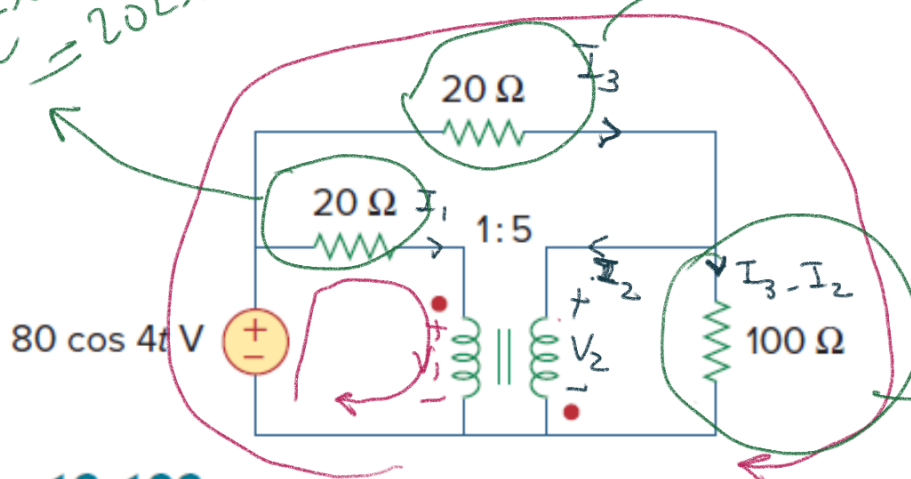
$$P = \frac{1}{2} \times 20 \times 1.6^2 = 25.6 \text{ W}$$



$$P = \frac{1}{2} \times 100 \times 0.475^2 = 11.28 \text{ W}$$

Figure 13.123

For Prob. 13.58.

$$(1) \quad 80 = 20 \bar{I}_1 + \bar{V}_1 \leftarrow$$

$$(2) \quad \bar{V}_2 = 100 (\bar{I}_3 - \bar{I}_2)$$

$$(3) \quad 80 = 20 \bar{I}_3 + 100 (\bar{I}_3 - \bar{I}_2)$$

$$(4) \quad V_2 = -5 V_1$$

$$(5) \quad I_1 = 5 I_2$$

$$(3) \quad 80 = 120 \bar{I}_3 - 100 \bar{I}_2 = 120 \bar{I}_3 - 20 \bar{I}_1$$

$$(3) \quad \bar{I}_3 = \frac{80 + 100 \bar{I}_2}{120}$$

$$(2) \quad \bar{V}_2 = 100 \left(\frac{80 + 100 \bar{I}_2}{120} - \bar{I}_2 \right)$$

$$= \frac{100}{120} (80 + 100 \bar{I}_2 - 120 \bar{I}_2)$$

$$\bar{V}_2 = \frac{100}{120} (80 - 20 \bar{I}_2) = -5 V_1$$

$$V_1 = -\frac{20}{120} (80 - 20 \bar{I}_2)$$

$$V_1 = -\frac{1}{6} (80 - 4 I_1)$$

$$(1) \quad 80 = 20 I_1 - \frac{1}{6} (80 - 4 I_1)$$

$$80 \times \frac{7}{6} = I_1 \left(20 + \frac{4}{6} \right)$$

$$\frac{560}{6} = \frac{124}{6} I_1 \Rightarrow I_1 \approx 4.5 \angle 0^\circ \text{ A}$$

$$\bar{I}_2 \approx 1.125 \angle 0^\circ \text{ A}$$

$$I_3 = \frac{80 + 100I_2}{120} = \frac{80 + 112.5}{120} = 1.6 \angle 0^\circ \text{ A}$$

$$I_3 - I_2 = 0.475 \angle 0^\circ \text{ A}$$

$$I_1 + I_3 = 6.1 \angle 0^\circ$$

13.63 Find the mesh currents in the circuit of Fig. 13.128

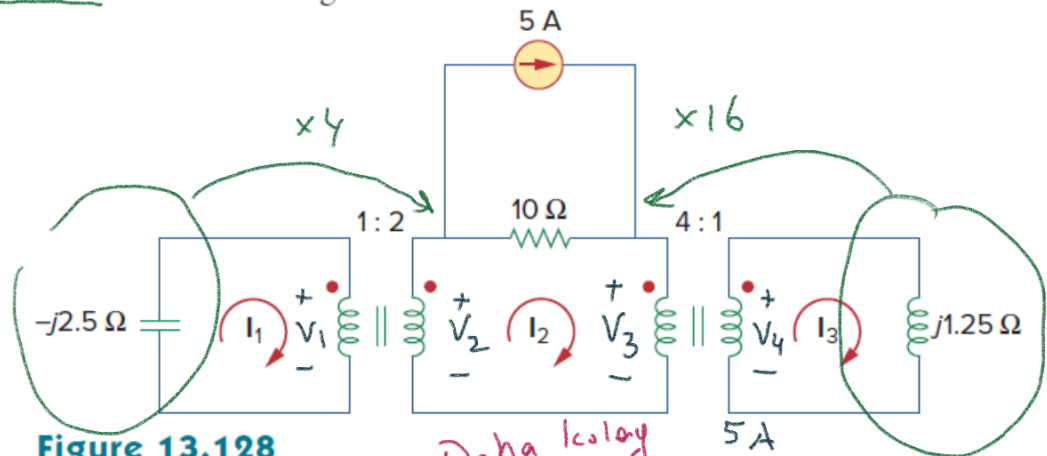


Figure 13.128
For Prob. 13.63.

① $V_1 = j2.5 I_1$

② $-V_2 + 10(I_2 - 5) + V_3 = 0$

③ $V_4 = j1.25 I_3$


④ $V_2 = 2V_1$

⑤ $I_1 = 2I_2$

⑥ $V_3 = 4V_4$

⑦ $I_3 = 4I_2$

*Daha kolay
yol*

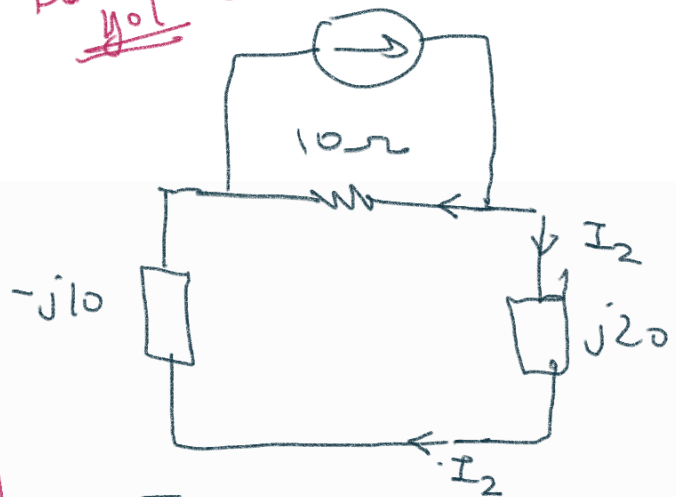

$$\bar{I}_2 = 5 \times \frac{10}{10 + j10}$$

$$= \frac{50}{10\sqrt{2} \angle 45^\circ} = \frac{5}{\sqrt{2}} \angle -45^\circ$$

$$\bar{I}_2 = 2.5 - j2.5 \text{ A}$$

⑤ $\bar{I}_1 = 5 - j5 \text{ A}$

$\bar{I}_3 = 10 - j10 \text{ A}$

13.68 In the ideal autotransformer of Fig. 13.131, calculate



ML $\bar{I}_1$, I_2 , and I_o . Find the average power delivered to the load.

ototrafo: Tek sarım üzerinde birincil ve ikincil sarmilar olusturulur.

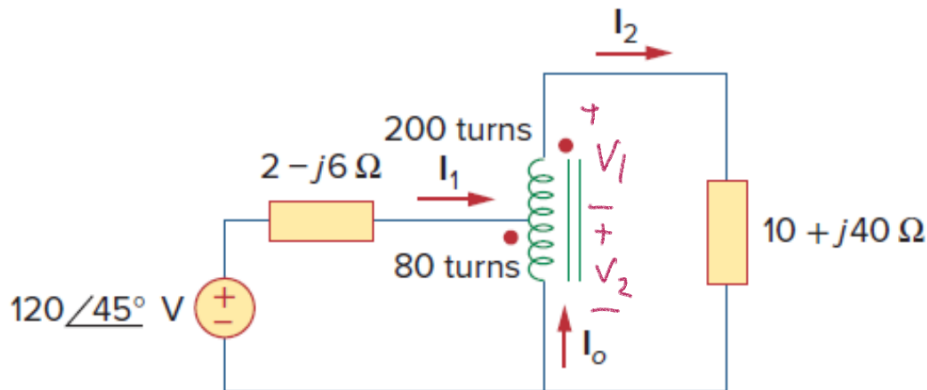


Figure 13.131

For Prob. 13.68.

$$\textcircled{1} \quad 120 \angle 45^\circ = (2-j6) I_1 + V_2$$

$$\textcircled{2} \quad V_1 + V_2 = (10+j40) I_2 \quad \textcircled{3} \Rightarrow 3.5 V_2 = (10+j40) I_2$$

$$\textcircled{3} \quad V_1 = 2.5 V_2$$

$$\textcircled{4} \quad I_o = -2.5 I_2$$

$$\textcircled{5} \quad I_o + I_1 = I_2 \quad \textcircled{4} \Rightarrow \boxed{I_1 = 3.5 I_2}$$

$$\textcircled{1} \quad 120 \angle 45^\circ = (7-j21) \bar{I}_2 + \bar{V}_2$$

$$120 \angle 45^\circ = (7-j21) \bar{I}_2 + \frac{10+j40}{3.5} \bar{I}_2$$

$$120 \angle 45^\circ = \bar{I}_2 \left[\frac{24.5 - j73.5 + 10 + j40}{3.5} \right]$$

$$I_2 = \frac{420 \angle 45^\circ}{34.5 - j33.5} = \frac{420 \angle 45^\circ}{48 \angle 44.2^\circ}$$

$$= 8.75 \angle 0.8^\circ \approx 8.75 \text{ A} //$$

$$I_0 = -2.5 I_2 \simeq -21.9 \text{ A} //$$

$$I_1 = I_2 - I_0 = 30.6 \text{ A} //$$

13.77 The three-phase system of a town distributes power with a line voltage of 13.2 kV. A pole transformer connected to single wire and ground steps down the high-voltage wire to 120 V rms and serves a house as shown in Fig. 13.139.

- (a) Calculate the turns ratio of the pole transformer to get 120 V.
 (b) Determine how much current a 100-W lamp connected to the 120-V hot line draws from the high-voltage line.

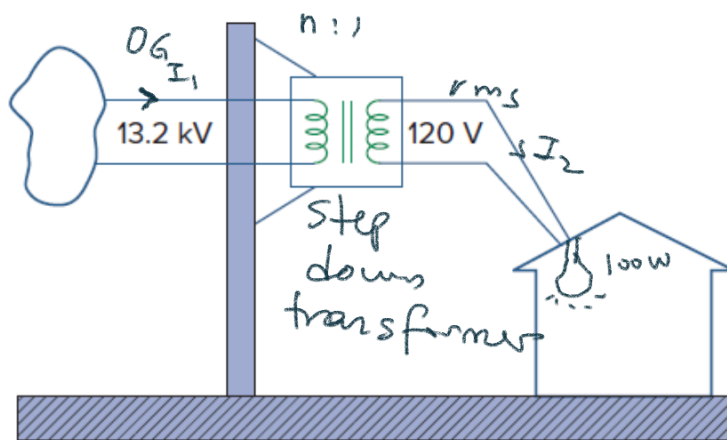


Figure 13.139
For Prob. 13.77.

$$a) \quad n = \frac{13200}{120} = 110$$

$$b) \quad P = 100 \text{ W} = 120 \times I_2$$

$$I_2 = \frac{1}{1.2} \text{ A}$$

$$I_1 = \frac{1}{110} \times \frac{1}{1.2}$$

$$I_1 = \frac{1}{132} \text{ A}$$

13.95 Ten bulbs in parallel are supplied by a 7,200/120-V transformer as shown in Fig. 13.147, where the bulbs are modeled by the 144-Ω resistors. Find:

- the turns ratio n ,
- the current through the primary winding.

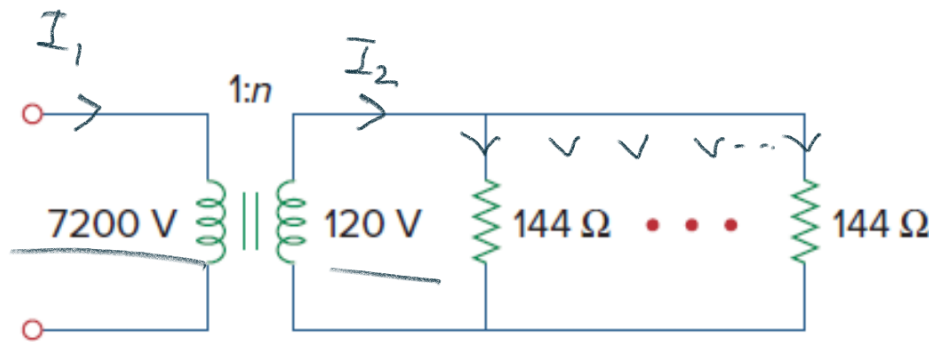


Figure 13.147

For Prob. 13.95.

$$a) n = \frac{1}{60}$$

$$b) I_2 = 10 \times \frac{120}{144} = \frac{10}{1.2} \text{ A} \quad \text{secondary current}$$

$$I_1 = \frac{I_2}{60} = \frac{10}{720} = \frac{1}{72} \text{ A} \quad \text{primary current}$$

13.91 A 25,000/240-V rms distribution transformer has a primary current rating of 75 A.

- Find the transformer kVA rating. $\rightarrow$ gönen güç.
- Calculate the secondary current.


13.92 A 4,800-V rms transmission line feeds a distribution transformer with 1,200 turns on the primary and 28 turns on the secondary. When a 10-Ω load is connected across the secondary, find:

- the secondary voltage,
- the primary and secondary currents,
- the power supplied to the load.

$$13.91) \quad a) S = |V I^*| = |V| |I| = 25000 \times 75 = 1875 \text{ kVA rating}$$

$$b) I_2 = 75 \times \frac{25000}{240} = 7812.5 \text{ A}$$

13.92)

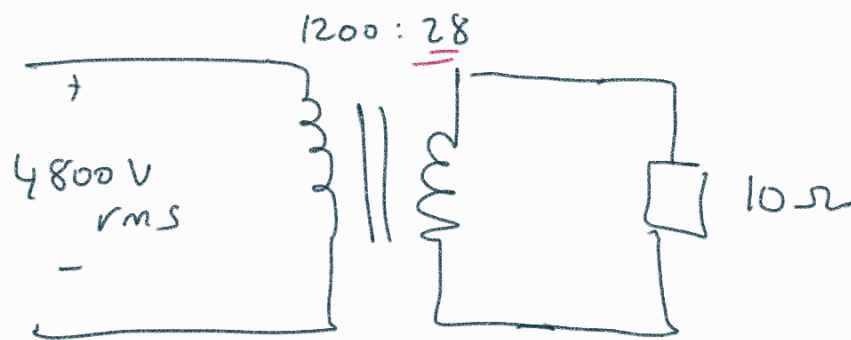

$$a) 4800 \times \frac{28}{1200} = 132 \text{ V}_{rms}$$


$$b) I_2 = \frac{132}{10} = 13.2 \text{ A}$$

$$I_1 = 13.2 \times \frac{28}{1200} = \frac{11 \times 28}{1000} = 0.308 \text{ A}$$

$$c) P_{10\Omega} = \frac{|V_2|^2}{10} = |I_2|^2 10 = 13.2^2 \times 10 = 1.742 \text{ kW}$$

9.74 The value of k in the circuit in Fig. P9.74 is adjusted so that Z_{ab} is purely resistive when $\omega = 4 \text{ krad/s}$. Find Z_{ab} .

Figure P9.74

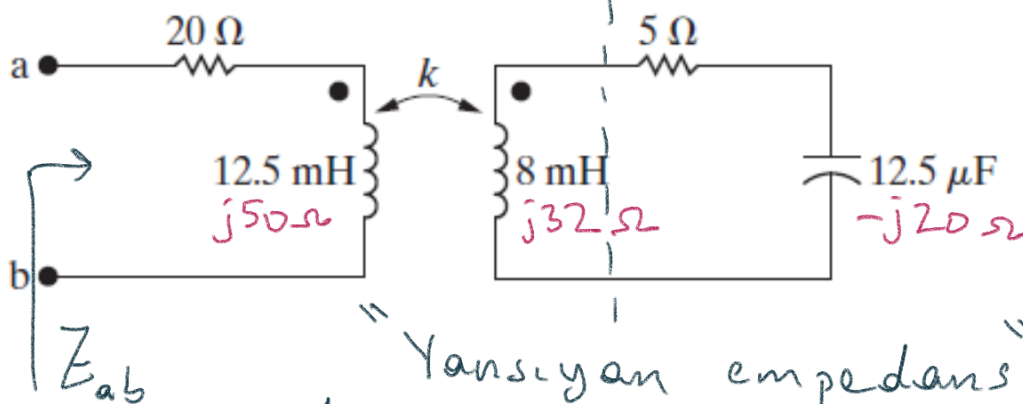

$$j4 \times 10^3 \times 12.5$$

$$\frac{1000}{j50}$$

"Yansıyan empedans"

$$M = k \sqrt{L_1 L_2}$$

manetik bağlaşım katsayısı $0 \leq k \leq 1$

$$M = k \sqrt{12.5 \times 8} \times 10^{-3} = 0.01 k$$

$$\omega M = 4 \times 10^3 \times 10^{-2} k = 40k$$

$$Z_{ab} = 20 + j50 + \frac{(40k)^2}{5 + j12} \Rightarrow \in \mathbb{R} \text{ olması isteniyor.}$$

$$= 20 + j50 + \frac{(40k)^2}{169} (5 - j12)$$

$$\text{Im}\{Z_{ab}\} = 0 = 50 - \frac{(40k)^2}{169} \times 12$$

$$\frac{50 \times 169}{12} = 1600k^2$$


$$k = \sqrt{\frac{50 \times 169}{12 \times 1600}} = 0.66 \text{ olmalıdır.}$$

9.77 The sinusoidal voltage source in the circuit seen in Fig. P9.77 is operating at a frequency of 200 krad/s. The coefficient of coupling is adjusted until the peak amplitude of i_1 is maximum.

PSPICE
MULTISIM

a) What is the value of k ?

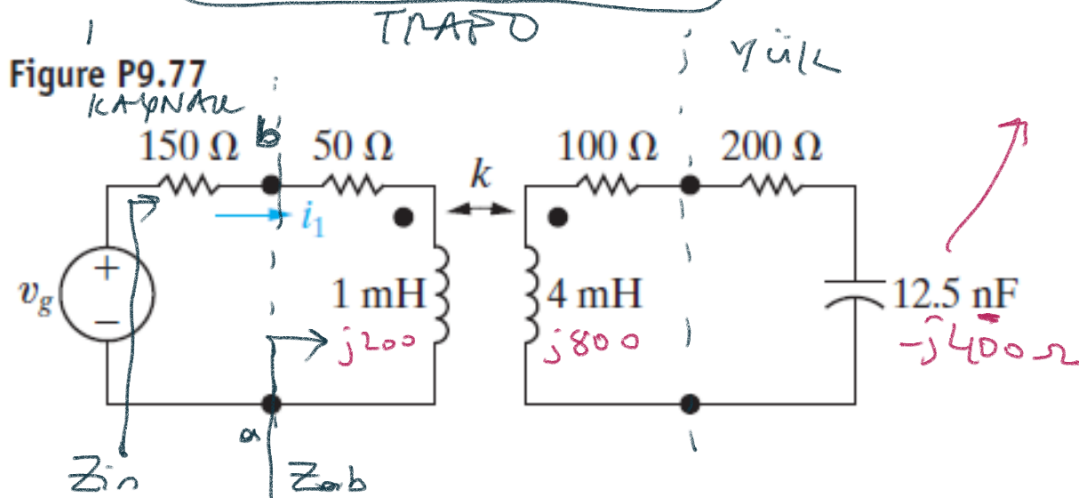b) What is the peak amplitude of i_1 if $v_g = 560 \cos(2 \times 10^5 t) \text{ V}$?



$$\frac{10^9}{j12.5 \times 2 \times 10^5}$$

$$\frac{10^4}{j25} = -j400\Omega$$

$$V_g = I_1 (150 + Z_{ab})$$

$$I_1 = \frac{V_g}{150 + Z_{ab}}$$

$$\max |I_1| \Rightarrow \max \left\{ \frac{|V_g|}{|150 + Z_{ab}|} \right\}$$

$$\Rightarrow \min |150 + Z_{ab}| \Rightarrow \min |Z_{in}|$$

$$\omega M = \omega k \sqrt{L_1 L_2}$$

$$= 2 \times 10^5 k \sqrt{1 \times 4} 10^{-3}$$

$$\omega M = 400k$$

$$Z_{in} = 200 + j200 + \frac{(400k)^2}{300 + j400}$$

$$= 200 + j200 + \frac{1600 k^2 (3 - j4)}{3 + j4 (3 - j4)} \rightarrow 25$$

$$= 200 + j200 + 64k^2 (3 - j4)$$

$$Z_{in} = 200 + 192k^2 + j(200 - 256k^2)$$

$$|Z_{in}| = \sqrt{(200 + 192k^2)^2 + (200 - 256k^2)^2} \Rightarrow \min$$

$$\arg \min_k |Z_{in}| \equiv \arg \min_k |Z_{in}|^2$$

$$\arg \min_k \left\{ (200 + 192k^2)^2 + (200 - 256k^2)^2 \right\}$$

$$\Rightarrow \frac{d}{dk} \left\{ 2(200 + 192k^2)384k - 2(200 - 256k^2)512k \right\} = 0$$

$$(200 + 192k^2)384 = (200 - 256k^2)512$$

$$(192 \times 384 + 256 \times 512) k^2 = 200 \times (512 - 384)$$

$$204224 k^2 = 25600$$

$$k = 0.353 \text{ olmalıdır.}$$

bu durumda

$$k^2 = 0.125$$

$$Z_{in} = 200 + j200 + 64 \times 0.125 \times (3 - j4)$$

$$= 200 + j200 + 24 - j32$$

$$Z_{in} = 224 + j168 \Omega$$

$$I_{in} = I_1 = \frac{560 \angle 0^\circ}{224 + j168} = \frac{70 \angle 0^\circ}{28 + j21} = \frac{10 \angle 0^\circ}{4 + j3}$$

$$I_1 = \frac{10 \angle 0^\circ}{5 \angle 37^\circ} = 2 \angle -37^\circ \text{ A}$$


I_1 tepe değeri 2 A olur.

(Not: soruda $560 \cos(\dots)$ rms deseydi, cevap $2\sqrt{2}$ olurdu)

10.40 The sinusoidal voltage source in the circuit in Fig. P10.40 is developing an rms voltage of 2000 V. The 4 Ω load in the circuit is absorbing four times as much average power as the 25 Ω load. The two loads are matched to the sinusoidal source that has an internal impedance of $500 \angle 0^\circ$ k Ω .

- Specify the numerical values of a_1 and a_2 .
- Calculate the power delivered to the 25 Ω load.
- Calculate the rms value of the voltage across the 4 Ω resistor.

Figure P10.40

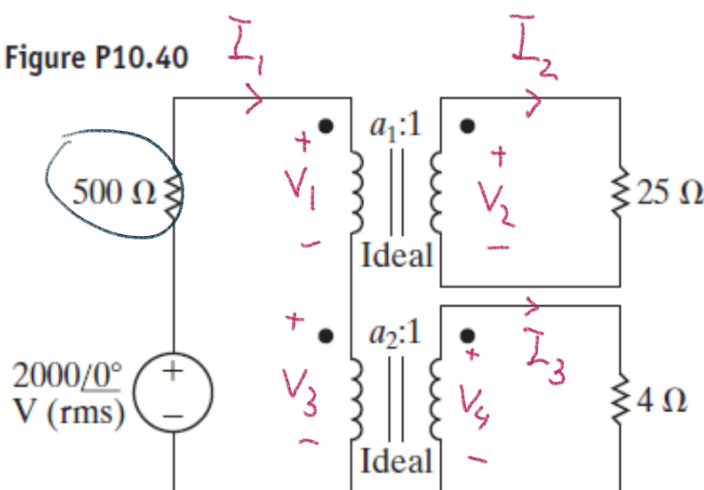

$$\Rightarrow P_{4\Omega} = 4 \times P_{25\Omega}$$

$\Downarrow$

$$4 |I_3|^2 = 4 \times 25 \times |I_2|^2$$

$$4 I_3^2 = 100 I_2^2$$

$$I_3^2 = 25 I_2^2$$

$$I_3 = 5 I_2$$

$$25 a_1^2 = 500$$

$$4 a_2^2 = 500$$

$\Downarrow$

$$a_1 = \sqrt{20}$$

$$a_2 = \sqrt{125}$$

$$2000 = 500 I_1 + V_1 + V_3 \quad (1)$$

$$V_2 = 25 I_2 \quad (2)$$

$$V_4 = 4 I_3 \quad (3)$$

$$V_1 = a_1 V_2 \quad (4)$$

$$V_3 = a_2 V_4$$

$$I_2 = a_1 I_1$$

$$I_3 = a_2 I_1$$


$$I_3 = 5 I_2$$

(5)

(6)

(7)

(8)

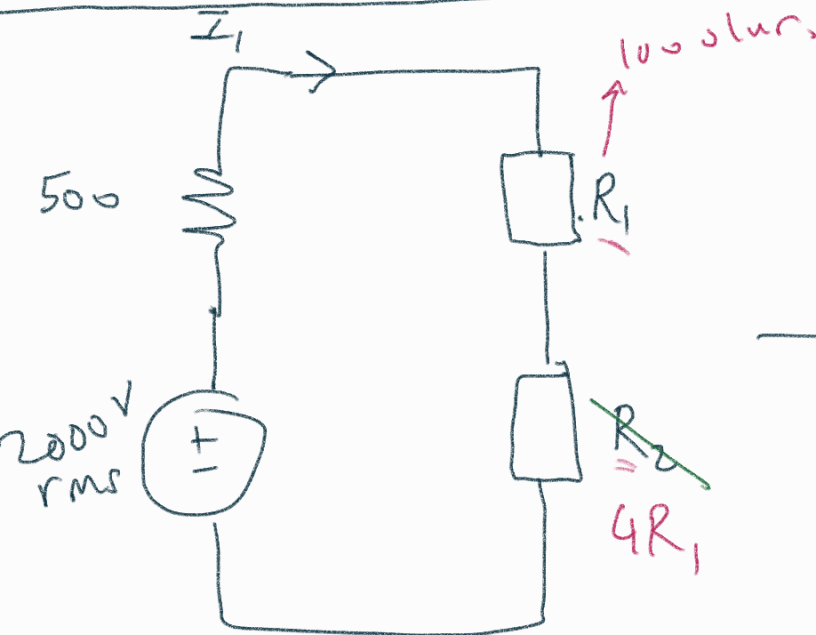

$$4 I_1^2 R_1 = I_1^2 R_2$$

$$4R_1 = R_2$$

$$I_1 = \frac{2000}{500 + 5R_1}$$

$$I_1 = \frac{400}{100 + R_1}$$

$$\max: \left(\frac{400}{100 + R_1} \right)^2 R_1$$

$$\max \left\{ 160000 \cdot \frac{R_1}{(100 + R_1)^2} \right\}$$


$$\frac{(100 + R_1)^2 - 2(100 + R_1) R_1}{(100 + R_1)^4} = 0 \Rightarrow 100 + R_1 = 2R_1$$

$$100 = R_1$$

$$a_1 = 2$$

$$a_2 = 10$$

olmalı

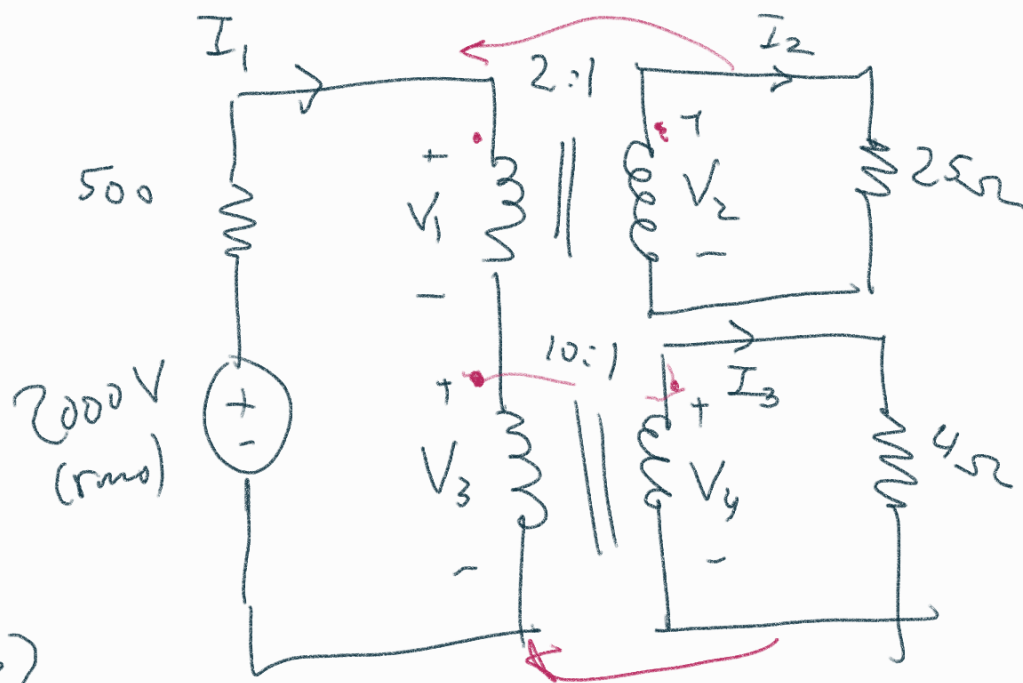

b)

$$I_1 = \frac{2000}{500 + 500} = 2A$$

$$I_2 = 4A \xrightarrow{\text{yonsu}} P_{25\Omega} = 16 \times 25 = 400W$$

$$I_3 = 20A$$

c)



$$V_{4\Omega} = \frac{V_3}{10}$$

$$V_3 = 2A \times 400 = 800 V_{rms}$$

$$V_{4\Omega} = V_4 = 80 V_{rms}$$

- 10.64** a) If N_1 equals 1000 turns, how many turns should be placed on the N_2 winding of the ideal transformer in the circuit seen in Fig. P10.64 so that maximum average power is delivered to the 6800Ω load?
- b) Find the average power delivered to the 6800Ω resistor.
- c) What percentage of the average power delivered by the ideal voltage source is dissipated in the linear transformer?

Figure P10.64

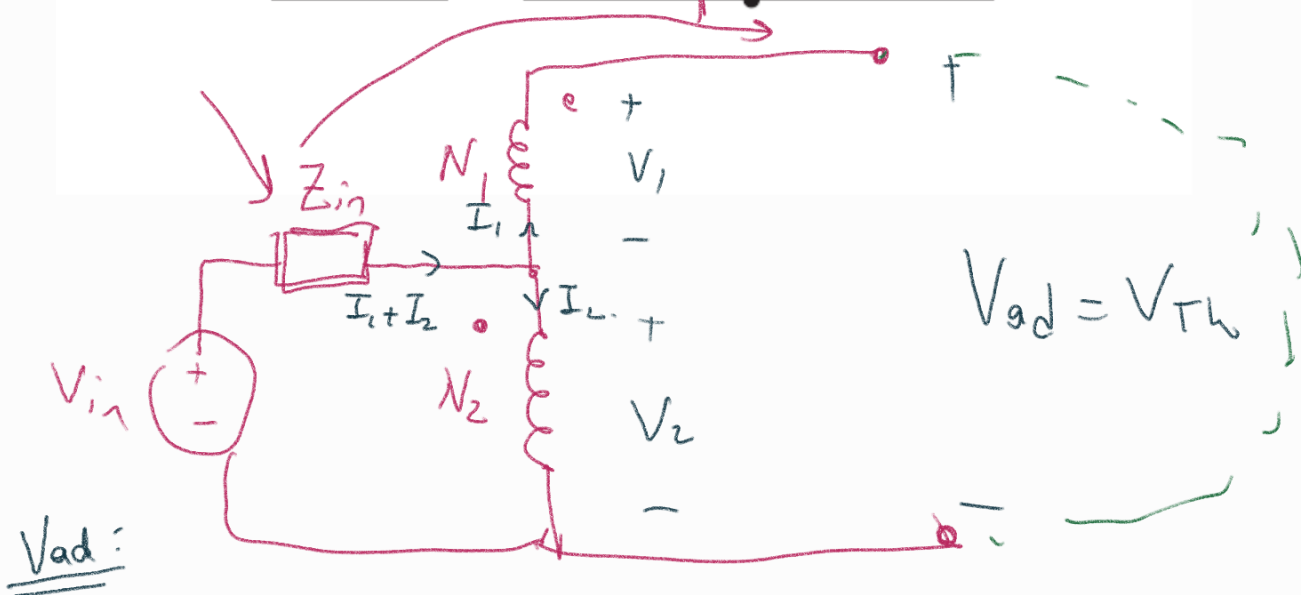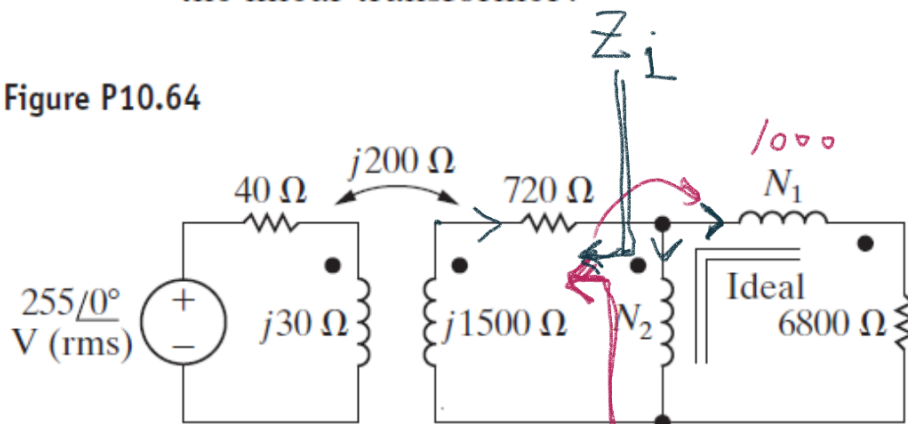

$$I_1 = 0 \Rightarrow I_2 = 0$$

$$I_1 + I_2 = 0 \Rightarrow$$

$$V_2 = V_{in}$$

$$V_1 = \frac{N_1}{N_2} V_{in}$$

$$V_{Th} = V_1 + V_2$$

$$= V_{in} \left(1 + \frac{N_1}{N_2} \right)$$

$$\underline{I_{kd}} \quad V_1 + V_2 = 0$$

$$V_1 = -V_2$$

aynı zamanda

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} \Rightarrow V_1 = V_2 = 0$$

$$\circ \text{ zaman } I_1 + I_2 = \frac{V_{in}}{Z_{in}}$$

$$\frac{I_1}{I_2} = \frac{N_2}{N_1}$$

$$I_2 = I_1 \frac{N_1}{N_2}$$

$$I_1 \left(1 + \frac{N_1}{N_2}\right) = \frac{V_{in}}{Z_{in}} \Rightarrow I_1 = I_{kd} = \frac{V_{in}}{Z_{in} \left(1 + \frac{N_1}{N_2}\right)}$$

$$Z_{Th} = \frac{V_{ad}}{I_{kd}} = \frac{\cancel{V_{in}} \left(1 + \frac{N_1}{N_2}\right)}{\cancel{V_{in}} / Z_{in} \left(1 + \frac{N_1}{N_2}\right)} = \underline{\underline{Z_{in} \left(1 + \frac{N_1}{N_2}\right)^2}}$$

$$Z_1 = \frac{200^2}{40 + j30} + j1500 + 720$$

$$Z_{Th} = \left(1 + \frac{N_1}{N_2}\right)^2 Z_1 \rightarrow \text{burun mutlak değeri 6800 olmalı.}$$

$$Z_1 = \frac{40000}{50 \angle 37^\circ} + j1500 + 720$$

$$= 800 \angle -37^\circ + j1500 + 720$$

$$= 640 - j480 + j1500 + 720$$

$$Z_1 = 1360 + j1020$$


$$\left| (1360 + j1020) \left(1 + \frac{N_1}{N_2}\right)^2 \right| = 6800$$

$$\simeq 1700 \left(1 + \frac{N_1}{N_2}\right)^2 = 6800$$

$$\frac{N_1}{N_2} = \sqrt{\frac{6800}{1700}} - 1 = \sqrt{4} - 1 = 1$$

$$\frac{N_1}{N_2} = 1 \Rightarrow \underline{N_2 = 1000 \text{ olmalidir.}}$$

$$b) Z_{Th} = 4(1360 + j1020)$$

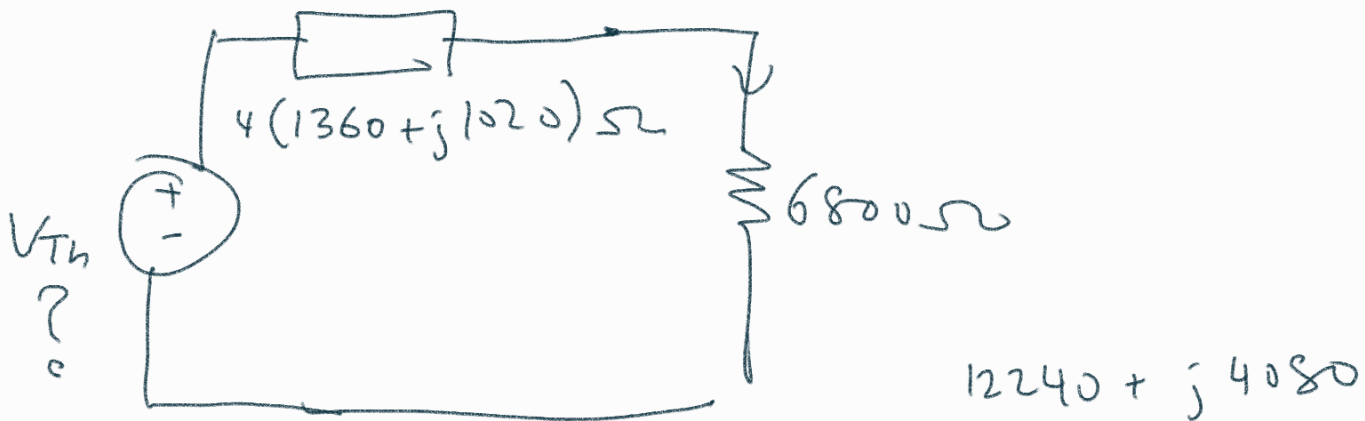

$$\underline{V_{Th} = V_{ad} :}$$

$$I_1 - I_2 = 0 \Rightarrow I_1 + I_2 = I_{720\Omega} = 0$$

$$I_{40\Omega} = \frac{255}{40 + j30} = \frac{255}{50 \angle 37^\circ} = 5.1 \angle -37^\circ \text{ A}$$

$$V_{j1500\Omega} = j\omega M I_{40\Omega}$$

$$= j200 \times I_{40\Omega} = 200 \angle 90^\circ \cdot 5.1 \angle -37^\circ$$

$$V_{j1500\Omega} = 1020 \angle 53^\circ \text{ V}$$

$$V_2 = 1020 \angle 53^\circ \text{ V}$$

$$V_1 = 1020 \angle 53^\circ \text{ V} \quad (N_1 = N_2)$$


$$V_{Th} = V_1 + V_2 = 2040 \angle 53^\circ$$

$$I_{6800\Omega} = \frac{2040 \angle 53^\circ}{12240 + j4080}$$

$$I_{6800} = \frac{204 \angle 53^\circ}{1224 + j408} = \frac{1 \angle 53^\circ}{6 + j2}$$

$$P_{6800} = |I_{6800}|^2 6800$$
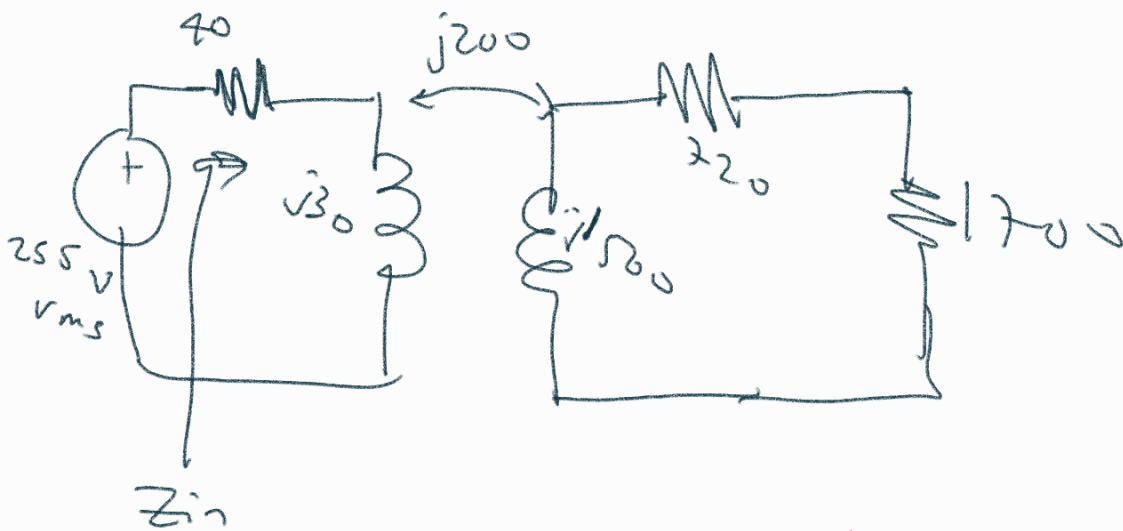
$$= \frac{1}{40} \times 6800 = \underline{\underline{170 \text{ W}}}$$



$$Z_{in} = 40 + j30 + \frac{4000}{2420 + j1500}$$

$$= 40 + j30 + \frac{2000}{(121 + j75)(121 - j75)}$$

$$I_{in} = \frac{255}{Z_{in}} \quad Z_{in} = 40 + j30 + \frac{2000(121 - j75)}{20226}$$

$$Z_{in} = 52.1 - j22.5$$

$$I_{in} = \frac{255}{52.1 - j22.5}$$

$$S_{in} = 255 \times I_{in}^* =$$

$$= \frac{255^2}{52.1 + j22.5}$$

$$\Rightarrow P_{in} = \text{Re}\{S_{in}\}$$

$$= \frac{255^2}{3220} (52.1 - j22.5)$$

$P_{in} = 1052 \text{ Watt}$ $\Rightarrow$ kaynağa üretilen ortalama güç.

güç aktarılan oran $\frac{170}{1052}$

CHAPTER 14: FREKANS TEPKİSİ

$$\frac{V_o}{V_i} = H$$

$$\frac{V_o(j\omega)}{V_i(j\omega)} = H(j\omega) \Rightarrow \text{Transfer fonksiyonu}$$

14.5 For the circuit shown in Fig. 14.72, find

$$H(s) = V_o/I_s$$

$$s = j\omega$$

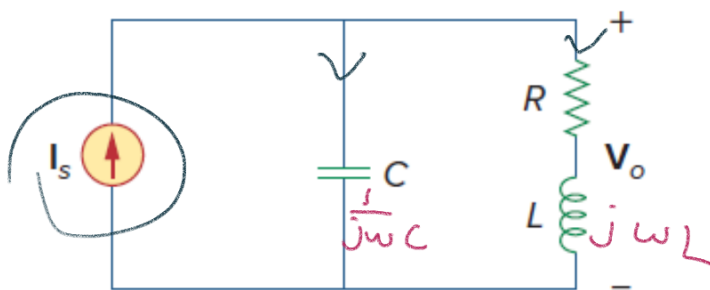


Figure 14.72

For Prob. 14.5.

$$\bar{V}_o = \frac{\bar{I}_s \frac{1}{j\omega C}}{\frac{1}{j\omega C} + R + j\omega L} \times (R + j\omega L)$$

$$H(j\omega) = \frac{\bar{V}_o}{\bar{I}_s} = \frac{R + j\omega L}{j\omega C \left(\frac{1}{j\omega C} + R + j\omega L \right)}$$

$$= \frac{R + j\omega L}{1 + j\omega RC - \omega^2 LC}$$

$$H(j\omega) = \frac{R + j\omega L}{1 - \omega^2 LC + j\omega RC}$$

$$|H(j\omega)| = \frac{\sqrt{R^2 + \omega^2 L^2}}{\sqrt{(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2}}$$

$$\omega \rightarrow 0 : |H(j\omega)| = R$$

$$\omega \rightarrow \infty : |H(j\omega)| \rightarrow 0$$

$$\theta(j\omega) = \angle H(j\omega) = \tan^{-1}\left(\frac{\omega L}{R}\right) - \tan^{-1}\left(\frac{\omega RC}{1 - \omega^2 LC}\right)$$

$$\omega \rightarrow 0 : \theta(j\omega) = 0$$

$$\omega \rightarrow \infty : \theta(j\omega) \rightarrow 90^\circ$$

Section 14.3 The Decibel Scale

14.7 Calculate $|H(\omega)|$ if H_{dB} equals büyüklük.

(a) 0.1 dB

(b) -5 dB

(c) 215 dB

$$\star X_{dB} = 20 \log_{10}(X) \Rightarrow X = 10^{(X_{dB}/20)} \quad \text{büyüklük}$$

$$Y_{dB} = 10 \log_{10}(Y) \quad \text{güs.}$$

a) 0.1 dB $\rightarrow 10^{0.1/20} \approx 1.012$

0 dB $\rightarrow 1$

b) -5 dB $\rightarrow 10^{-5/20} = 0.56$

c) 215 dB $\rightarrow 10^{215/20} = 10^{10.75} = 10 \text{ milyar katları fazla}$

2 $\rightarrow$ 6 dB

16 $\rightarrow$ 24 dB

32 $\rightarrow$ 30 dB

4 $\rightarrow$ 12 dB

20 $\rightarrow$ 26 dB

8 $\rightarrow$ 18 dB

40 $\rightarrow$ 32 dB

10 $\rightarrow$ 20 dB

100 $\rightarrow$ 40 dB

14.14 Draw the Bode plots for

$$H(\omega) = \frac{250(j\omega + 1)}{j\omega(-\omega^2 + 10j\omega + 25)}$$

$$j\omega \rightarrow s \quad H(s) = \frac{250(s+1)}{s(s^2+10s+25)} = \frac{250(s+1)}{s(s+5)^2}$$

Bode Diyagramı

$|H(j\omega)|_{dB}$ büyüklük

$\theta(j\omega)$, derece "ağı"

yatay eksen $\omega \rightarrow$ Logaritmik 1, 10, 100, 1000
dikey $\rightarrow |H|_{dB} \rightarrow dB$

Asimptotik Bode diyagramı, $|j\omega| = \omega$

$$(1+j\omega) = \frac{0dB}{1} \rightarrow \frac{1}{1+j\omega} \rightarrow \frac{1}{P}$$



zero pole

1) Kazanç K

2) Basit bir kutup veya sıfır.

3) Orijinde " " " " $j\omega, \frac{1}{j\omega}$

4) Kuadratik " " " "

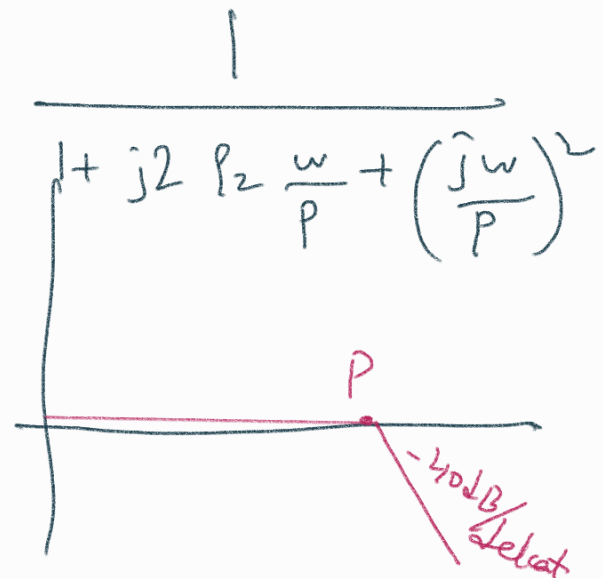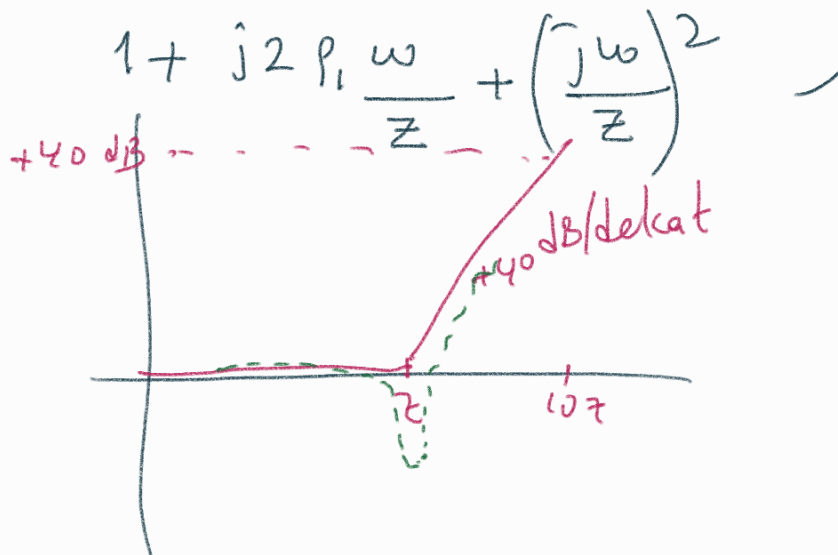


$$H(s) = \frac{250(s+1)}{s(s+5)^2} \Rightarrow H(j\omega) = \frac{250(1+j\omega)}{(j\omega)(j\omega+5)^2}$$

$$= \cancel{250} (1+j\omega) 10$$

$$\cancel{(j\omega)(1+j\frac{\omega}{5})^2 25}$$

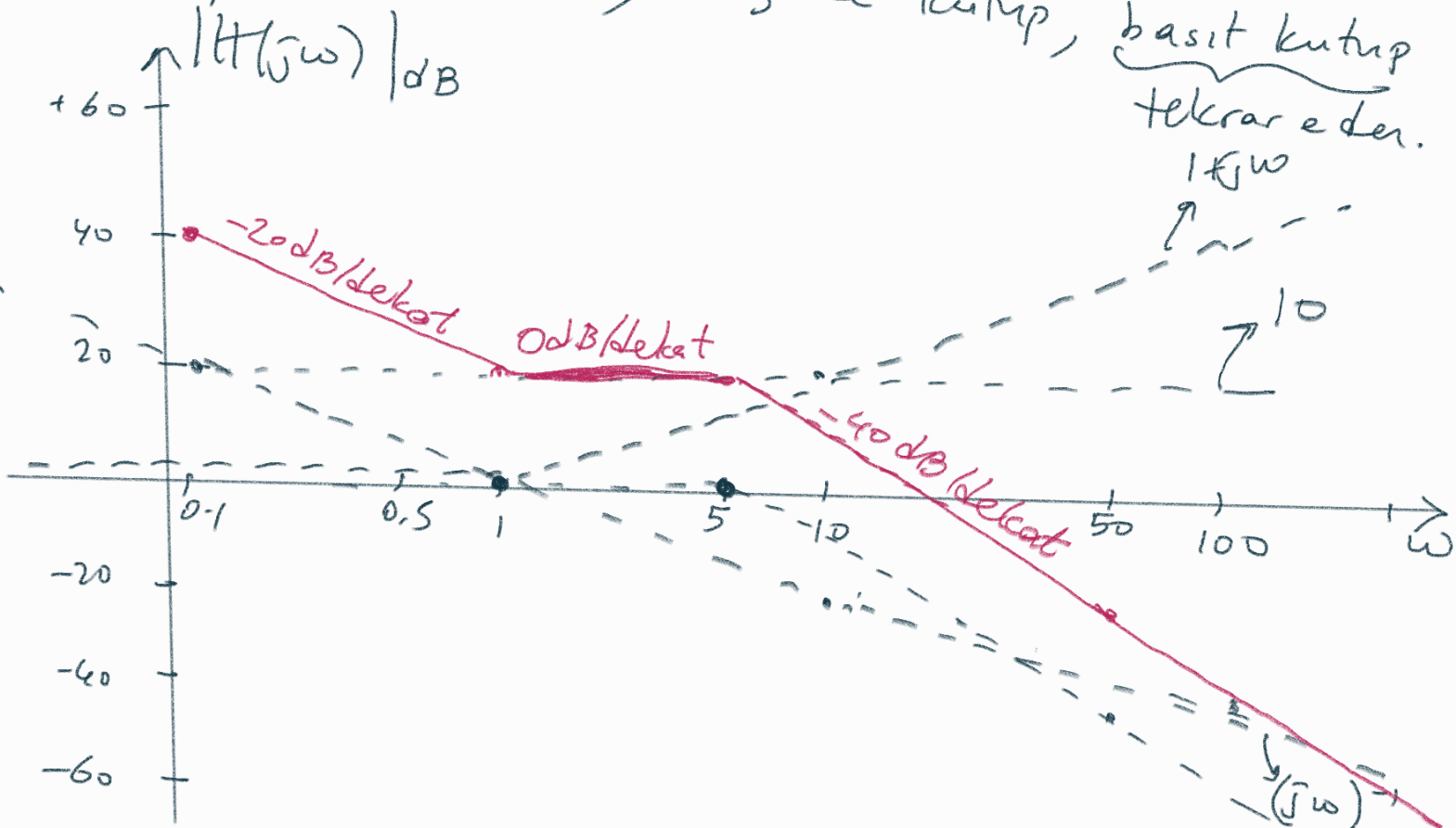Kazanç, basit sıfır, orijinde kutup, basit kutup
tekrar eden.




Önemli noktalar : $\omega = 0.1, 0.5, 1, 5, 10, 50$


$\theta(j\omega)$?

1) Kazanç K : $\theta_K = 0^\circ$

2) Orijinde sıfır $j\omega \rightarrow \theta = 90^\circ$, $\frac{1}{j\omega} = -90^\circ$


3) Basit sıfır : $1 + \frac{j\omega}{5}$

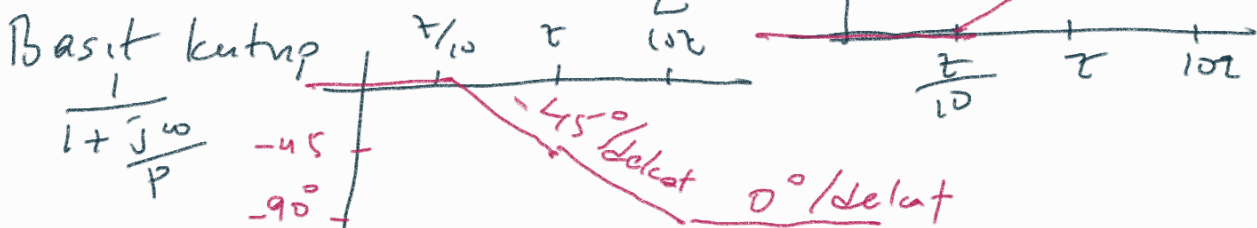

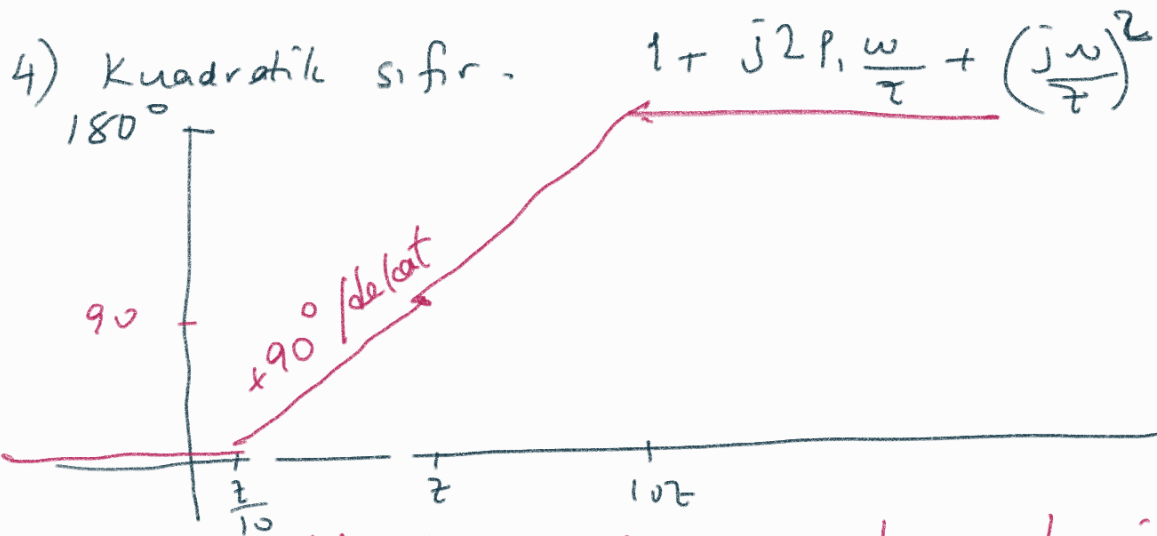

kuadratik kutup bunun tam tersidir
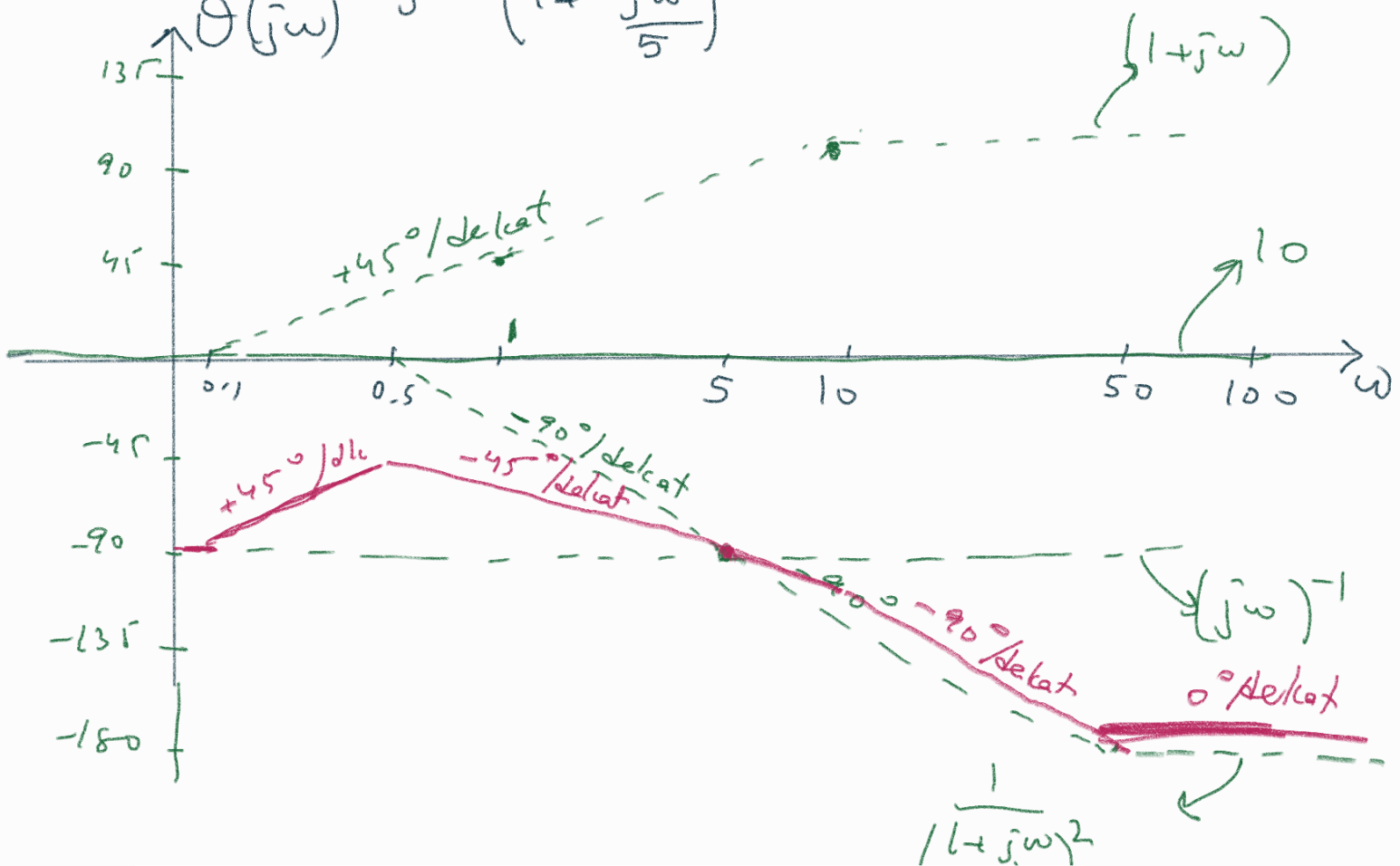
$$H(j\omega) = \frac{10(1+j\omega)}{j\omega \left(1 + \frac{j\omega}{5}\right)^2}$$



14.19 Sketch the asymptotic Bode plots of the magnitude and phase for

$$H(s) = \frac{80s}{(s+10)(s+20)(s+40)}, \quad \underline{s = j\omega}$$

$$H(j\omega) = \frac{80(j\omega)}{(j\omega+10)(j\omega+20)(j\omega+40)}$$



$$H(j\omega) = \frac{80(j\omega)}{100(1 + \frac{j\omega}{10})^2(1 + \frac{j\omega}{20}) \cdot 40(1 + \frac{j\omega}{40})}$$

$$100(1 + \frac{j\omega}{10})^2(1 + \frac{j\omega}{20}) \cdot 40(1 + \frac{j\omega}{40})$$

$|H(j\omega)|$ Bode diagramını, kendiniz yapalım.

uzaktan takip edenler $\rightarrow$ tgrici@gmail.com (11:05)
asimptotik

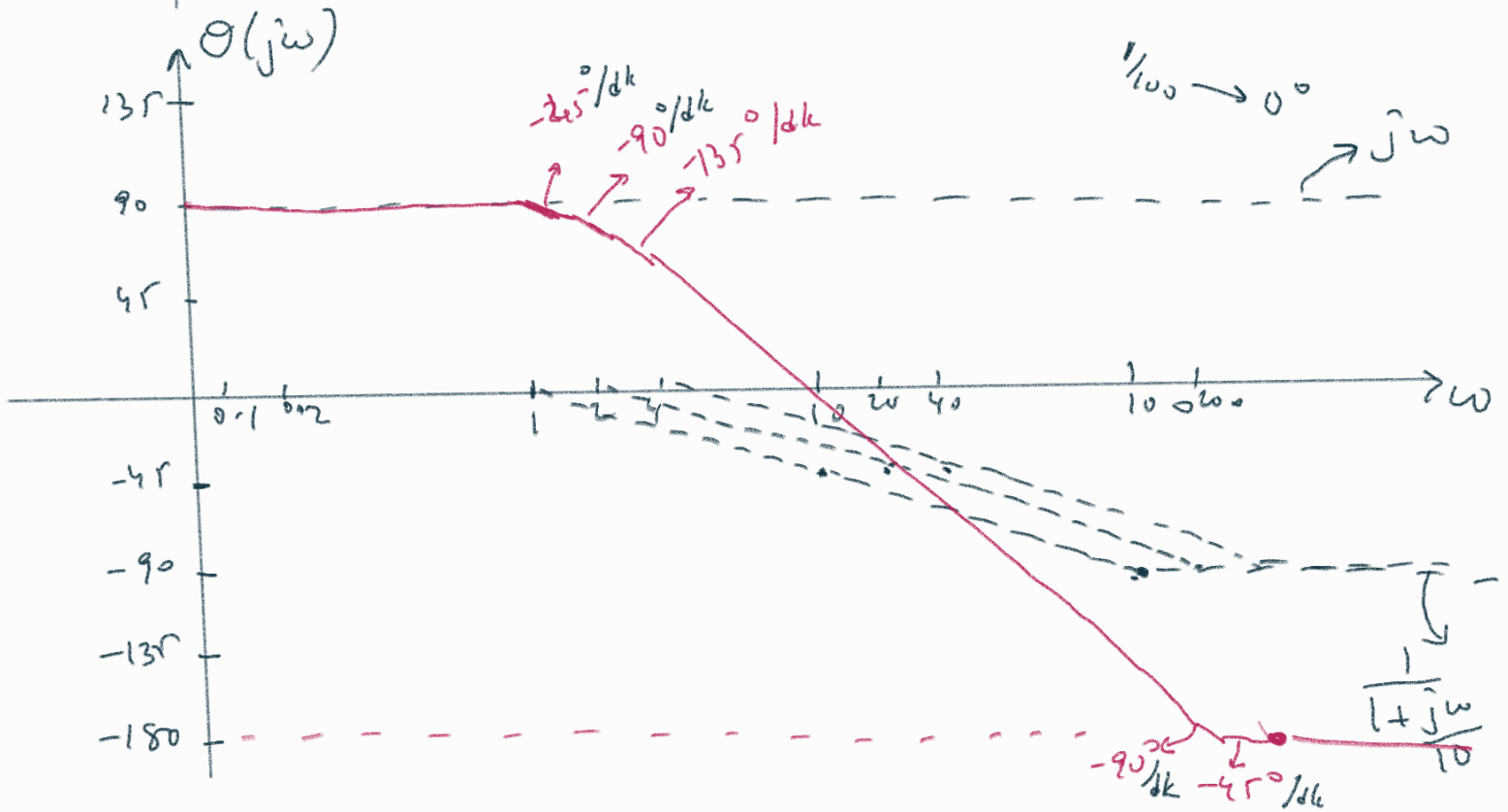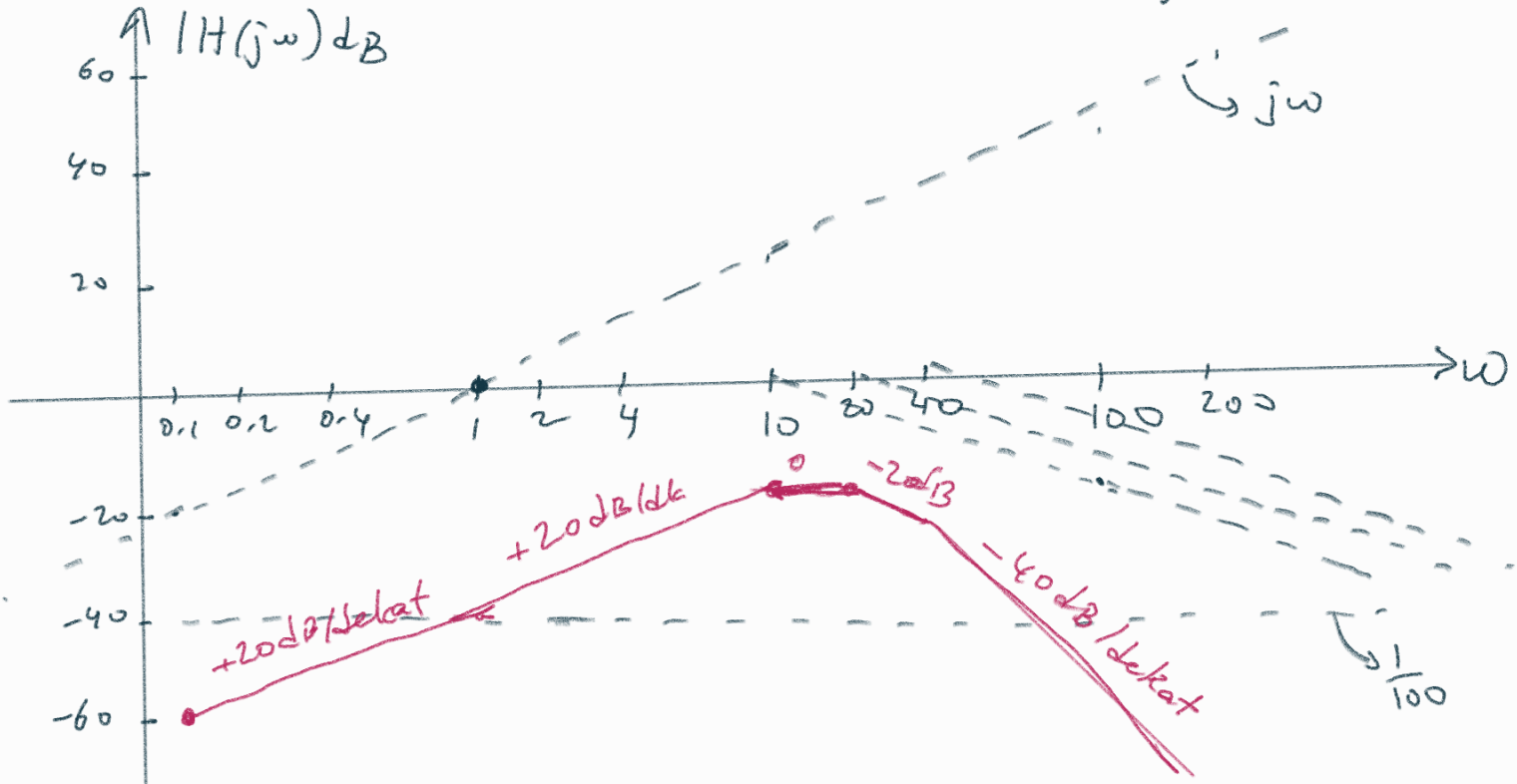Önemli noktalar: 0.1, 1, 2, 4, 10, 20, 40, 100, 200, 400



14.16 Sketch Bode magnitude and phase plots for

$$H(s) = \frac{1.6}{s(s^2 + s + 16)}, \quad s = j\omega$$

(gerçek)
daher fazla şarpanlara
ayırabiliyoruz

kuadratik kutup oldu.


$$\frac{j\omega}{16} = \frac{2j\omega^{1/8}}{4}$$

$$p = 1/8 \text{ ki s\u00fc\u00fch}$$

$$H(j\omega) = \frac{1.6}{(j\omega) \left((j\omega)^2 + j\omega + 16 \right)}$$

$$= \frac{1.6}{10 (j\omega) \left(\left(\frac{j\omega}{4} \right)^2 + \frac{j\omega}{16} + 1 \right)}$$

Önemli noktalar: 0.1, 4, 1, 4, 10, 40

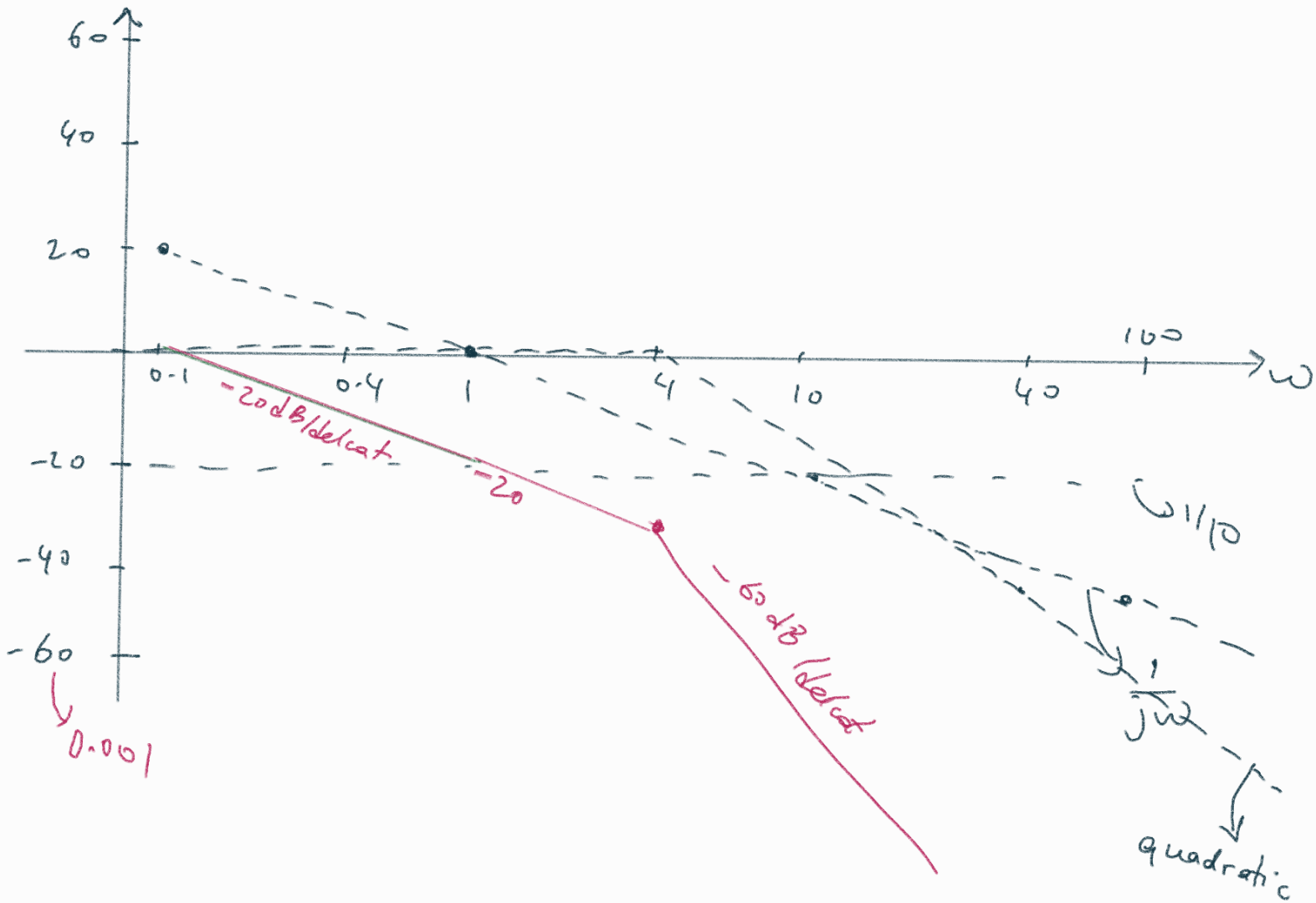

14.21 Sketch the magnitude Bode plot for

$$H(s) = \frac{10s(s+20)}{(s+1)(s^2+60s+400)}, \quad s = j\omega$$

$$\frac{-60 \pm \sqrt{3600 - 1600}}{2}$$

$$\frac{-60 \pm \sqrt{2000}}{2} = -30 \pm 5\sqrt{20} = -30 \pm 10\sqrt{5}$$


$$H(s) = \frac{10s(s+20)}{(s+1)(s+7.6)(s+52.4)}$$


$$H(j\omega) = \frac{10(j\omega)(j\omega+20)}{(1+j\omega)(j\omega+7.6)(j\omega+52.4)}$$

$$= 200(j\omega) \left(1 + \frac{j\omega}{20}\right)$$

$$\frac{(1+j\omega)7.6 \left(1 + \frac{j\omega}{7.6}\right) 52.4 \left(1 + \frac{j\omega}{52.4}\right)}{2(1+j\omega) \left(1 + \frac{j\omega}{7.6}\right) \left(1 + \frac{j\omega}{52.4}\right)}$$
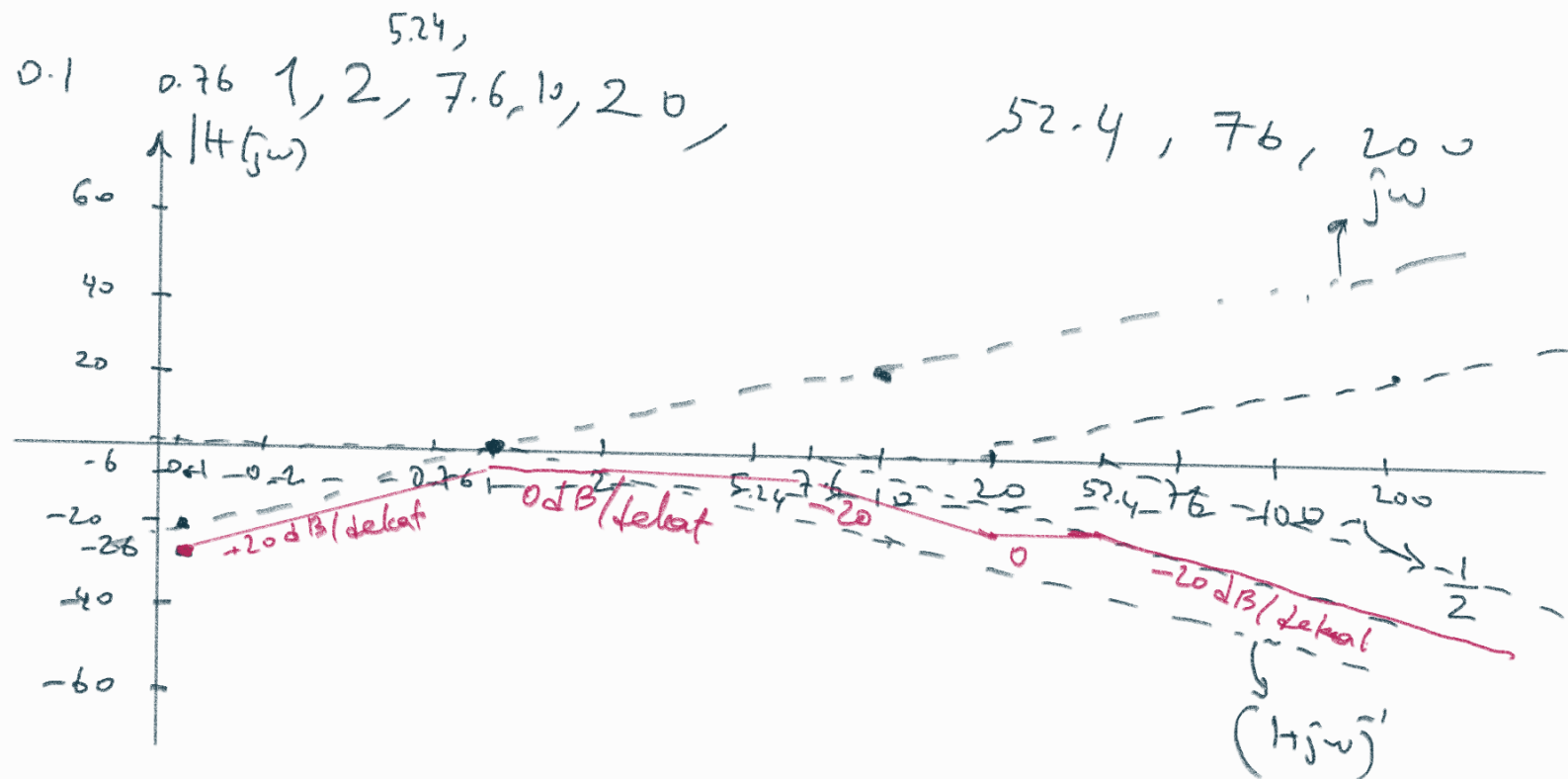
$$= \frac{j\omega \left(1 + \frac{j\omega}{20}\right)}{2}$$



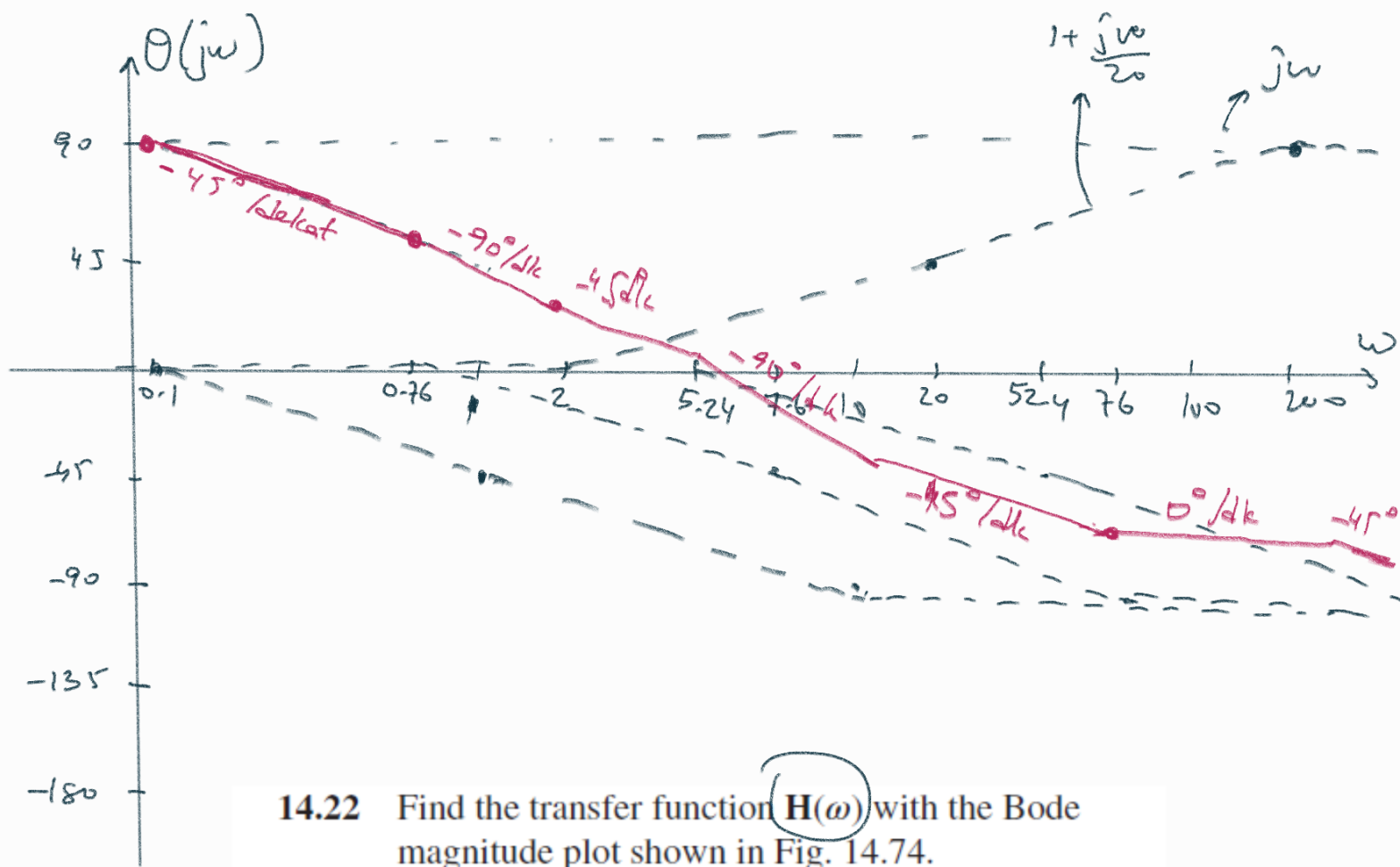

14.22 Find the transfer function $H(\omega)$ with the Bode magnitude plot shown in Fig. 14.74.

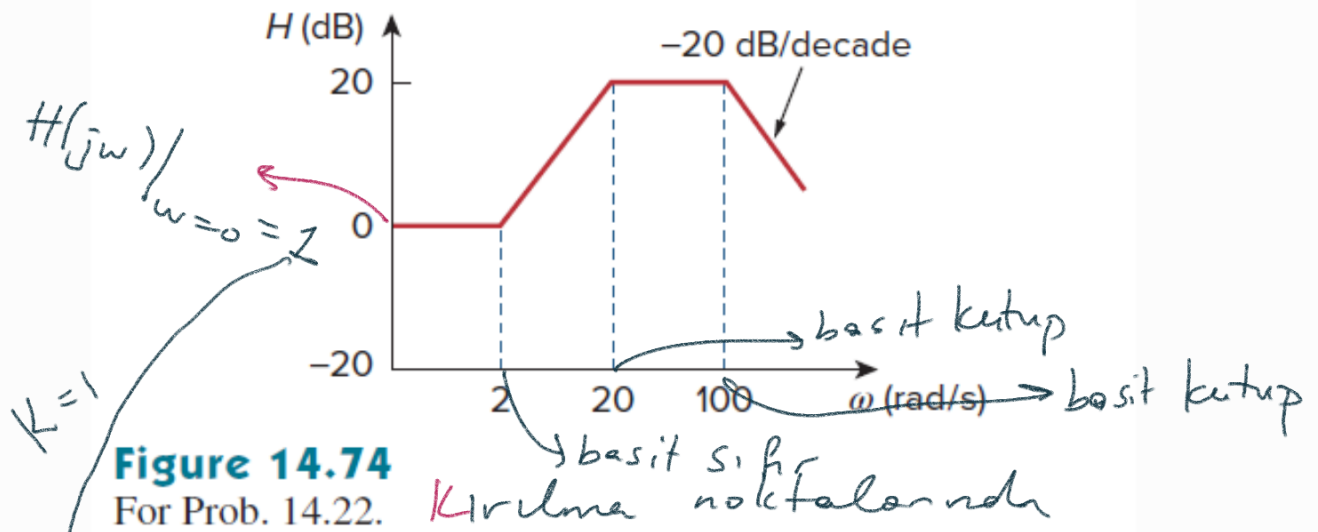


Figure 14.74

For Prob. 14.22.

Kırılma noktalarında

$$H(j\omega) = \frac{K \left(1 + \frac{j\omega}{20}\right)}{\left(1 + \frac{j\omega}{2}\right) \left(1 + \frac{j\omega}{100}\right)}$$

$$\Rightarrow H(s) = \frac{1 + \frac{s}{20}}{\left(1 + \frac{s}{2}\right) \left(1 + \frac{s}{100}\right)}$$

$$= \frac{s + 20}{2 \left(\frac{s+20}{20}\right) \left(\frac{s+100}{100}\right)}$$

$$H(s) = \frac{1000(s+2)}{(s+20)(s+100)}$$

14.50 Determine what type of filter is in Fig. 14.87.

Calculate the corner frequency (f_c)

Yüksek geçiren

$$\frac{V_o}{V_i} = H$$

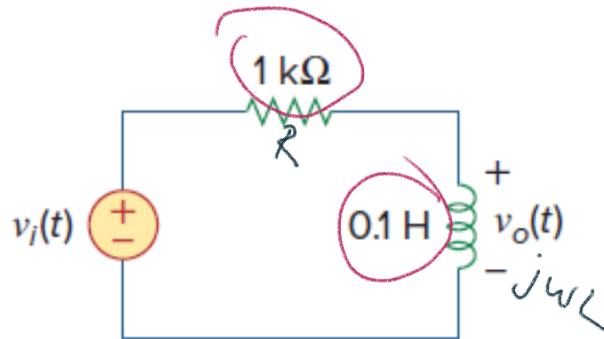


Figure 14.87


For Prob. 14.50.

$$\bar{V}_o = \bar{V}_i \frac{j\omega L}{R + j\omega L}$$

$$H(j\omega) = \frac{\bar{V}_o}{\bar{V}_i} = \frac{j\omega L}{R + j\omega L}$$

$$|H(j\omega)| = \frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}} \Rightarrow H_{\max} = 1$$

$$|H(j\omega_c)| = \frac{H_{\max}}{\sqrt{2}}$$

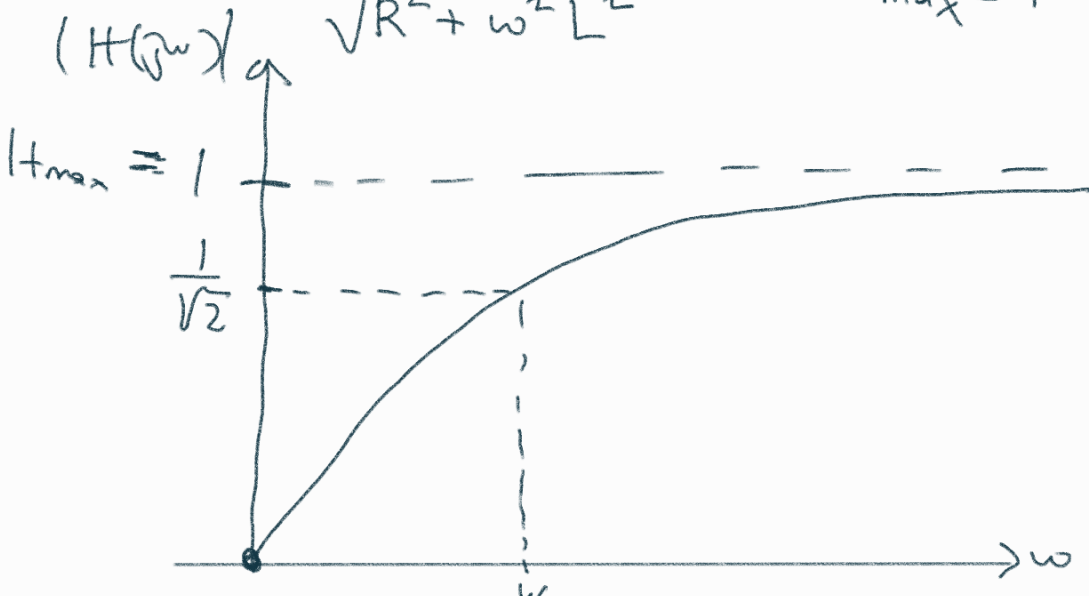

$\omega_c \rightarrow$ Kesim frekansı
Cutoff freq.
Corner freq.

$$\frac{\omega_c L}{\sqrt{R^2 + \omega_c^2 L^2}} = \frac{1}{\sqrt{2}} \Rightarrow 2\omega_c^2 L^2 = R^2 + \omega_c^2 L^2$$

$$\omega_c^2 L^2 = R^2$$

$$\omega_c^2 = \frac{R^2}{L^2} \Rightarrow \omega_c = \frac{R}{L}$$

$$\omega_c = \frac{1000}{0.1} = 10000 \text{ rad/s}$$

$$f_c = \frac{5000}{\pi} \text{ Hz}$$

14.57 Determine the center frequency and bandwidth of the band-pass filters in Fig. 14.88.

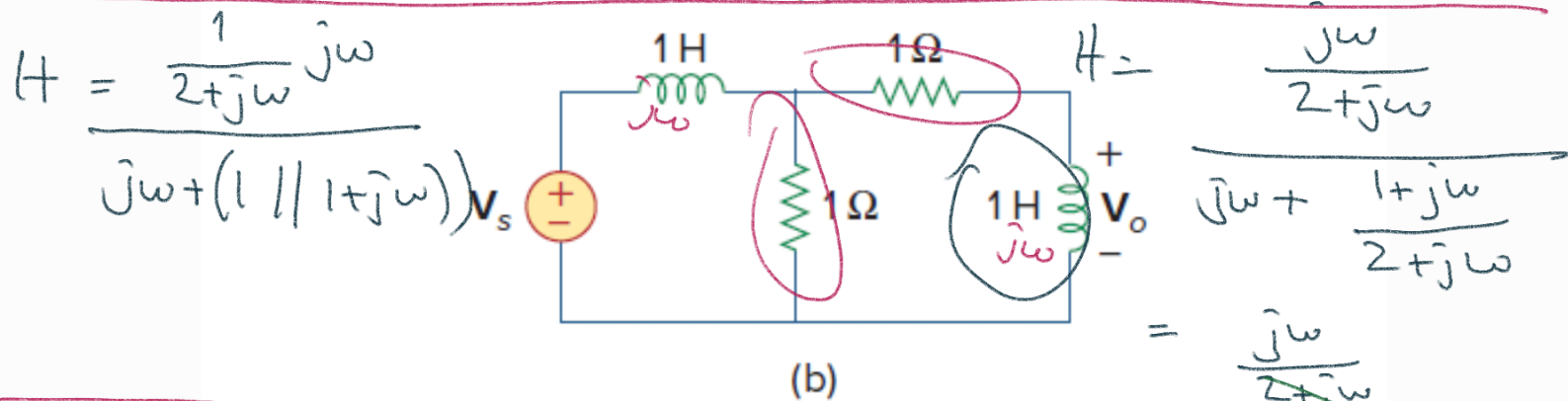
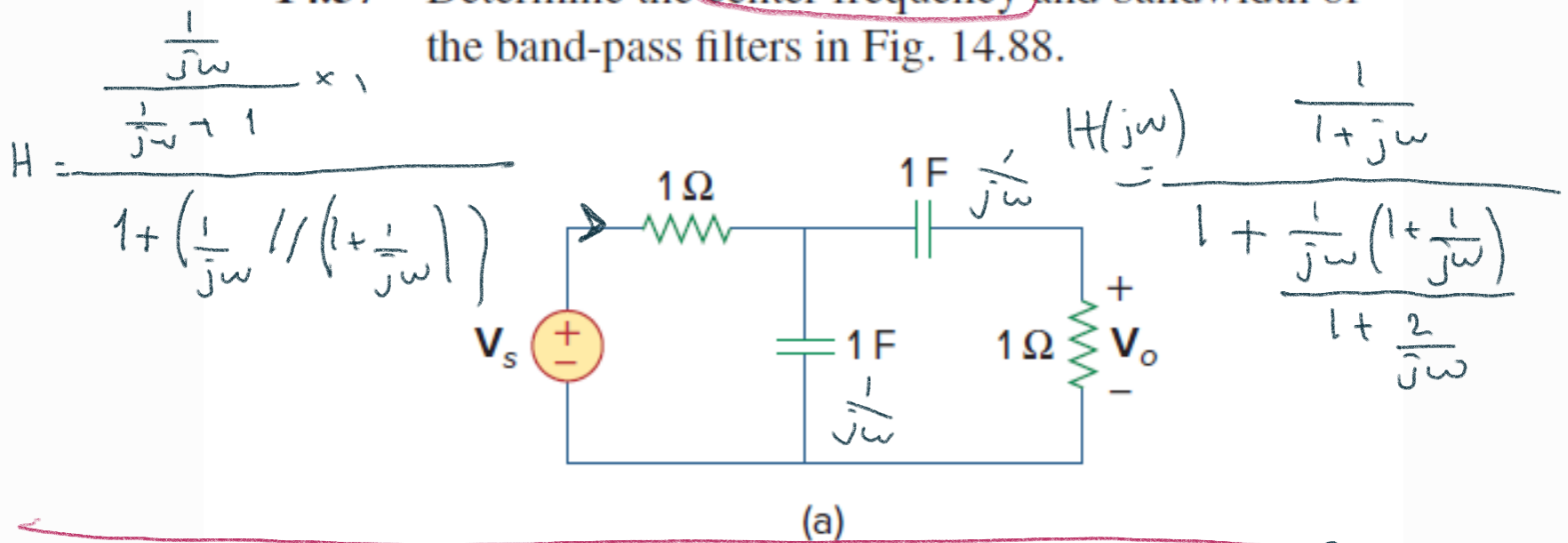


Figure 14.88
For Prob. 14.57.

a)

$$\frac{\frac{1}{1+j\omega}}{1 + \frac{2}{j\omega} + \frac{1}{j\omega} - \frac{1}{\omega^2}} = \frac{\frac{1}{1+j\omega}}{1 + \frac{3}{j\omega} - \frac{1}{\omega^2}}$$

$$= \frac{\frac{1}{1+j\omega}}{1 + \frac{2}{j\omega}}$$

$$H(j\omega) = \frac{1}{1+j\omega} \frac{\frac{2+j\omega}{j\omega}}{1 + \frac{3}{j\omega} - \frac{1}{\omega^2}}$$

$$= \frac{1}{1+j\omega} \frac{2+j\omega}{j\omega \left(1 + \frac{3}{j\omega} + \frac{1}{(j\omega)^2}\right)} = \frac{2+j\omega}{(1+j\omega) \left(j\omega + 3 + \frac{1}{j\omega}\right)}$$

$$H(j\omega) = \frac{(2+j\omega) j\omega}{(1+j\omega)(3j\omega + 3 - \omega^2)}$$

$$|H(j\omega)| = \frac{\sqrt{4+\omega^2} \omega}{\sqrt{1+\omega^2} \sqrt{9\omega^2 + (3-\omega^2)^2}}$$

$$\boxed{\omega_0 = \sqrt{3}}$$

burası, sıfır olduğunda
tepe noktası olur.

$$\begin{aligned} |H|^2 &= \frac{(4+\omega^2)\omega^2}{(1+\omega^2)(9\omega^2 + 9 - 6\omega^2 + \omega^4)} = \frac{\omega^4 + 4\omega^2}{(1+\omega^2)(\omega^4 + 3\omega^2 + 9)} \\ &= \frac{\omega^4 + 4\omega^2}{\omega^4 + 3\omega^2 + 9 + \omega^6 + 3\omega^4 + 9\omega^2} = \frac{\omega^4 + 4\omega^2}{\omega^6 + 4\omega^4 + 12\omega^2 + 9} \\ &= \frac{(4\omega^3 + 8\omega)(\omega^6 + 4\omega^4 + 12\omega^2 + 9)}{(\omega^4 + 4\omega^2)(6\omega^5 + 16\omega^3 + 24\omega)} = 0 \end{aligned}$$

$$\begin{aligned} &4\omega^9 + 16\omega^7 + 48\omega^5 + 36\omega^3 + 8\omega^7 + 32\omega^5 + 96\omega^3 + 72\omega \\ &- 6\omega^9 - 16\omega^7 - 24\omega^5 - 24\omega^7 - 64\omega^5 - 96\omega^3 = 0 \end{aligned}$$

$$-2\omega^9 - 16\omega^7 - 8\omega^5 + 36\omega^3 + 72\omega = 0$$

$$-2\omega^8 - 16\omega^6 - 8\omega^4 + 36\omega^2 + 72 = 0$$

$$-162 - 432 - 72 + 108 + 72 \neq 0$$

$$b) \quad H(j\omega) = \frac{j\omega}{3j\omega + 1 - \omega^2}$$

$$|H(j\omega)| = \frac{\omega}{\sqrt{9\omega^2 + (1 - \omega^2)^2}}$$


$$|H|^2 = \frac{\omega^2}{9\omega^2 + 1 + \omega^4 - 2\omega^2} = \frac{\omega^2}{\omega^4 + 7\omega^2 + 1}$$

$$2\omega(\omega^4 + 7\omega^2 + 1) = \omega^2(4\omega^3 + 14\omega)$$

$$2\omega^4 + 14\omega^2 + 2 = 4\omega^4 + 14\omega^2$$

$$2 = 2\omega^4$$
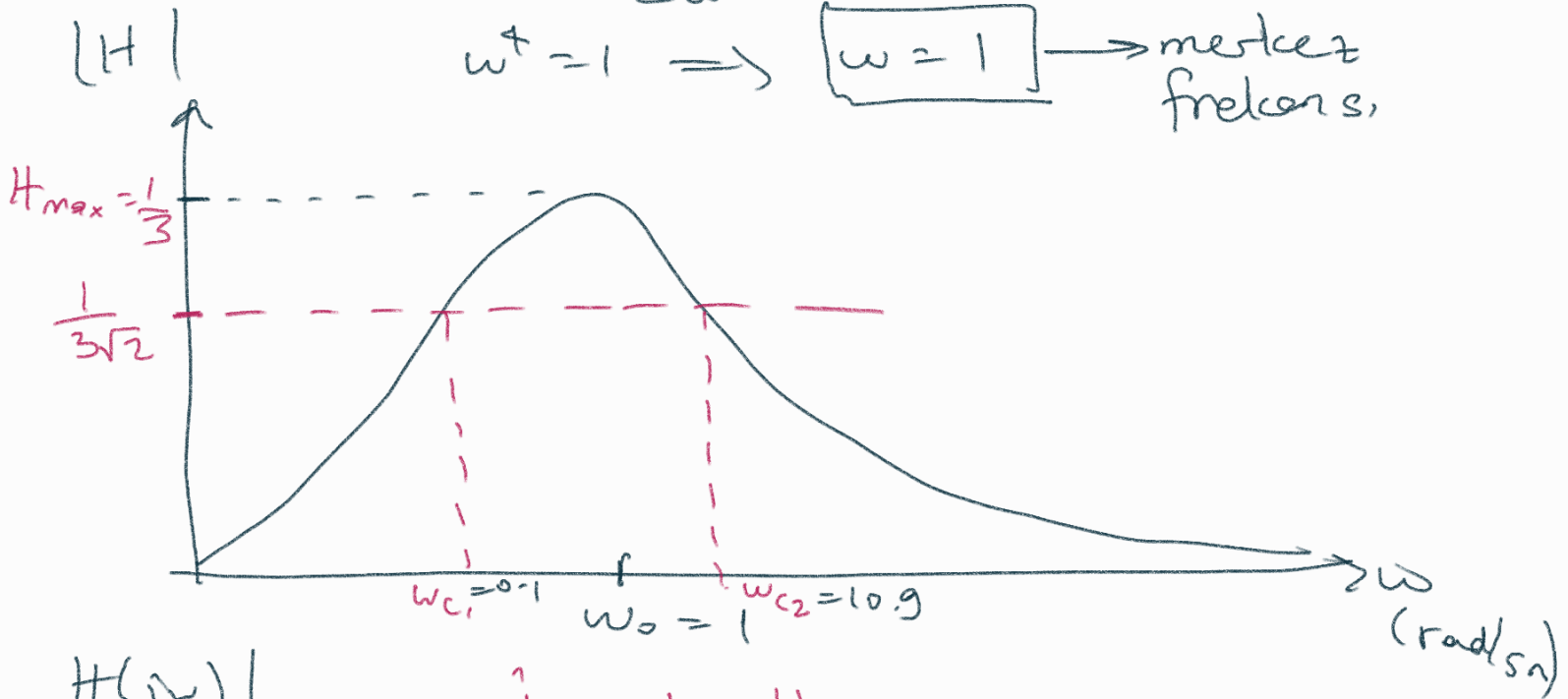
$$\omega^4 = 1 \Rightarrow \boxed{\omega = 1} \rightarrow \text{merkmal frequenz}$$



$$|H(j\omega)|_{\omega=1} = \frac{j}{3j} = \frac{1}{3} = H_{\max}$$

$$\frac{\omega_c}{\sqrt{9\omega_c^2 + (1 - \omega_c^2)^2}} = \frac{1}{3\sqrt{2}}$$


$$18\omega_c^2 = 9\omega_c^2 + 1 - 2\omega_c^2 + \omega_c^4$$

$$\omega_c^4 - 11\omega_c^2 + 1 = 0$$

$$A^2 - 11A + 1 = 0$$

$$\omega_c^2 = A$$

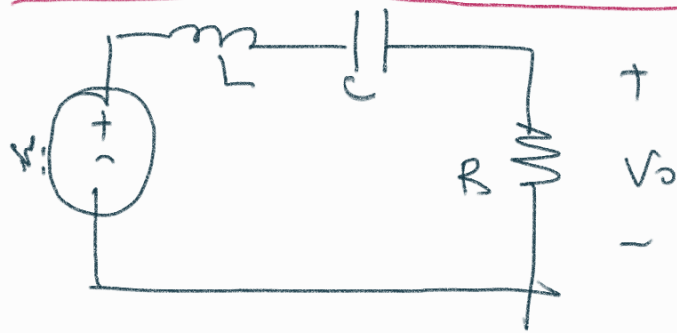
$$\frac{11 \pm \sqrt{117}}{2} = \frac{11 \pm 10.8}{2} = (0.1, 10.9) \text{ rad/s}$$



Bant gesirgen

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$B = \frac{R}{L}$$


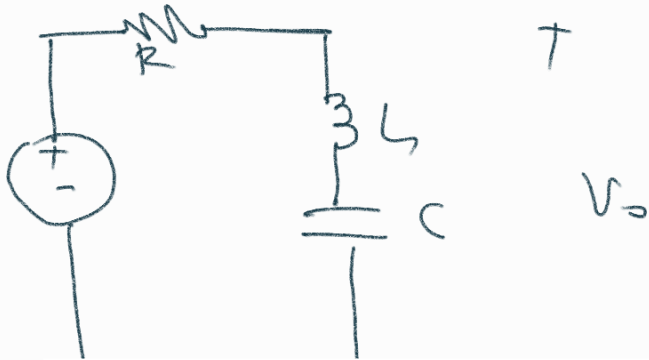


Bant dardner

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$B = R\sqrt{C}$$

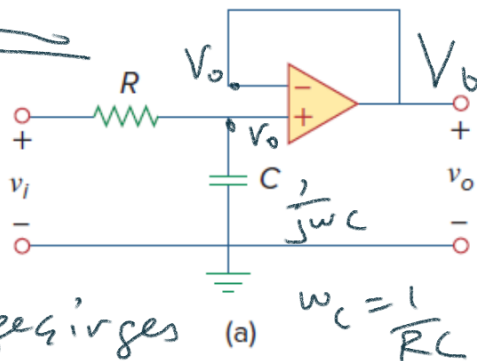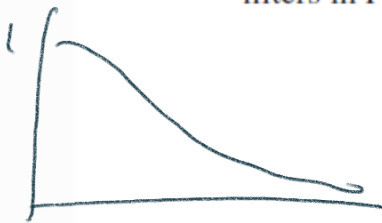14.61 Find the transfer function for each of the active filters in Fig. 14.90.




$$V_o = V_i; \frac{1}{j\omega C}$$

$$H(j\omega) = \frac{1}{1 + j\omega RC}$$

Alsak gesirges

$$\omega_c = \frac{1}{RC}$$

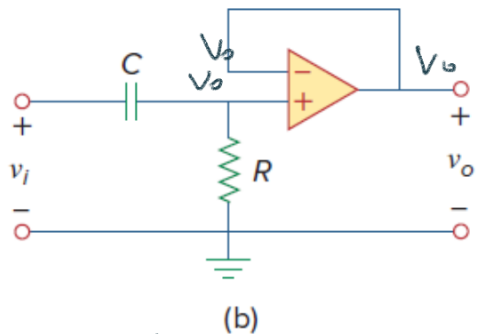


$$V_o = V_i; \frac{R}{R + \frac{1}{j\omega C}}$$

$$H(j\omega) = \frac{j\omega RC}{1 + j\omega RC}$$

Figure 14.90

For Probs. 14.61 and 14.62.

Alsak gesirges

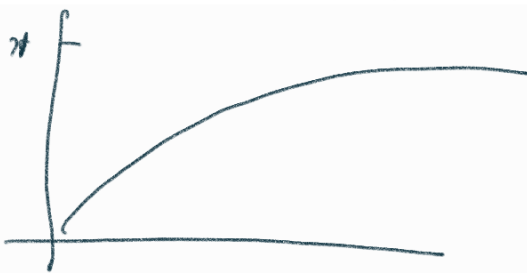

$$\omega_c = \frac{1}{RC}$$

14.69 Design the filter in Fig. 14.94 to meet the following requirements:

- (a) It must attenuate a signal at 2 kHz by 3 dB compared with its value at 10 MHz.
- (b) It must provide a steady-state output of $v_o(t) = 10 \sin(2\pi \times 10^8 t + 180^\circ)$ V for an input $v_s(t) = 4 \sin(2\pi \times 10^8 t)$ V.

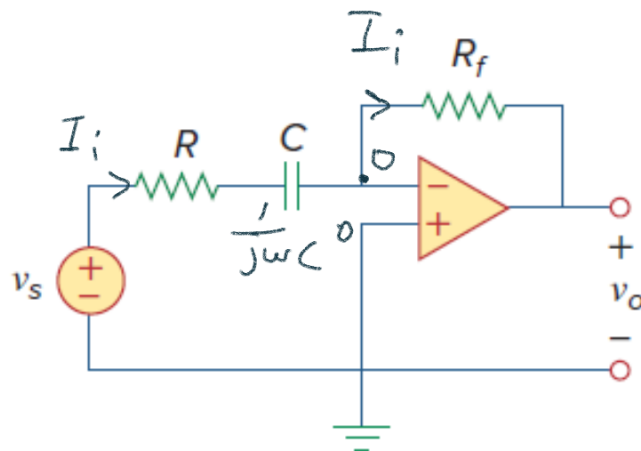



Figure 14.94
For Prob. 14.69.

$$\frac{V_s}{R + \frac{1}{j\omega C}} \Rightarrow V_o = \frac{V_s R_f}{R + \frac{1}{j\omega C}}$$

$$H(j\omega) = \frac{V_o}{V_s} = \frac{-R_f}{R + \frac{1}{j\omega C}} = \frac{-j\omega R_f C}{1 + j\omega R C}$$

$$= -\frac{R_f}{R} \cdot \frac{j\omega R C}{1 + j\omega R C} \Rightarrow H(s) = -\frac{R_f}{R} \frac{s R C}{1 + s R C}$$

$$|H(j\omega)| = \frac{R_f}{R} \frac{\omega R C}{\sqrt{1 + \omega^2 R^2 C^2}} \quad 1 = \omega^2 R^2 C^2 \Rightarrow \omega = \frac{1}{R C}$$

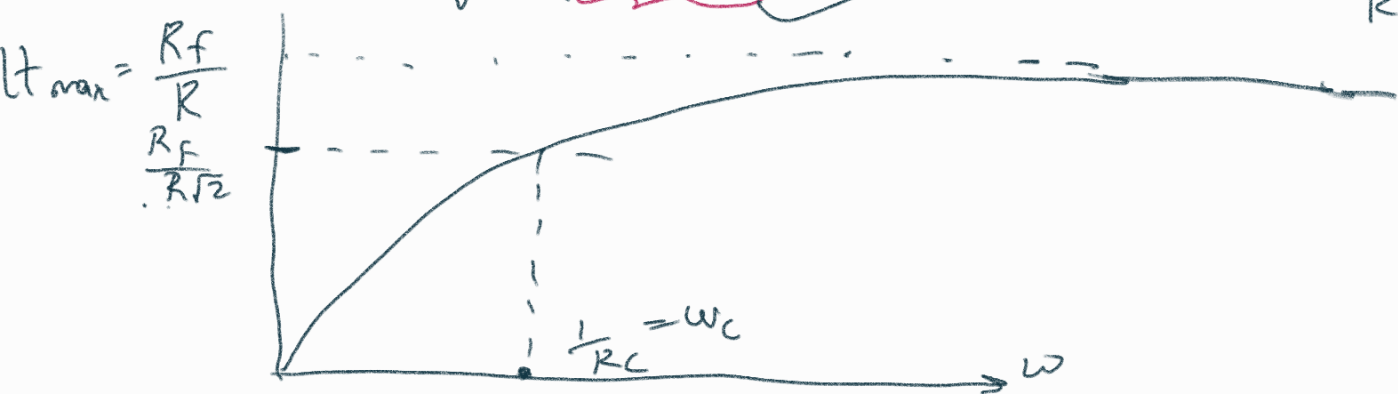

$$a) 2000 \times 2\pi = \frac{1}{RC} \quad \left. \begin{array}{l} \\ b) \frac{R_f}{R} = \frac{10}{4} \end{array} \right\} \text{Tasarla: } R, R_f, C$$

$$R = 1k\Omega \text{ diyoruz}$$

$$\frac{1}{RC} = 4000\pi \text{ a)} \quad C = \frac{1}{4000\pi \times 1000} = \frac{1}{4 \times 10^6 \pi}$$

$$b) \frac{R_f}{R} = \frac{5}{2} \Rightarrow R_f = 2500\Omega = 2.5k\Omega$$

$$C = 100nF = 10^{-7} \text{ olsun}$$

$$\frac{1}{RC} = 4000\pi \Rightarrow R = \frac{1}{10^{-7} \times 4 \times 10^3 \pi} = \frac{10^4}{4\pi} = 796\Omega$$



$$R_f = 2.5 \times 796 \approx 2k\Omega$$

14.18 For the bandpass filter shown in Fig. P14.18, find

PSPICE
MULTISIM

(a) ω_o , (b) f_o , (c) Q , (d) ω_{c1} , (e) f_{c1} , (f) ω_{c2} , (g) f_{c2} , and (h) β .

Figure P14.18

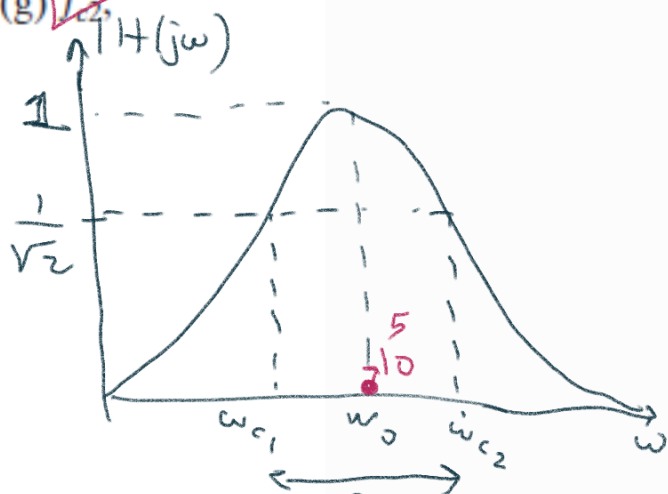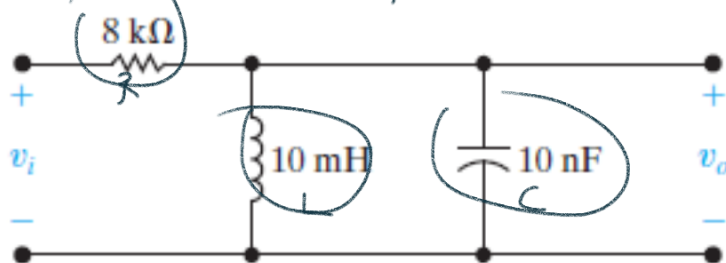

$$\bar{V}_o = \bar{V}_i \frac{(j\omega L \parallel \frac{1}{j\omega C})}{R + (j\omega L \parallel \frac{1}{j\omega C})}$$

$$H(j\omega) = \frac{\bar{V}_o}{\bar{V}_i} =$$

$$H(j\omega) = \frac{\frac{j\omega L}{j\omega C}}{R + \frac{j\omega L}{j\omega C + \frac{1}{j\omega C}}} = \frac{j\omega L}{1 - \omega^2 LC} \cdot \frac{j\omega L}{R + \frac{j\omega L}{1 - \omega^2 LC}}$$

$$H(j\omega) = \frac{j\omega L}{R(1 - \omega^2 LC) + j\omega L}$$

$$|H(j\omega)| = \frac{\omega L}{\sqrt{R^2(1 - \omega^2 LC)^2 + \omega^2 L^2}}$$

$$\boxed{H_{\max} = 1} \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-2} \times 10^{-8}}} = 10^5 \text{ rad/s}$$

a)

$$b) f_0 = \frac{10^5}{2\pi} = 15924 \text{ Hz}$$

c) $\varphi = \frac{\omega_0}{\beta} \Rightarrow |H(j\omega_c)| = \frac{1}{\sqrt{2}}$

$$\frac{\omega_c L}{\sqrt{R^2(1 - \omega_c^2 LC)^2 + \omega_c^2 L^2}} = \frac{1}{\sqrt{2}}$$

~~$$2\omega_c^2 L^2 = R^2(1 - \omega_c^2 LC)^2 + \omega_c^2 L^2$$~~

$$\omega_c^2 L^2 = R^2 - 2R^2 LC \omega_c^2 + R^2 L^2 C^2 \omega_c^4$$

$$R^2 L^2 C^2 \omega_c^4 - \omega_c^2 (L^2 + 2R^2 LC) + R^2 = 0$$

$$0 = \omega_c^4 - \omega_c^2 \left(\frac{1}{R^2 C^2} + \frac{2}{LC} \right) + \frac{1}{L^2 C^2}$$

$$\omega_c^2 = A$$

$$0 = A^2 - A \left(\frac{1}{R^2 C^2} + \frac{2}{LC} \right) + \frac{1}{L^2 C^2}$$

$$A_{1,2} = \frac{\frac{1}{R^2 C^2} + \frac{2}{LC} \mp \sqrt{\left(\frac{1}{R^2 C^2} + \frac{2}{LC} \right)^2 - \frac{4}{L^2 C^2}}}{2}$$

$$\frac{1}{RC} = \frac{1}{8 \times 10^3 \times 10^{-8}} = \frac{10^5}{8}$$

$$\frac{1}{LC} = \frac{1}{10^{-2} \times 10^{-8}} = 10^{10}$$

$$\frac{2}{LC} = 2 \times 10^{10} \quad \frac{4}{L^2 C^2} = 4 \times 10^{20}$$

$$A_{1,2} = \frac{\frac{10^{10}}{64} + 2 \times 10^{10} \mp \sqrt{\left(2 + \frac{1}{64} \right)^2 10^{20} - 4 \times 10^{20}}}{2}$$

$$= \frac{2.015625 \times 10^{10} \mp 0.25 \times 10^{10}}{2}$$

$$A_{1,2} = (0.883 \times 10^{10}, 1.133 \times 10^{10})$$

$$\omega_{c1,2} = 0.94 \times 10^5, 1.064 \times 10^5$$

$$\omega_{c2} - \omega_{c1} = 0.124 \times 10^5 = 12400 \text{ rad/s} = \beta$$

$$d) \beta = \frac{12400}{2\pi} = 1974 \text{ Hz}$$


$$\left(\frac{1}{RC} \right) = \frac{1}{8 \times 10^3 \times 10^{-8}} = \frac{10^5}{8} = 12500 \text{ rad/s}$$

14.27 Use a 5 nF capacitor to design a series *RLC* band-pass filter, as shown at the top of Fig. 14.27. The center frequency of the filter is 8 kHz, and the quality factor is 2.

DESIGN
PROBLEM
PSPICE
MULTISIM

- Specify the values of R and L .
- What is the lower cutoff frequency in kilohertz?
- What is the upper cutoff frequency in kilohertz?
- What is the bandwidth of the filter in kilohertz?

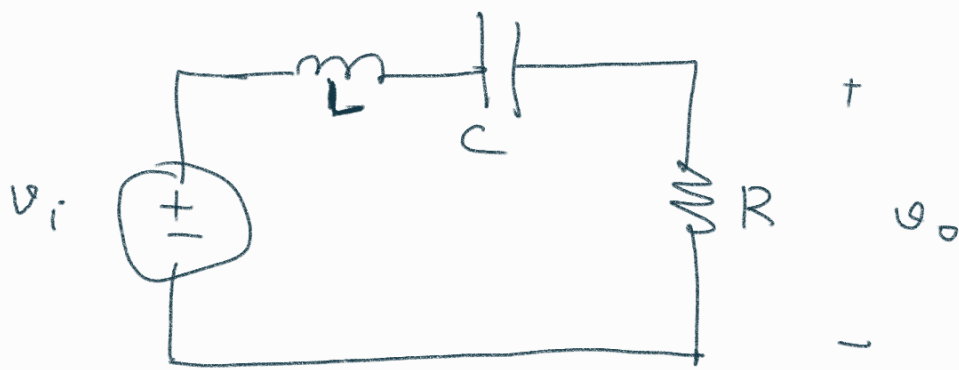14.28 Design a series *RLC* bandpass filter using only



$$H(j\omega) = \frac{R}{R + j\omega L + \frac{1}{j\omega C}} = \frac{R j\omega C}{j\omega RC + 1 - \omega^2 LC}$$

$$= \frac{j\omega RC}{j\omega RC + 1 - \omega^2 LC} \Rightarrow |H| = \frac{\omega RC}{\sqrt{\omega^2 R^2 C^2 + (1 - \omega^2 LC)^2}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \text{ 'de } |H| = 1 = H_{\max}$$

$$\omega_0 = 8000 \times 2\pi = 16000\pi$$

$$Q = \frac{\omega_0}{B} = \frac{16000\pi}{B} = 2 \Rightarrow B_c = 8000\pi \text{ olmalı.}$$

$$\frac{1}{\sqrt{2}} = \frac{\omega_c RC}{\sqrt{\omega_c^2 R^2 C^2 + (1 - \omega_c^2 LC)^2}}$$

$$\cancel{\omega_c^2 R^2 C^2} + 1 - 2\omega_c^2 LC + \cancel{\omega_c^4 L^2 C^2} = \cancel{2\omega_c^2 R^2 C^2}$$

$$\omega_c^4 L^2 C^2 - \omega_c^2 (2LC + R^2 C^2) + 1 = 0$$

$$\omega_c^4 - \omega_c^2 \left(\frac{2}{LC} + \frac{R^2}{L^2} \right) + \frac{1}{L^2 C^2} = 0$$

$$A^2 - A \left(\frac{2}{LC} + \frac{R^2}{L^2} \right) + \frac{1}{L^2 C^2} = 0$$

$$A_{1,2} = \frac{\frac{2}{LC} + \frac{R^2}{L^2} \pm \sqrt{\left(\frac{2}{LC} + \frac{R^2}{L^2} \right)^2 - \frac{4}{L^2 C^2}}}{2}$$

$$= \frac{2}{LC} + \frac{R^2}{L^2} \mp \sqrt{\frac{4}{L^2 C^2} + \frac{4R^2}{L^3 C} + \frac{R^4}{L^4} - \frac{4}{L^2 C^2}}$$

$$A_{1,2} = \frac{\frac{2}{LC} + \frac{R^2}{L^2} \mp \sqrt{\frac{R^4}{L^4} \left(1 + \frac{4L}{C}\right)}}{2} =$$

$$A_1 = \omega_{c_1}^2$$

$$A_2 = \omega_{c_2}^2$$

$$A_2 - A_1 = \omega_{c_2}^2 - \omega_{c_1}^2 = \underbrace{(\omega_{c_2} - \omega_{c_1})}_{\beta} \underbrace{(\omega_{c_2} + \omega_{c_1})}_{\beta}$$

$$\frac{1}{2} \sqrt{\frac{R^4}{L^2} \left(1 + \frac{4L}{C}\right)}$$

$$\frac{1}{\sqrt{2}} = \frac{\omega R C}{\sqrt{\omega^2 R^2 C^2 + (1 - \omega^2 LC)^2}}$$

$$H(j\omega) = \frac{R}{R + j\omega L + \frac{1}{j\omega C}}$$

$$|H| = \frac{R}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} = \frac{1}{\sqrt{2}}$$

$$\sqrt{2} R^2 = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\mp \sqrt{2} R = R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2$$

$$\cancel{2} R^2 = \left(\omega L - \frac{1}{\omega C}\right)^2 + \cancel{R^2}$$

$$\mp R = \omega L - \frac{1}{\omega C}$$

$$\omega^2 LC - 1 \mp \omega RC = 0$$

$$\omega^2 LC \pm \omega RC - 1 = 0$$

$$\omega^2 \pm \omega \frac{R}{L} - \frac{1}{LC} = 0$$

$$\omega_{1,2} = \frac{\mp \frac{R}{L} \mp \sqrt{\frac{R^2}{L^2} + \frac{4}{LC}}}{2} = \mp \frac{R}{2L} \mp \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\boxed{\omega_{c2} - \omega_{c1} = \frac{R}{L}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 16000\pi \Rightarrow \frac{1}{16000^2 \pi^2 \times 5 \times 10^{-9}} = L$$

$\swarrow$ 5 nF

$$L = \frac{1}{256\pi^2 10^{-3} \times 5} = \frac{1000}{256\pi^2 \times 5} = 79 \text{ mH}$$

$$\frac{R}{L} = 8000\pi$$

$$R = 79 \times 10^{-3} \times 8000\pi = 1985 \Omega$$

$$\begin{aligned} \omega_{c1,2} &= \mp \frac{R}{2L} \mp \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}} \\ &= \pm B/2 \mp \sqrt{\left(\frac{B}{2}\right)^2 + \omega_0^2} \\ &= \pm 4000\pi \mp \sqrt{4000^2 \pi^2 + 8000^2 \pi^2} \\ &= \pm 4000\pi \mp 1000\pi \sqrt{16+64} \end{aligned}$$



$$\begin{aligned} \omega_{c1,2} &= (\sqrt{80} \mp 4) 1000\pi \\ &= (4940\pi, 12940\pi) \text{ kesim fr.} \end{aligned}$$

14.32 A block diagram of a system consisting of a sinusoidal voltage source, an *RLC* series bandpass filter, and a load is shown in Fig. P14.32. The internal impedance of the sinusoidal source is $80 + j0 \Omega$, and the impedance of the load is $480 + j0 \Omega$.

The *RLC* series bandpass filter has a 20 nF capacitor, a center frequency of 50 krad/s, and a quality factor of 6.25.

- Draw a circuit diagram of the system.
- Specify the numerical values of L and R for the filter section of the system.
- What is the quality factor of the interconnected system?
- What is the bandwidth (in hertz) of the interconnected system?

Figure P14.32

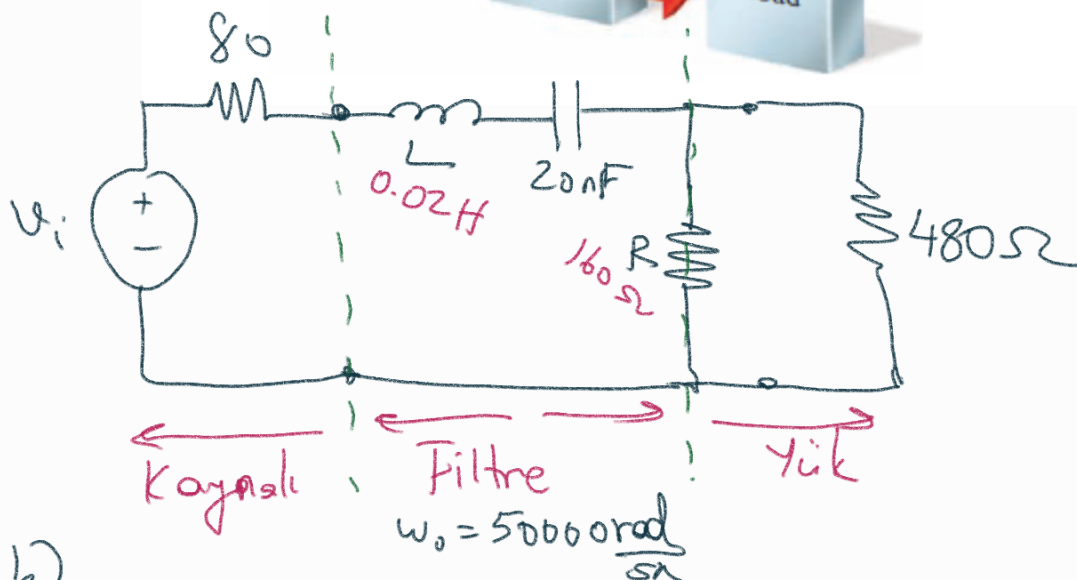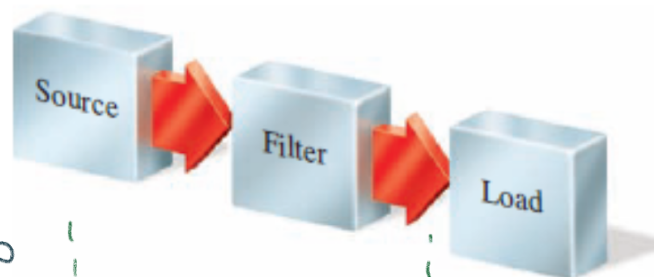

b)


$$Q = \frac{\omega_0}{B} = \frac{50000}{B} = 6.25$$

$$B = 8000 \text{ rad/s} = \frac{R}{L}$$


$$\omega_0 = 50000 = \frac{1}{\sqrt{LC}} \Rightarrow L = \frac{1}{50000^2 \times 20 \times 10^{-9}} = \frac{10}{25 \times 20} = 0.02 \text{ H}$$

$$\frac{R}{L} = \underline{\underline{8000}} \Rightarrow R = 8000 \times 0.02 = 160 \Omega$$

$$c) 160 // 480 = 120 \Omega$$

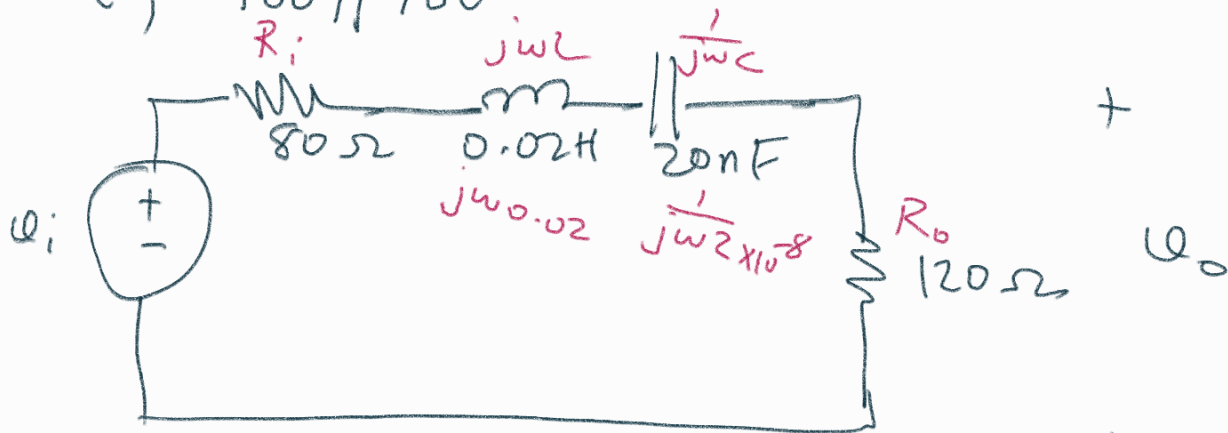

$$|H|_{\max} = \frac{120}{120 + 80} = \underline{\underline{0.6}}$$

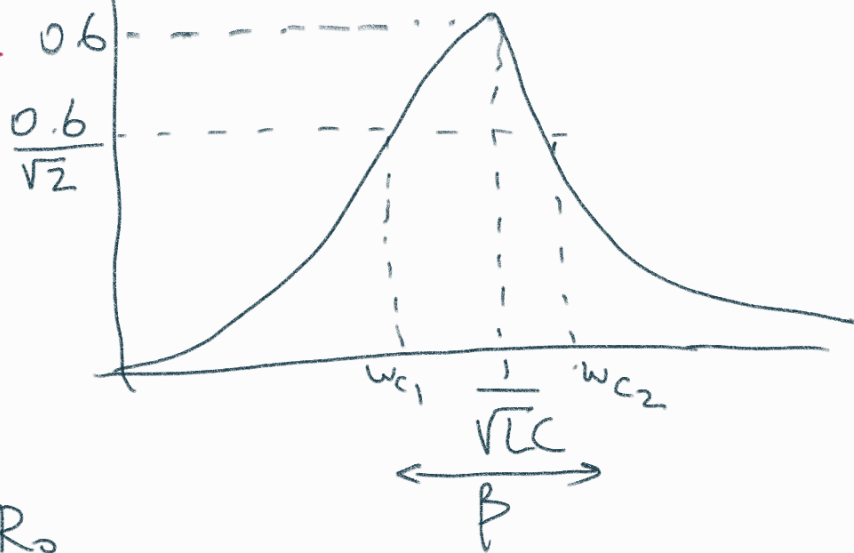

$$H(j\omega) = \frac{R_o}{R_i + j\omega L + \frac{1}{j\omega C} + R_o}$$

$$= \frac{R_o}{R_i + R_o + j\left(\omega L - \frac{1}{\omega C}\right)}$$

$$|H(j\omega_c)| = \frac{R_o}{\sqrt{(R_i + R_o)^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} = \frac{R_o}{(R_i + R_o)\sqrt{2}}$$

~~$$2R_o^2(R_i + R_o)^2 = R_o^2(R_i + R_o)^2 + R_o^2\left(\omega L - \frac{1}{\omega C}\right)^2$$~~

$$\mp R_o(R_i + R_o) = R_o\left(\omega L - \frac{1}{\omega C}\right)$$

$$0 = R_o\omega^2 LC - R_o \pm R_o(R_i + R_o)\omega C$$

$$0 = \omega^2 \pm \frac{R_i + R_o}{L}\omega - \frac{1}{LC}$$

$$\omega_{c1,2} = \frac{\frac{R_i + R_o}{L} \mp \sqrt{\left(\frac{R_i + R_o}{L}\right)^2 + \frac{4}{LC}}}{2}$$

$$= \frac{R_i + R_o}{2L} \pm \sqrt{\left(\frac{R_i + R_o}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_{c2} - \omega_{c1} = \beta = \frac{R_i + R_o}{L} = \frac{80 + 120}{0.02} = 10000 \frac{\text{rad}}{\text{sn}}$$

$$\begin{aligned} B, & \quad 8000 \text{ 'den} & 10000 \text{ 'e} & \text{gilt} & \left(\frac{\text{rad}}{\text{sn}}\right) \\ B, & \quad \frac{4000}{\pi} \text{ " & } \frac{5000}{\pi} & \text{" & (\text{Hz}) \end{aligned}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}, \text{ DEĞİŞMEDİ.}$$

$$Q = \frac{50000}{10000} = 5, \text{ AZALDI}$$

14.42 Use a 500 nF capacitor to design a bandreject filter,

DESIGN
PROBLEM
PSPICE
MULTISIM

as shown in Fig. P14.42. The filter has a center frequency of 4 kHz and a quality factor of 5.

a) Specify the numerical values of R and L .


b) Calculate the upper and lower corner, or cutoff, frequencies in kilohertz.

c) Calculate the filter bandwidth in kilohertz.

$$5 = \frac{8000\pi}{B}$$

$$B = 1600\pi$$

Figure P14.42

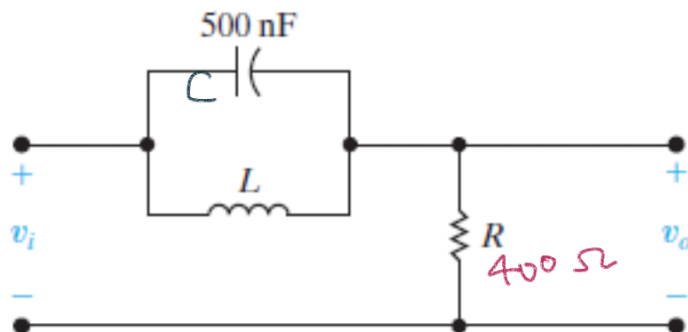

$$H(j\omega) = \frac{R}{R + j\omega L \parallel \frac{1}{j\omega C}} = \frac{R}{R + \frac{j\omega L}{j\omega C + \frac{1}{j\omega L}}}$$


$$= \frac{R}{R + \frac{j\omega L}{1-\omega^2 LC}} = \frac{R(1-\omega^2 LC)}{R(1-\omega^2 LC) + j\omega L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

oldeyunda $H(j\omega_0) = 0$ olw.

$$\omega_0 = 8000\pi$$

$$= \frac{1}{\sqrt{LC}}$$

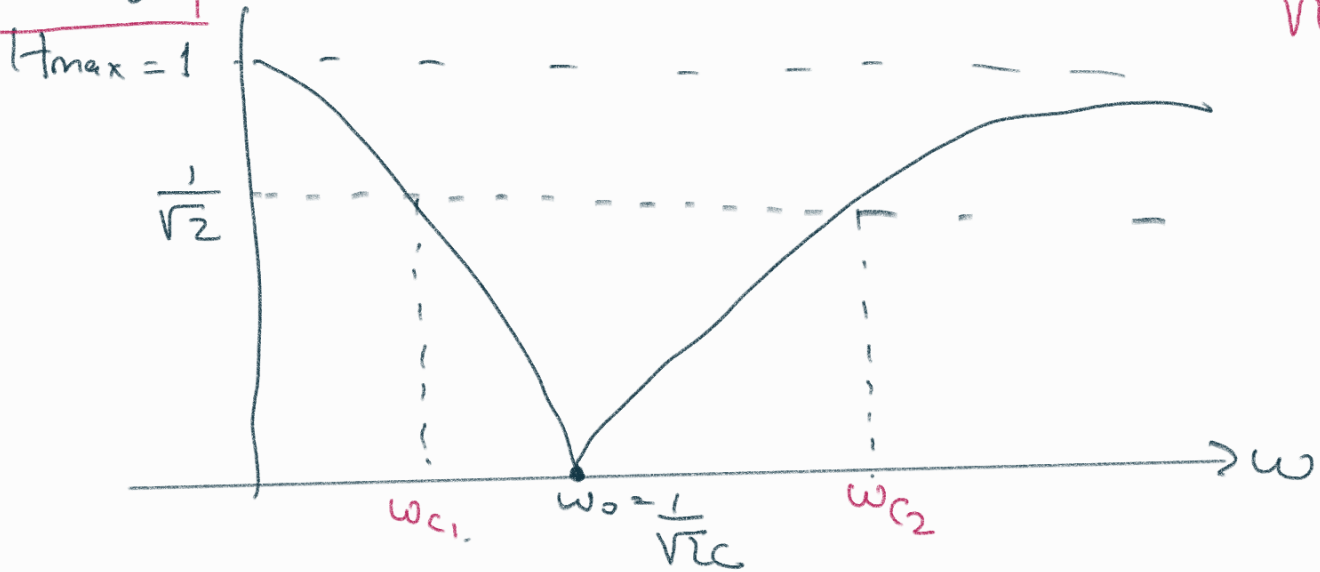

$$\frac{R(1-\omega^2 LC)}{\sqrt{R^2(1-\omega^2 LC)^2 + \omega^2 L^2}} = \frac{1}{\sqrt{2}}$$

$$\cancel{2R^2(1-\omega^2 LC)^2} = \cancel{R^2(1-\omega^2 LC)^2} + \omega^2 L^2$$

$$R(1-\omega^2 LC) = \mp \omega L$$

$$0 = \omega^2 RLC \mp \omega L - R$$

$$= \omega^2 \mp \omega \frac{1}{RC} - \frac{1}{LC}$$

$$\omega_{1,2} = \frac{\pm \frac{1}{RC} \mp \sqrt{\frac{1}{R^2 C^2} + \frac{4}{LC}}}{2}$$

$$= \pm \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$= \pm 800\pi + \sqrt{(800\pi)^2 + (8000\pi)^2}$$

$$\beta = \omega_{c2} - \omega_{c1} = \frac{1}{RC} = \underline{\underline{1600\pi}}$$

$$\frac{1}{1600\pi \times 500 \times 10^{-9}} = R$$

$$\frac{10^5}{80\pi} = \frac{10^4}{8\pi} = R \approx 400 \Omega$$

$$\frac{1}{\sqrt{LC}} = 8000\pi$$

$$L = \frac{1}{64 \times 10^6 \times \pi^2 \times 5 \times 10^{-7}} = \frac{10}{320 \pi^2} \approx \underline{\underline{3.2 \text{ mH}}}$$

$$\omega_{c_{1,2}} = \pm 800\pi + \sqrt{64.64} \cdot 1000\pi$$

$$8040\pi \pm 800\pi = 8840\pi, 7240\pi$$

$\downarrow \qquad \qquad \downarrow$
 $4420 \text{ Hz}, 3620 \text{ Hz}$

$$c) \beta = \frac{1600\pi}{2\pi} = 800 \text{ Hz}$$

bandgrenzfrequenz

14.48 Given the following voltage transfer function:

$$H(s) = \frac{V_o}{V_i}$$

$$= \frac{25 \times 10^6}{s^2 + 1000s + 25 \times 10^6}$$

- ✓ a) At what frequencies (in radians per second) is the magnitude of the transfer function equal to unity? $0, 7000 \text{ rad/s}$
- b) At what frequency is the magnitude of the transfer function maximum?
- c) What is the maximum value of the transfer function magnitude?

$$H(j\omega) = \frac{25 \times 10^6}{-\omega^2 + j1000\omega + 25 \times 10^6}$$

$$a) |H(j\omega)| = \frac{25 \times 10^6}{\sqrt{(10000\omega)^2 + (25 \times 10^6 - \omega^2)^2}} = 1$$

$$(25 \times 10^6)^2 = 10^6 \omega^2 + (25 \times 10^6 - \omega^2)^2$$


$$\cancel{(25 \times 10^6)^2} = 10^6 \omega^2 + \cancel{(25 \times 10^6)^2} - 50 \times 10^6 \omega^2 + \omega^4$$

$$0 = \omega^4 - 49 \times 10^6 \omega^2$$

$$0 = \omega^2 (\omega^2 - 49 \times 10^6)$$

$$\omega = 0 \rightarrow |H| = 1$$

$$\omega = 7000 \text{ rad/s} \rightarrow |H| = 1$$

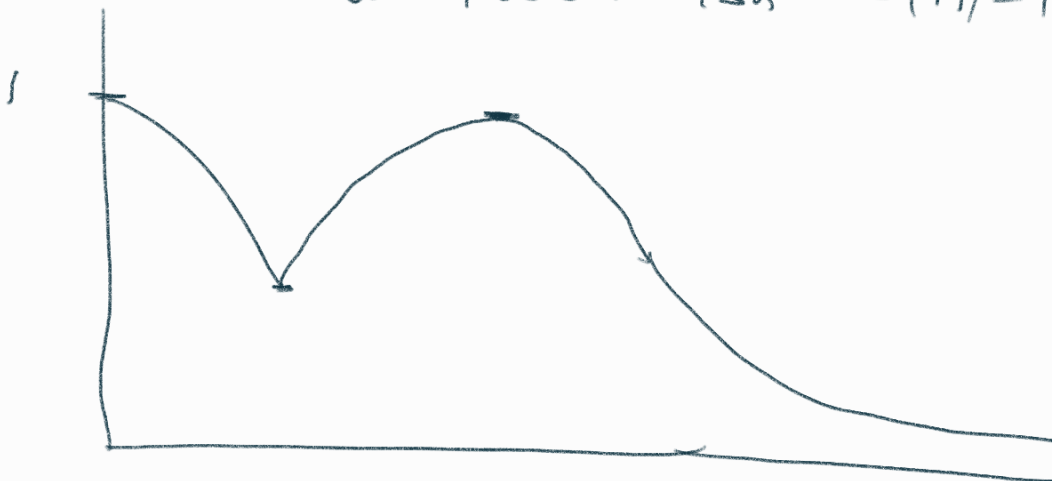

$$b) \min \{ 10^6 \omega^2 + (25 \times 10^6 - \omega^2)^2 \}$$

$$2 \times 10^6 \omega + 2(25 \times 10^6 - \omega^2)(-2\omega) = 0$$

$$2 \times 10^6 \omega - 100 \times 10^6 \omega + 4\omega^3 = 0$$

$$\omega (4\omega^2 - 98 \times 10^6) = 0$$

$$\boxed{\omega = 0} \rightarrow |H| = 1$$

$$\omega = \sqrt{\frac{49}{2}} \times 10^3$$

AKTİF FİLTRELER (Butterworth)

1. derece alçak geçiren filtre.


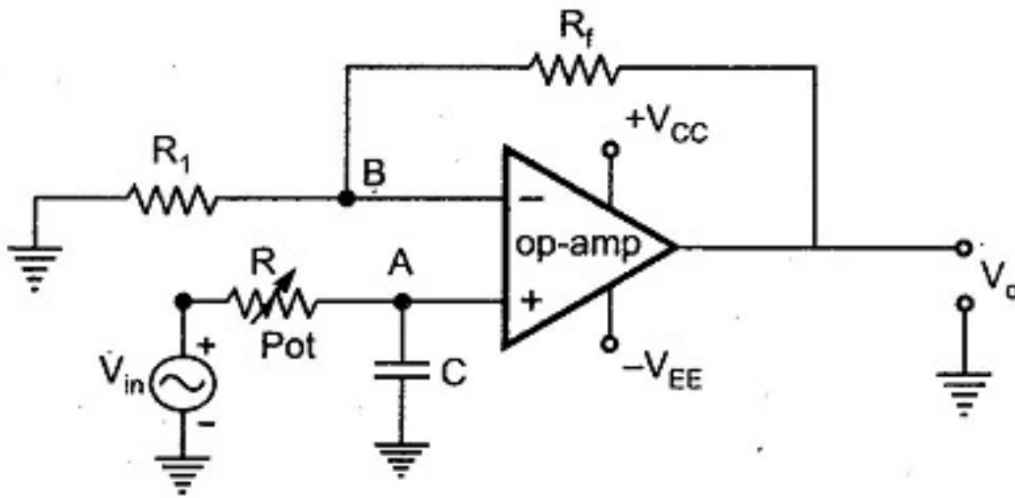


Fig. 2.74 First order low pass butterworth filter

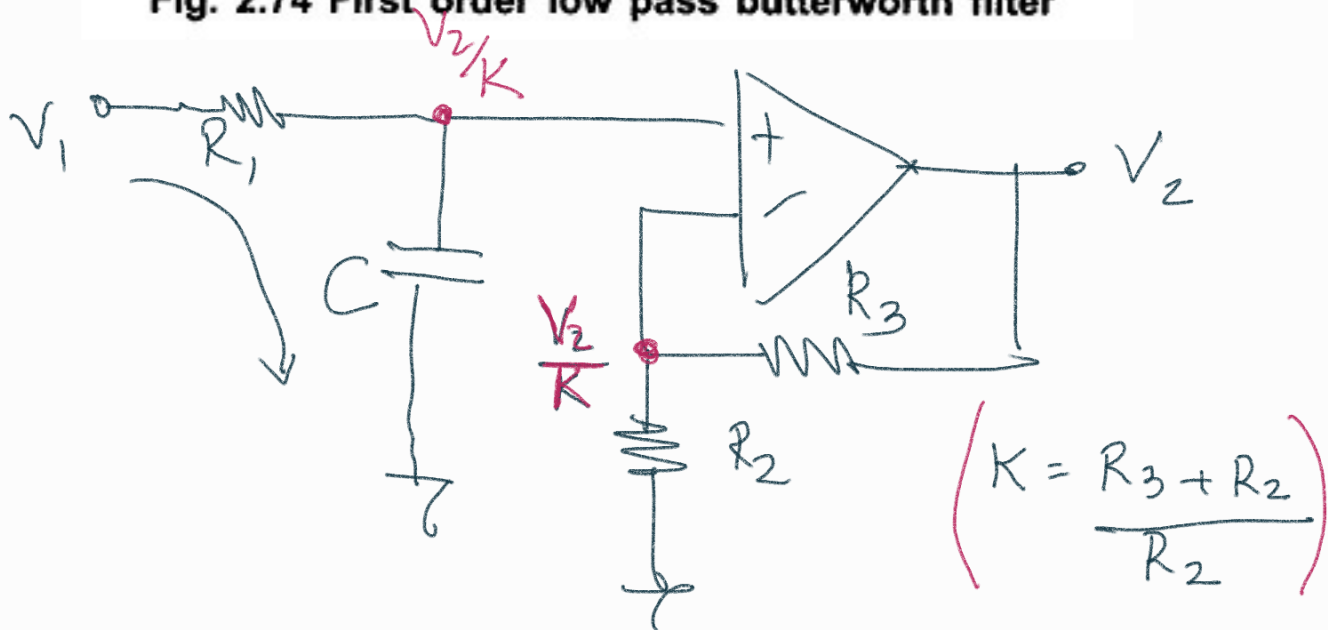

$$\frac{V_1 - \frac{V_2}{K}}{R_1} = \frac{V_2}{K \frac{1}{j\omega C}} \Rightarrow \frac{V_1}{R_1} = \frac{V_2}{KR_1} + \frac{V_2 j\omega C}{K}$$

$$\frac{V_1}{R_1} = \frac{V_2}{K} \left(\frac{1}{R_1} + \frac{j\omega C R_1}{R_1} \right)$$

$$\frac{V_2}{V_1} = H(j\omega) = \frac{K}{1 + j\omega C R_1} = \frac{K \frac{1}{R_1 C}}{j\omega + \frac{1}{R_1 C}}$$

Genel form: $K \frac{\omega_c}{s + b \omega_c}$

← kazanç

← kesim frek. $\rightarrow 1$ (Butterworth için)

Burada:

$$K = \frac{R_2 + R_3}{R_2}$$

$$\omega_c = \frac{1}{R_1 C}$$

$$b = 1$$

Birinci Derece Yüksek geçiren


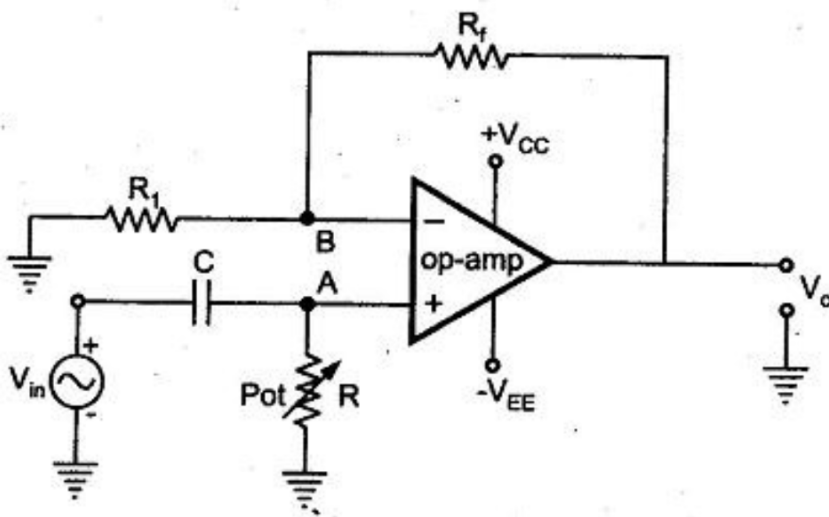


Fig. 2.79 First order high pass Butterworth filter

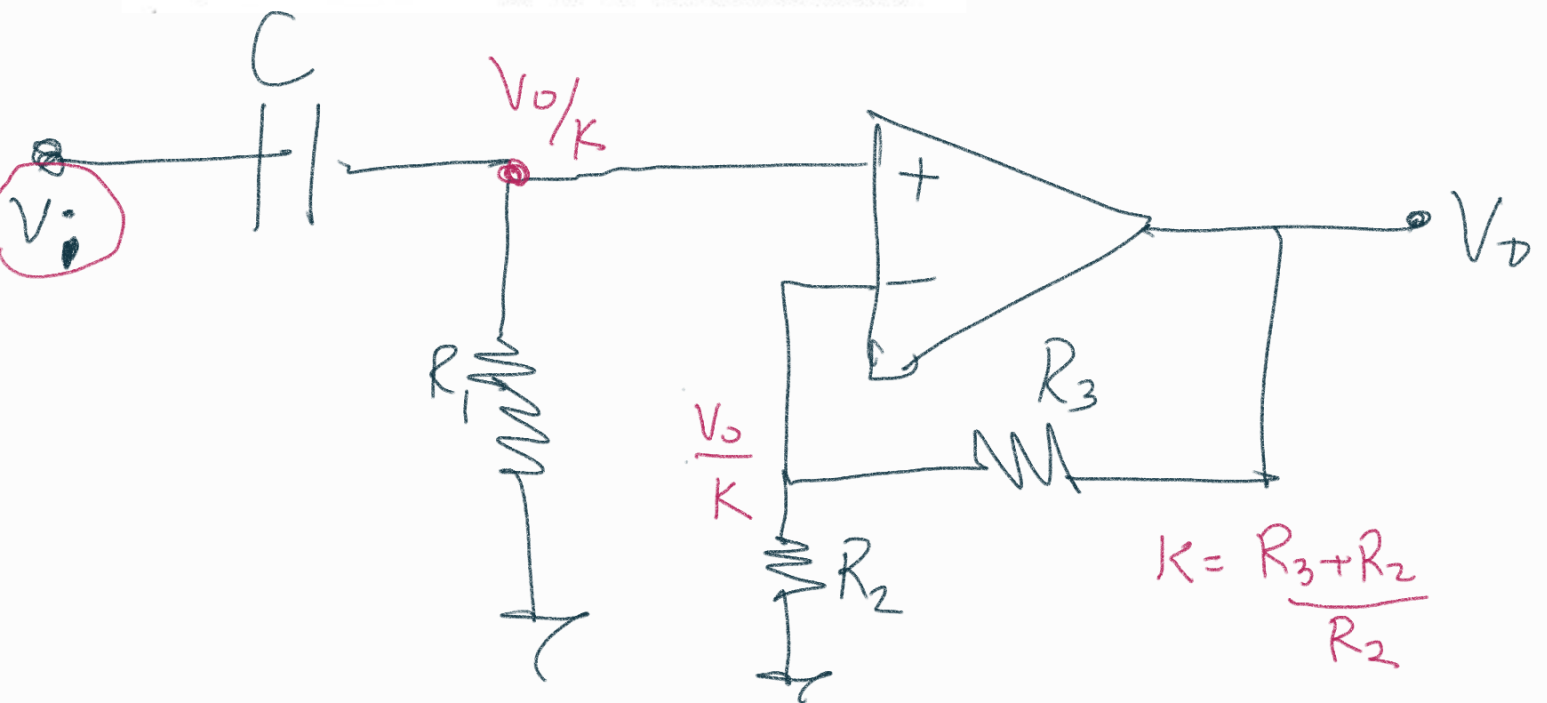

$$\left(V_i - \frac{V_o}{K}\right) j\omega C = \frac{V_o}{KR_1}$$

$$V_i j\omega C = \frac{V_o}{K} \left(j\omega C + \frac{1}{R_1} \right)$$

$$\frac{V_o}{V_i} = \frac{j\omega C \cdot K}{j\omega C + \frac{1}{R_1}} = K \frac{(j\omega)}{j\omega + \frac{1}{R_1 C}}$$

Genel form: $H(s) = K \frac{s}{s + \frac{\omega_c}{b}}$



Annotations:
 K → Kazanç.
 $\frac{\omega_c}{b}$ → Kesim fr.
 b → 1

Bu derrede:


$$\left(\begin{array}{l} K = \frac{R_2 + R_3}{R_1} \\ \omega_c = \frac{1}{R_1 C} \\ b = 1 \end{array} \right)$$

Not: Butterworth ($b=1$)

Chebyshev ($b \neq 1$)

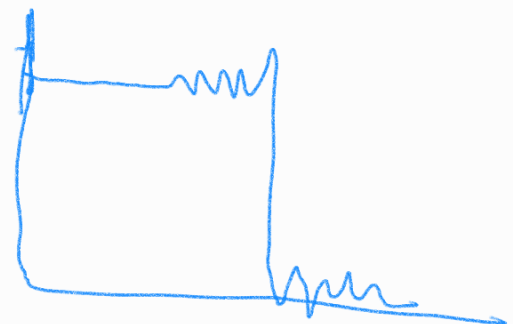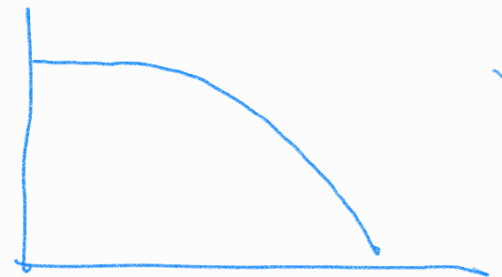


1. derece Bant Geçirgen Filtre



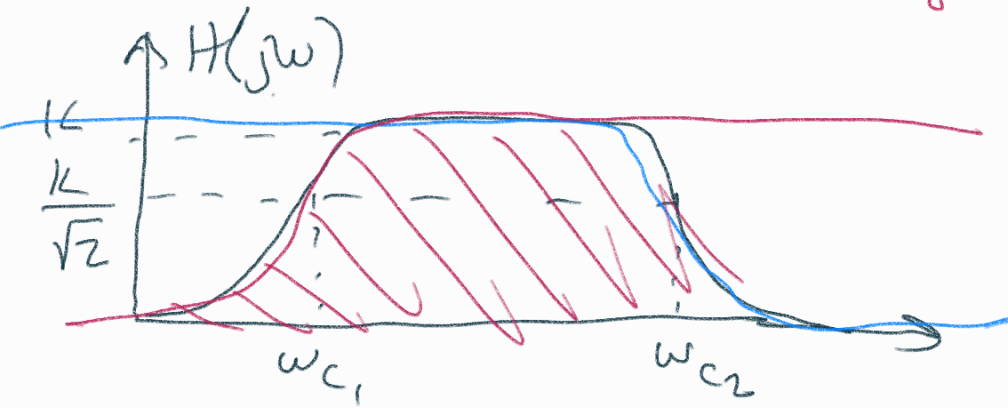


LPF

HPF

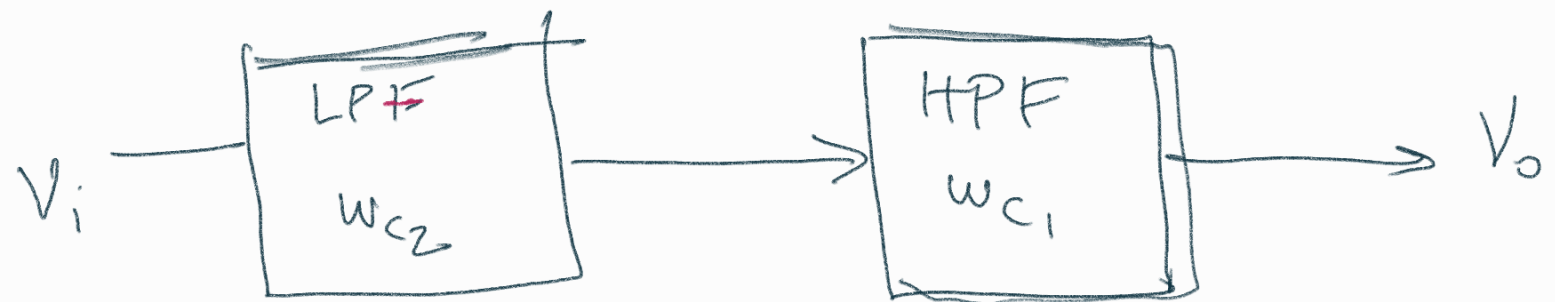

1. derece bant durdurucu:

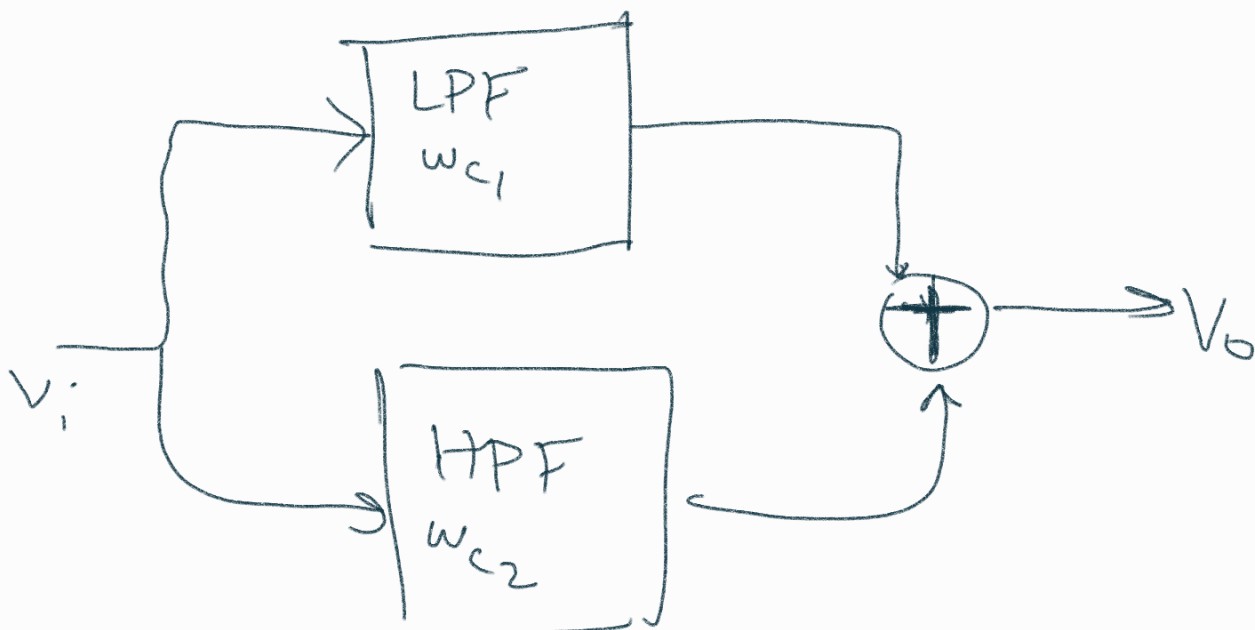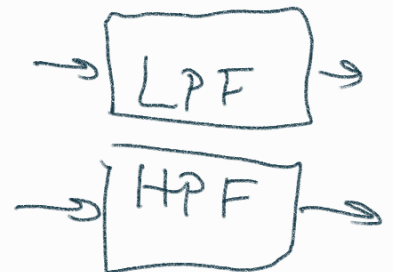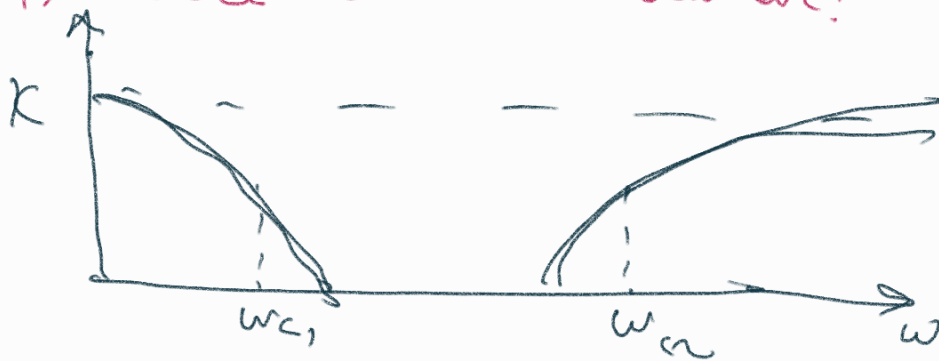

2. derece Düşük Geçiren Filtre

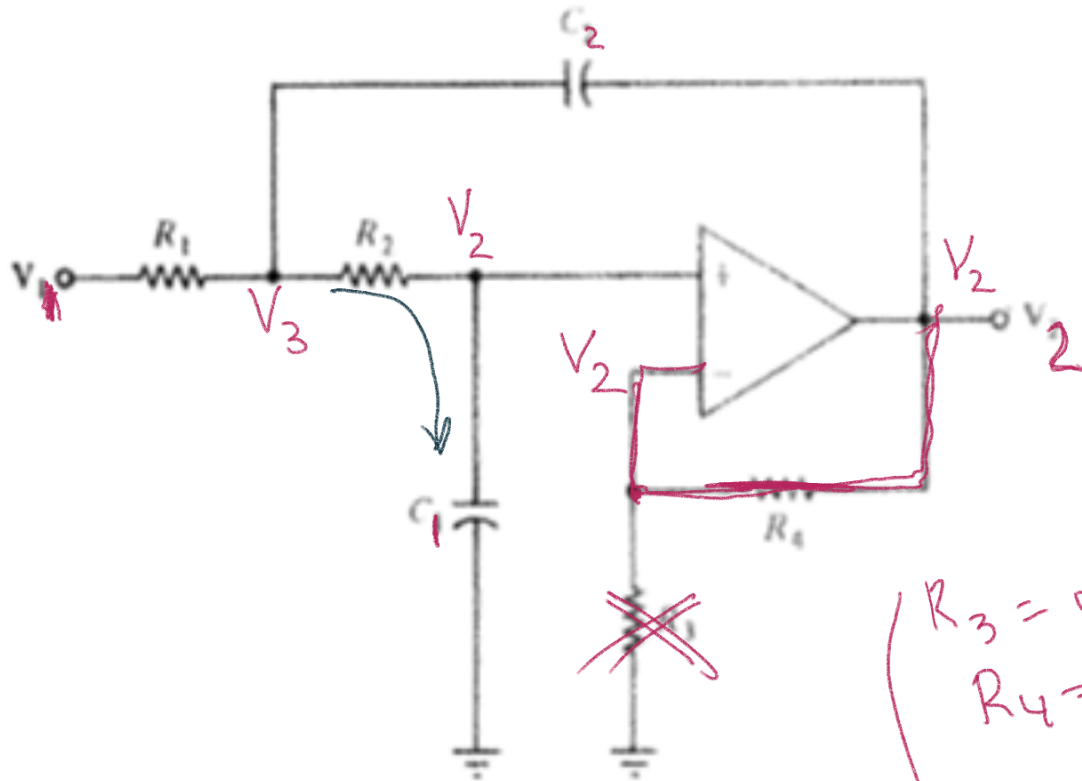


FIGURE 5.12 Second-order VCVS low-pass filter circuit.

$$(1) \quad \frac{V_1 - V_3}{R_1} = \frac{V_3 - V_2}{R_2} + (V_3 - V_2) j\omega C_2$$

$$(2) \quad \frac{V_3 - V_2}{R_2} = V_2 j\omega C_1$$

$$(1) \quad \frac{V_1}{R_1} = V_3 \left(\frac{1}{R_1} + \frac{1}{R_2} + j\omega C_2 \right) - V_2 \left(\frac{1}{R_2} + j\omega C_2 \right)$$

$$(2) \quad \frac{V_3}{R_2} = V_2 \left(\frac{1}{R_2} + j\omega C_1 \right)$$

$$V_3 = V_2 (1 + j\omega C_1 R_2)$$

$$\frac{V_1}{R_1} = V_2 \left[(1 + j\omega C_1 R_2) \left(\frac{1}{R_1} + \frac{1}{R_2} + j\omega C_2 \right) - \frac{1}{R_2} - j\omega C_2 \right]$$

$$\frac{V_1}{R_1} = V_2 \left[\cancel{\frac{1}{R_1}} + \cancel{\frac{1}{R_2}} + \cancel{j\omega C_2} + j\omega C_1 \frac{R_2}{R_1} + \cancel{j\omega C_1} - \omega^2 C_1 C_2 R_2 - \cancel{\frac{1}{R_2}} - \cancel{j\omega C_2} \right]$$

$$\frac{V_1}{R_1} \rightarrow V_2 \left[\frac{1}{R_1} + j\omega \left(C_1 \frac{R_2}{R_1} + C_1 \right) - \omega^2 C_1 C_2 R_2 \right]$$

$$V_1 = V_2 \left[1 + j\omega (C_1 R_2 + C_1 R_1) - \omega^2 C_1 C_2 R_1 R_2 \right]$$

$$\frac{V_2}{V_1} = H(j\omega) = \frac{1}{1 + j\omega C_1 (R_1 + R_2) - \omega^2 C_1 C_2 R_1 R_2}$$

$$= \frac{1}{C_1 C_2 R_1 R_2}$$

$$\frac{1}{C_1 C_2 R_1 R_2} + j\omega \frac{1}{C_2} \frac{R_1 + R_2}{R_1 R_2} - \omega^2$$

Genel form:

$$(s=j\omega) \quad H(s) = \frac{K b \omega_c^2}{s^2 + a \omega_c s + b \omega_c^2} \rightarrow \text{kesim}$$

Burada:

$$K=1$$

$$b=1 \quad (\text{Butterworth})$$

$$\omega_c = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$\begin{aligned} \rightarrow a \omega_c &= \frac{1}{C_2} \frac{R_1 + R_2}{R_1 R_2} \\ \rightarrow b \omega_c^2 &= \frac{1}{R_1 R_2 C_1 C_2} \end{aligned} \quad \left. \vphantom{\begin{aligned} \rightarrow a \omega_c &= \frac{1}{C_2} \frac{R_1 + R_2}{R_1 R_2} \\ \rightarrow b \omega_c^2 &= \frac{1}{R_1 R_2 C_1 C_2} \end{aligned}} \right\} 2 \text{ denklem}$$

R_1, R_2 'ye değer ver, C_2 'yi bul. Sonra C_1 'i bul.

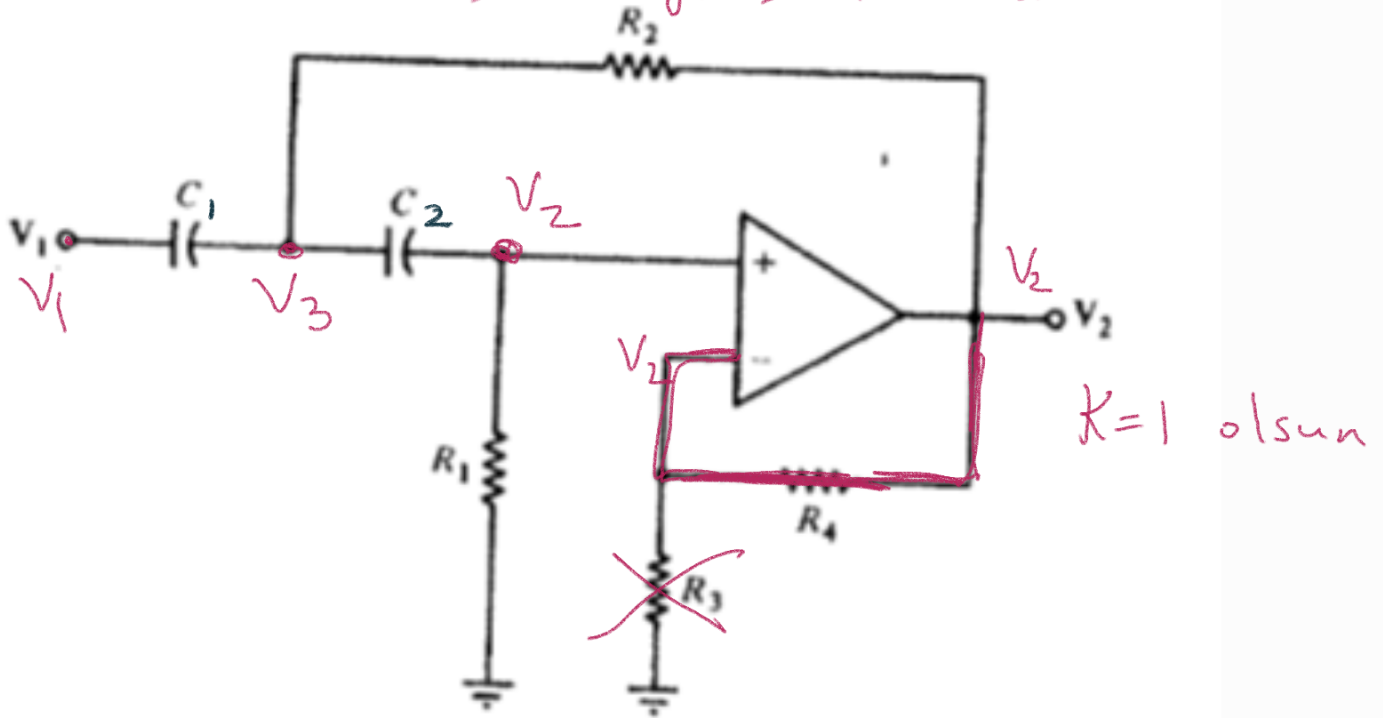


FIGURE 6.4 Second-order VCVS high-pass filter circuit.

$$(1) (V_1 - V_3) j\omega C_1 = (V_3 - V_2) j\omega C_2 + \frac{V_3 - V_2}{R_2}$$

$$(2) (V_3 - V_2) j\omega C_2 = \frac{V_2}{R_1}$$

$$(2) V_3 j\omega C_2 = V_2 \left(j\omega C_2 + \frac{1}{R_1} \right)$$

$$V_3 = V_2 \left(1 + \frac{1}{j\omega R_1 C_2} \right)$$

$$(1) V_1 j\omega C_1 = V_2 \left(j\omega (C_1 + C_2) + \frac{1}{R_2} \right) - V_2 \left(j\omega C_2 + \frac{1}{R_2} \right)$$

$$V_1 j\omega C_1 = V_2 \left[\left(1 + \frac{1}{j\omega R_1 C_2} \right) \left(j\omega (C_1 + C_2) + \frac{1}{R_2} \right) - j\omega C_2 - \frac{1}{R_2} \right]$$

$$V_1 j\omega C_1 = V_2 \left[\cancel{j\omega C_1} + \cancel{j\omega C_2} + \cancel{\frac{1}{R_2}} + \frac{C_1 + C_2}{R_1 C_2} + \frac{1}{j\omega R_1 R_2 C_2} - \cancel{j\omega C_2} - \cancel{\frac{1}{R_2}} \right]$$

$$V_1 = V_2 \left[1 + \frac{C_1 + C_2}{j\omega C_1 C_2 R_1} + \frac{1}{-\omega^2 R_1 R_2 C_1 C_2} \right]$$

$$V_1 = V_2 \left[\frac{-\omega^2 R_1 R_2 C_1 C_2 + j\omega R_2 (C_1 + C_2) + 1}{-\omega^2 R_1 R_2 C_1 C_2} \right]$$

$$\frac{V_2}{V_1} = H(j\omega) = \frac{-\omega^2 R_1 R_2 C_1 C_2}{-\omega^2 R_1 R_2 C_1 C_2 + j\omega R_2 (C_1 + C_2) + 1}$$

$$H(j\omega) = \frac{-\omega^2}{-\omega^2 + j\omega \frac{1}{R_1} \frac{C_1 + C_2}{C_1 C_2} + \frac{1}{R_1 R_2 C_1 C_2}}$$

Genel Form:

$$\frac{Ks^2}{s^2 + \frac{a\omega_c}{b}s + \frac{\omega_c^2}{b}}$$

Butterworth: $b=1$


(2)

$$\omega_c = \sqrt{\frac{1}{R_1 R_2 C_1 C_2}}$$

Kesim fr.

① $a\omega_c = \frac{1}{R_1} \frac{C_1 + C_2}{C_1 C_2}$

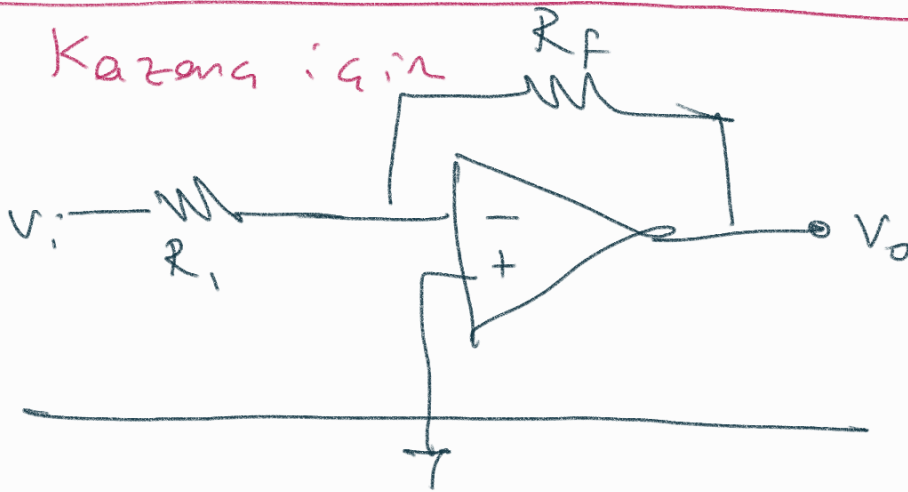C_1, C_2 'ye değeri ver. R_1 'i bul. Sonra R_2 'yi bul.



YÜKSEK DERECE FİLTRELER:

Butterworth: $|H(j\omega)| = A_{LP}$

$$\frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^{2n}}}$$

n . arttıkça filtre
ideale yaklaşır.

dergee $\leftarrow n=1, 2, 3, \dots$

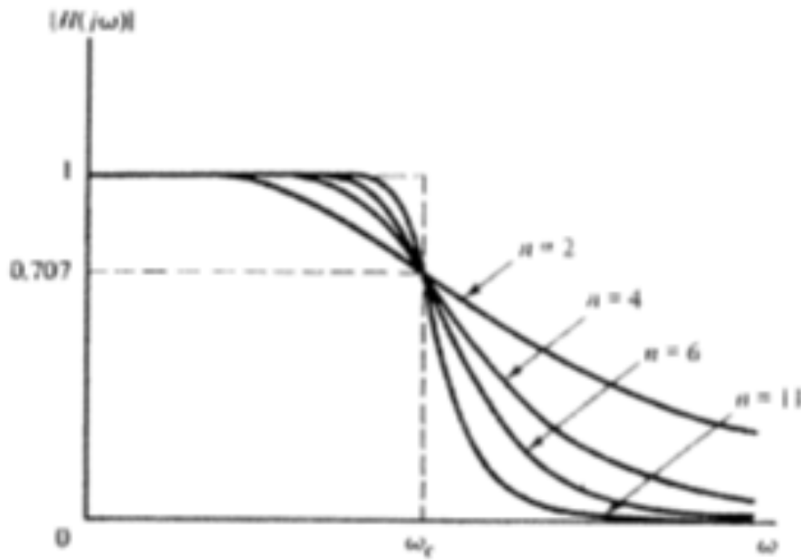


FIGURE 5.5 Low-pass Butterworth magnitudes.

LPF, HPF ayn. katsayılar.

n	a	b
1	-	1
2	1.414214 $\sqrt{2}$	1
3	1.000000	1 → 2. derece
	-	1 → 1. derece
4	0.765367	1 → 2. derece
	1.847759	1 → 2. derece
5	-	1 → 1. derece
	0.618	1 → 2. derece
	1.618	1 → 2. derece
6		
7		
8		


Example: 1st order LPF
 $K=4$
 $f_c = 1000 \text{ Hz}$

$$\frac{K \omega_c}{s + b \omega_c}$$

$$\omega_c = \frac{1}{RC} = 2000\pi$$

$$C = 100 \text{ nF} \quad (10^{-7})$$
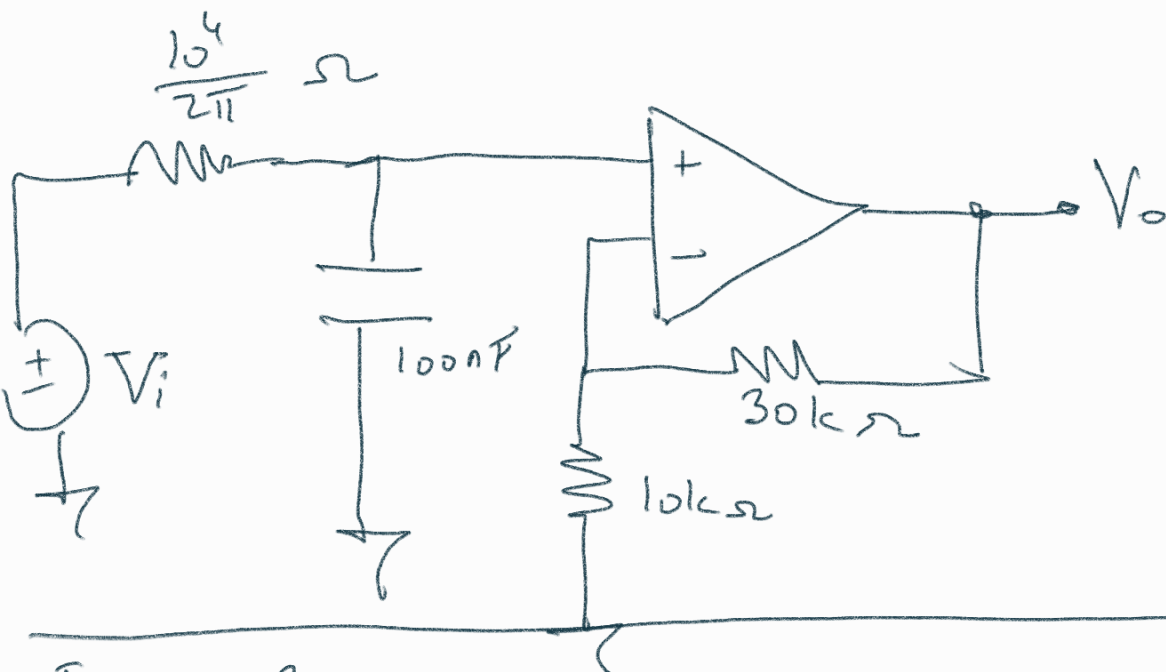
$$R = \frac{1}{2\pi \times 10^3 \times 10^{-7}} = \frac{10^4}{2\pi} \Omega$$



Example: 2nd order Butterworth LPF

$$K=1 \quad f_c=1000 \text{ Hz}$$

$$(a=\sqrt{2} \quad b=1 : \text{Tablodan})$$

$$H(s) = \frac{\frac{1}{C_1 C_2 R_1 R_2}}{s^2 + s \frac{1}{C_1} \frac{R_1 + R_2}{R_1 R_2} + \frac{1}{C_1 C_2 R_1 R_2}}$$

$$\text{Genel Form: } \frac{b \omega_c^2}{s^2 + a \omega_c s + b \omega_c^2}$$

R_1, R_2, C_1, C_2 taserlayın

$$\omega_c = 2000\pi$$

R_1, R_2 'ye değer ver. C_1 'i bul

$$\sqrt{2} \cdot 2000\pi = \frac{1}{C_1} \frac{R_1 + R_2}{R_1 R_2}$$

$$R_1 = R_2 = 10^4 \Omega$$

$$C_1 = \frac{1}{2000\sqrt{2}\pi} \cdot \frac{2 \times 10^4}{10^8}$$

$$C_1 = \frac{1}{\sqrt{2}\pi} 10^{-7} = \frac{100}{\sqrt{2}\pi} \text{ nF} //$$

$$4 \times 10^6 \pi^2 = \frac{1}{C_1 C_2 R_1 R_2}$$

$$4 \times 10^6 \pi^2 = \frac{1}{C_2 \frac{10^{-7}}{\sqrt{2}\pi} 10^8}$$

$$4 \times 10^6 \pi^2 = \frac{\sqrt{2}\pi}{10 C_2} \Rightarrow C_2 = \frac{\sqrt{2}\pi}{4 \times 10^7 \pi^2}$$

$$= \frac{100}{2\sqrt{2}\pi} \text{ nF} //$$

CHAPTER 15: LAPLACE DÖNÜŞÜMÜ:

TABLE 15.1

Properties of the Laplace transform.

Property	$f(t)$	$F(s)$
Linearity	$a_1 f_1(t) + a_2 f_2(t)$	$a_1 F_1(s) + a_2 F_2(s)$
Scaling	$f(at)$	$\frac{1}{a} F\left(\frac{s}{a}\right)$
Time shift	$f(t-a)u(t-a)$	$e^{-as} F(s)$
Frequency shift	$e^{-at} f(t)$	$F(s+a)$
Time differentiation	$\frac{df}{dt}$	$sF(s) - f(0^-)$
	$\frac{d^2 f}{dt^2}$	$s^2 F(s) - sf(0^-) - f'(0^-)$
	$\frac{d^3 f}{dt^3}$	$s^3 F(s) - s^2 f(0^-) - sf'(0^-) - f''(0^-)$
	$\frac{d^4 f}{dt^4}$	$s^4 F(s) - s^3 f(0^-) - s^2 f'(0^-) - sf''(0^-) - f'''(0^-)$
Time integration	$\int_0^t f(x) dx$	$\frac{1}{s} F(s)$
Frequency differentiation	$tf(t)$	$-\frac{d}{ds} F(s)$
Frequency integration	$\frac{f(t)}{t}$	$\int_s^\infty F(x) dx$
Time periodicity	$f(t) = f(t+nT)$	$\frac{F_1(s)}{1 - e^{-sT}}$
Initial value	$f(0)$	$\lim_{s \rightarrow \infty} sF(s)$
Final value	$f(\infty)$	$\lim_{s \rightarrow 0} sF(s)$
Convolution	$f_1(t) * f_2(t)$	$F_1(s)F_2(s)$

TABLE 15.2

Laplace transform pairs.*

$f(t)$	$F(s)$
$\delta(t)$	1
$u(t)$	$\frac{1}{s}$
e^{-at}	$\frac{1}{s+a}$
t	$\frac{1}{s^2}$
t^n	$\frac{n!}{s^{n+1}}$
te^{-at}	$\frac{1}{(s+a)^2}$
$t^n e^{-at}$	$\frac{n!}{(s+a)^{n+1}}$
$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
$\sin(\omega t + \theta)$	$\frac{s \sin \theta + \omega \cos \theta}{s^2 + \omega^2}$
$\cos(\omega t + \theta)$	$\frac{s \cos \theta - \omega \sin \theta}{s^2 + \omega^2}$
$e^{-at} \sin \omega t$	$\frac{\omega}{(s+a)^2 + \omega^2}$
$e^{-at} \cos \omega t$	$\frac{s+a}{(s+a)^2 + \omega^2}$

*Defined for $t \geq 0$; $f(t) = 0$, for $t < 0$.

15.5 Find the Laplace transform of each of the following functions:

(a) $t^2 \cos(2t + 30^\circ) u(t)$

(b) $3t^4 e^{-2t} u(t)$

(c) $2tu(t) - 4\frac{d}{dt} \delta(t)$

(d) $2e^{-(t-1)} u(t)$

(e) $5u(t/2)$

(f) $6e^{-t/3} u(t)$

(g) $\frac{d^n}{dt^n} \delta(t)$

a) $\cos(2t) = \frac{s}{s^2 + 4}$

$\sin(2t) = \frac{2}{s^2 + 4}$

$\cos(2t + 30^\circ) = \cos(2t) \cos(30^\circ)$

$- \sin(2t) \sin(30^\circ)$

$\downarrow \mathcal{L}$

$\frac{s \cos(30^\circ) - 2 \sin(30^\circ)}{s^2 + 4}$

$t^2 \xrightarrow{\mathcal{L}} \frac{d^2}{ds^2}$

$F(s) = \frac{d^2}{ds^2} \left\{ \frac{s \cos(30^\circ) - 2 \sin(30^\circ)}{s^2 + 4} \right\}$

$$b) 3 t^4 e^{-2t} u(t)$$

$$\underbrace{\quad}_{\frac{1}{s}} \underbrace{\quad}_{\frac{1}{s+2}}$$

$$3 \frac{d^4}{ds^4} \left\{ \frac{1}{s+2} \right\}$$

$$= \frac{3 \times 24}{(s+2)^5}$$

$$① \frac{-1}{(s+2)^2}$$

$$② \frac{2}{(s+2)^3}$$

$$③ \frac{-6}{(s+2)^4}$$

$$④ \frac{24}{(s+2)^5}$$

$$c) 2t u(t+1) - 4 \frac{d}{dt} \delta(t)$$

$$\underbrace{\quad}_{\frac{1}{s}} \underbrace{\quad}_{\frac{1}{s}}$$

$$\underbrace{(t+1)}_{\frac{1}{s^2}} \underbrace{\quad}_{\frac{1}{s}}$$

$$+ \frac{2}{s^2} - 4s$$

$$\frac{d}{dt} \rightarrow sF(s) - f(0^-)$$

$$\downarrow \emptyset$$

$$F(s) = \frac{2}{s^2} - 4s$$

$$d) 2e^{-(t+1)} u(t)$$

$$2e e^{-t} u(t)$$

$$\underbrace{\quad}_{\frac{1}{s}} \underbrace{\quad}_{\frac{1}{s+1}}$$

$$\frac{2e}{s+1}$$

$$F(s) = \frac{2e}{s+1}$$

$$e) 5 u\left(\frac{t}{2}\right)$$

$$f(at) \xrightarrow{\mathcal{L}} \frac{1}{a} F\left(\frac{s}{a}\right)$$

$$a = \frac{1}{2}$$

$$u(t) \rightarrow \frac{1}{s}$$

$$u\left(\frac{t}{2}\right) \rightarrow 2 \cdot \frac{1}{2s} = \frac{1}{s}$$

$$f) 6e^{-t/3} u(t)$$

$$\parallel$$

$$6e^{-t/3} u(t/3)$$

$$e^{-t} u(t) \xrightarrow{\mathcal{L}} \frac{1}{s+1}$$

$$e^{-t/3} u(t/3) \xrightarrow{\mathcal{L}} 3 \frac{1}{3s+1}$$

$$6e^{-t/3} u(t/3) \xrightarrow{\mathcal{L}} 18 \frac{1}{3s+1}$$

$$g) \frac{d^n \delta(t)}{dt^n} \xrightarrow{\quad} s^n$$

$$\begin{aligned} sF(s) - f(0^-) \\ s(sF(s) - f(0^-)) - f'(0^-) \\ s(s(sF(s) - f(0^-)) - f'(0^-)) - f''(0^-) \\ \vdots \end{aligned}$$

15.10 In two different ways, find the Laplace transform of

$$g(t) = \frac{d}{dt}(te^{-t}\cos t) \xrightarrow{\quad} \frac{s}{s^2+1}$$

$$e^{-t}\cos t \xrightarrow{\mathcal{L}} \frac{s+1}{(s+1)^2+1} = \frac{s+1}{s^2+2s+2}$$

$$te^{-t}\cos t \xrightarrow{\mathcal{L}} -\frac{d}{ds} \left\{ \frac{s+1}{(s+1)^2+1} \right\} = -\frac{s^2+2s+2 - (2s+2)(s+1)}{(s^2+2s+2)^2}$$

$$\frac{d}{dt}(te^{-t}\cos t) \rightarrow s \left[-\frac{d}{ds} \left\{ \frac{s+1}{(s+1)^2+1} \right\} \right] - te^{-t}\cos t \Big|_{t=\infty} \rightarrow 0$$

$$= -s \left[\frac{s^2+2s+2 - 2s^2-2s-2}{(s^2+2s+2)^2} \right]$$

$$= \frac{-s(-s^2-2s)}{(s^2+2s+2)^2} = \frac{s^2(s+2)}{(s^2+2s+2)^2} \quad \checkmark$$

$$\frac{d}{dt}(te^{-t}\cos t) = e^{-t}\cos t + t(-e^{-t}\cos t - e^{-t}\sin t)$$

$$= \underbrace{e^{-t}\cos t}_{\frac{s+1}{(s+1)^2+1}} - \underbrace{te^{-t}\cos t}_{-\frac{d}{ds} \left\{ \frac{s+1}{s^2+2s+2} \right\}} - \underbrace{te^{-t}\sin t}_{-\frac{d}{ds} \left\{ \frac{1}{s^2+2s+2} \right\}}$$

$$= \frac{s+1}{s^2+2s+2} + \frac{s^2+2s+2 - (s+1)(2s+2)}{(s^2+2s+2)^2} - \frac{2s+2}{(s^2+2s+2)^2}$$

$$= \frac{s+1}{s^2+2s+2} + \frac{s^2+2s+2 - 2s^2-2s-2}{(s^2+2s+2)^2} - \frac{2s+2}{(s^2+2s+2)^2}$$

$$= \frac{s+1}{s^2+2s+2} - \frac{s^2+2s+2s+2}{(s^2+2s+2)^2}$$

$$= \frac{s^3+2s^2+\cancel{2s}+\cancel{s^2+2s+2} - \cancel{s^2} - \cancel{2s} - \cancel{2s} - \cancel{2}}{(s^2+2s+2)^2}$$

$$= \frac{s^2(s+2)}{(s^2+2s+2)^2} \quad \checkmark$$

15.14 Find the Laplace transform of the signal in Fig. 15.26.

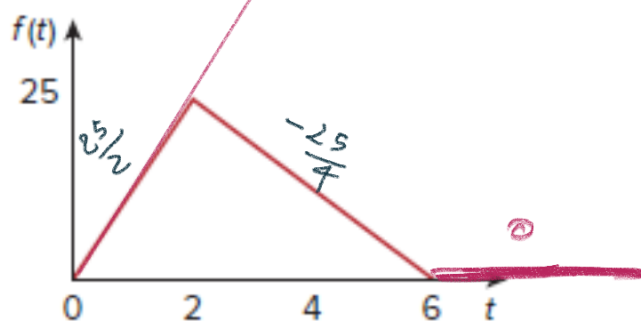


Figure 15.26
For Prob. 15.14.

$$f(t) = \frac{25}{2} t u(t) - \frac{75}{4} (t-2) u(t-2) + \frac{25}{4} (t-6) u(t-6)$$

$$= \frac{25}{2} \frac{1}{s^2} - \frac{75}{4} e^{-2s} \frac{1}{s^2} + \frac{25}{4} e^{-6s} \frac{1}{s^2}$$

15.19 Calculate the Laplace transform of the infinite train of unit impulses in Fig. 15.31.

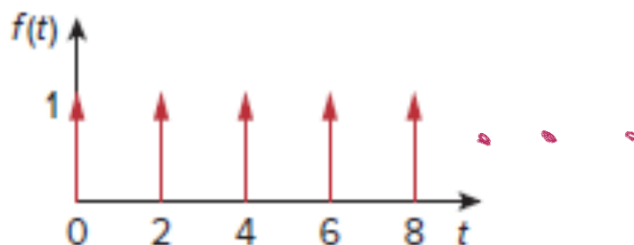


Figure 15.31
For Prob. 15.19.

$$f(t) = \sum_{i=0}^{\infty} \delta(t - 2i) \xrightarrow{\mathcal{L}} \sum_{i=0}^{\infty} e^{-2is} \cdot 1$$

$$F(s) = \sum_{i=0}^{\infty} (e^{-2s})^i$$

$$F(s) = \frac{1}{1 - e^{-2s}}$$

15.26 Determine the initial and final values of $f(t)$, if they exist, given that:

$$(a) F(s) = \frac{5s^2 + 3}{s^3 + 4s^2 + 6}$$

$$(b) F(s) = \frac{s^2 - 2s + 1}{4(s - 2)(s^2 + 2s + 4)}$$

$$\lim_{t \rightarrow 0} f(t) = \lim_{s \rightarrow \infty} sF(s)$$

$$\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} sF(s)$$

Not: Bunu uygulama-
yabilmek için
bu limit var
olmalıdır.

a) $F(s)$ 'nin sağ yarı düzlemde kutbu varsa limit yoktur. Ayrıca 0'da 1'den fazla kutbu varsa, yine limit yoktur.

$$\frac{1}{s-2} \xrightarrow{\mathcal{L}^{-1}} e^{2t} u(t) \rightarrow \infty \text{ limit yok}$$

$$\frac{1}{s^2} \xrightarrow{\mathcal{L}^{-1}} t u(t) \rightarrow \infty \text{ limit yok.}$$

$$\frac{1}{s-2-j} + \frac{1}{s-2+j} \xrightarrow{\mathcal{L}^{-1}} e^{2t} \cos(t+\theta)$$

$$\frac{s}{s^2+4} \xrightarrow{\mathcal{L}^{-1}} \cos(2t) \text{ limit yok.}$$

$$\lim_{s \rightarrow \infty} sF(s) = \lim_{s \rightarrow \infty} \frac{s(5s^2+3)}{s^3+4s^2+6} = 5 = f(0)$$

$0.16 + 1.16j, 0.16 - 1.16j$
 -4.32

Pozitif yarı düzlemde kutbu olduğun için
 $(\alpha + j\omega, \alpha - j\omega)$ $\alpha > 0$ limit yoludur.

$$b) \frac{s^2 - 2s - 1}{4(s-2)(s^2+2s+4)}$$

pozitif kutbu var $\rightarrow e^{2t}$ gelir
 $f(\infty)$ bulunamaz.

$$\lim_{s \rightarrow \infty} sF(s) = \lim_{s \rightarrow \infty} \frac{s(s^2 - 2s - 1)}{4(s-2)(s^2+2s+4)} = \frac{1}{4} = f(0)$$

BAŞLANGIÇ ✓

kutuplar, $2, -1 \pm \sqrt{3}j$

$\downarrow$
 e^{2t} limit yoludur.

son değer teoremi kullanılmaz.

yani $\lim_{s \rightarrow 0} sF(s)$ kullanılmaz

15.32 Determine the inverse Laplace transform of each of

the following functions:

(a) $\frac{8(s+1)(s+3)}{s(s+2)(s+4)}$

$K_1? + K_2? + K_3?$
 $\frac{K_1}{s} + \frac{K_2}{s+2} + \frac{K_3}{s+4}$

(b) $\frac{s^2 - 2s + 4}{(s+1)(s+2)^2}$

(c) $\frac{s^2 + 1}{(s+3)(s^2 + 4s + 5)}$

a) $K_1 = sF(s) \Big|_{s=0} = \frac{8 \times 1 \times 3}{2 \times 4} = 3$

$K_2 = (s+2)F(s) \Big|_{s=-2} = \frac{8(-1)(1)}{(-2)(2)} = -2$

$K_3 = (s+4)F(s) \Big|_{s=-4} = \frac{8(-3)(-1)}{(-4)(-2)} = 3$

$$f(t) = (3 + 2e^{-2t} + 3e^{-4t})u(t)$$

$$b) \frac{s^2 - 2s + 4}{(s+1)(s+2)^2} = \frac{K_1}{s+1} + \frac{K_2}{(s+2)^2} + \frac{K_3}{s+2}$$

$$K_1 = (s+1)F(s) \Big|_{s=-1} = \frac{1+2+4}{1} = 7$$

$$K_2 = (s+2)^2 F(s) \Big|_{s=-2} = \frac{4+4+4}{(-1)} = -12$$

$$K_3 = \frac{d}{ds} \left\{ (s+2)^2 F(s) \right\} \Big|_{s=-2} = \frac{d}{ds} \left\{ \frac{s^2 - 2s + 4}{s+1} \right\} \Big|_{s=-2}$$

$$= \frac{(2s-2)(s+1) - (s^2 - 2s + 4)}{(s+1)^2} \Big|_{s=-2}$$

$$= \frac{(-6)(-1) - (4+4+4)}{(-1)^2} = -6$$

$$F(s) = \frac{7}{s+1} - \frac{12}{(s+2)^2} - \frac{6}{s+2}$$

$\downarrow \mathcal{L}^{-1}$

$$f(t) = (7e^{-t} - 12te^{-2t} - 6e^{-2t})u(t)$$

$$f(0) = 1$$

$$f(\infty) = 0$$

$$c) \frac{s^2 + 1}{(s+3)(s^2 + 4s + 5)} = \frac{K_1}{s+3} + \frac{K_2}{s+2-j} + \frac{K_2^*}{s+2+j}$$

$\downarrow \mathcal{L}^{-1}$

$$2|K_2|e^{-2t}\cos(t + \theta_{12})$$

$s_{1,2} = \frac{-4 \pm \sqrt{16-20}}{2} = -2 \pm j$

$$K_1 = (s+3)F(s) \Big|_{s=-3} = \frac{9+1}{9-12+5} = 5$$

$$K_2 = (s+2-j)F(s) \Big|_{s=-2+j} = \frac{(-2+j)^2 + 1}{(-2+j+3)(2j)}$$

$$= \frac{4-4j-1+1}{(1+j)(2j)} = \frac{4\sqrt{2} \angle -45^\circ}{\sqrt{2} \angle 45^\circ \cdot 2 \angle 90^\circ}$$

$$K_2 = 2 \angle -180^\circ = -2$$

$$f(t) = 5e^{-3t} + 2 \times 2 e^{-2t} \cos(t-180^\circ)$$

$$= 5e^{-3t} - 4e^{-2t} \cos(t)$$

Alternatif

$$F(s) = \frac{K_1}{s+3} + \frac{K_2 s + K_3}{s^2 + 4s + 5}$$

$$= \frac{5}{s+3} - \frac{4s+8}{s^2+4s+5}$$

$$= \frac{5}{s+3} - \frac{4(s+2)}{(s+2)^2 + 1}$$

payda eşitleyerek
K₂ ve K₃
bulunur.
(4s+8)

$$F(s) = 5e^{-3t} - 4e^{-2t} \cos(t)$$

15.40 Show that

$$\mathcal{L}^{-1} \left[\frac{4s^2 + 7s + 13}{(s+2)(s^2 + 2s + 5)} \right] =$$

$$\rightarrow [\sqrt{2}e^{-t} \cos(2t + 45^\circ) + 3e^{-2t}] u(t)$$

$$\frac{4s^2 + 7s + 13}{(s+2)(s^2 + 2s + 5)} = \frac{K_1}{s+2} + \frac{K_2}{s+1-2j} + \frac{K_2^*}{s+1+2j}$$

$$\frac{-2 \mp \sqrt{-16}}{2}$$

$$K_1 = (s+2)F(s) \Big|_{s=-2} = \frac{16-14+13}{4-4+5} = \frac{15}{5} = 3$$

$$K_2 = (s+1-2j)F(s) \Big|_{s=-1+2j} = \frac{4(-1+2j)^2 + 7(-1+2j) + 13}{(-1+2j+2)(-1+2j+1+2j)}$$

$$= \frac{4-16j-16-7+14j+13}{(1+2j)(4j)}$$

$$= \frac{-6-2j}{(1+2j)(4j)} = \frac{-2+6j}{4(1+2j)(1-2j)} = \frac{-2+4j+6j+12}{20} = \frac{10+10j}{20} = \frac{1+j}{2}$$

$$K_2 = \frac{1}{\sqrt{2}} \angle 45^\circ$$

$$f(t) = \left[3e^{-2t} + \sqrt{2}e^{-t} \cos(2t+45^\circ) \right] u(t)$$

(c) $Z(s) = \frac{5}{s(s+1)(s^2+6s+10)}$

*15.41 Let $x(t)$ and $y(t)$ be as shown in Fig. 15.36. Find $z(t) = x(t) * y(t)$. Convolution

15.42 Design a problem to help other students better understand how to convolve two functions together.

Envision


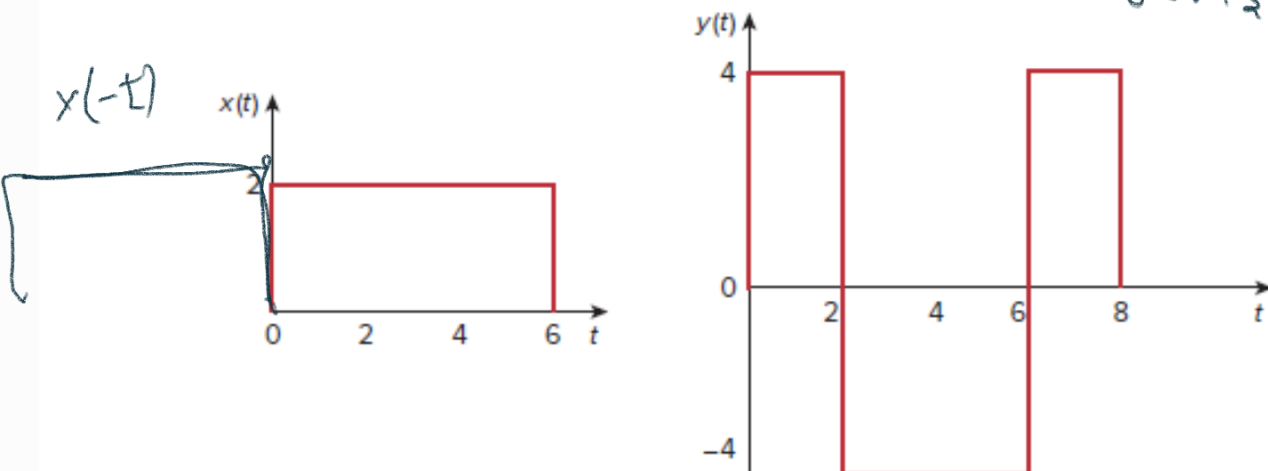


Figure 15.36
For Prob. 15.41.

$$x(t) * y(t) = \int_{-\infty}^{\infty} x(\tau) y(t-\tau) d\tau$$
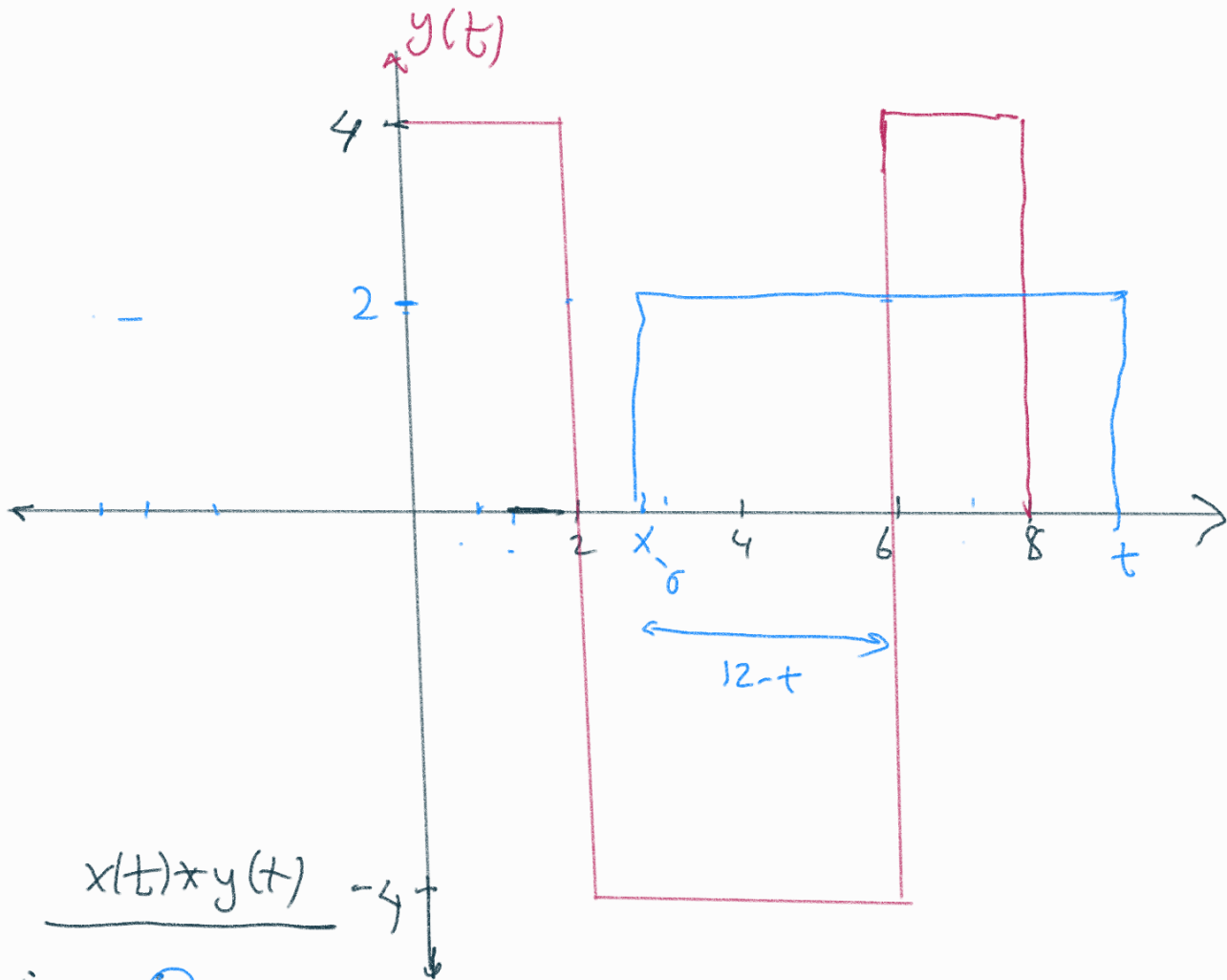
$$= \int_{-\infty}^{\infty} y(z) x(t-z) dz \quad (\otimes)$$



$$\frac{x(t) * y(t)}{-4}$$

$$t < 0 : 0$$

$$0 < t < 2 : 8t$$

$$2 < t < 6 : 32 - 8t$$

$$6 < t < 8 : -16$$

$$8 < t < 12 : 8t - 80$$

$$12 < t < 14 : 112 - 8t$$

$$14 < t : 0$$

+ örtüşme süresi:

$$2 - \cancel{t+6} + \cancel{t-6} = 2$$

$$\text{int: } 2 \times 8 - 32$$


$$16 - 8(12 - t)$$

$$8t - 80$$

→ örtüşme $t-6 \rightarrow 8$ olan

14-t süre boyunca

$$\text{int: } 8 \times (14 - t)$$

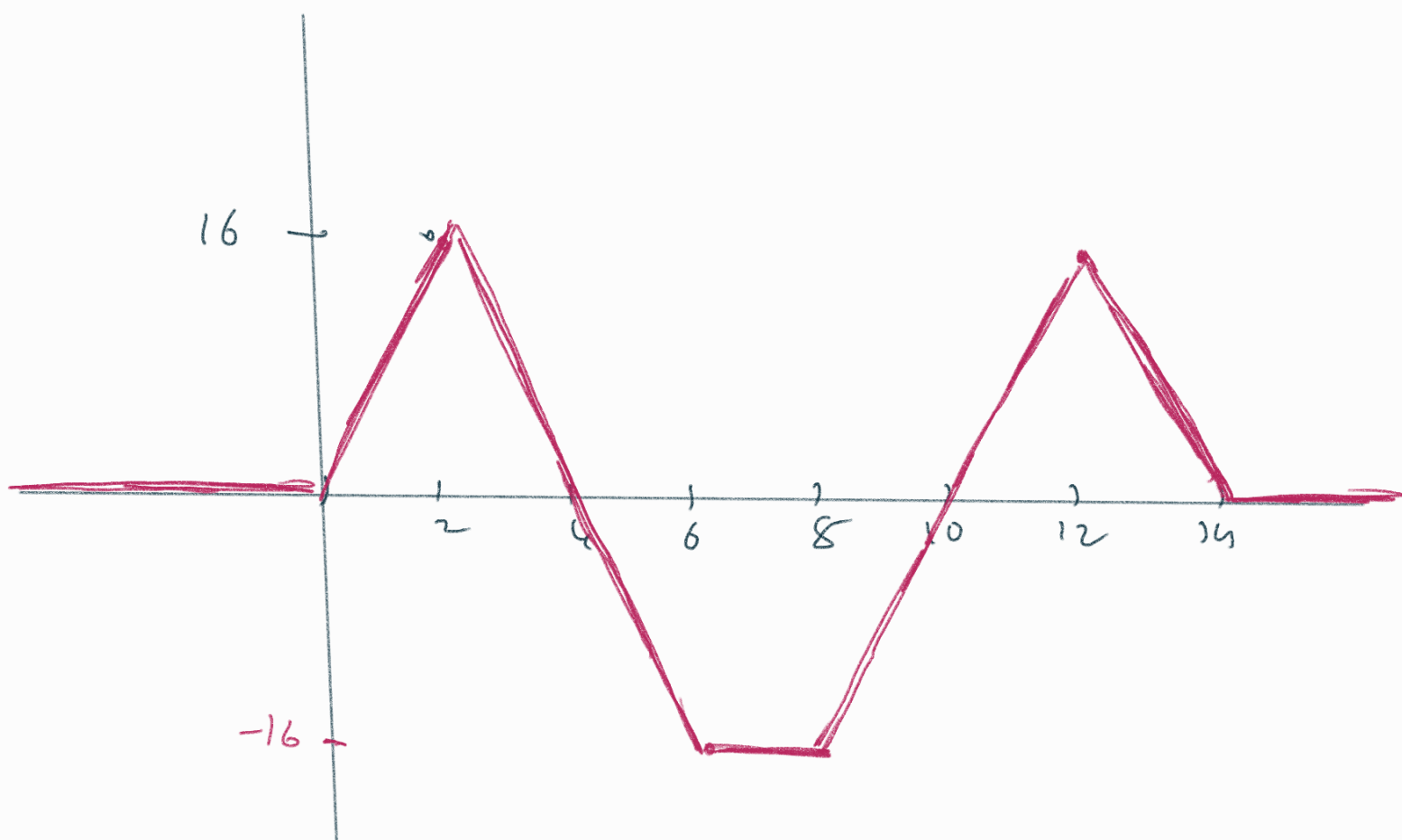

***15.49** Use the convolution integral to find:

(a) $t * e^{at}u(t)$ $t u(t) * e^{at} u(t)$

(b) $\cos(t) * \cos(t)u(t)$

a)
$$= \int_{-\infty}^t \cancel{z} \cancel{u(z)} e^{a(t-\tau)} \cancel{u(t-\tau)} d\tau$$

$$= \int_0^t \tau e^{at} e^{-a\tau} d\tau$$

$$\left[\begin{array}{l} \tau = u \\ d\tau = du \end{array} \right] \left[\begin{array}{l} e^{-a\tau} d\tau = dv \\ v = \frac{1}{a} e^{-a\tau} = v \end{array} \right] \int u dv = uv - \int v du$$

$$e^{at} \left[\underbrace{-\frac{\tau}{a} e^{-a\tau}}_0^t - \underbrace{\int_0^t \frac{1}{a} e^{-a\tau} d\tau}_0^t \right]$$

$$e^{at} \left[\frac{-te^{-at}}{a} + \left. -\frac{1}{a^2} e^{-a\tau} \right|_0^t \right]$$

$$= e^{at} \left[\frac{-te^{-at}}{a} + \frac{1}{a^2} - \frac{e^{-at}}{a^2} \right]$$

$$= -\frac{t}{a} + \frac{e^{at}}{a^2} - \frac{1}{a^2}$$

b) $\cos(t)u(t) * \cos t \cdot u(t)$

$$\int_0^t \cos(\tau) \cos(t-\tau) d\tau$$

$$\int_0^t \frac{\cos(t) + \cos(2\tau - t)}{2} d\tau$$

$$= \frac{\cos(t)}{2} \tau \Big|_0^t + \frac{1}{4} \sin(2\tau - t) \Big|_0^t$$

$$\frac{t \cos(t)}{2} + \frac{\sin(t) - \sin(-t)}{4}$$

$$= \left[\frac{t \cos(t)}{2} + \frac{\sin(t)}{2} \right] u(t)$$

15.52 Use the Laplace transform to find $i(t)$ for $t > 0$ if

$$\frac{d^2 i}{dt^2} + 3 \frac{di}{dt} + 2i + \delta(t) = 0,$$

$$i(0) = 0, \quad i'(0) = 3$$

$$\frac{di}{dt} \xrightarrow{\mathcal{L}} sI - i(0)$$

$$\frac{d^2 i}{dt^2} \xrightarrow{\mathcal{L}} s^2 I - s \cancel{i(0)} - \underbrace{i'(0)}_3$$

$$s^2 I - 3 + 3sI + 2I + 1 = 0$$

$$\frac{2}{s^2 + 3s + 2} = I = \frac{K_1 \xrightarrow{2}}{s+1} + \frac{K_2 \xrightarrow{-2}}{s+2}$$

$$i(t) = (2e^{-t} - 2e^{-2t})u(t)$$

15.60 Solve the following integrodifferential equation

$$2 \frac{dx}{dt} + 5x + 3 \int_0^t x dt + 4 = \sin 4t, \quad x(0) = 1$$

$$2sX - 2 \cancel{x(0)} + 5X + 3 \frac{X}{s} + \frac{4}{s} = \frac{4}{s^2 + 16}$$

$$X \left(2s + 5 + \frac{3}{s} \right) = 2 - \frac{4}{s} + \frac{4}{s^2 + 16}$$

$$X \left(\frac{2s^2 + 5s + 3}{s} \right) = 2 - \frac{4}{s} + \frac{4}{s^2 + 16}$$

$$(2s^2 + 5s + 3)X = 2s - 4 + \frac{4s}{s^2 + 16}$$

$$(s^2 + 2.5s + 1.5)X = s - 2 + \frac{2s}{s^2 + 16}$$

$$\frac{\sqrt{6.25 - 6} - 2.5 \pm \sqrt{0.25}}{2}$$

$$\frac{-3, -2}{2} = (-1, -1.5)$$

$$X = \frac{s - 2}{(s + 1)(s + 1.5)} + \frac{2s}{(s^2 + 16)(s + 1)(s + 1.5)}$$

$$= \frac{k_1}{s + 1} + \frac{k_2}{s + 1.5}$$

$$k_1 = \frac{-3}{0.5} \quad k_2 = \frac{-3.5}{-0.5}$$

$$= \frac{k_3}{s + 1} + \frac{k_4}{s + 1.5} + \frac{k_5 s + k_6}{s^2 + 16}$$

$$= \frac{k_3}{s + 1} + \frac{k_4}{s + 1.5} + \frac{k_5}{s - 4j} + \frac{k_6}{s + 4j}$$

$$k_3 = \frac{-2}{(17)(0.5)}$$

$$k_4 = \frac{-3}{18.25(-0.5)}$$

$$k_5 = \frac{8j}{8j(1 - 4j)(1.5 - 4j)}$$

$$k_5 = \frac{1}{1.5 - 4j - 6j - 16} = \frac{1}{-14.5 - 10j}$$

$$x(t) = -6e^{-t} + 7e^{-1.5t} - \frac{4}{17}e^{-t} + \frac{6}{18.25}e^{-1.5t} + 2|k_5|\cos(4t + \theta_{k_5})$$

16.10 The step responses of a series RLC circuit are


$$\rightarrow V_c = 40 - 10e^{-2000t} - 10e^{-4000t} \text{ V}, t > 0$$

$$\rightarrow i_L(t) = 3e^{-2000t} + 6e^{-4000t} \text{ mA}, t > 0 \rightarrow$$

(a) Find C .

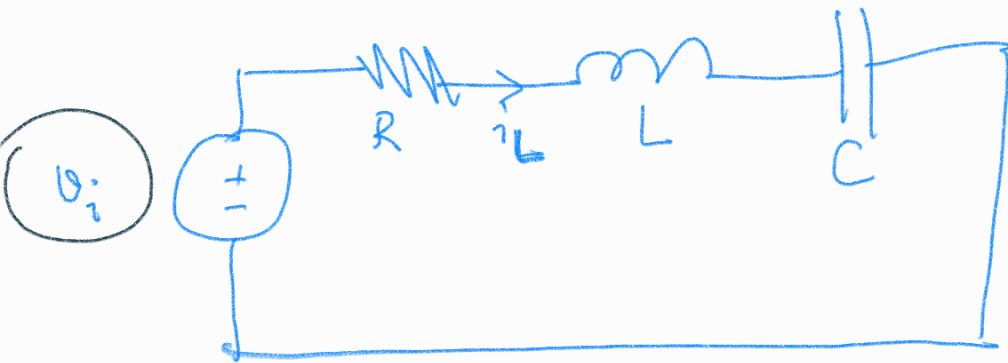(b) Determine what type of damping is exhibited by the circuit.

$\rightarrow$ Aşırı sönümlenme
2 farklı $e^{-\alpha t}$ var.
+ V_c -



$$C \frac{dV_c}{dt} = i_c = i_L$$

$$C \left(+20000e^{-2000t} + 40000e^{-4000t} \right) = \left(3e^{-2000t} + 6e^{-4000t} \right) \times 10^{-3}$$

$$\left. \begin{array}{l} 20000C = 3 \times 10^{-3} \\ 40000C = 6 \times 10^{-3} \end{array} \right\} C = \frac{3 \times 10^{-3}}{2 \times 10^4} = 1.5 \times 10^{-7} = 150 \text{ nF}$$

$$\boxed{V_i = 40u(t)} = V_R + V_L + V_C$$

$$= i_L R + L \frac{di_L}{dt} + V_C$$

$$\cancel{40} = \left(3Re^{-2000t} + 6Re^{-4000t} \right) 10^{-3} - 6Le^{-2000t} - 24Le^{-4000t} + 40 - 10e^{-2000t} - 10e^{-4000t}$$

$\nearrow$ verilmiş

$$2 \times \begin{cases} 3 \times 10^{-3} R - 6L - 10 = 0 \\ 6 \times 10^{-3} R - 24L - 10 = 0 \end{cases}$$

$$12L = 10 \Rightarrow L = \frac{10}{12}$$

$$15 = 3 \times 10^{-3} R \Rightarrow R = 5k \Omega$$

16.19 The switch in Fig. 16.42 moves from position A to position B at $t = 0$ (please note that the switch must connect to point B before it breaks the connection at A, a make before break switch). Find $v(t)$ for $t > 0$.



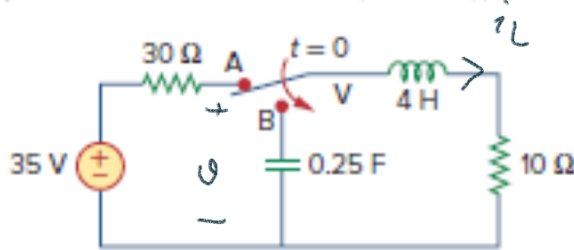


Figure 16.42
For Prob. 16.19.

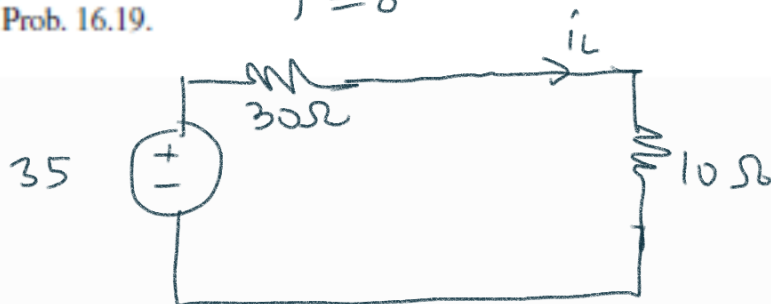

$$v(0^-) = 0 \text{ V}$$

$$i_L(0^-) = \frac{7}{8} \text{ A}$$

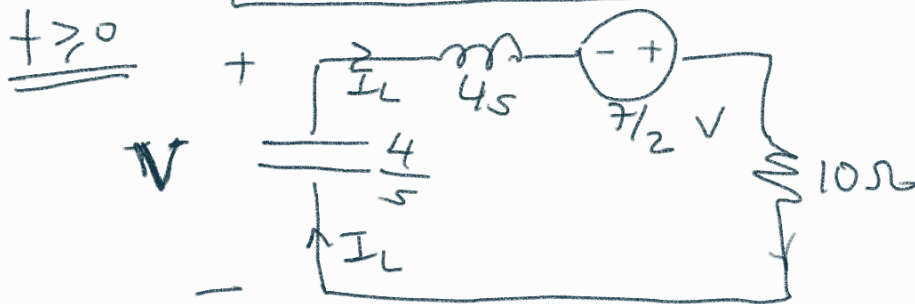

$$v_L = L \frac{di_L}{dt} \xrightarrow{\mathcal{L}} V_L = \underbrace{sL I_L}_{4s} - \underbrace{L i_L(0^-)}_{4 \times \frac{7}{8}}$$

$$I_L \left(\frac{4}{s} + 4s + 10 \right) = \frac{7}{2}$$

$$I_L \left(\frac{4s^2 + 10s + 4}{s} \right) = \frac{7}{2}$$

$$I_L = \frac{7s}{2(4s^2 + 10s + 4)}$$

$$= \frac{7s}{8(s^2 + \frac{5}{2}s + 1)}$$

$$V \Rightarrow I_L \frac{4}{s}$$

$$= \frac{-7}{2(s^2 + \frac{5}{2}s + 1)}$$

$$= \frac{-7}{2(s+2)(s+0.5)}$$

$$= \frac{K_1}{s+2} + \frac{K_2}{s+0.5}$$

$$K_1 = \frac{-7}{2(-1.5)} = \frac{7}{3}$$

$$K_2 = \frac{-7}{2(1.5)} = -\frac{7}{3}$$

$$s_{1,2} = \frac{-\frac{5}{2} \pm \sqrt{\frac{25}{4} - 4}}{2}$$

$$= \frac{-\frac{5}{2} \pm \sqrt{\frac{9}{4}}}{2}$$

$$= \frac{-2.5 \pm 1.5}{2}$$

$$s_{1,2} = (-2, -0.5)$$

$$v(t) = \left(\frac{7}{3}e^{-2t} - \frac{7}{3}e^{-0.5t} \right) u(t)$$

16.23 Obtain $v(t)$ for $t > 0$ in the circuit of Fig. 16.46.


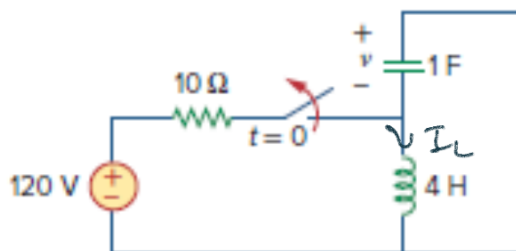



Figure 16.46
For Prob. 16.23.

$t = 0^-$

$$i_L(0^-) = 12 \text{ A}$$

$$v(0^-) = 0$$

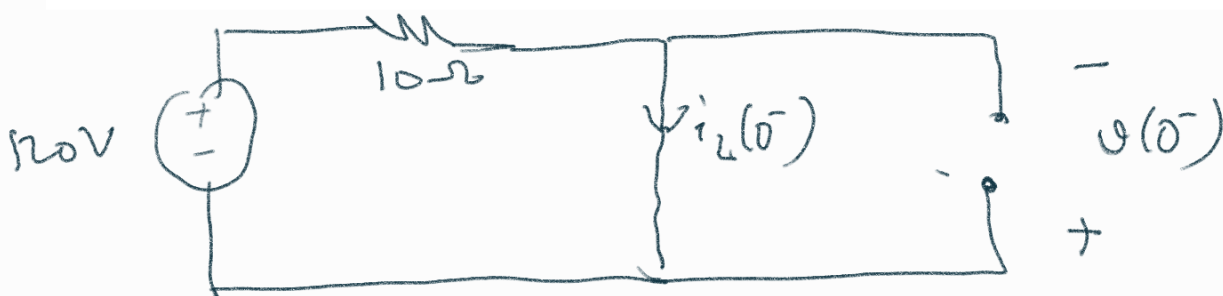

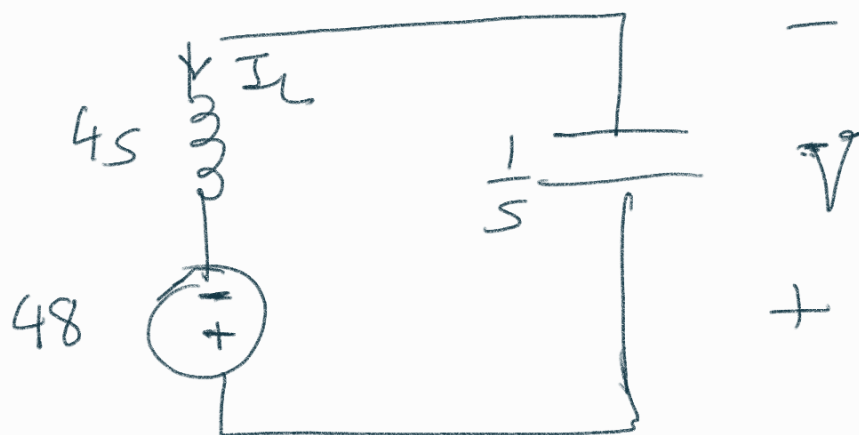

$$v_L = L \frac{di_L}{dt} \xrightarrow{\mathcal{L}} sL I_L - L i_L(0^-)$$

$\underbrace{\hspace{10em}}_{-48}$

$$I_L \left(4s + \frac{1}{s} \right) = 48$$

$$I_L = \frac{48s}{4s^2 + 1}$$

$$V = \frac{1}{s} I_L = \frac{48}{4s^2 + 1} = \frac{12}{s^2 + \frac{1}{4}} = 24 \cdot \frac{\frac{1}{2}}{s^2 + \left(\frac{1}{2}\right)^2}$$

$$\downarrow \mathcal{L}^{-1}$$

$$v(t) = 24 \sin\left(\frac{1}{2}t\right)$$

$$= 24 \cos\left(\frac{1}{2}t - 90^\circ\right)$$

16.25 Calculate $v(t)$ for $t > 0$ in the circuit of Fig. 16.48.


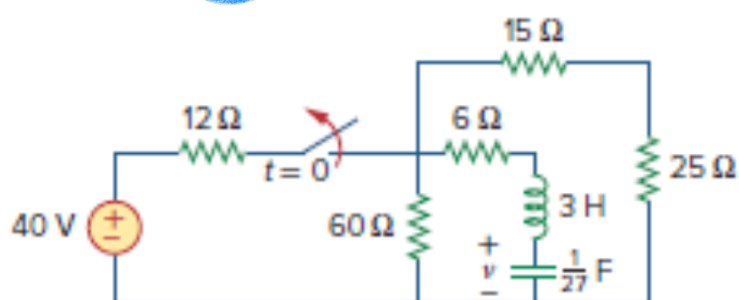


Figure 16.48
For Prob. 16.25.

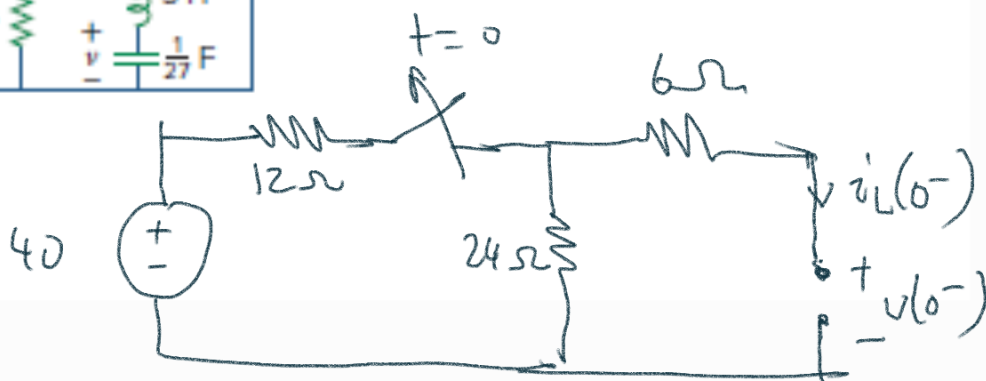


$$i_L(0^-) = 0 \text{ A}$$

$$v(0^-) = 40 \times \frac{24}{36} = \frac{80}{3}$$

$$i_c = C \frac{dv_c}{dt}$$

$t \geq 0$

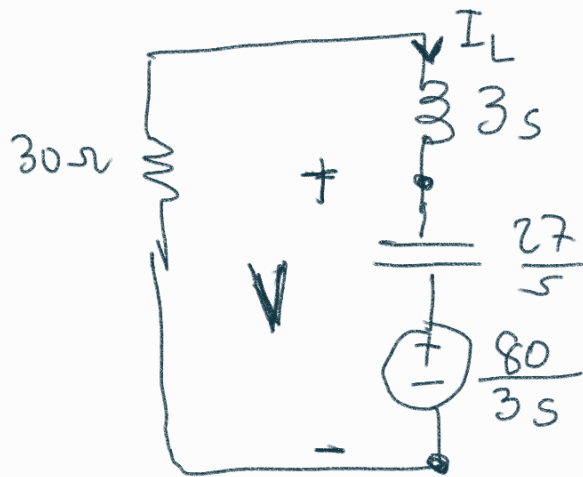

$$I_c = sC V_c - C v_c(0^-)$$

$$V_c = \frac{I_c + C v_c(0^-)}{sC}$$

$$V_c = \frac{I_s}{sC} + \frac{v_c(0^-)}{s}$$

$$I_L \left(30 + 3s + \frac{27}{s} \right) + \frac{80}{3s} = 0$$

$$I_L \left(\frac{3s^2 + 30s + 27}{s} \right) = -\frac{80}{3s}$$

$$I_L = \frac{-80}{9(s^2 + 10s + 9)}$$

$$V = \frac{27}{s} I_L + \frac{80}{3s}$$

$$= \frac{-240}{s(s^2 + 10s + 9)} + \frac{80}{3s}$$

$-\frac{80}{3}$

$$= \frac{K_1}{s} + \frac{K_2}{s+1} + \frac{K_3}{s+9} + \frac{80/3}{s}$$

$$K_1 = \frac{-240}{9} = -\frac{80}{3} \quad K_2 = \frac{-240}{(-1)(8)} = 30 \quad K_3 = \frac{-240}{(-9)(-8)} = -\frac{10}{3}$$

$$v(t) = \left(30e^{-t} - \frac{10}{3}e^{-9t} \right) u(t)$$

16.28 For the circuit in Fig. 16.51, find $v(t)$ for $t > 0$.



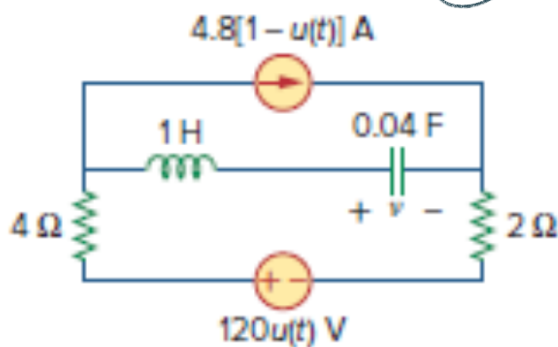


Figure 16.51
For Prob. 16.28.

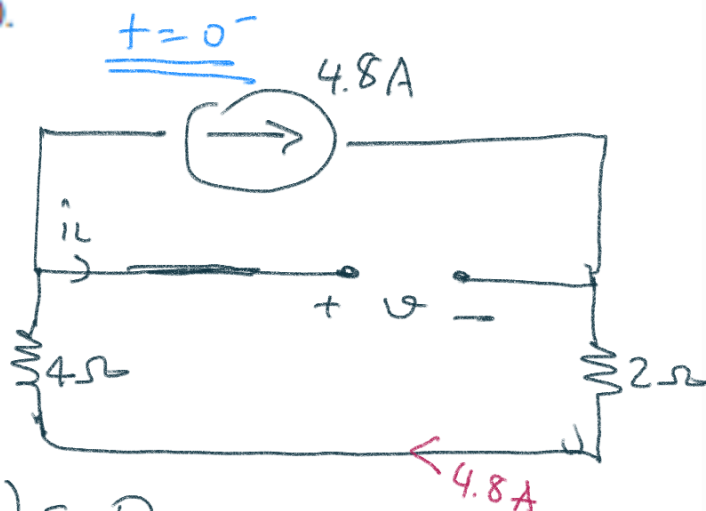

$$i_L(0^-) = 0$$
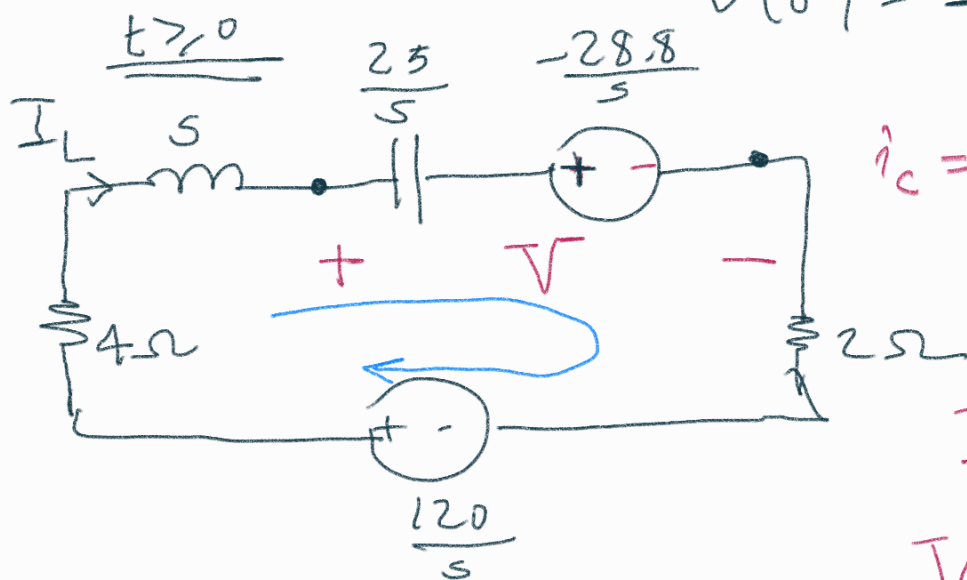
$$v(0^-) = -6 \times 4.8 = -28.8 \text{ V}$$



$$i_c = C \frac{dv_c}{dt}$$

$$I_c = sC V_c - C v(0^-)$$

$$V_c = \frac{I_c + C v(0^-)}{sC}$$

$$V_c = \frac{I_c}{sC} + \frac{v(0^-)}{s}$$

$$I_L \left(s + \frac{25}{s} + 6 \right) - \frac{28.8}{s} - \frac{120}{s} = 0$$

$$I_L \left(\frac{s^2 + 6s + 25}{s} \right) = \frac{148.8}{s}$$

$$I_L = \frac{148.8}{s^2 + 6s + 25}$$

$$V = \frac{25}{s} I_L - \frac{28.8}{s}$$

$$= \frac{3720}{s(s^2+6s+25)} - \frac{28.8}{s}$$

$$= \frac{K_1}{s} + \frac{K_2 s + K_3}{s^2 + 6s + 25} - \frac{28.8}{s}$$

$$K_1 = \frac{3720}{25} = 148.8$$

$$(K_1 s^2 + 6K_1 s + 25K_1 + K_2 s^2 + K_3 s) = 3720$$

$$K_1 + K_2 = 0 \Rightarrow K_2 = -148.8$$

$$6K_1 + K_3 = 0 \Rightarrow K_3 = -6K_1 = -892.8$$


$$V = \frac{148.8}{s} + \frac{-148.8s - 892.8}{(s+3)^2 + 4^2} - \frac{28.8}{s}$$

$$= \frac{120}{s} - 148.8 \left(\frac{s+3+3}{(s+3)^2 + 4^2} \right)$$

$$= \frac{120}{s} - 148.8 \frac{s+3}{(s+3)^2 + 4^2} - \frac{148.8 \times 3}{4} \frac{4}{(s+3)^2 + 4^2}$$

$$v(t) = \left[120 - 148.8 e^{-3t} \cos(4t) - 111.6 e^{-3t} \sin(4t) \right] u(t) //$$

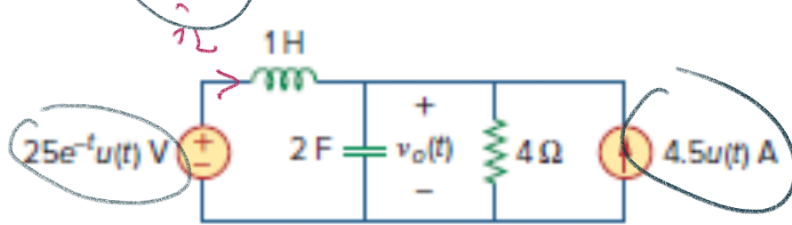16.35 Find $v_o(t)$ in the circuit of Fig. 16.58.




$$i_L(0^-) = 0$$

$$v_o(0^-) = 0$$

Figure 16.58

For Prob. 16.35.

$t \geq 0$

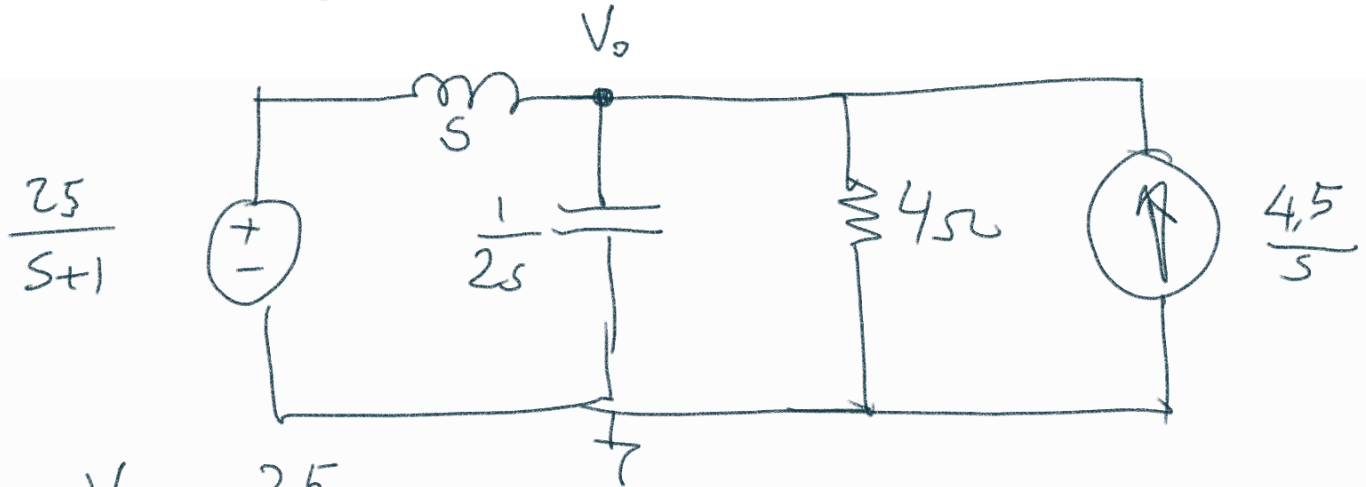

$$\frac{V_o - \frac{25}{s+1}}{s} + V_o 2s + \frac{V_o}{4} = \frac{4.5}{s}$$

$$V_o \left[\frac{1}{s} + 2s + \frac{1}{4} \right] = \frac{25}{s(s+1)} + \frac{4.5}{s}$$

$$V_o \left[\frac{8s^2 + s + 4}{4s} \right] = \frac{4.5s + 29.5}{s(s+1)}$$

$$V_o = \frac{4.5s + 29.5}{8(s+1) \left(s^2 + \frac{1}{8}s + \frac{1}{2} \right)}$$

$$= \frac{K_1}{s+1} + \frac{K_2s + K_3}{s^2 + \frac{s}{8} + \frac{1}{2}}$$

$$K_1 = \frac{25}{8 \left(1 - \frac{1}{8} + \frac{1}{2}\right)} = \frac{25}{8 \cdot \frac{11}{8}} = \frac{25}{11}$$

$$\cancel{K_1 s^2} + \cancel{\frac{K_1 s}{8}} + \frac{K_1}{2} + \cancel{K_2 s^2} + \cancel{K_3 s} + \cancel{K_2 s} + K_3 = \frac{4.5s + 29.5}{8}$$

$$K_1 + K_2 = 0 \Rightarrow K_2 = -\frac{25}{11}$$

$$\frac{K_1}{8} + K_3 + K_2 = \frac{4.5}{8}$$

$$\frac{25}{88} - \frac{25}{11} + K_3 = \frac{4.5}{8} \Rightarrow K_3 = 2.55$$

$$\frac{K_1}{2} + K_3 = \frac{29.5}{8}$$

$$= \frac{25/11}{s+1} + \frac{-\frac{25}{11}s + 2.5}{\left(s + \frac{1}{16}\right)^2 + \frac{1}{2} - \frac{1}{256}} \rightarrow \text{ihmadret}$$

$$= \frac{25/11}{s+1} + \frac{-\frac{25}{11} \left(s + \frac{1}{16}\right) + 0.14 + 2.5}{\left(s + \frac{1}{16}\right)^2 + \left(\frac{1}{\sqrt{2}}\right)^2}$$

$$= \frac{25/11}{s+1} - \frac{25}{11} \frac{s + \frac{1}{16}}{\left(s + \frac{1}{16}\right)^2 + \frac{1}{\sqrt{2}}} + 2.64\sqrt{2} \frac{\frac{1}{\sqrt{2}}}{\left(s + \frac{1}{16}\right)^2 + \left(\frac{1}{\sqrt{2}}\right)^2}$$

$$= \frac{25}{11} e^{-t} - \frac{25}{11} e^{-\frac{1}{16}t} \cos\left(\frac{1}{\sqrt{2}}t\right) + 2.64\sqrt{2} e^{-\frac{1}{16}t} \sin\left(\frac{1}{\sqrt{2}}t\right)$$

16.42 Given the circuit in Fig. 16.65, find $i(t)$ and $v(t)$ for $t > 0$.


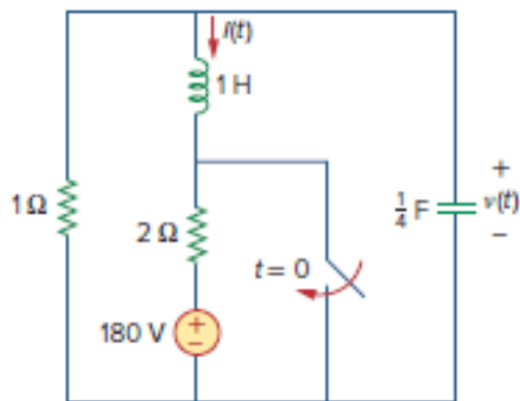


Figure 16.65
For Prob. 16.42.


$t = 0^-$

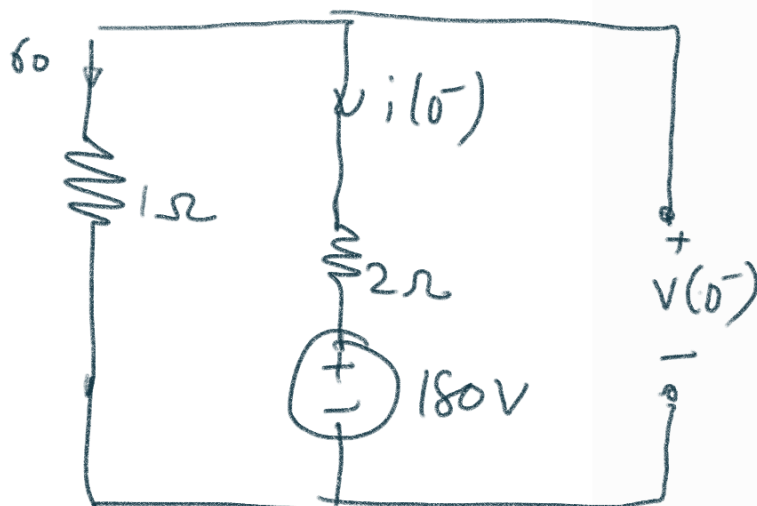

$$i(0^-) = -60 \text{ A}$$

$$v(0^-) = 60 \text{ V}$$

$t > 0$

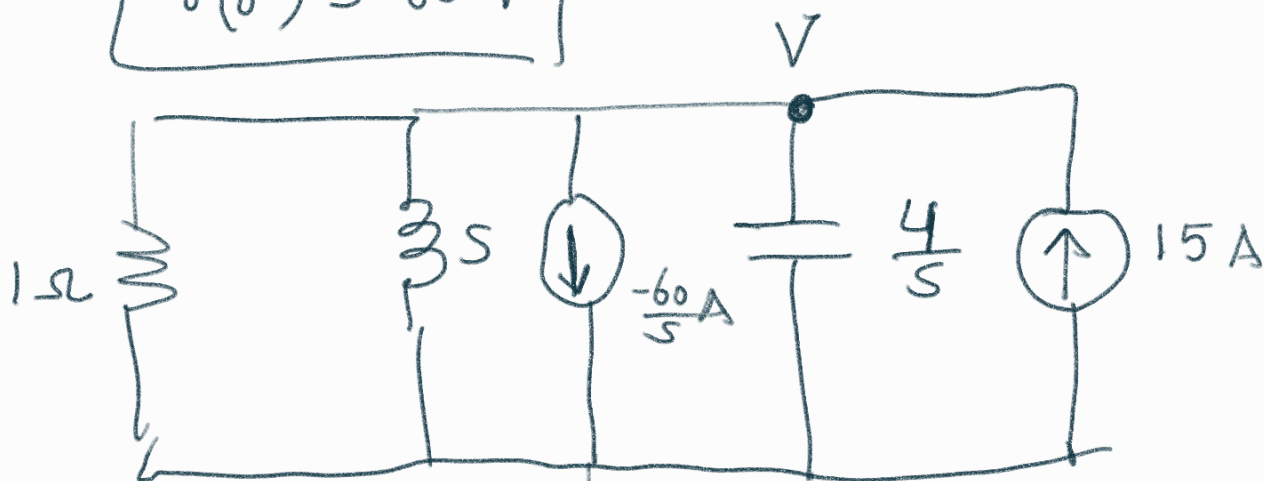

$$v_L = L \frac{di_L}{dt}$$

$$\xrightarrow{\mathcal{L}} V_L = sL I_L - L i_L(0^-)$$

$$I_L = \frac{V_L + L i_L(0^-)}{sL}$$

$$= \frac{V_L}{sL} + \frac{i_L(0^-)}{s}$$

$$i_C = C \frac{dv_C}{dt}$$

$$\xrightarrow{\mathcal{L}} I_C = sC V_C - C v_C(0^-)$$

$$\frac{V}{1} + \frac{V}{s} - \frac{60}{s} + \frac{Vs}{4} = 15$$

$$V \left[1 + \frac{1}{s} + \frac{s}{4} \right] = \frac{60 + 15s}{s}$$

$$V \frac{s^2 + 4s + 4}{4s} = \frac{15(s+4)}{s}$$

$$V = \frac{60(s+4)}{(s+2)^2} = \frac{K_1}{(s+2)^2} + \frac{K_2}{s+2}$$


$\nearrow 120$ $\nearrow 60$

$$K_1 = 120 \quad K_2 = \left\{ \frac{d}{ds} 60(s+4) \right\} \bigg|_{s=-2}$$

$$= 60$$

$$v(t) = (120e^{-2t} + 60e^{-2t})u(t)$$

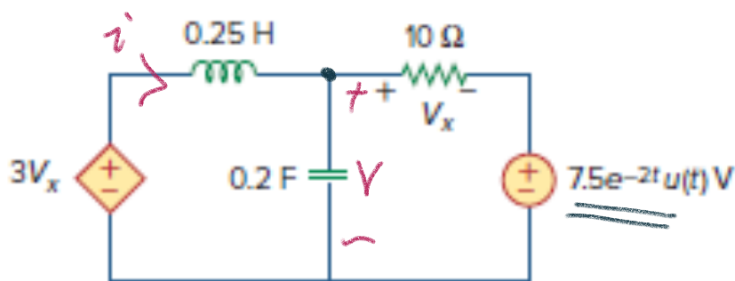
16.48 Find $V_x(s)$ in the circuit shown in Fig. 16.71.



$$v(0^-) = 0$$

$$i(0^-) = 0$$

Figure 16.71
For Prob. 16.48.

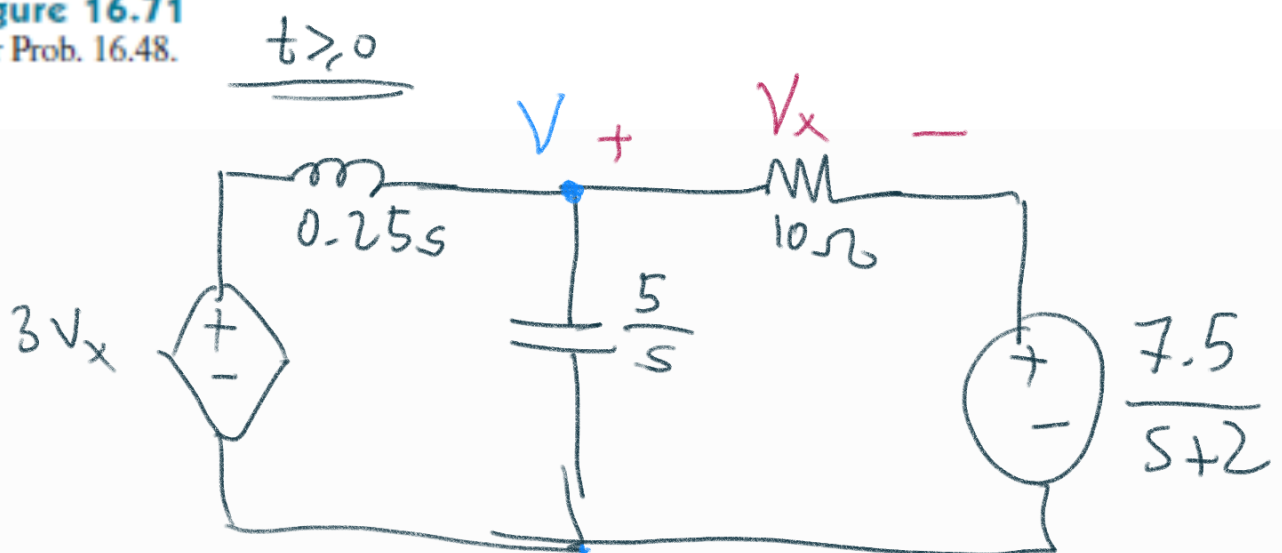

$$\frac{V - 3V_x}{0.25s} + \frac{V}{5} + \frac{V}{10} - \frac{7.5}{s+2} = 0$$

(1)

$$V_x = V - \frac{7.5}{s+2} \quad (2)$$

$$40V - 120V_x + 2s^2V + sV - \frac{7.5s}{s+2} = 0$$


$$V(2s^2 + s + 40) = 120V_x + \frac{7.5s}{s+2}$$

$$V(2s^2 + s - 80) = \frac{7.5s - 900}{s+2}$$


$$V = \frac{7.5s - 900}{(s+2)(2s^2 + s - 80)}$$

içerisiz kök.

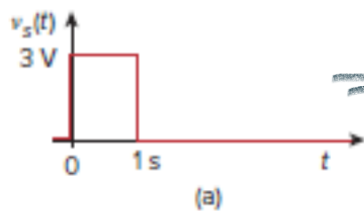ama biri pozitif
0 nedeniyle $v(t) \rightarrow \infty$



$$\Rightarrow 3u(t) - 3u(t-1)$$

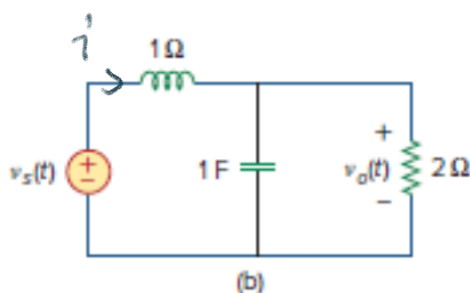

$$\frac{3}{s} - \frac{3e^{-s}}{s} = \frac{3}{s}(1 - e^{-s})$$

$t > 0$

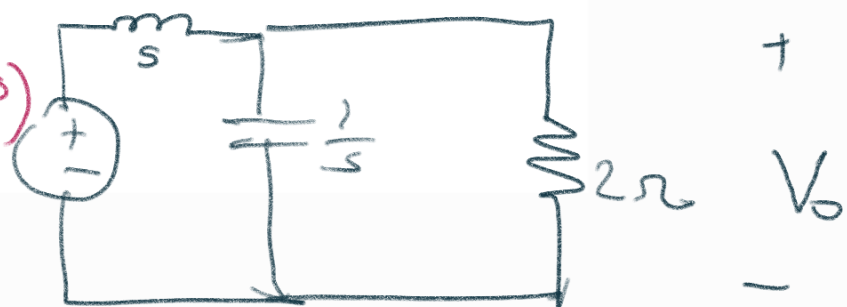


Figure 16.80
For Prob. 16.57.

$$i(0^-) = 0$$

$$v_o(0^-) = 0$$

$$\frac{3}{s}(1 - e^{-s})$$

$$\frac{3}{s}(1-e^{-s}) \cdot \frac{\frac{1}{s} \parallel 2}{\frac{1}{s} \parallel 2 + s} = V_o$$

$$\frac{3}{s}(1-e^{-s}) \frac{\frac{\frac{2}{s}}{2 + \frac{1}{s}}}{\frac{2/s}{2 + \frac{1}{s}} + s} = \frac{3}{s}(1-e^{-s}) \frac{\frac{2}{2s+1}}{\frac{2}{2s+1} + s}$$

$$= \frac{3}{s}(1-e^{-s}) \frac{2}{2+2s^2+s}$$

$$= (1-e^{-s}) \frac{3}{s(s^2 + \frac{s}{2} + 1)}$$

$$\xrightarrow{\mathcal{L}^{-1}} \left(K_1 + 2|K_2| e^{-\alpha t} \cos(\omega t + \theta_{K_2}) \right) u(t) - \left(K_1 + 2|K_2| e^{-\alpha(t-1)} \cos(\omega(t-1) + \theta_{K_2}) \right) u(t-2)$$

$$s_{1,2} = \frac{-\frac{1}{2} \pm \sqrt{\frac{1}{4} - 4}}{2}$$

16.66 For the op amp circuit in Fig. 16.89, find $v_o(t)$ for $t > 0$. Take $v_s = 12 e^{-5t} u(t)$ V.

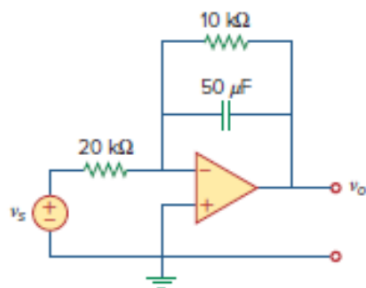


Figure 16.89
For Prob. 16.66.

